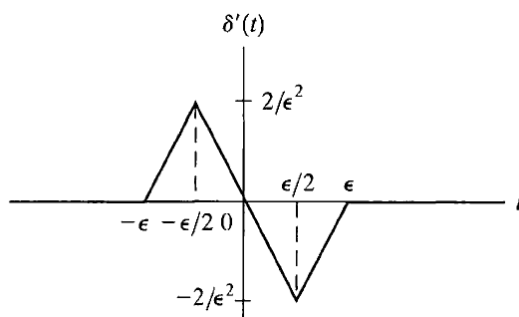
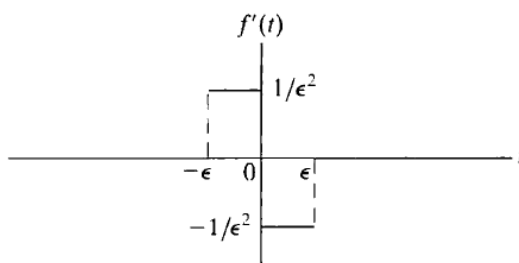


EE233 HW3Oct. 17thDue Date: Oct. 24th

1. Make a sketch of $f(t)$ for $-10s \leq t \leq 30s$ when $f(t)$ is given as follows.

$$f(t) = (10t - 100)u(t + 10) - (10t + 50)u(t + 5) + (50 - 10t)u(t - 5) \\ - (150 - 10t)u(t - 15) + (10t - 250)u(t - 25) - (10t - 300)u(t - 30)$$

2. The triangular pulses shown in below figure P.2.a are equivalent to the rectangular pulses in figure P.2.b, because they both enclose the same area $1/\epsilon$, and they both approach infinity proportional to $1/\epsilon^2$ as $\epsilon \rightarrow 0$. Use this triangular pulse representation for $\delta'(t)$ to find the Laplace transform of $\delta''(t)$.

**Figure P.2.a****Figure P.2.b**

3. (a) Find the Laplace transform of the function illustrated in figure below.
 (b) Find the Laplace transform of the first derivative of the function illustrated in the

figure below.

(c) Find the Laplace transform of the second derivative of the function illustrated in the figure below.

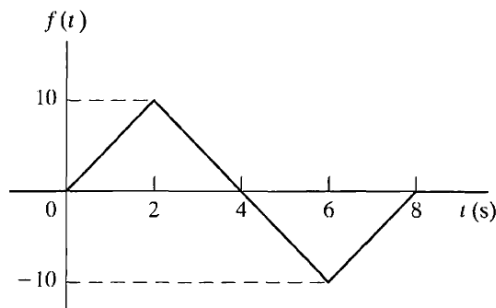


Figure P.3

4. The switch in the circuit in figure below has been in position a for a long time. At $t = 0$, the switch moves instantaneously to position b.
- Derive the integrodifferential equation that governs the behavior of the voltage v_o for $t \geq 0^+$.
 - Show that:

$$V_o(s) = \frac{V_{dc} \left[s + \left(\frac{R}{L} \right) \right]}{\left[s^2 + \left(\frac{R}{L} \right) s + \left(\frac{1}{LC} \right) \right]}$$

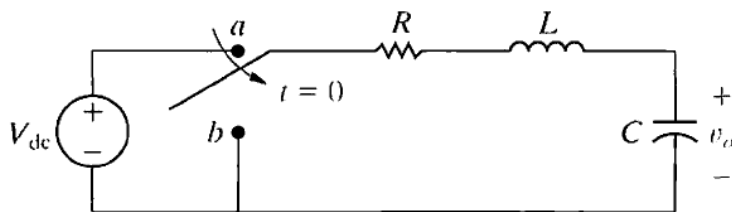
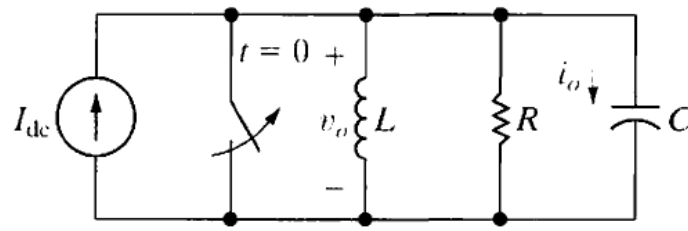


Figure P.4

5. The circuit parameters in the circuit in below figure have the following values:

$$R = 1k\Omega, L = 12.5H, C = 2\mu F, I_{dc} = 30mA$$

- Find $v_o(t)$ for $t \geq 0$.
- Find $i_o(t)$ for $t \geq 0$.
- Does your solution for $i_o(t)$ make sense when $t=0$? Explain.

**Figure P.5**