


EE233 HW5 Solution

Oct. 31stDue Date: Nov. 7th

Textbook problems: P.13.28, P.13.55

P.13.28 Solution:

(a)

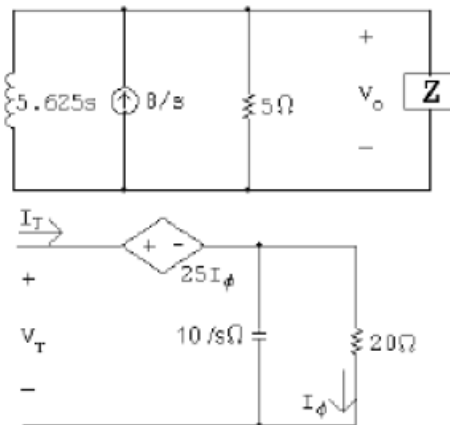

$$i_L(0^-) = i_L(0^+) = \frac{24}{3} = 8A : \text{directed upward}$$

$$V_T = 25I_\phi + \frac{20(10/s)}{20 + (10/s)} I_T = \frac{25(10/s)I_T}{20 + (10/s)} + \frac{200}{10 + 20s} I_T$$

$$\frac{V_T}{I_T} = \frac{45}{2s+1}$$

then,

$$\frac{V_o}{5} + \frac{V_o(2s+1)}{45} + \frac{V_o}{5.625s} = \frac{8}{s}$$

simplifying

$$V_o = \frac{180}{s^2 + 5s + 4}$$


(b)

$$V_o = \frac{180}{s^2 + 5s + 4} = \frac{60}{s+1} - \frac{60}{s+4}$$

$$v_o(t) = [60e^{-t} - 60e^{-4t}]u(t) [\text{Volt}]$$

P.13.55 Solution:

(a)

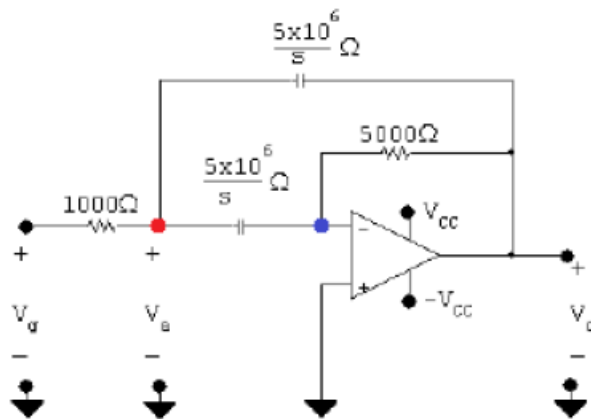

$$\frac{V_a - V_g}{1000} + \frac{sV_a}{5 \times 10^6} + \frac{s(V_a - V_o)}{5 \times 10^6} = 0 \text{ at node red}$$

$$5000V_a - 5000V_g + 2sV_a - sV_o = 0$$

$$(5000 + 2s)V_a - sV_o = 5000V_g$$

$$\frac{s(0 - V_a)}{5 \times 10^6} + \frac{0 - V_o}{5000} = 0 \text{ at node blue}$$

$$V_a = \frac{-1000}{s} V_o$$

By plugging the result at node blue to the equation at node red,

$$(2s + 5000) \left(\frac{-1000}{s} \right) V_o - sV_o = 5000V_g$$

$$1000V_o(2s + 5000) + s^2V_o = -5000sV_g$$

$$V_o(s^2 + 2000s + 5 \times 10^6) = -5000sV_g$$

$$\frac{V_o}{V_g} = \frac{-5000s}{s^2 + 2000s + 5 \times 10^6}$$

$$s_{1,2} = -1000 \pm \sqrt{10^6 - 5 \times 10^6} = -1000 \pm j2000$$

$$\frac{V_o}{V_g} = \frac{-5000s}{(s + 1000 - j2000)(s + 1000 + j2000)}$$

(b)


$$z_1 = 0, p_1 = 1000 - j2000, p_2 = 1000 + j2000$$

1. A $1\text{ k}\Omega$ resistor is in series with a 625 nF capacitor. This series combination is in parallel with a 100 mH inductor.

- (a) Express the equivalent s-domain impedance of these parallel branches as a rational function.
 (b) Determine the numerical values of the poles and zeros.

Solution:

(a)

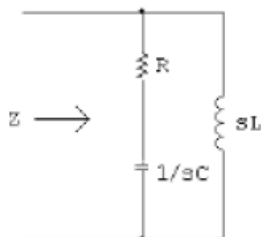

$$Z = \frac{(R + 1/sC)(sL)}{R + sL + (1/sC)} = \frac{(Rs)(s + 1/RC)}{s^2 + (R/L)s + (1/LC)}$$

So, plugging in the values,

$$Z = \frac{1000s(s + 1600)}{s^2 + 10000s + 16 \times 10^6}$$

(b)

$$Z = \frac{1000s(s + 1600)}{(s + 2000)(s + 8000)}$$

$$z_1 = 0, \quad z_2 = 1600 \text{ rad/s}$$

$$p_1 = 2000 \text{ rad/s}, \quad p_2 = 8000 \text{ rad/s}$$

2. The switch in the circuit in Figure P.2 has been closed for a long time before opening at $t = 0$.

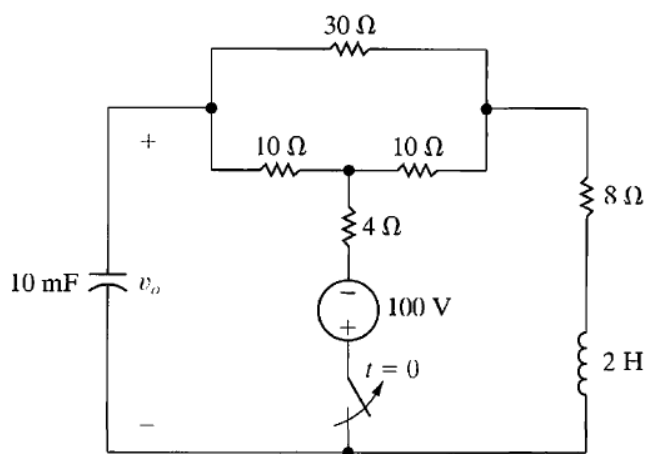


Figure P.2.a

(a) Construct the s-domain equivalent circuit for $t > 0$.


(b) Find V_o

(c) Find v_o for $t \geq 0$.

Solution:

(a)

For $t < 0$:

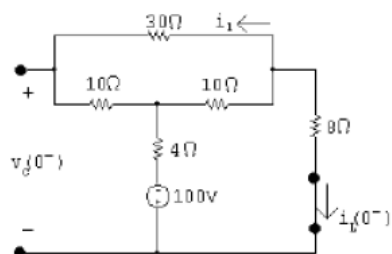


$$i_L(0^-) = \frac{-100}{4 + 10 \parallel 40 + 8} = \frac{-100}{20} = -5A$$

$$i_1 = \frac{10}{50} \times 5 = 1A$$

$$v_c(0^-) = 10 \times 1 + 4 \times 5 - 100 = -70V$$

For $t > 0$:

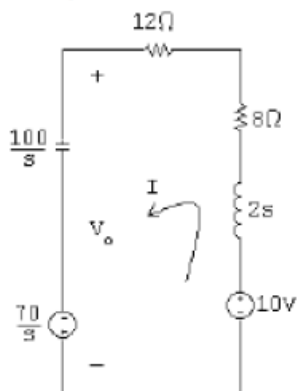

(b)

$$(20 + 2s + \frac{100}{s})I = 10 + \frac{70}{s}$$

$$\text{so, } I = \frac{5(s+7)}{s^2 + 10s + 50}$$

$$V_o = \frac{100}{s} I - \frac{70}{s} = \frac{-70(s+20/7)}{s^2 + 10s + 50} = \frac{K}{s+5-j5} + \frac{K^*}{s+5+j5}$$

$$\text{where } K = 38.1 \angle -156.8^\circ$$

$$(c) \quad v_o(t) = 76.2e^{-5t} \cos(5t - 156.8^\circ)u(t) [\text{Volt}]$$

3. There is no energy stored in the circuit in figure P.3 at $t = 0^-$.

(a) Find V_o

(b) Find v_o

(c) Does your solution for v_o make sense in terms of known circuit behavior? Explain.


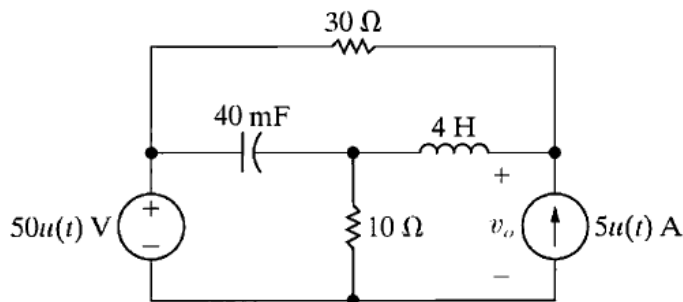


Figure P.3

Solution:

(a)

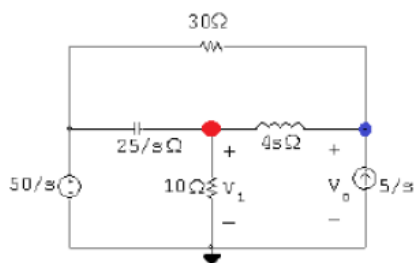

$$\frac{V_1}{10} + \frac{V_1 - 50/s}{25/s} + \frac{V_1 - V_0}{4s} = 0$$

$$\frac{-5}{s} + \frac{V_0 - V_1}{4s} + \frac{V_0 - 50/s}{30} = 0$$

Then,

$$(4s^2 + 10s + 25)V_1 - 25V_0 = 200s$$

$$-15V_1 + (2s + 15)V_0 = 400$$

Then, solve for V_0 ,

$$V_0 = \frac{200(8s^2 + 35s + 50)}{8s(s+5)^2}$$

$$V_0 = \frac{200(8s^2 + 35s + 50)}{8s(s+5)^2} = \frac{K_1}{s} + \frac{K_2}{(s+5)^2} + \frac{K_3}{(s+5)}$$

$$K_1 = 50, K_2 = -375, K_3 = 150$$


So,

$$V_0 = \frac{50}{s} - \frac{375}{(s+5)^2} + \frac{150}{(s+5)}$$


(b)

$$v_o(t) = [50 - 375te^{-5t} + 150e^{-5t}]u(t) [\text{Volt}]$$

(c)

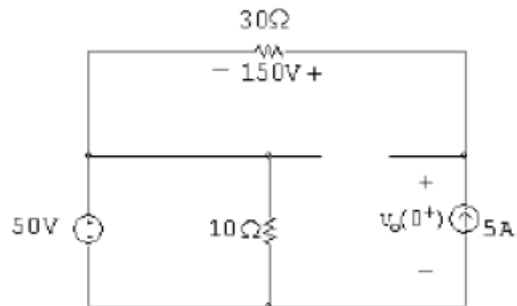At $t = 0^+$:

$$v_o(0^+) = 50 + 150 = 200[\text{Volt}]$$

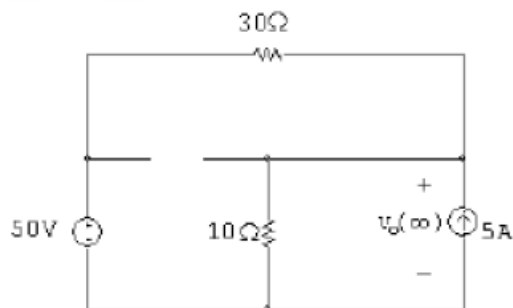At $t = \infty$:

$$\frac{v_o(\infty)}{10} - 5 + \frac{v_o(\infty) - 50}{30} = 0$$

$$3v_o(\infty) - 150 + v_o(\infty) - 50 = 0$$

$$\text{so, } v_o(\infty) = 50[\text{Volt}]$$