

# EE 233 Homework8 solution

Autumn 2016

November 30, 2016

## 1 Problem 15.28

(a) The lower cutoff frequency will belong to the high pass stage, and the upper cut off to the low pass stage. For the high pass:

$$H(s) = \frac{S}{S + 1/R_H C_H}$$

where  $\omega_{C_H} = \frac{1}{R_H C_H}$

$$R_H = 1/(2\pi f_H C_H) = 1/(2\pi \times 200 \times 50nF) = 15.9k\Omega$$

For the low pass:

$$H(S) = \frac{1/R_L C_L}{S + 1/R_L C_L}$$

where  $\omega_{C_L} = \frac{1}{R_L C_L}$

$$R_L = 1/(2\pi f_L C_L) = 1/(2\pi \times 2000 \times 50nF) = 1.59k\Omega$$

The bandpass filter gain is 20dB, which means

$$K = R_f/R_i = 10$$

The designed bandpass filter is shown below:

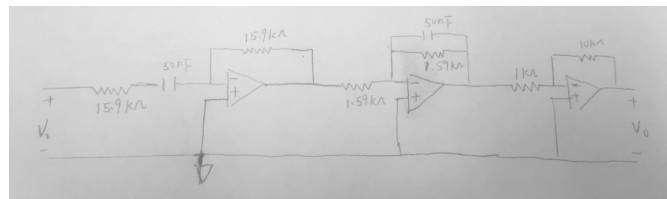


Figure 1: bandpass filter for problem 15.28

(b) Combining the 2 stages gives:

$$H(s) = 10 \cdot \frac{s}{s + 1/R_H C_H} \cdot \frac{1/R_L C_L}{s + 1/R_L C_L}$$

$$H(s) = 10 \cdot \frac{s}{s + 2\pi(200)} \cdot \frac{2\pi(2000)}{s + 2\pi(5000)} = \frac{40000\pi s}{(s + 400\pi)(s + 4000\pi)}$$

(c)

$$\omega_0 = \sqrt{\omega_{C_1}\omega_{C_2}} = \sqrt{400\pi \cdot 4000\pi} = 3973.8 \text{ rad/s}$$

$$H(j\omega) = \frac{jw(40000\pi)}{(jw + 400\pi)(jw + 4000\pi)}$$

$$\begin{aligned} H(j\omega_0) &= \frac{(40000\pi)(3973.8\angle 90^\circ)}{(3973.8j + 400\pi)(3973.8j + 4000\pi)} \\ &= \frac{(40000\pi)(3973.8\angle 90^\circ)}{(4167.8\angle 72.45^\circ)(13179.7\angle 17.55^\circ)} \\ &= 9.091\angle 0^\circ \end{aligned}$$

(d)  $\text{gain} = 20\log(9.091) = 19.17 \text{ dB}$

(e) The graph is shown below:

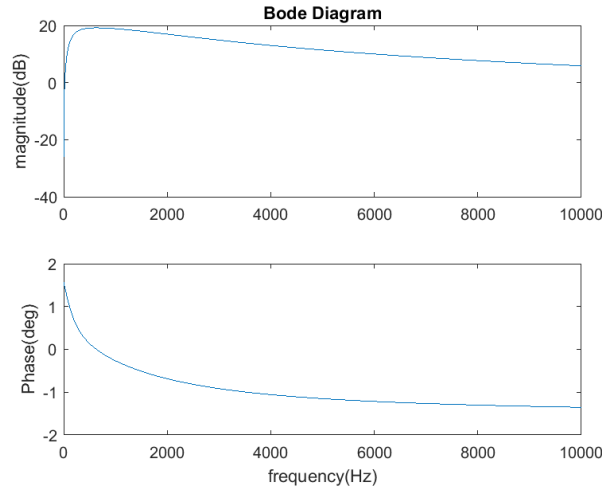


Figure 2: Bode diagram plot for problem 15.28

## 2 Problem 15.45

From Problem 15.44, you just need to find the order of the low pass filter and high pass filter.

$$\text{HPF: } \text{slope} = \frac{40}{\log(200/40)} = 57.23 \text{ dB/dec} \therefore n = 3$$

$$\text{LPF: } \text{slope} = \frac{-40}{\log(12500/2500)} = -57.23 \text{ dB/dec} \therefore n = 3$$

P15.45 (a) Unscaled high-pass stage

$$H_{hp}(s) = \frac{s^3}{(s + 1)(s^2 + s + 1)}$$

The frequency scaling factor is  $k_f = (\omega'_0/\omega_0) = 400\pi$ . Therefore the scaled transfer function is

$$H'_{hp}(s) = \frac{(s/400\pi)^3}{(s/400\pi + 1)[(s/400\pi)^2 + s/400\pi + 1]} = \frac{s^3}{(s + 400\pi)(s^2 + 400\pi s + 400^2\pi^2)}$$

Unscaled low-pass stage:

$$H_{hp}(s) = \frac{1}{(s + 1)(s^2 + s + 1)}$$

The frequency scaling factor is  $k_f = (\omega'_0/\omega_0) = 5000\pi$ . Therefore the scaled transfer function is

$$H'_{lp}(s) = \frac{1}{(s/5000\pi + 1)[(s/5000\pi)^2 + s/5000\pi + 1]} = \frac{(5000\pi)^3}{(s + 5000\pi)(s^2 + 5000\pi s + 25 \times 10^6\pi^2)}$$

Thus the transfer function for the filter is

$$H'(s) = 100H'_{hp}(s)H'_{lp}(s) = \frac{125 \times 10^{11}\pi^3 s^3}{D_1 D_2 D_3 D_4}$$

where

$$\begin{aligned} D_1 &= s + 400\pi \\ D_2 &= s + 5000\pi \\ D_3 &= s^2 + 400\pi s + 16 \times 10^4\pi^2 \\ D_4 &= s^2 + 5000\pi s + 25 \times 10^6\pi^2 \end{aligned}$$

(b) at 40 Hz,  $\omega = 80\pi \text{ rad/s}$

$$\begin{aligned} D_1(j80\pi) &= 80\pi(5 + j) \\ D_2(j80\pi) &= 80\pi(62.5 + j) \\ D_3(j80\pi) &= 3.2 \times 10^4\pi^2(4.8 + j) \\ D_4(j80\pi) &= 4 \times 10^5\pi^2(62.484 + j) \end{aligned}$$

Therefore

$$\begin{aligned} D_1 D_2 D_3 D_4(j80\pi) &= 8.192 \times 10^{13}\pi^6(97659.4 \angle 24.91^\circ) \\ H'(j80\pi) &= \frac{(125\pi^3 \times 10^{11})(512000\pi^3 \angle -90^\circ)}{8.192 \times 10^{13}\pi^6(97659.4 \angle 24.91^\circ)} = 0.8 \angle -114.91^\circ \\ \therefore \text{gain} &= 20 \log_{10}(|H'(j80\pi)|) = 20 \log_{10}(0.8) = -1.94 \text{ dB} \end{aligned}$$

at 1000Hz,  $\omega = 2000\pi \text{ rad/s}$  Then

$$\begin{aligned} D_1(j2000\pi) &= 400\pi(1 + 5j) \\ D_2(j2000\pi) &= 2000\pi(2.5 + j) \\ D_3(j2000\pi) &= 8 \times 10^5\pi^2(-4.8 + j) \\ D_4(j2000\pi) &= 10^7\pi^2(2.1 + j) \end{aligned}$$

$$\begin{aligned}
D_1 D_2 D_3 D_4(j2000\pi) &= 64 \times 10^{17} \pi^6 (156.575\angle - 65.81^\circ) \\
H'(j2000\pi) &= \frac{(125\pi^3 \times 10^{11})(8 \times 10^9 \pi^3 \angle - 90^\circ)}{64 \times 10^{17} \pi^6 (156.575\angle - 65.81^\circ)} = 99.79\angle - 24.19^\circ \\
\therefore gain &= 20 \log_{10}(|H'(j2000\pi)|) = 20 \log_{10}(99.79) = 39.98 \text{ dB}
\end{aligned}$$

(c) From the transfer function the gain is down 39.98+ 1.94 or 41.92 dB at 40 Hz, which is greater than 40 dB. 1000 Hz is in the passband for this bandpass filter. Hence we expect the gain at 1000 Hz to nearly equal 40 dB as specified in problem 15.44. Thus our scaled transfer function confirms that the filter meets the specifications.

Problem 15.53

From 15.50 we have something like

$$H(s) = \frac{-Kb_o}{s^2 + b_1s + b_o}$$

$$\text{where } K = \frac{G_1}{G_2}; \quad b_o = \frac{G_2G_3}{C_1C_2} \quad G_i = \frac{1}{R_i}$$

$$\text{and } b_1 = \frac{G_1 + G_2 + G_3}{C_2}$$

Rearranging we see that

$$G_1 = KG_2$$

$$G_3 = \frac{b_oC_1C_2}{G_2} = \frac{b_oC_1}{G_2}$$

since by hypothesis  $C_2 = 1 \text{ F}$

$$b_1 = \frac{G_1 + G_2 + G_3}{C_2} = G_1 + G_2 + G_3$$

$$\therefore b_1 = KG_2 + G_2 + \frac{b_oC_1}{G_2}$$

$$b_1 = G_2(1 + K) + \frac{b_oC_1}{G_2}$$

Solving this quadratic equation for  $G_2$  we get

$$\begin{aligned} G_2 &= \frac{b_1}{2(1+K)} \pm \sqrt{\frac{b_1^2 - b_oC_14(1+K)}{4(1+K)^2}} \\ &= \frac{b_1 \pm \sqrt{b_1^2 - 4b_o(1+K)C_1}}{2(1+K)} \end{aligned}$$

For  $G_2$  to be realizable

$$C_1 < \frac{b_1^2}{4b_o(1+K)}$$

From Problem 15.52 we have

$$\begin{aligned} H(s) &= \frac{\frac{-C_1}{C_2}s^2}{\left[s^2 + \frac{G_1}{C_2C_3}(C_1 + C_2 + C_3)s + \frac{G_1G_2}{C_2C_3}\right]} \\ &= \frac{-Ks^2}{s^2 + b_1s + b_o} \end{aligned}$$

Therefore the circuit implements a second-order high-pass filter with a passband gain of  $C_1/C_2$ .

$$C_1 = K: \quad (\text{Choose } C_1 = K, C_2 = 1, C_3 = 1)$$

$$b_1 = \frac{G_1}{(1)(1)}(K + 2) = G_1(K + 2)$$

$$\therefore G_1 = \frac{b_1}{K + 2}; \quad R_1 = \left(\frac{K + 2}{b_1}\right)$$

$$b_o = \frac{G_1G_2}{(1)(1)} = G_1G_2$$

$$\therefore G_2 = \frac{b_o}{G_1} = \frac{b_o}{b_1}(K + 2)$$

$$\therefore R_2 = \frac{b_1}{b_o(K + 2)}$$

problem 1533 [a] low-pass filter

$$\text{slope} = \frac{-24}{\log(2k/1k)} = -79.726 \text{ dB/dec} \therefore n=4$$

In the first prototype second-order section: <sup>weset</sup>  $b_1 = 0.765$ ,  $b_0 = 1$ ,  $C_2 = 1 \text{ F}$ ,  $k=1$   
then we can determine  $R_1, R_2, R_3, C_1, C_2$

$$C_1 \leq \frac{b_1^2}{4b_0(1+k)} \leq \frac{(0.765)^2}{4(1+1)} \leq 0.0732$$

choose  $C_1 = 0.03 \text{ F}$

$$G_2 = \frac{0.765 \pm \sqrt{(0.765)^2 - 4(2)(0.03)}}{4} = \frac{0.765 \pm 0.588}{4}$$

Arbitrarily select the larger value for  $G_2$ , then

$$G_2 = 0.338 \text{ S} \therefore R_2 = \frac{1}{G_2} = 2.96 \Omega$$

$$G_1 = kG_2 = G_2 = 0.338 \text{ S} \therefore R_1 = \frac{1}{G_1} = 2.96 \Omega$$

$$G_3 = \frac{b_0 C_1}{G_2} = \frac{1(0.03)}{0.338} = 0.089 \therefore R_3 = 1/G_3 = 11.3 \Omega$$

\* Therefore in the first second order prototype circuit

$$R_1 = R_2 = 2.96 \Omega \quad R_3 = 11.3 \Omega$$

$$C_1 = 0.03 \text{ F} \quad C_2 = 1 \text{ F}$$

in the second second-order prototype circuit; weset

$$b_1 = 1.848 \quad b_0 = 1 \quad C_2 = 1 \text{ F}$$

$$\therefore C_1 \leq \frac{(1.848)^2}{8} \leq 0.427$$

choose  $C_1 = 0.30 \text{ F}$

$$G_2 = \frac{1.848 \pm \sqrt{1.848^2 - 8 \times 0.3}}{4} = \frac{-1.848 \pm 1.008}{4}$$

\* Arbitrarily select the larger value, then

$$G_2 = 0.7139 \text{ S} \therefore R_2 = \frac{1}{G_2} = 1.4008 \Omega$$

$$G_1 = kG_2 = 0.7139 \text{ S} \therefore R_1 = \frac{1}{G_1} = 1.4008 \Omega$$

$$G_3 = \frac{b_0 C_1}{G_2} = \frac{(1) \times (0.30)}{0.7139} = 0.4202 \text{ S} \therefore R_3 = 1/G_3 = 2.3796 \Omega$$

In the low-pass section of the filter

$$K_f = \frac{W_0'}{W_0} = 2\pi(1000) = 2000\pi$$

$$K_m = \frac{C}{C' K_f} = \frac{1}{(25 \times 10^{-9}) K_f} = \frac{2 \times 10^4}{\pi}$$

Therefore in the first scaled second-order section

$$R_1' = R_2' = 2.96 K\Omega = 18.8 K\Omega$$

$$R_3' = 11.3 K\Omega = 71.9 K\Omega$$

$$C_1' = \frac{0.03}{K_f K_m} = \frac{0.03}{4 \times 10^7} = 7.5 \times 10^{-10} F = 750 pF$$

$$C_2' = 25 nF \quad (\text{this is the value supplied in problem})$$

In the second scaled second-order section

$$R_1' = R_2' = 1.4008 K\Omega = 8.9 K\Omega \quad R_3' = 2.38 K\Omega = 15.1 K\Omega$$

$$C_1' = \frac{0.3}{K_f K_m} = 7.5 nF \quad C_2'' = 25 nF$$

\* High-pass filter selection:

$$\text{slope} = \frac{-24}{\log(8K/4K)} = -79.7 \text{ dB/dec} \quad \therefore n=4$$

In the first prototype second-order section, we select

$$b_1 = 0.765; b_0 = 1. \quad C_2 = C_3 = 1 F = C_1, \quad K=1$$

$$R_1 = \frac{K+2}{b_1} = \frac{3}{0.765} = 3.92 \Omega \quad R_2 = \frac{b_1}{b_0(K+2)} = \frac{0.765}{3} = 0.255 \Omega$$

In the second prototype second-order filter section, we set  $b_1 = 1.848, b_0 = 1$ ;

$$C_2 = C_3 = 1 F = C_1 \quad K=1 F$$

$$R_1 = \frac{K+2}{b_1} = \frac{3}{1.848} = 1.623 \Omega \quad R_2 = \frac{b_1}{b_0(K+2)} = \frac{1.848}{3} = 0.616 \Omega$$

In the high-pass section of the filter, we still do scaling.

$$K_f = \frac{W_0'}{W_0} = 2\pi(8000) = 16000\pi$$

$$K_m = \frac{C}{C' K_f} = \frac{1}{(25 \times 10^{-9}) \times (16000\pi)} = \frac{795.77}{\pi}$$



In the first scaled second-order section

$$R_1' = \frac{3.92 \text{ km}}{1.623} = 2419.94 \Omega$$

$$R_2' = 0.255 \text{ km} = 255 \Omega$$

$$C_1' = C_2' = C_3' = 25 \text{ nF}$$

In the second scaled second-order section

$$R_1' = 1.623 \text{ km} = 1623 \Omega$$


$$R_2' = 0.616 \text{ km} = 616 \Omega$$

$$C_1' = C_2' = C_3' = 10 \text{ nF}$$

\* In the gain section, since we want the gain to be 20 dB

so we can choose  $R_i = 1 \text{ k}\Omega$  and  $R_f = 10 \text{ k}\Omega$

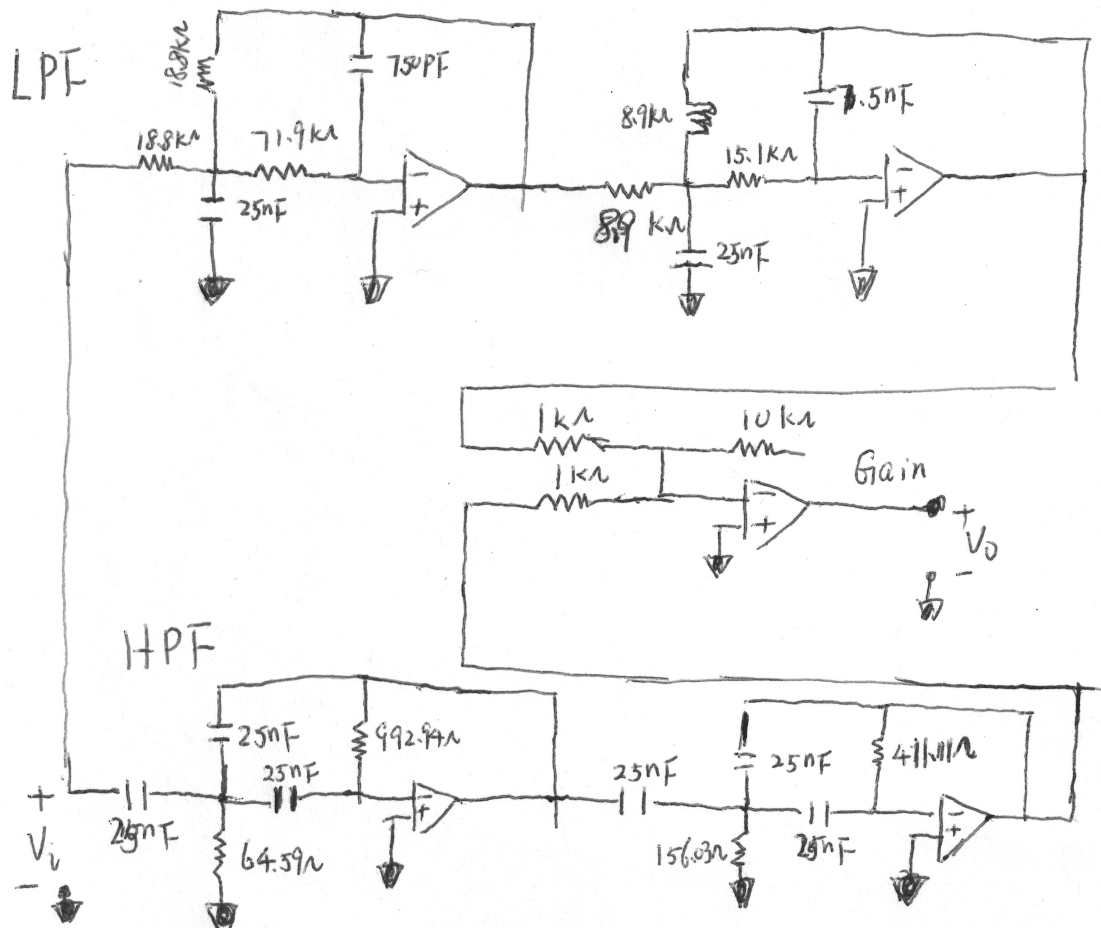[b] the circuit is shown below, we have low pass filter and high-pass filter in parallel, and each filter has two cascading second-order filter.



15.55 (a) At low frequencies the capacitors can be thought of as open circuits, and the gain of the circuit is approximately 1. At high frequencies, the capacitors will act like short circuits, and the outputs will be zero. So the circuit acts like a unity gain low pass filter.

(b) Node A is to the right of  $R_1$  and Node B is to the right of  $R_2$ . Node A:

$$\begin{aligned}
 0 &= \frac{V_a - V_{in}}{R_1} + \frac{V_a - V_{out}}{\frac{1}{SC_1}} \\
 &= \frac{V_a - V_{in}}{R_1} + (V_a - V_{out})SC_1 \\
 &= \frac{V_a}{R_1} - \frac{V_{in}}{R_1} + V_a(SC_1) - V_{out}(SC_1) \\
 V_a(SC_1 + \frac{1}{R_1}) - \frac{V_{in}}{R_1} &= V_{out}(SC_1)
 \end{aligned}$$

Node B:

$$\begin{aligned}
 0 &= \frac{V_b - V_a}{R_2} + \frac{V_b}{\frac{1}{SC_2}}, (V_b = V_{out}) \\
 &= \frac{V_b}{R_2} - \frac{V_a}{R_2} + V_b(SC_2) \\
 \frac{V_a}{R_2} &= V_b(SC_2 + \frac{1}{R_2}) \\
 V_a &= V_b(SR_2C_2 + 1) \\
 &= V_{out}(SR_2C_2 + 1)
 \end{aligned}$$

$$\begin{aligned}
 V_{out}(SC_1) &= V_{out}(SC_2R_2 + 1)(SC_1 + \frac{1}{R_1}) - \frac{V_{in}}{R_1} \\
 V_{out}(SC_1R_1) &= V_{out}(SC_2R_2 + 1)(SC_1R_1 + 1) - V_{in} \\
 V_{in} &= V_{out}[S^2C_2R_2C_1R_1 + SC_1R_1 + SC_2R_2 + 1] - V_{out}(SC_1R_1) \\
 V_{in} &= V_{out}[S^2C_2R_2C_1R_1 + SC_1R_1 + SC_2R_2 + 1 - SC_1R_1] \\
 V_{in} &= V_{out}[S^2C_2R_2C_1R_1 + SC_2R_2 + 1] \\
 \frac{V_{out}}{V_{in}} &= \frac{1}{S^2C_2R_2C_1R_1 + SC_2R_2 + 1} \\
 &= \frac{\frac{1}{R_2R_1C_2C_1}}{S^2 + S(\frac{1}{R_1C_1} + \frac{1}{R_1R_2C_2C_1})} \\
 &= \frac{b_0}{S^2 + b_1S + b_0}
 \end{aligned}$$

Or written with  $G_1 = \frac{1}{R_1}$ ,  $G_2 = \frac{1}{R_2}$ ,

$$\frac{\frac{G_1G_2}{C_1C_2}}{S^2 + S(\frac{G_1}{C_1}) + \frac{G_1G_2}{C_1C_2}}$$

(c) There are 2 restraints from  $b_0$ , and  $b_1$ , and 4 circuit components. This gives a total of 2 free choices.

(d) From inspection, we see  $b_1 = \frac{G_1}{C_1}$  and  $b_0 = \frac{G_1G_2}{C_1C_2}$

(e) No, all physically realizable capacitors yield physically realizable resistors.

(f)

$$\begin{aligned}\frac{V_{out}}{V_{in}} &= \frac{\frac{1}{R_2 R_1 C_2 C_1}}{S^2 + S\left(\frac{1}{R_1 C_1} + \frac{1}{R_1 R_2 C_2 C_1}\right)} \\ &= \frac{b_0}{S^2 + b_1 S + b_0}\end{aligned}$$

The corner frequency in radians per second is  $\sqrt{\frac{1}{R_1 R_2 C_1 C_2}} = \sqrt{b_0}$  and the pass band gain is 1. So there must be a relationship between  $b_1$  and  $b_0$  for a gain of 1 at the corner frequency.

$$H(j\omega) = \frac{b_0}{(j\omega)^2 + j\omega b_1 + b_0}$$

If we take the magnitude and set it equal to 1,


$$1 = |H(j\omega)| = \frac{b_0}{\sqrt{(b_0 - \omega_0^2)^2 + (\omega_0 b_1)^2}}$$

Substitute  $\omega_0 = \sqrt{b_0}$

$$\begin{aligned}1 &= \frac{b_0}{\sqrt{(b_0 - b_0)^2 + (\sqrt{b_0} b_1)^2}} \\ &= \frac{b_0}{\sqrt{(b_0 b_1^2)}} \\ &= \frac{1}{b_1} \cdot \frac{b_0}{\sqrt{b_0}} \\ &= \frac{\sqrt{b_0}}{b_1}\end{aligned}$$

So  $b_1 = \sqrt{b_0}$  for gain at corner frequency equal to passband gain 1.  $b_0 = (20,000)^2$  so  $b_1 = 20,000$ . This means we can set  $R_1 = R_2$  and  $C_1 = C_2$ ,

$$\begin{aligned}\omega_0 &= 1/RC, \text{ Let's choose } c = 10nF. \\ R &= \frac{1}{\omega_0 C} = \frac{1}{(20000)(10nF)} = 5k\Omega.\end{aligned}$$

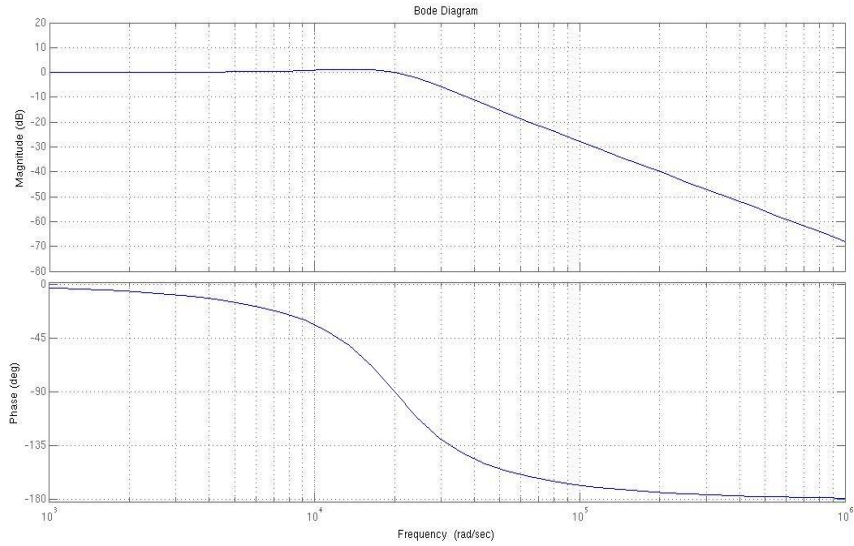

Problem 1

[a]  $\text{slope} = \frac{-48}{\log\left(\frac{32}{8}\right)} = -79.72 \text{ dB/dec} \quad \therefore n = 4$

From Table 15.1 the transfer function is

$$H(s) = \frac{1}{(s^2 + 0.765s + 1)(s^2 + 1.848s + 1)}$$

The capacitor values for the first stage prototype circuit are

$$\frac{2}{C_1} = 0.765 \quad \therefore C_1 = 2.61 \text{ F}$$

$$C_2 = \frac{1}{C_1} = 0.38 \text{ F}$$

The values for the second stage prototype circuit are

$$\frac{2}{C_1} = 1.848 \quad \therefore C_1 = 1.08 \text{ F}$$

$$C_2 = \frac{1}{C_1} = 0.92 \text{ F}$$

The scaling factors are

$$k_m = \frac{R'}{R} = 1000; \quad k_f = \frac{\omega'_o}{\omega_o} = 16,000\pi$$

Therefore the scaled values for the components in the first stage are

$$R_1 = R_2 = R = 1000 \Omega$$

$$C_1 = \frac{2.61}{(16,000\pi)(1000)} = 52.01 \text{ nF}$$

$$C_2 = \frac{0.38}{(16,000\pi)(1000)} = 7.61 \text{ nF}$$

The scaled values for the second stage are

$$R_1 = R_2 = R = 1000 \Omega$$

$$C_1 = \frac{1.08}{(16,000\pi)(1000)} = 21.53 \text{ nF}$$

$$C_2 = \frac{0.92}{(16,000\pi)(1000)} = 18.38 \text{ nF}$$

[b]

