

## EE233 HW1 Solution

Oct. 3rd

Due Date: Oct. 10th

Problems from the textbook: P.9.49, P.9.59, and P.9.60

1. At  $t = -2\text{ms}$ , a sinusoidal voltage is known to be zero and going positive. The voltage is next zero is  $t = 8\text{ms}$ . It is also known that the voltage is  $80.9\text{V}$  at  $t = 0\text{ms}$ .
  - a) What is the frequency of voltage  $v$  in hertz?

$$\frac{T}{2} = 8 + 2 = 10 \text{ ms}; \quad T = 20 \text{ ms}$$

$$f = \frac{1}{T} = \frac{1}{20 \times 10^{-3}} = 50 \text{ Hz}$$

- b) What is the expression for  $v$ ?

$$v = V_m \sin(\omega t + \theta)$$

$$\omega = 2\pi f = 100\pi \text{ rad/s}$$

$$100\pi(-2 \times 10^{-3}) + \theta = 0; \quad \therefore \theta = \frac{\pi}{5} \text{ rad} = 36^\circ$$

$$v = V_m \sin[100\pi t + 36^\circ]$$

$$80.9 = V_m \sin 36^\circ; \quad V_m = 137.64 \text{ V}$$


$$v = 137.64 \sin[100\pi t + 36^\circ] = 137.64 \cos[100\pi t - 54^\circ] \text{ V}$$

2. A  $10 \Omega$  resistor and  $5 \mu\text{F}$  capacitor are connected in parallel. This parallel combination is also in parallel with the series combination of  $8 \Omega$  resistor and a  $300 \mu\text{H}$  inductor. These three parallel branches are driven by a sinusoidal current source whose current is  $922 \cos(20000t + 30^\circ) \text{ A}$ .

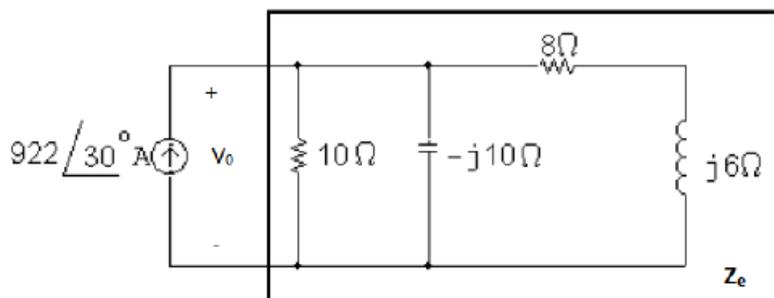a) Draw frequency-domain equivalent circuit.

$$j\omega L = j(2 \times 10^4)(300 \times 10^{-6}) = j6 \Omega$$

$$\frac{1}{j\omega C} = -j \frac{1}{(2 \times 10^4)(5 \times 10^{-6})} = -j10 \Omega; \quad \mathbf{I}_g = 922/30^\circ \text{ A}$$



b) Reference the voltage across the current source as a rise in the direction of the current, and find the phasor voltage.

$$\mathbf{V}_o = 922/30^\circ Z_e$$

$$Z_e = \frac{1}{Y_e}; \quad Y_e = \frac{1}{10} + j\frac{1}{10} + \frac{1}{8 + j6}$$

$$Y_e = 0.18 + j0.04 \text{ S}$$

$$Z_e = \frac{1}{0.18 + j0.04} = 5.42/-12.53^\circ \Omega$$

$$\mathbf{V}_o = (922/30^\circ)(5.42/-12.53^\circ) = 5000.25/17.47^\circ \text{ V}$$

c) Find the steady-state expression for  $v(t)$ .

$$v_o = 5000.25 \cos(2 \times 10^4 t + 17.47^\circ) \text{ V}$$

3. Find the impedance  $Z_{ab}$  in the circuit seen in below. Express  $Z_{ab}$  in both polar and rectangular form.

$$Z_{ab} = 1 - j8 + (2 + j4) \parallel (10 - j20) + (40 \parallel j20)$$

$$= 1 - j8 + 3 + j4 + 8 + j16 = 12 + j12 \Omega = 16.97/45^\circ \Omega$$


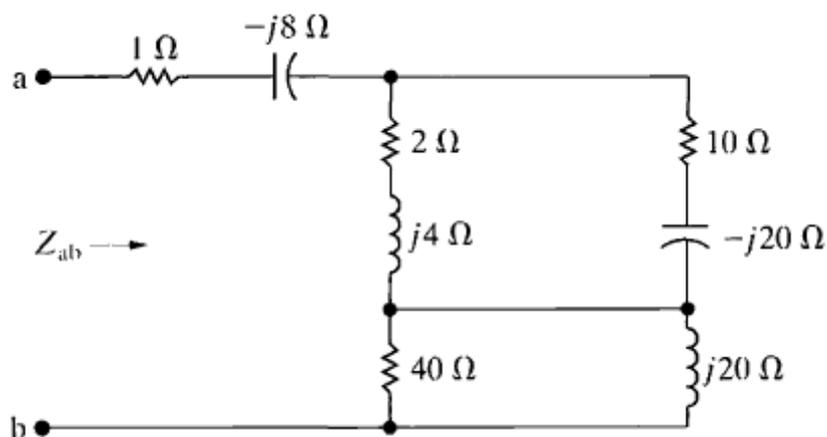


Figure Problem 3

For circuit analysis:

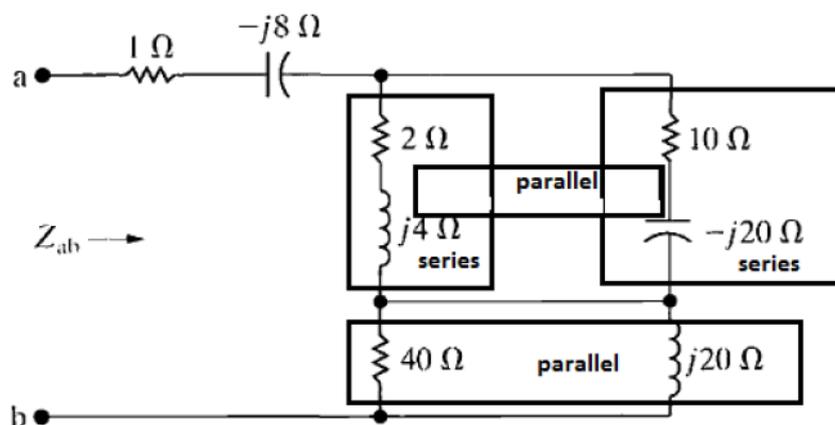

4. Solve:

- a) The frequency of the source voltage in the circuit below is adjusted until  $i_g$  is in phase with  $v_g$ . What is value of  $\omega$  in radian per second?

$$\begin{aligned}
 Z_g &= 500 - j\frac{10^6}{\omega} + \frac{10^3(j0.5\omega)}{10^3 + j0.5\omega} \\
 &= 500 - j\frac{10^6}{\omega} + \frac{500j\omega(1000 - j0.5\omega)}{10^6 + 0.25\omega^2} \\
 &= 500 - j\frac{10^6}{\omega} + \frac{250\omega^2}{10^6 + 0.25\omega^2} + j\frac{5 \times 10^5\omega}{10^6 + 0.25\omega^2}
 \end{aligned}$$

For  $i_g$  to be in phase with  $v_g$ ,  $Z_g$  have to be purely real

$$\therefore \text{ If } Z_g \text{ is purely real, } \frac{10^6}{\omega} = \frac{5 \times 10^5\omega}{10^6 + 0.25\omega^2}$$

- b) If  $v_g = 20 \cos(\omega t)$  [V] where  $\omega$  is the frequency found in part a, what is the steady-state expression for  $v_o$ ?

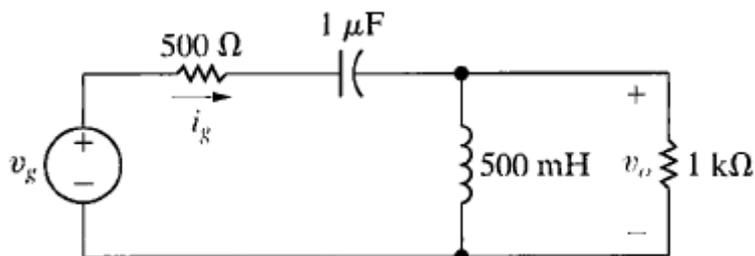


Figure Problem 4

When  $\omega = 2000 \text{ rad/s}$

$$Z_g = 500 - j500 + (j1000 \parallel 1000) = 1000 \Omega$$

$$\therefore \mathbf{I}_g = \frac{20/\underline{0^\circ}}{1000} = 20/\underline{0^\circ} \text{ mA}$$

$$\mathbf{V}_o = \mathbf{V}_g - \mathbf{I}_g Z_1$$


$$Z_1 = 500 - j500 \Omega$$

$$\mathbf{V}_o = 20/\underline{0^\circ} - (0.02/\underline{0^\circ})(500 - j500) = 10 + j10 = 14.14/\underline{45^\circ} \text{ V}$$

$$v_o = 14.14 \cos(2000t + 45^\circ) \text{ V}$$

Problem 9.49

Open circuit voltage:

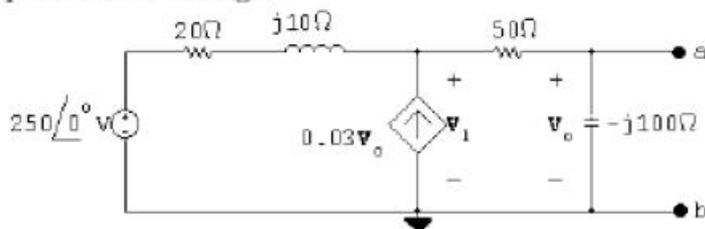


$$\frac{V_1 - 250}{20 + j10} - 0.03V_o + \frac{V_1}{50 - j100} = 0$$

$$\therefore V_o = \frac{-j100}{50 - j100} V_1$$

$$\frac{V_1}{20 + j10} + \frac{j3V_1}{50 - j100} + \frac{V_1}{50 - j100} = \frac{250}{20 + j10}$$

$$V_1 = 500 - j250 \text{ V}; \quad V_o = 300 - j400 \text{ V} = V_{Th}$$


Short circuit current:

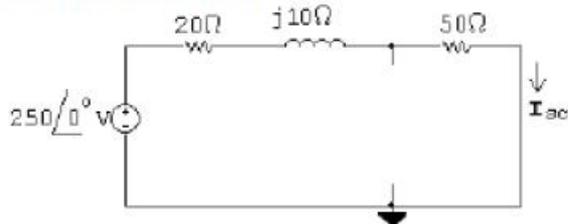


$$I_{sc} = \frac{250\angle 0^\circ}{70 + j10} = 3.5 - j0.5 \text{ A}$$

$$Z_{Th} = \frac{V_{Th}}{I_{sc}} = \frac{300 - j400}{3.5 - j0.5} = 100 - j100 \Omega$$

The Thévenin equivalent circuit:

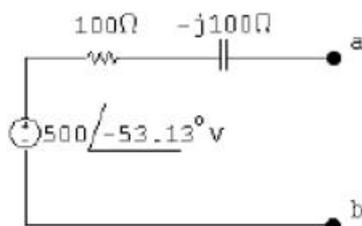

Problem 9.59

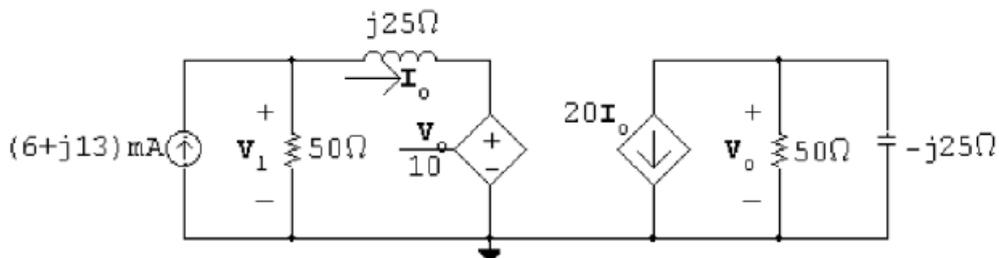

$$\frac{V_o}{50} + \frac{V_o}{-j25} + 20I_o = 0$$

$$(2 + j4)V_o = -2000I_o$$

$$V_o = (-200 + j400)I_o$$

$$I_o = \frac{V_1 - (V_o/10)}{j25}$$


$$\therefore V_1 = (-20 + j65)I_o$$

$$0.006 + j0.013 = \frac{V_1}{50} + I_o = (-0.4 + j1.3)I_o + I_o = (0.6 + j1.3)I_o$$

$$\therefore I_o = \frac{0.6 + j1.3(10 \times 10^{-3})}{(0.6 + j1.3)} = 10 \angle 0^\circ \text{ mA}$$

$$V_o = (-200 + j400)I_o = -2 + j4 = 4.47 \angle 116.57^\circ \text{ V}$$

Problem 9.60

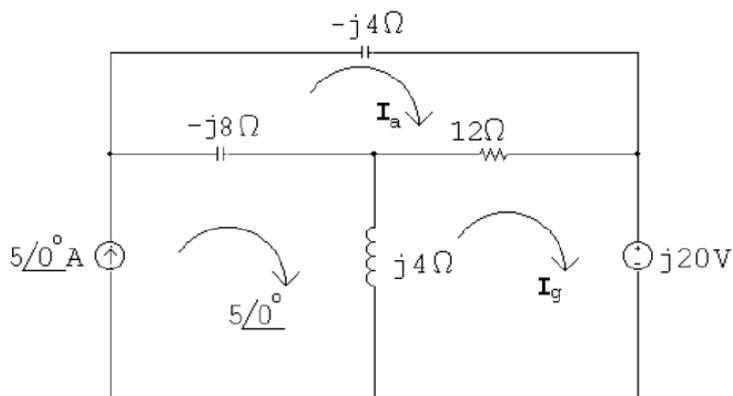

$$(12 - j12)\mathbf{I}_a - 12\mathbf{I}_g - 5(-j8) = 0 \quad (\text{Loop } \mathbf{I}_a)$$

$$-12\mathbf{I}_a + (12 + j4)\mathbf{I}_g + j20 - 5(j4) = 0 \quad (\text{Loop } \mathbf{I}_g)$$

Solving,

$$\mathbf{I}_g = 4 - j2 = 4.47 \angle -26.57^\circ \text{ A}$$