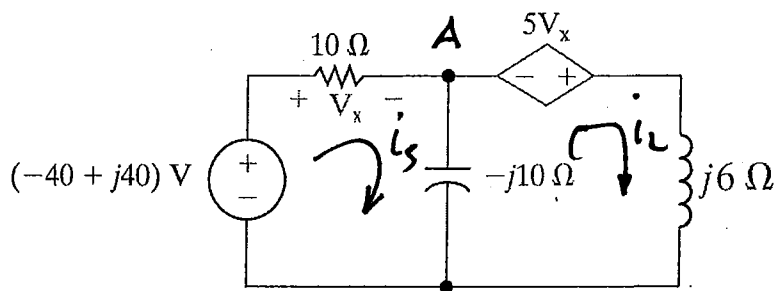


2. For the circuit to the right, calculate the current through the inductor (clockwise) as a phasor (magnitude and phase). (14)



Many possible approaches

Option #1: Use V_x as unknown

$$\sum \Pi_i = 0 = -\frac{V_x}{10\Omega} + \frac{V_s - V_x}{-j10\Omega} + \frac{V_s - V_x + 5V_x}{j6\Omega} \quad \text{where } V_s = (-40 + j40)V = 40\sqrt{2} \angle 135^\circ$$

$$V_x \left[\frac{1}{10} + \frac{j}{10} + \frac{j4}{6} \right] = V_s \left[\frac{j}{10} - \frac{j}{6} \right]$$

$$V_x = \frac{j3 - j5}{3 + j3 + j20} = \left(\frac{-j2}{3 + j23} \right) V_s$$

Note, angle is not -45° which is in wrong quadrant, but has same $\tan^{-1}(\frac{b}{a})$

$$i_L = \frac{V_s + 4V_x}{j6} = \frac{-jV_s}{6} \left[1 + 4 \left(\frac{-j2}{3 + j23} \right) \right] = \frac{V_s [23 - j3 - 8]}{6(3 + j23)}$$

$$= \frac{V_s [15 - j3]}{6(3 + j23)} = \frac{40\sqrt{2} \angle 135^\circ (5 - j)}{6 + j46} = \frac{40\sqrt{2} \sqrt{26} \angle 135^\circ - 11.3^\circ}{\sqrt{6^2 + 46^2}} \angle 82.6^\circ$$

$$= \underline{\underline{6.22 \angle 41.1^\circ}}$$

Option #2: Loop currents

$$V_x = 10 i_s$$

$$\text{Loop 1: } -(-40 + j40) + 10 i_s + (-j10)(i_s - i_L) = 0$$

$$\text{Loop 2: } -5V_x + j6 i_L + (-j10)(i_L - i_s) = 0$$

Eliminate V_x and i_s to get $i_L = 6.22 \angle 41.1^\circ$