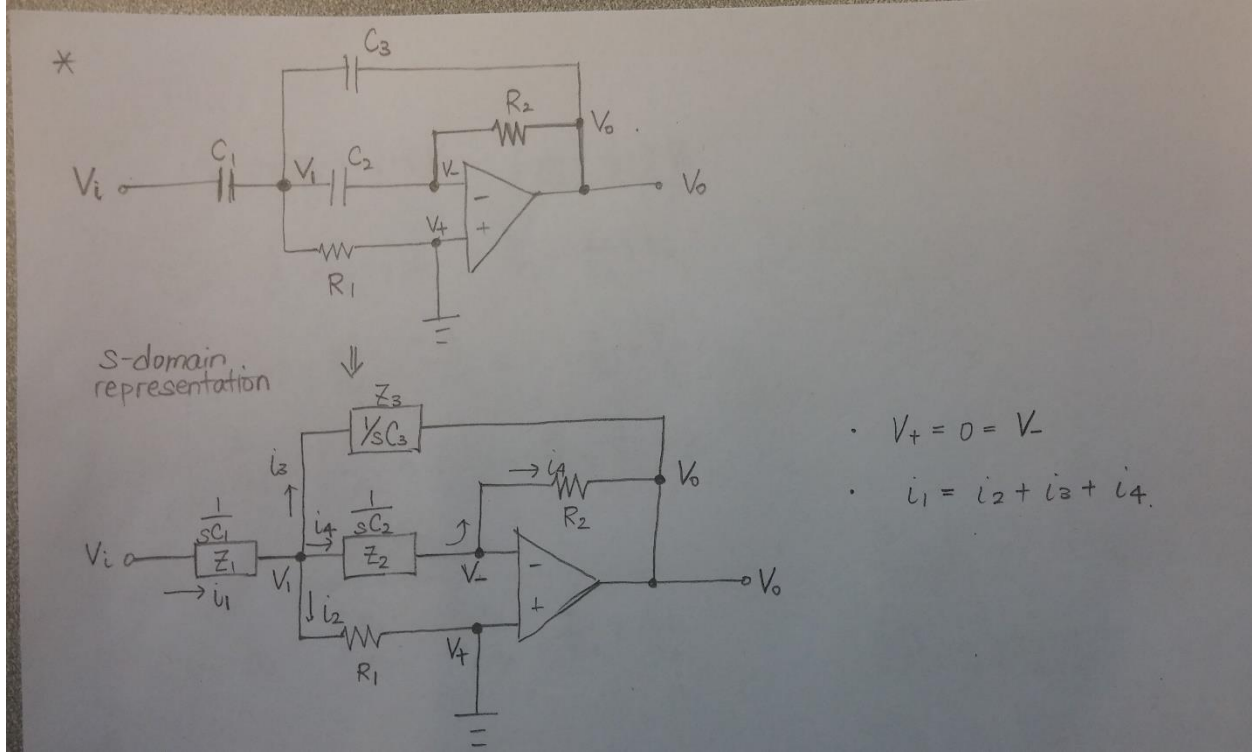


Solution of Exam 3 Problem 1

1. Solution



$$i_1 = \frac{V_i - V_1}{Z_1}, \quad i_2 = \frac{V_1 - V_+}{R_1} = \frac{V_1}{R_1}, \quad i_3 = \frac{V_1 - V_o}{Z_3}, \quad i_4 = \frac{V_1 - V_-}{Z_2} = \frac{V_1}{Z_2} = \frac{V_1 - V_o}{R_2} = \frac{-V_o}{R_2}$$

Then, since $i_1 = i_2 + i_3 + i_4$,

$$\frac{V_i - V_1}{Z_1} = \frac{V_1}{R_1} + \frac{V_1 - V_o}{Z_3} + \frac{-V_o}{R_2} \quad (1)$$

$$\text{and } \frac{V_1}{Z_2} = \frac{-V_o}{R_2} \quad (2)$$

$$\text{First simplify (1). So, we get } V_i = \left(1 + \frac{Z_1}{R_1} + \frac{Z_1}{Z_3}\right)V_1 - \left(\frac{Z_1}{Z_3} + \frac{Z_1}{R_2}\right)V_o \quad (3).$$

$$\text{Then, we plug (2) in (3). So, we get } V_i = -\left(\frac{Z_2}{R_2} + \frac{Z_1 Z_2}{R_1 R_2} + \frac{Z_1 Z_2}{R_2 Z_3} + \frac{Z_1}{Z_3} + \frac{Z_1}{R_2}\right)V_o.$$

Then, we present Z_1, Z_2 , and Z_3 in terms of s, C_1, C_2 , and C_3 . The relation is shown in the picture above.

Hence, we get
$$\frac{V_o(s)}{V_i(s)} = \frac{-R_1 R_2 C_1 C_2 s^2}{R_1 R_2 C_2 C_3 s^2 + (R_1 C_1 + R_1 C_2 + R_1 C_3)s + 1}.$$

Finally, it is a high pass filter because it rejects the low frequency as we set s is zero. And it passes the high frequency as we set s is infinity.