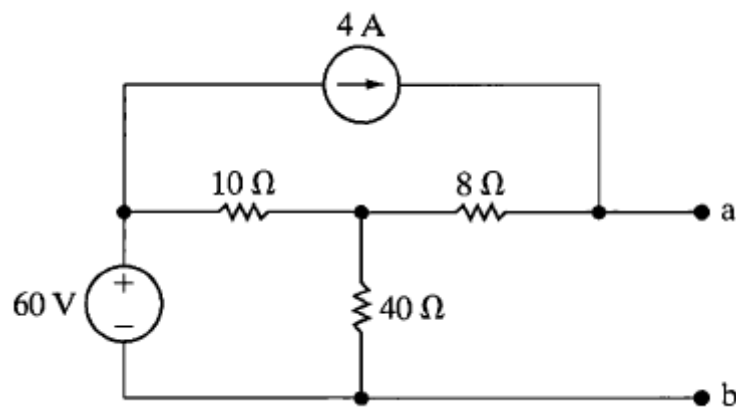


EE233 HW0Sept. 28thDue Date: Oct. 3rd

1. Find the Norton equivalent with respect to the terminals a, b for the circuit in the following figure.

**Figure Problem 1**

2. The op-amp in the circuit below is ideal.
 - a) Calculate v_o when v_g equals 4V.
 - b) Specify the range of values of v_g so that the op-amp operates in linear mode.
 - c) Assume that v_g equals 2V and that the 63Ω resistor is replaced with variable resistor. What value of the variable resistor will cause the op-amp to saturate?

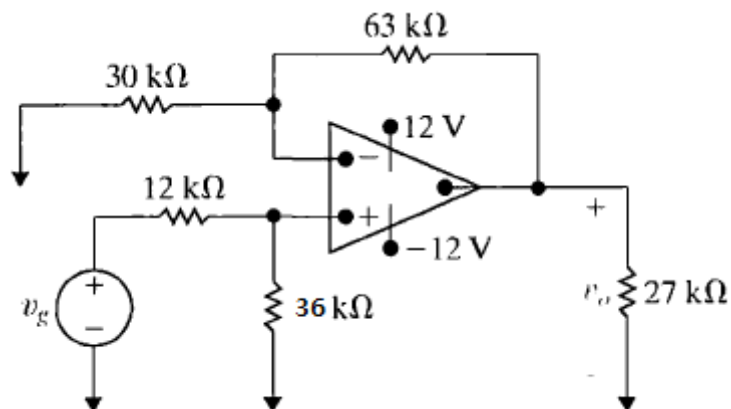


Figure Problem 2

3. The three inductors in the circuit below are connected across the terminals of a black box at $t = 0$. The resulting voltage for $t > 0$ is known to be $v_o = 2000e^{-100t} \text{ V}$.

If $i_1(0) = -6 \text{ A}$ and $i_2(0) = 1 \text{ A}$, find

- $i_0(0)$
- $i_0(t), t \geq 0$
- $i_1(t), t \geq 0$
- $i_2(t), t \geq 0$
- the initial energy stored in the three inductors
- the total energy delivered to the black box
- the energy trapped in the ideal inductors

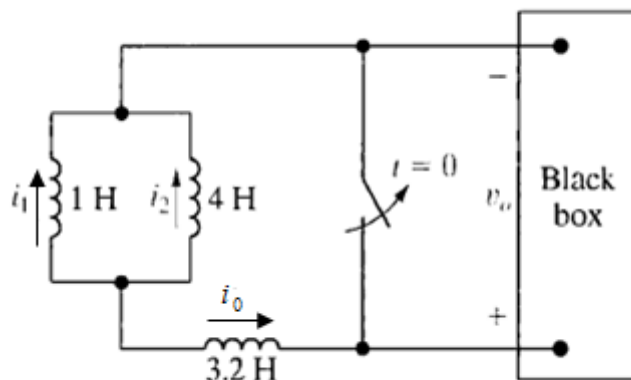


Figure Problem 3

4. After the circuit below has been in operation for a long time, a screwdriver is

inadvertently connected across the terminals a, b. Assume the resistance of the screwdriver is negligible.

- Find the current in the screwdriver at $t = 0^+$ and $t = \infty$.
- Derive the expression for the current in the screwdriver for $t \geq 0^+$.

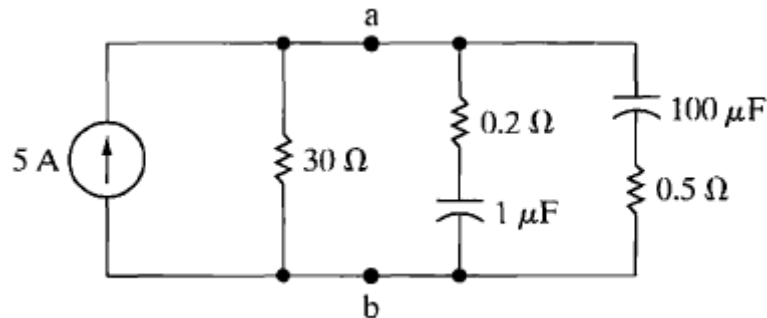


Figure Problem 4

- The switch in the circuit below has been in position *a* for a long time. At $t = 0$, the switch moves instantaneously to position *b*. Find
 - $v_o(0^+)$
 - $dv_o(0^+)/dt$
 - $v_o(t)$ for $t \geq 0^+$

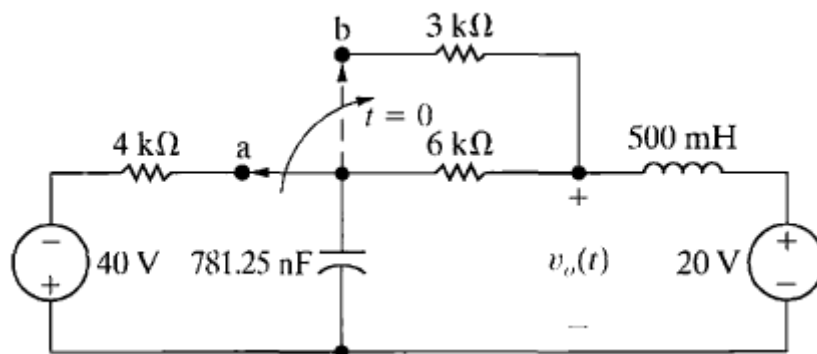


Figure Problem 5

- Calculate the following complex number: $(1 - 3j) + \frac{2 + 2j}{1 - 2j}$

Give answer in both Cartesian (rectangular) and angular (polar, magnitude and phase) form.