


$R, L, C \Rightarrow$ Passive Filter

Gain ≤ 1

Subject to Loading

2nd order High $\&$ requires

both $L \& C$

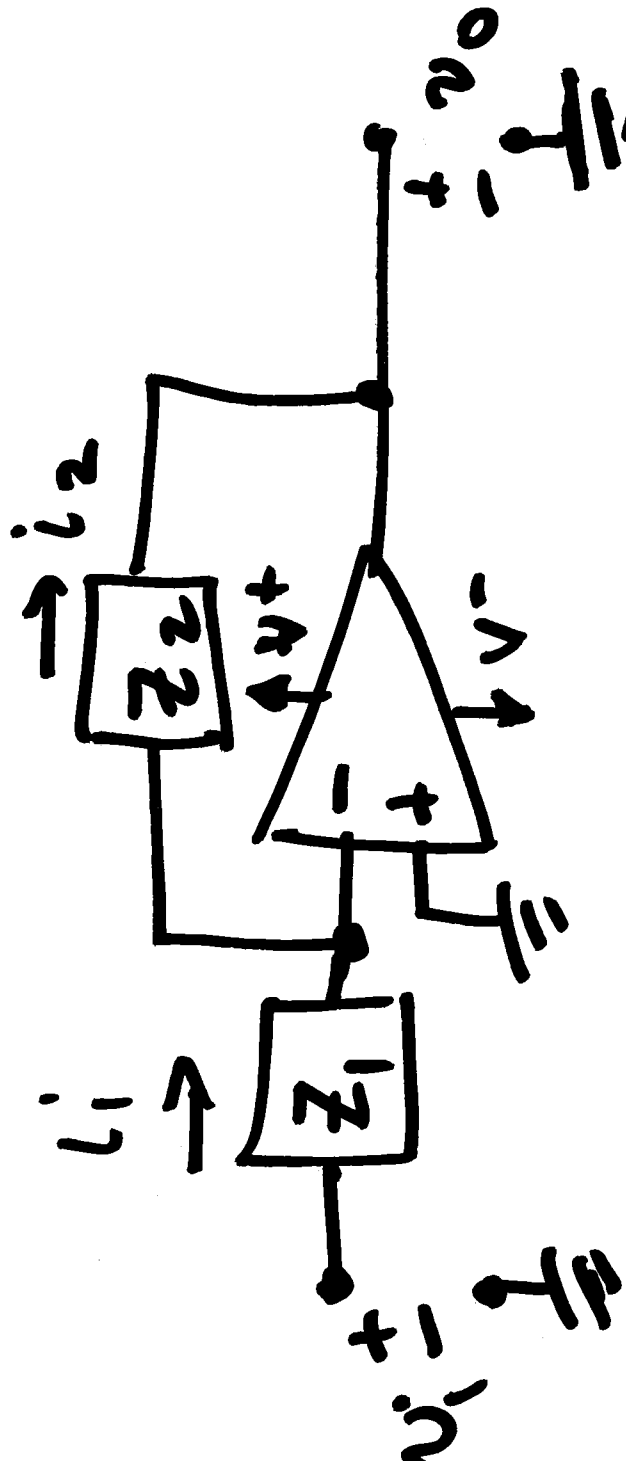

(1) Assume op-amp is in linear regime

a) $V_+ - V_- = 0$

b) $i_+, i_- = 0$

c) Very high gain

(2) Analyse circuit


(3) Check (1) valid (if not, assume at limit & repeat)

$$V_+ = 0 \Rightarrow V_- = 0$$

$$i_1 = \frac{v_i}{Z_1} = i_2$$

$$V_o = -Z_2 i_2 = -\frac{Z_2}{Z_1} v_i$$

$$\frac{V_o}{v_i} = -\frac{Z_2}{Z_1}$$

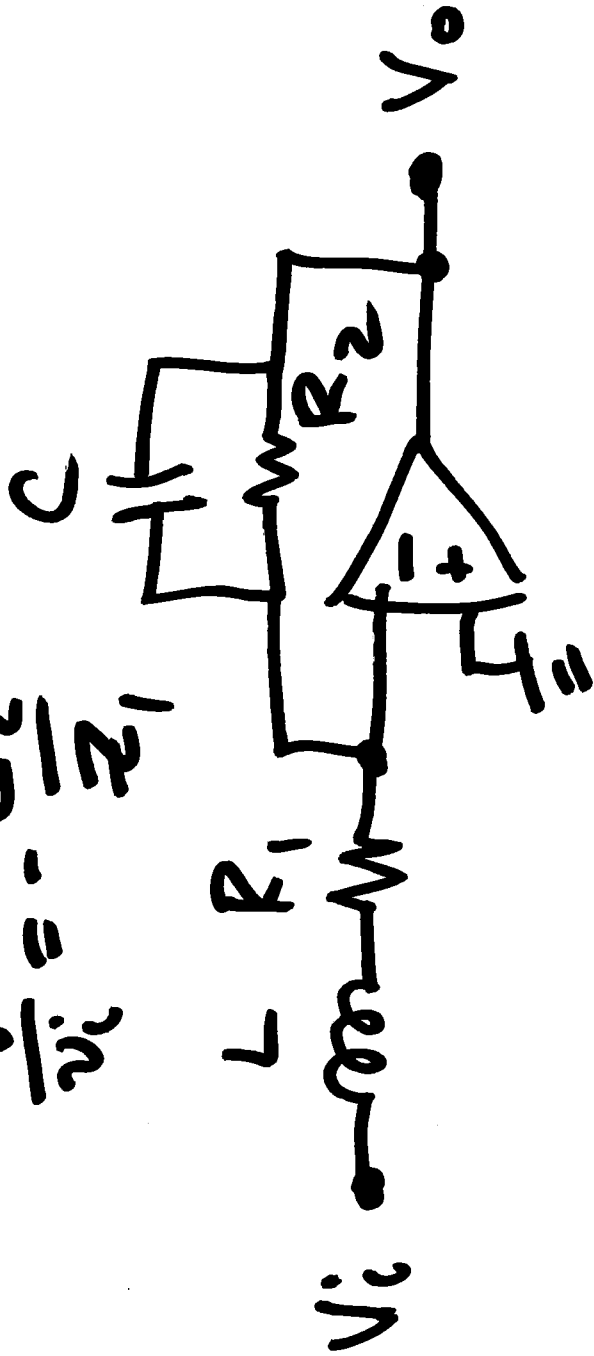

$$Z_1 = R_1 + sL$$

$$Z_2 = \frac{1}{sC + 1/R_2} = \frac{1/C}{s + 1/R_2 C}$$


$$\frac{V_o}{V_i} = - \frac{1/C}{(s + 1/R_2 C)(s + R_1/L)}$$

2nd order LPF

2 real roots: $-1/R_2 C, -R_1/L$

$$\omega_c = 1/R_2 C, R_1/L \quad \omega_{c1}, \omega_{c2}$$

$$R_1 = R_2$$

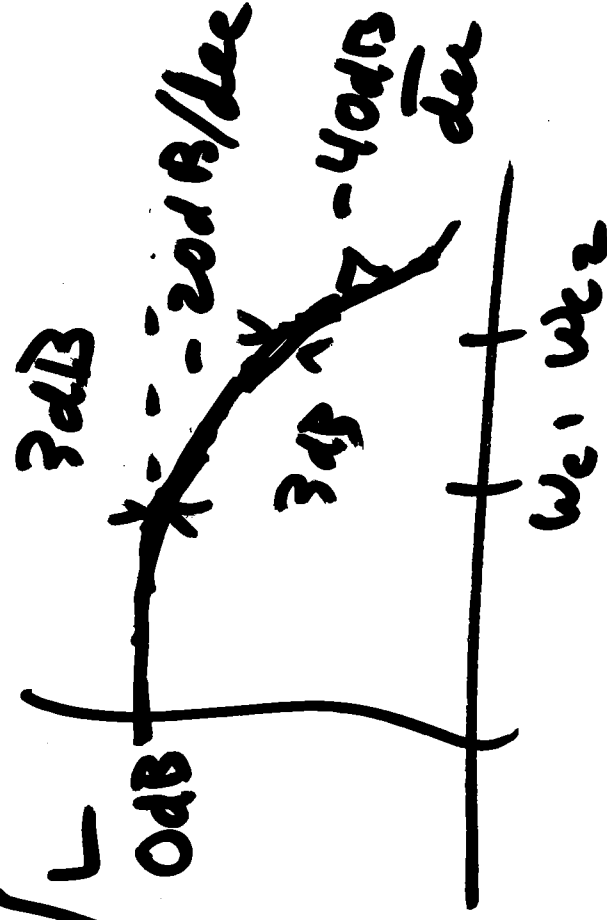


$$\frac{V_o}{V_i} = \frac{-1/LC}{s^2 + \underbrace{\left(\frac{R_1}{L} + \frac{1}{R_2 C}\right)}_{2\zeta\omega_0} s + \underbrace{\frac{R_1}{R_2 LC}}_{\omega_0^2}}$$

$$2\zeta\omega_0 = 2\alpha = b = \frac{\omega_0}{Q}$$

$$b = BW \geq 2\omega_0$$

$$Q \leq 1/2$$

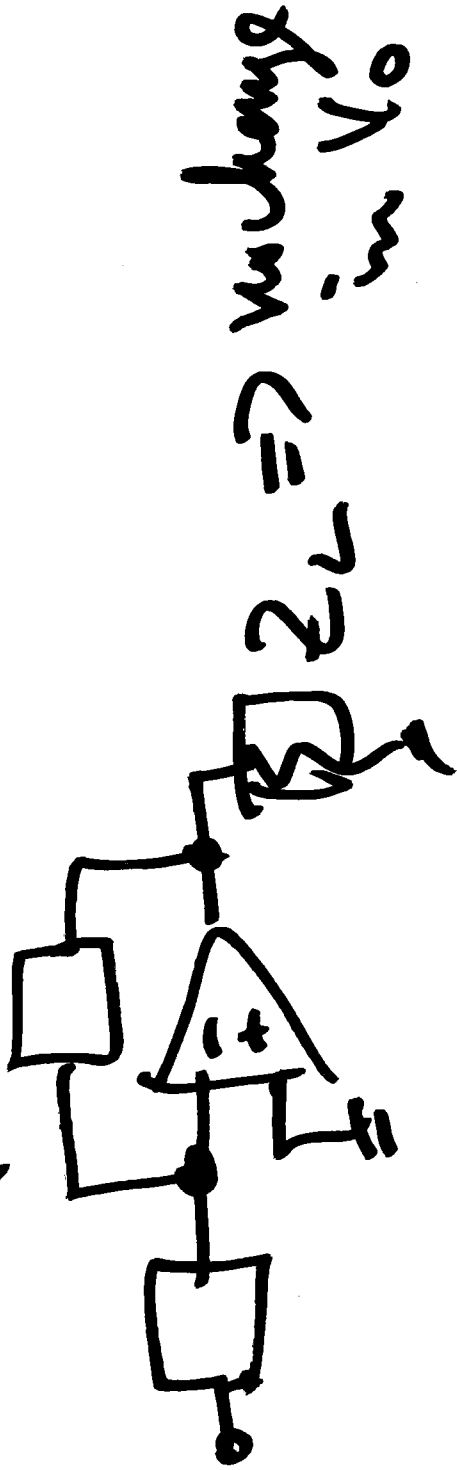

Scaling:

Example

$$R_c = 1\Omega = R_z$$

$$C = 1F, L = 1H$$

Magnitude Scaling $k_m * Z \Rightarrow$ ~~constant~~

filter unchanged

$$\frac{V_o}{V_i} \text{ or } \frac{I_o}{I_i}$$

$$Z \times \frac{1}{Z} \Rightarrow 1 \times Z$$

$$R' = k_m R \quad L' = k_m L \quad C' = C/k_m$$

$$Z_c = 1/sC$$

$$\text{Frequency: } k_f \quad Z_R = R, \quad Z_c = sL, \quad Z_c = \frac{1}{sC}$$

$$R' = R, \quad L' = L/k_f \Rightarrow C' = C/k_f$$

$$R' = k_m R, \quad L' = \frac{k_m L}{k_f}, \quad C' = C / k_m k_f$$



$$\frac{V_o}{V_i} = -\frac{Z_2}{Z_1} = -\frac{R_2}{1 + 1/s}$$

$$= -\frac{s R_2}{s + 1}$$

HPF corner/cuttoff

$$10^6 \text{ rad/s} \Rightarrow k_f = 10^6$$


$$\text{Gain } 26 \text{ dB} = (20 + 6) \text{ dB} \Rightarrow 10 \times 2 = 20$$

$$R_1 = 1 \Omega, R_2 = 20 \Omega, C' = 1 \mu\text{F} / 10^6 = 1 \text{ nF}$$

$$R_1: 1 \Omega \Rightarrow 1 \text{ k}\Omega \quad k_m = 10^3$$


$$R'_2 = 20 \text{ k}\Omega, \quad C'' = \frac{1 \mu\text{F}}{10^3} = 1 \text{ nF}$$

Higher Order Filter

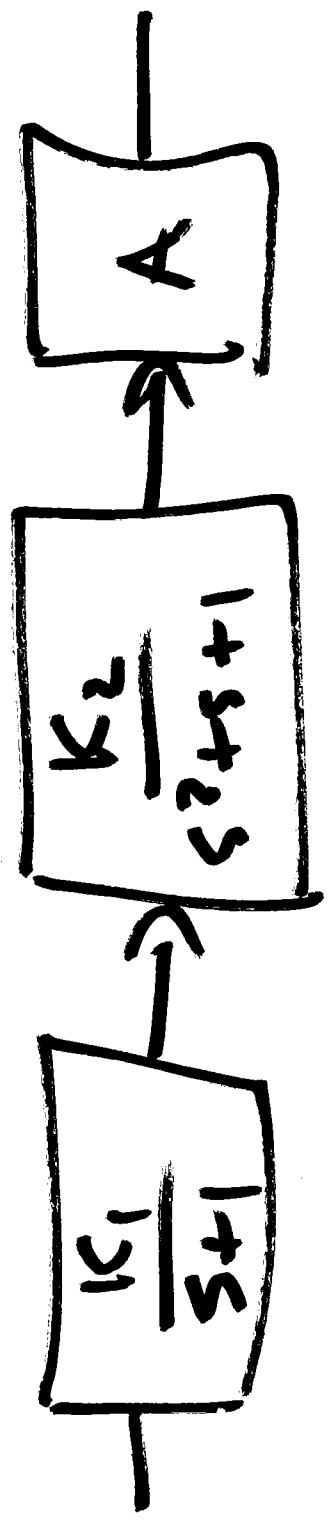

3rd order LPF



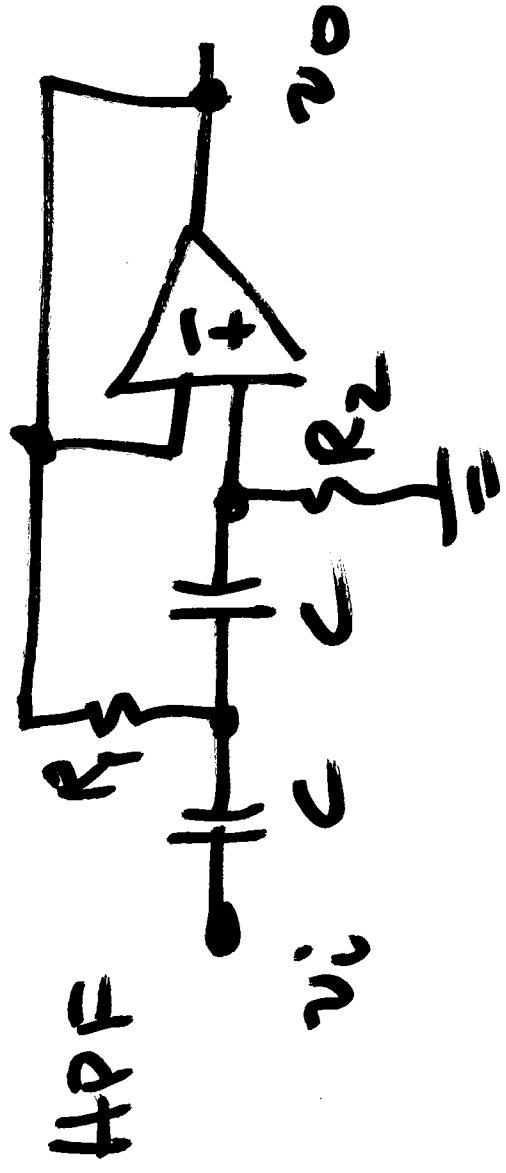

$$H(s) = \frac{s^2}{s^2 + \left(\frac{2}{R_2 C}\right) + \left(\frac{1}{R_1 R_2 C^2}\right)}$$

$$\omega_0 = \frac{1}{\sqrt{R_1 R_2}}$$

$$\frac{1}{\sqrt{R_1 R_2}} = \frac{\omega_0}{Q} = \frac{2}{R_2 Q} \Rightarrow Q = \sqrt{\frac{R_2}{R_1}} \left(\frac{1}{2}\right)$$

$$\omega_0 = 1: C = 1F, \quad \frac{1}{R_1 R_1} = 1 \Omega^{-2} \Rightarrow b = 2/R_2$$

Designing a Filter

Wide band

LPF $\Rightarrow$ HRL $\Rightarrow$ BPF




Narrow band: Pick center frequency

Then $\frac{1}{R} \approx \frac{R}{L} \rightarrow \frac{1}{\sqrt{LC}}$ to give desired Q


$$\left(s^2 + \frac{\omega_0}{Q} s + \omega_0^2 \right)$$

LPF

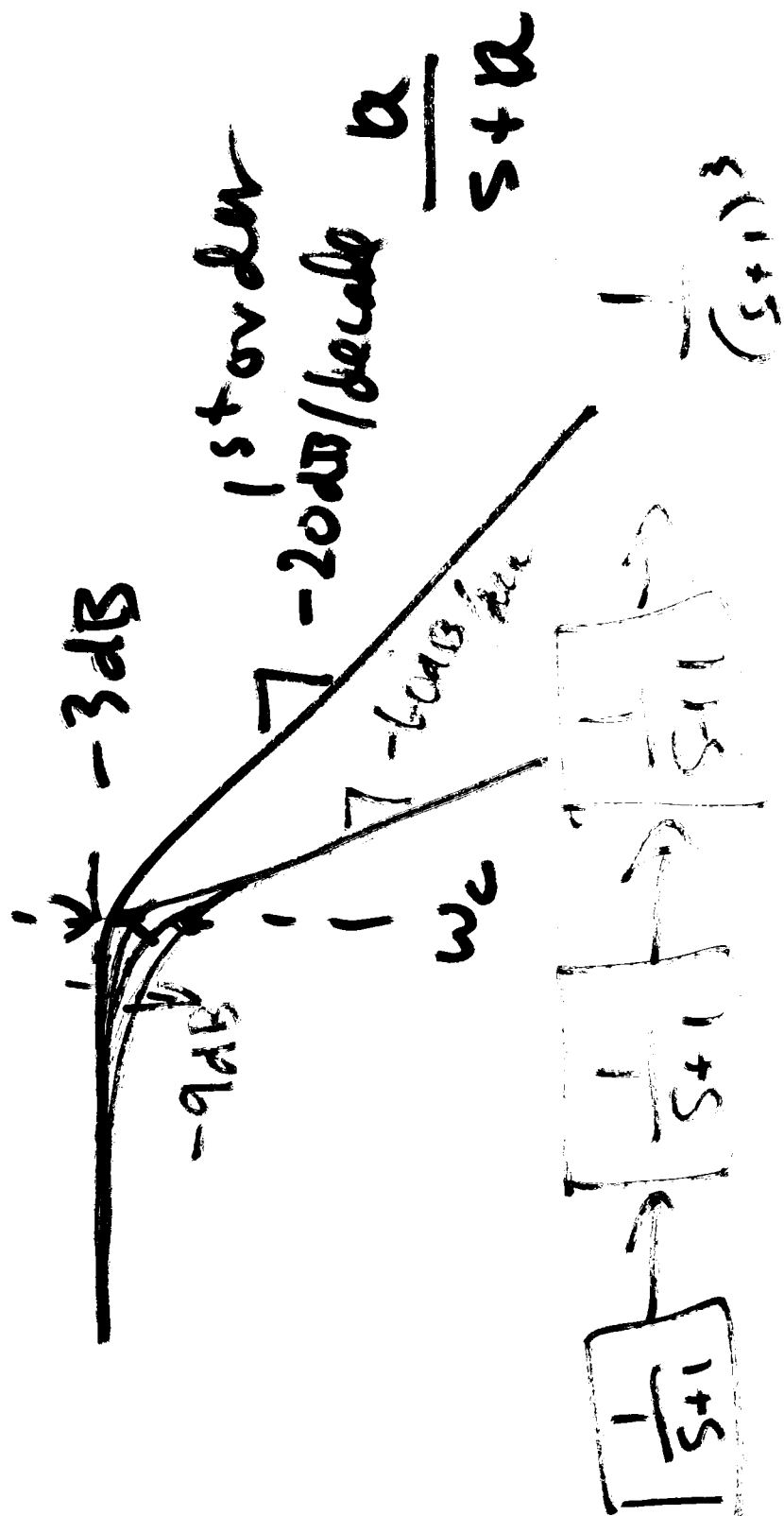

2nd order
LPF
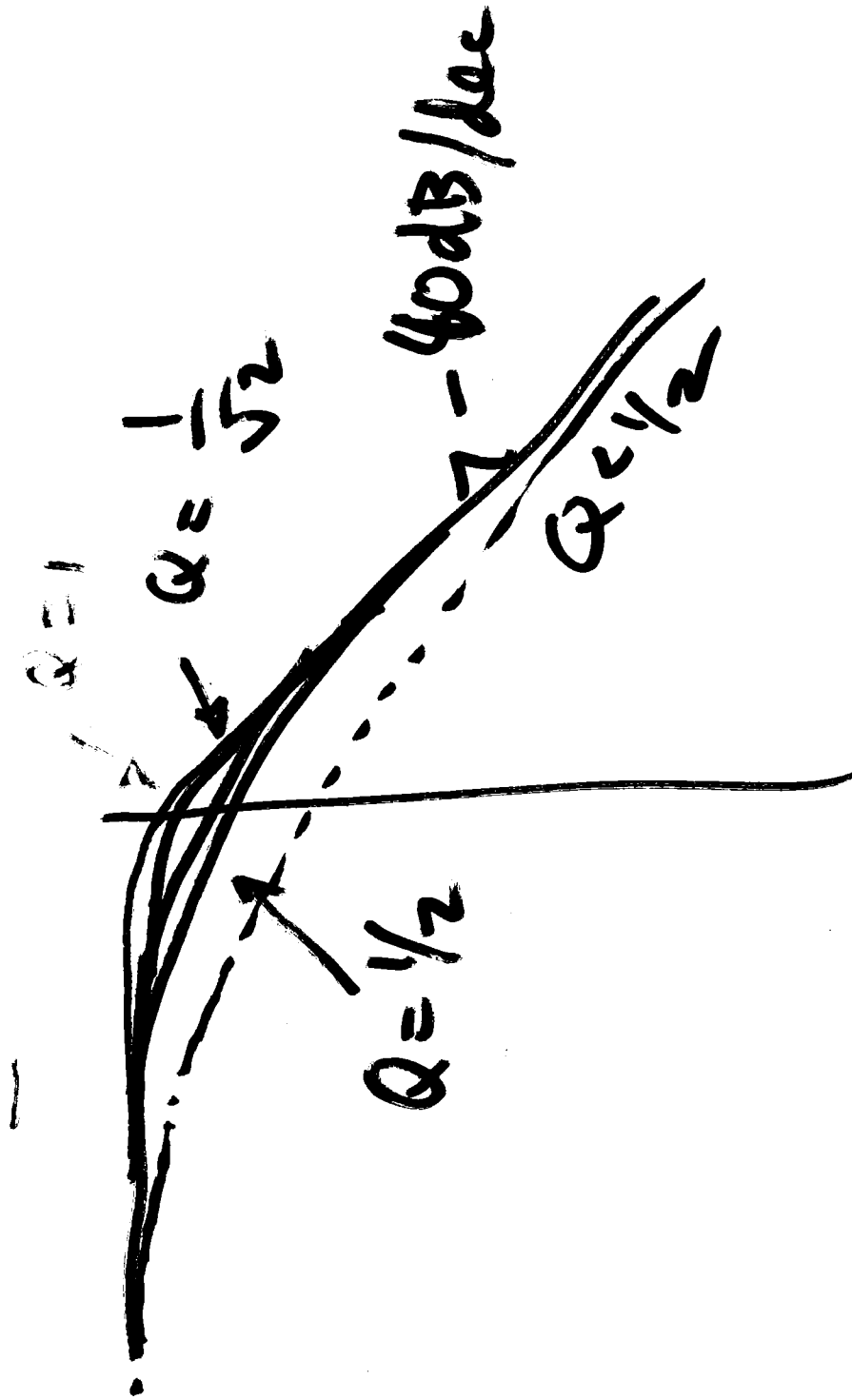
$$\frac{\omega_0^2}{s^2 + \frac{\omega_0}{Q}s + \omega_0^2}$$



Butterworth Filters

Multiple order filter

$$H(s) = \frac{\omega_n^n}{(s + \omega_n)^n}$$



$$H(s) = \frac{\omega_n^n}{(s + \omega_n)^n}$$

$$|H(j\omega)| = \left| \frac{\omega_n^n}{(j\omega + \omega_n)^n} \right| = \frac{1}{\sqrt{1 + (\omega/\omega_n)^{2n}}}$$

$$|H(j\omega)| = \frac{1}{\sqrt{1 + (\omega/\omega_c)^{2n}}}$$

1st order

$$\frac{1}{s+1}$$

2nd order

$$\frac{1}{s^2 + 2\sqrt{2}s + 1}$$

$$Q = \frac{1}{\sqrt{2}}$$

3rd order

$$\frac{1}{(s+1)(s^2+s+1)}$$

↑ -3dB


↑ Q=1

⇒ 0dB drop

TABLE 15.1 Normalized (so that $\omega_c = 1 \text{ rad/s}$) Butterworth Polynomials up to the Eighth Order

n th-Order Butterworth Polynomial

1	$(s + 1)$
2	$(s^2 + \sqrt{2}s + 1)$
3	$(s + 1)(s^2 + s + 1)$
4	$(s^2 + 0.765s + 1)(s^2 + 1.848s + 1)$
5	$(s + 1)(s^2 + 0.618s + 1)(s^2 + 1.618s + 1)$
6	$(s^2 + 0.518s + 1)(s^2 + \sqrt{2} + 1)(s^2 + 1.932s + 1)$
7	$(s + 1)(s^2 + 0.445s + 1)(s^2 + 1.247s + 1)(s^2 + 1.802s + 1)$
8	$(s^2 + 0.390s + 1)(s^2 + 1.111s + 1)(s^2 + 1.6663s + 1)(s^2 + 1.962s + 1)$

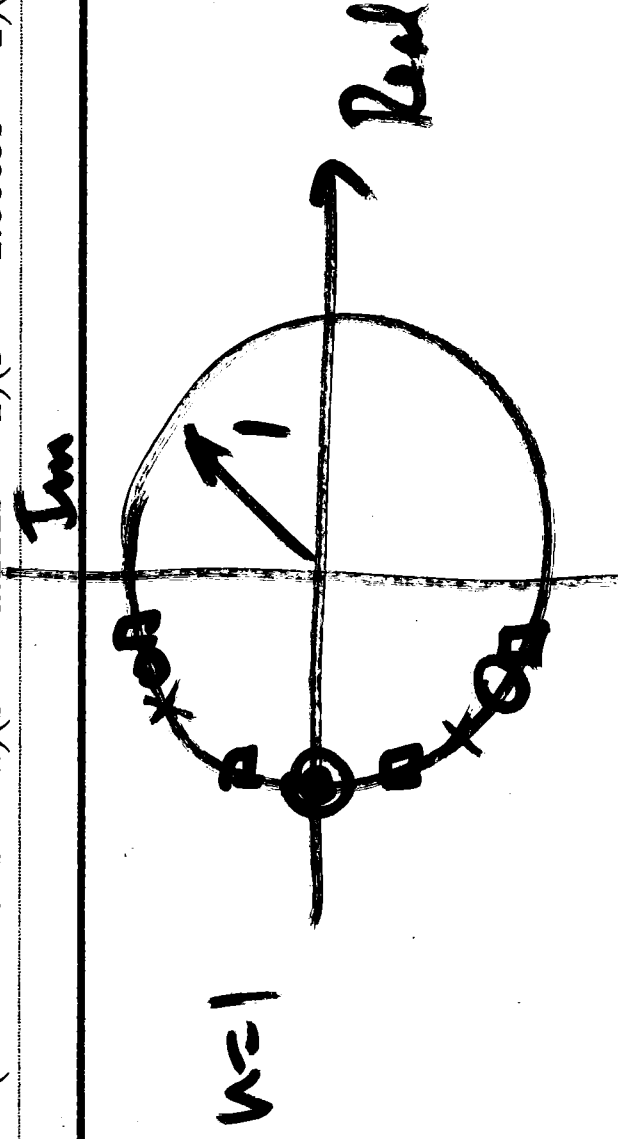

$$|H(j\omega)|^2 = H(j\omega)H(-j\omega) =$$

$$\frac{1}{1 + \left[\left(\frac{\omega}{\omega_c}\right)^2\right]^n}$$

$$s = j\omega \Rightarrow \omega^2 = -s^2$$

$$|H(j\omega)|^2 = \frac{1}{1 + \left[\left(\frac{s}{\omega_c}\right)^2\right]^n (-1)^n} = H(s)H(-s)$$

$$\omega_c = 1$$

$$\frac{1}{1 + (-1)^n s^{2n}} = H(s)H(-s)$$

$$H(s)H = \frac{1}{D(s)}$$

Butterworth
HPF

$$\frac{s^n}{s^n D_n(s)}$$

$$\frac{\text{LPF}}{D_n(s)}$$

How high a filter order?

$$|H(j\omega)| = \frac{A}{\sqrt{1+(\omega/\omega_c)^{2n}}}$$

$$A_{dB}(\omega) - A_{dB}(\text{pass band}) = 20 \log_{10} \frac{1}{\sqrt{1+(\omega/\omega_c)^{2n}}}$$

$$\omega \gg \omega_c \quad \approx -20n \log_{10} \left(\frac{\omega}{\omega_c} \right)$$

$$A_{dB}(\omega_i) < A_s \quad n > \frac{-A_s}{20 \log_{10} \left(\frac{\omega_i}{\omega_c} \right)}$$

$$\omega_c = 10^5 \text{ rad/s}$$

$$\begin{aligned} A_{dB}(\text{dB}) &= 0 \text{ dB} & n &> \frac{-(-30)}{20(1)} \\ A_{dB}(10^6 \text{ rad/s}) &= -30 \text{ dB} & &> 1.5 \end{aligned}$$

$$A = -10 \log_{10} \left[1 + \left(\frac{\omega}{\omega_c} \right)^{2n} \right]$$

$$10^{-A/10} = 1 + \left(\frac{\omega}{\omega_c} \right)^{2n}$$


$$\left(\frac{\omega}{\omega_c} \right)^{2n} = 10^{-A/10} - 1$$

$$-dB \quad \frac{2n \log_{10} \left(\frac{\omega}{\omega_c} \right) = \log_{10} \left(10^{-A/10} - 1 \right)}{n \geq \frac{\log_{10} (10^{-A/10} - 1)}{2 \log_{10} (\omega/\omega_c)}}$$

Assume linear

$$V_+ = V_-$$

$$i_+ = i_- = 0$$

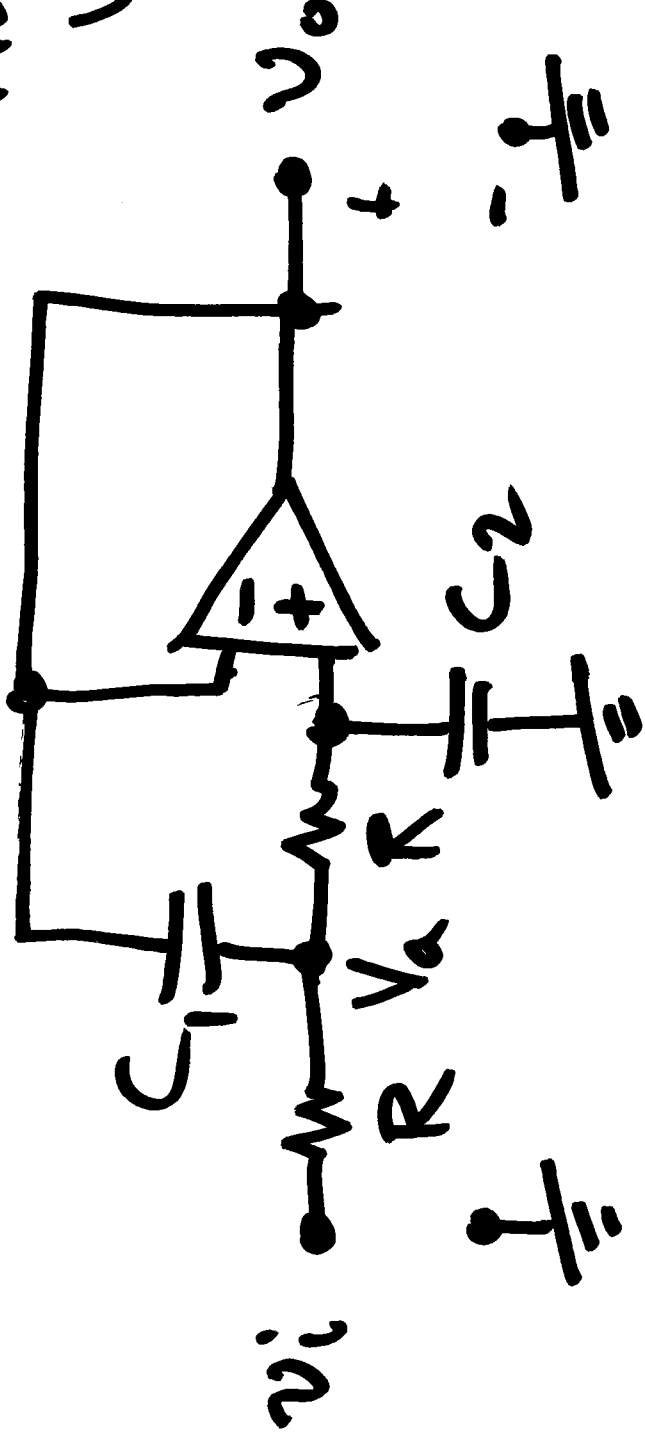

$$V_- = V_+ = 0$$

$$V_a: \frac{V_i - V_a}{R} + \frac{V_o - V_a}{1/sC_1} + \frac{V_o - V_a}{R} = 0$$

$$\underline{V_o} = \frac{1/sC_2}{R + 1/sC_2} V_a$$

$$\frac{V_o}{V_i} = \frac{\left(\frac{1}{R^2 C_1 C_2} \right)}{s^2 + \frac{2}{RC_1} s + \frac{1}{R^2 C_1 C_2}} \quad \omega_0^2$$

LPF

2nd order

$$\omega_0 = 1$$

$$R = 1 \Omega$$

$$\frac{1}{C_1 C_2} = 1 = \omega_0^2$$

$$\frac{2}{C_1} = \frac{\omega_0}{Q} = \frac{1}{Q}$$

$$H(s) = \frac{1/C_1 C_2}{s^2 + \frac{2}{C_1} s + \frac{1}{C_1 C_2}}$$

Butterworth $Q = \frac{1}{\sqrt{2}}$

$$\frac{2}{C_1} = \sqrt{2} \Rightarrow C_1 = \sqrt{2}$$

$$C_2 = 1/\sqrt{2}$$

$$\omega_0 = 10^5$$

$$k_f = 10^5$$

$$R = 1 \Omega$$

$$C_1 = \sqrt{2}/10^5 = 14.14 \mu F$$

$$C_2 = 1/\sqrt{2} \times 10^5 = 7.07 \mu F$$

$$k_m = 10^3$$


$$R = 1 k \Omega$$

$$C_1 = 14.14 \mu F$$

$$C_2 = 7.07 \mu F$$

$$C_{krit} = C_2$$

$$C_1 = 2 C_{krit}$$

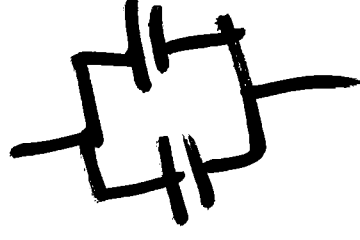

Filter Design

1. Determine Specs (e.g. LPF, BPF gains PB or SB)
2. Choose $H(s) \Rightarrow H(j\omega)$ to meet specs
3. Decompose 1st & 2nd order terms/stages
4. Choose circuits for each stage and cascade (or sum for band reject)
5. Correct gain, scale component (magnitude, frequency)
6. Check result

LPF w/ corner @ 10^4 rad/s $20 \log_{10} 50$

Pass band gain of 50 $\Rightarrow 40 \text{ dB} - 6 \text{ dB} = 34 \text{ dB}$

Gain at corner freq. of 37 dB

Gain less than 0.5 at ~~0.5~~ 8×10^4 rad/s


$$20 \log_{10}(0.5) = -6 \text{ dB}$$

$$\log_{10} 5 = 0.9 \text{ dec (0.9 bel)}$$

$$34 - (-6) = 40 \text{ dB down}$$

over 0.9 decades
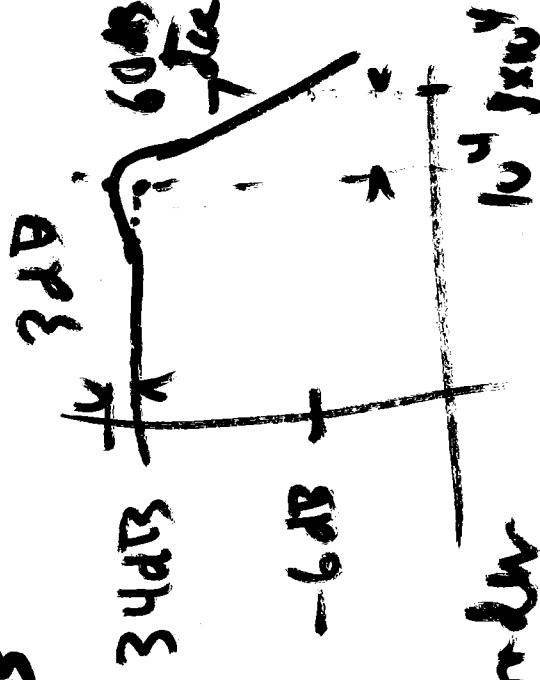
$$\frac{40}{0.9} = 44.4 \text{ dB/decade} \Rightarrow 3^{\text{rd}} \text{ order}$$



$$H(s) = \frac{A}{(s+10^4) \left[s^2 + \frac{10^4}{Q}s + (10^4)^2 \right]}$$

66 dB/dec

$Q = \sqrt{2}$


$$\lim_{\omega \rightarrow 0} |H(j\omega)| = \frac{A}{10^4 \times 10^8} = \frac{A}{10^{12}} = 50 \Rightarrow A = 5 \times 10^{13}$$

$$H(s) = \frac{5 \times 10^{13}}{(s+10^4) \left[s^2 + \frac{10^4}{\sqrt{2}} s + 10^8 \right]}$$

$$\text{Check } |H(j8 \times 10^4)| = \frac{5 \times 10^{13} / 10^{12}}{(18+1) \left(-8^2 + \frac{18}{\sqrt{2}} + 1 \right)}$$

$$= \frac{50}{(1+j8)(-63+j452)} \quad \} < 0.5$$

$$|1| > 8 \times |3| > 63 > 100$$

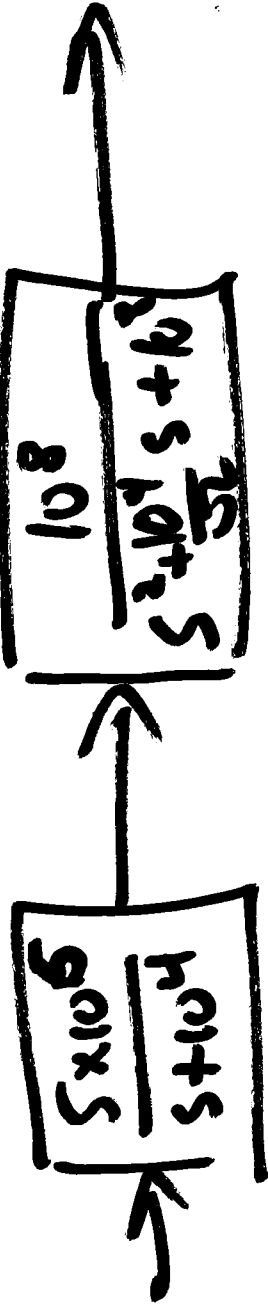


2nd order
LPTF
w/ unity
gain

1st order
LPTF
w/ gain of 50

$$H(s) = \frac{A}{(s+\omega_0)^3}$$

Gain @ 10⁴ rad/s
25 dB

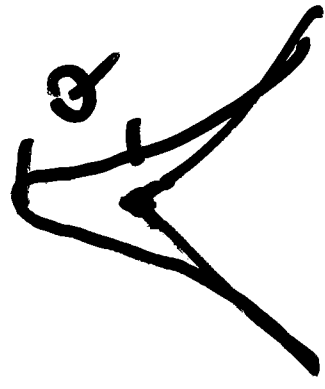

$$H(s) = \frac{\omega_0^2}{s^2 + \frac{\omega_0}{Q}s + \omega_0^2}$$

$$H(j\omega) = \frac{\omega_0^2}{(j\omega)^2 + \frac{\omega_0}{Q}j\omega + \omega_0^2}$$

$$H(j\omega_0) = \frac{\omega_0^2}{-\omega_0^2 + j\frac{\omega_0^2}{Q} + \omega_0^2} = \frac{jQ}{1}$$

$$|H(j\omega_0)| = Q$$

$$\angle H(j\omega_0) = -90^\circ$$


LPF

$$\frac{A_v \omega_c^2}{s^2 + \frac{\omega_c}{Q}s + \omega_c^2}$$

$$s^2, \frac{\omega_c}{Q}s, \text{HPF BPF}$$

Second-Order Sallen-Key Filters

S.K. Low-Pass Filter

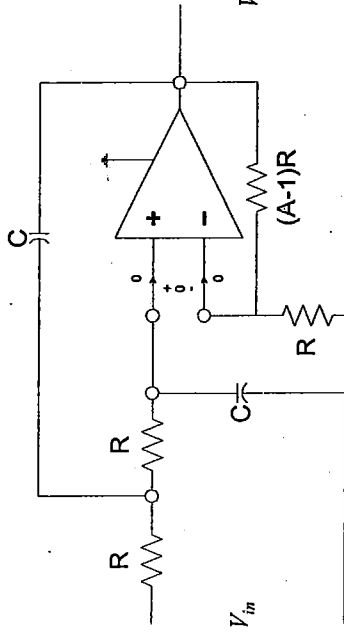

$$\omega_c = \frac{1}{RC},$$

$$A_v = A,$$


$$Q = \frac{1}{3-A}$$

$$\omega_c = \frac{1}{RC},$$


$$A_v = A,$$

$$Q = \frac{1}{3-A}$$


S.K. High-Pass Filter

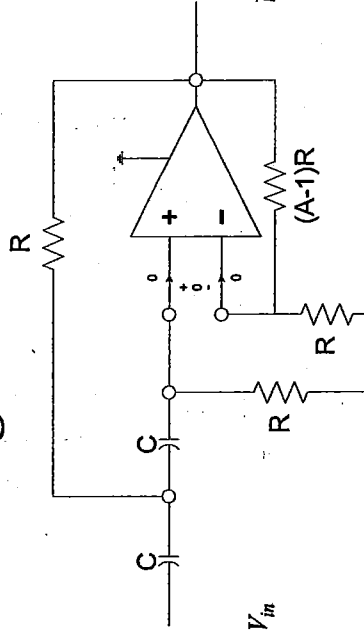

S.K. Band-Pass Filter

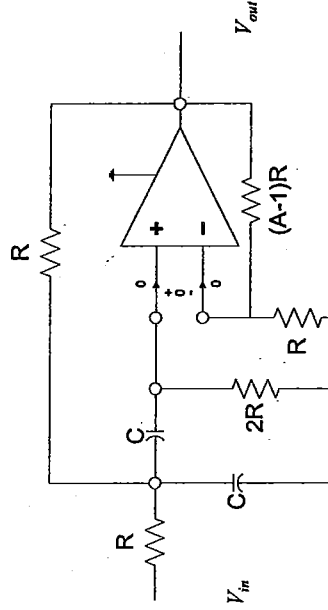

S.K. Band-Reject Filter

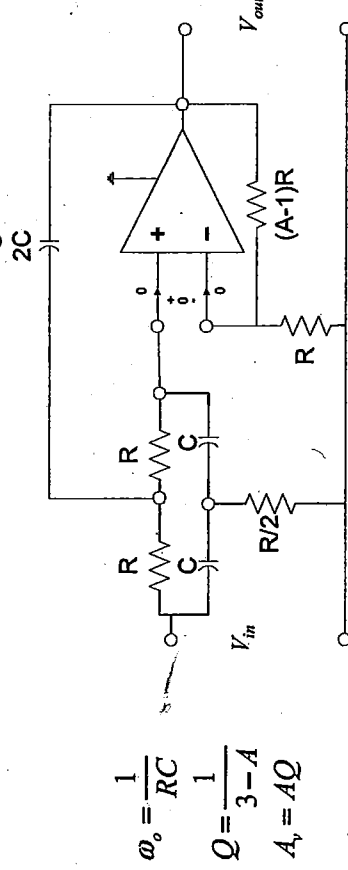


Properties of Sallen-Key Filters:

1. Simplicity of the design
2. Non-Inverting Amplifier (positive Gain)
3. Replication of elements

Limitations of Sallen-Key Filters:

1. The Gain and Q are related
2. Q must be $> \frac{1}{2}$, since A must be > 1

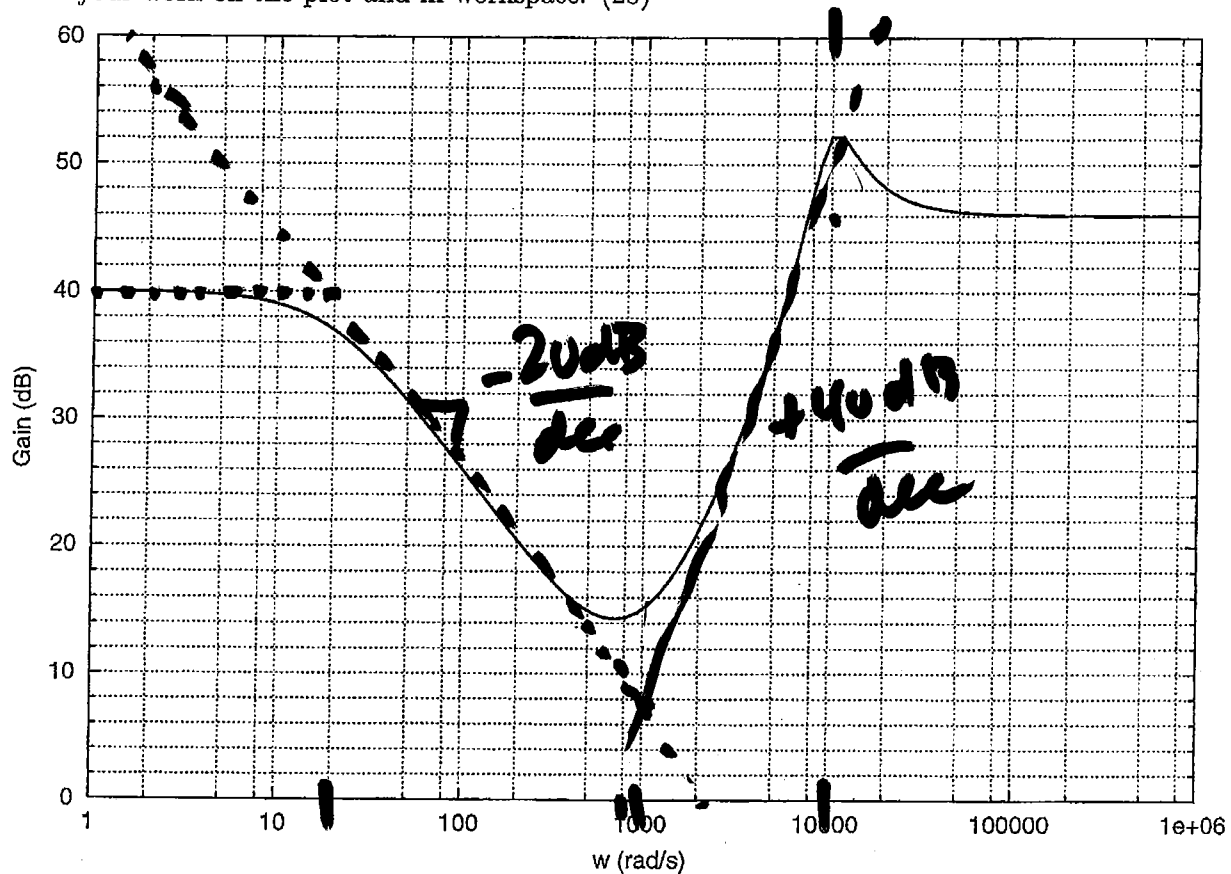5. Determine the s-domain transfer function associated with Bode magnitude plot below. Show your work on the plot and in workspace. (25)



pule at
20 rad/s

3 zeroes
@ 1000 rad/s

2 poles @ 10^4 rad/s

$$H(s) = \frac{A(s+1000) \left(s^2 + \frac{1000}{Q_z} s + 10^6 \right)}{(s+20) \left(s + \frac{10^4}{Q_p} + 10^8 \right)}$$