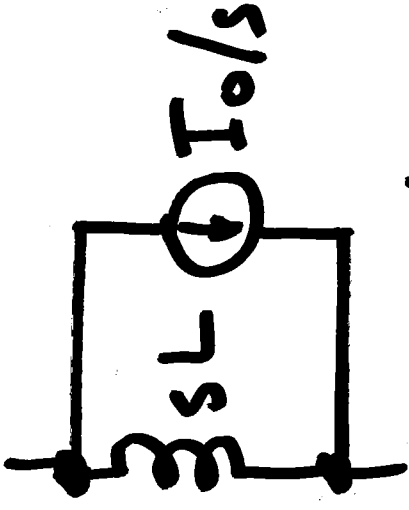



$H(s) \Rightarrow$ Sinusoidal Steady-State

$$\underline{H(j\omega)}$$




Design of frequency-selective
circuits A $H(j\omega)$


Low pass filter

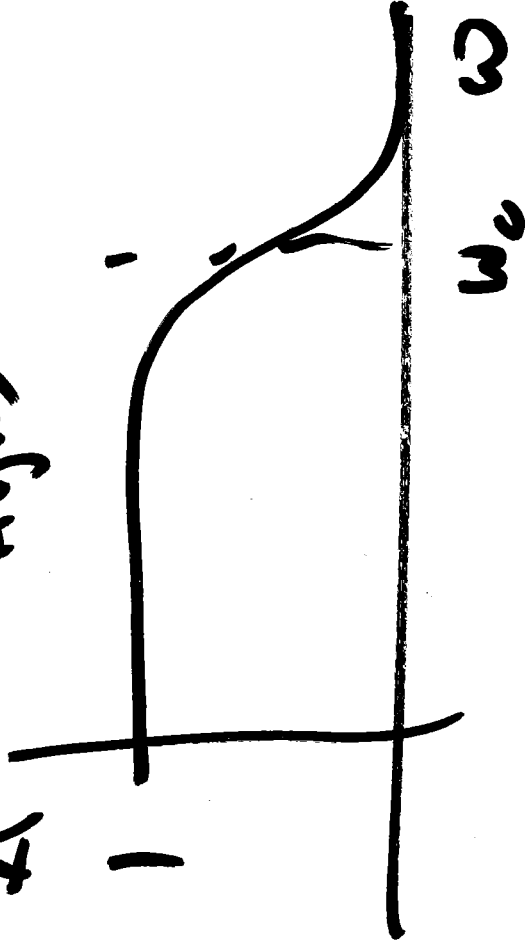


High Pass Filter

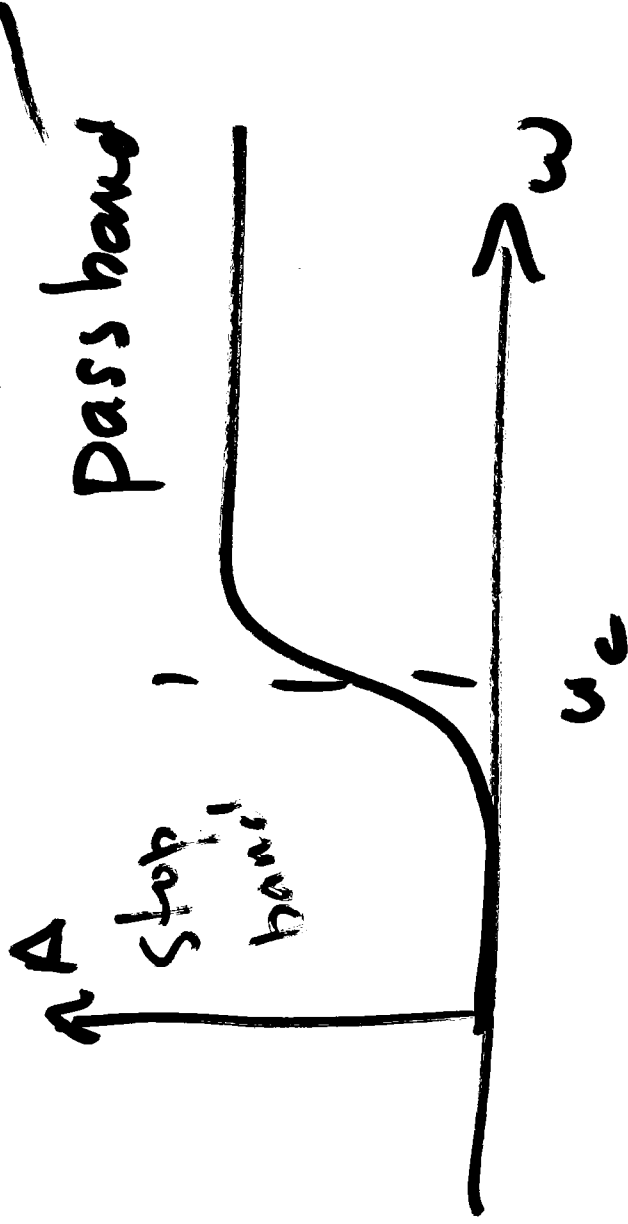


Band Pass

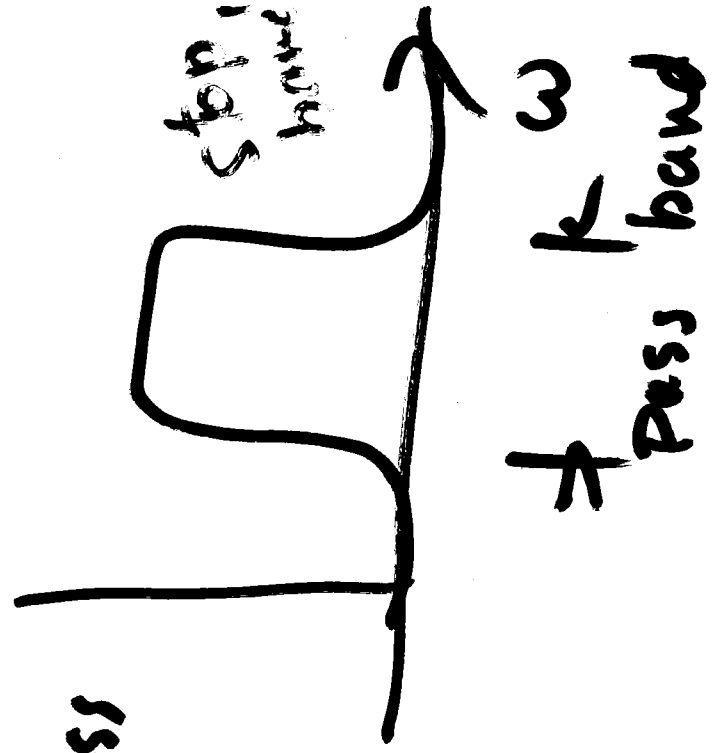

Band Reject

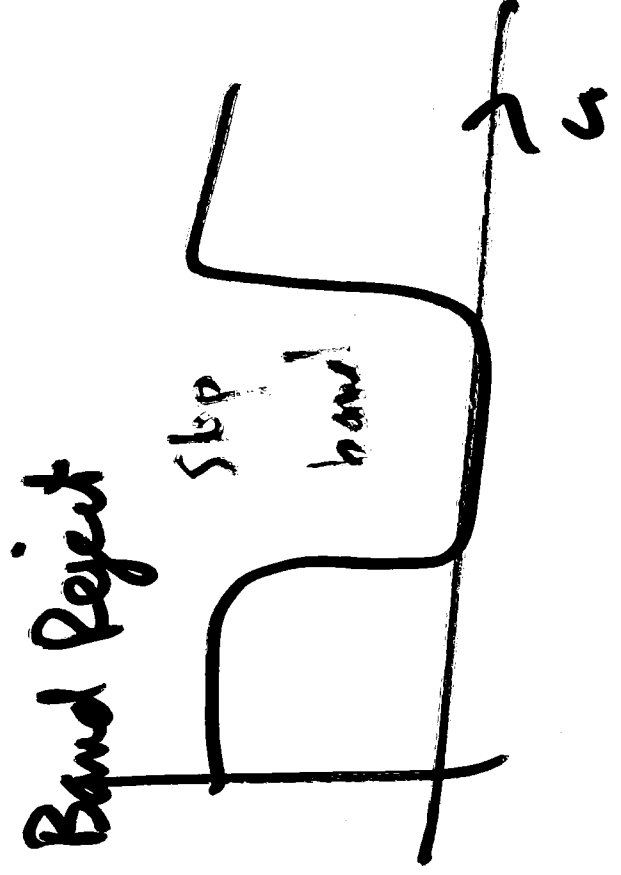

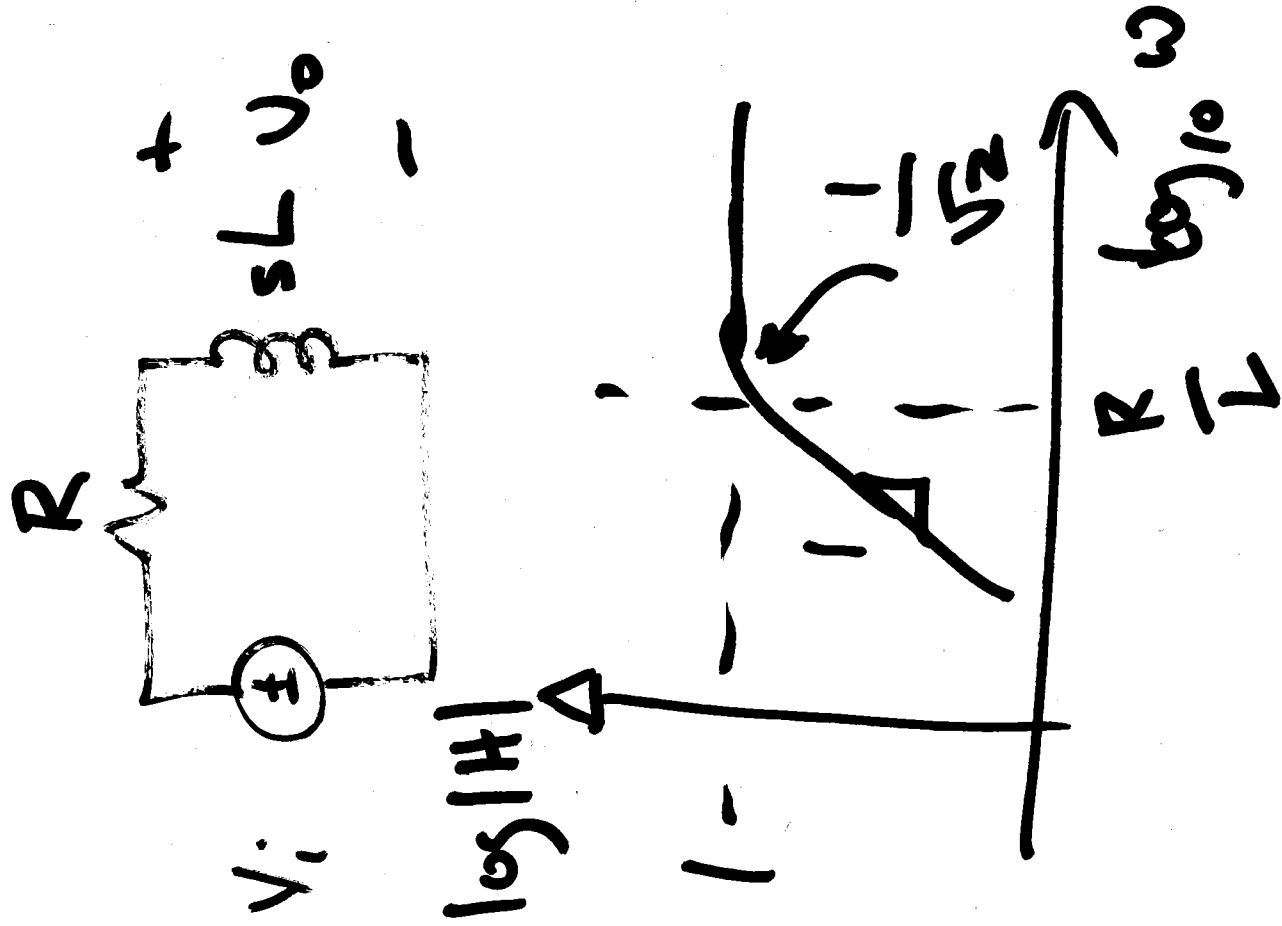




$$V_o(s) = \frac{sL}{R+sL} V_i(s)$$

$$\frac{V_o}{V_i} = \frac{sL}{R+sL}$$

$$H(j\omega) = \frac{j\omega L}{R+j\omega L}$$


$$R = \omega_c L$$

$$\omega_c = \frac{R}{L}$$

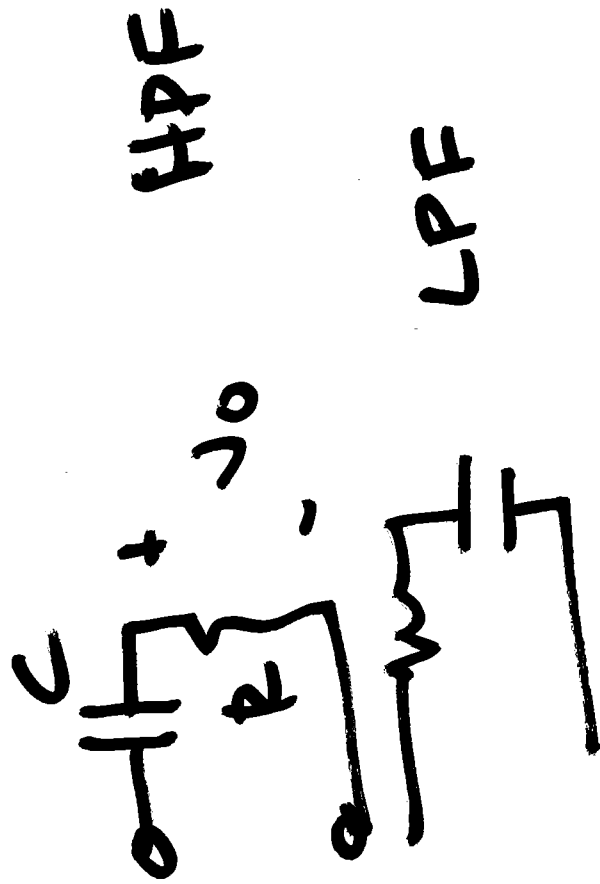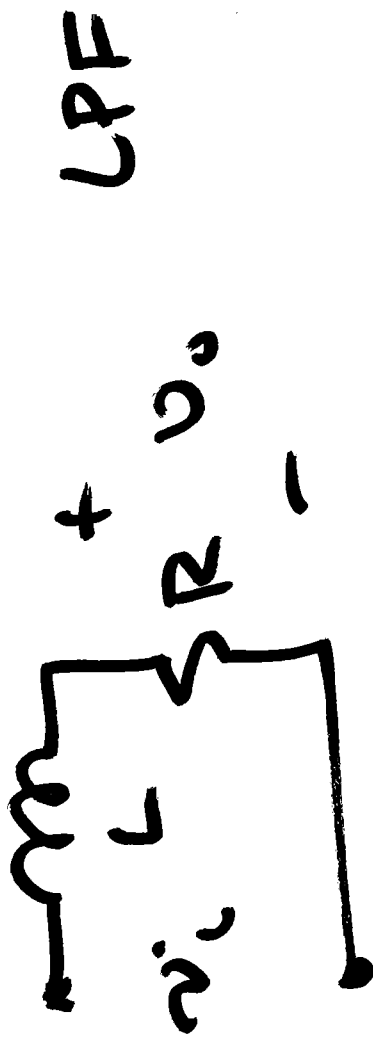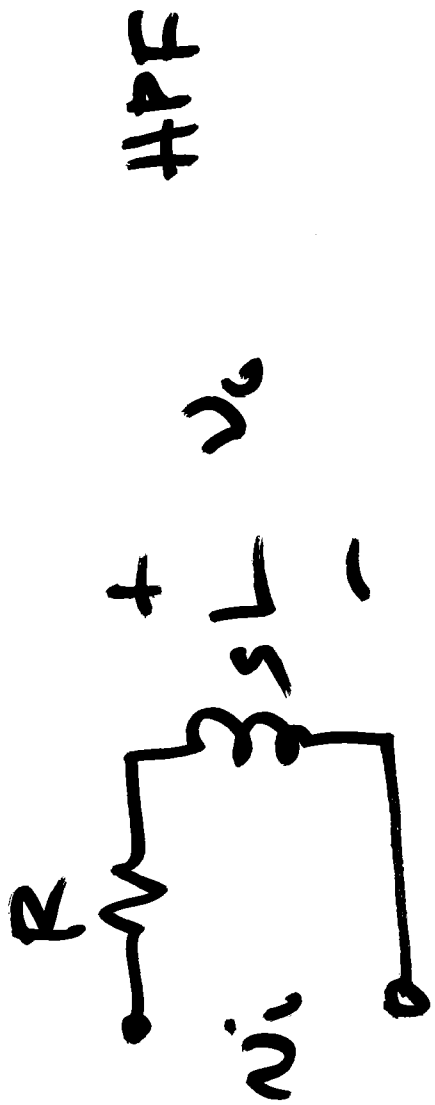


$$\log_{10} |H(j\omega)|$$

dB

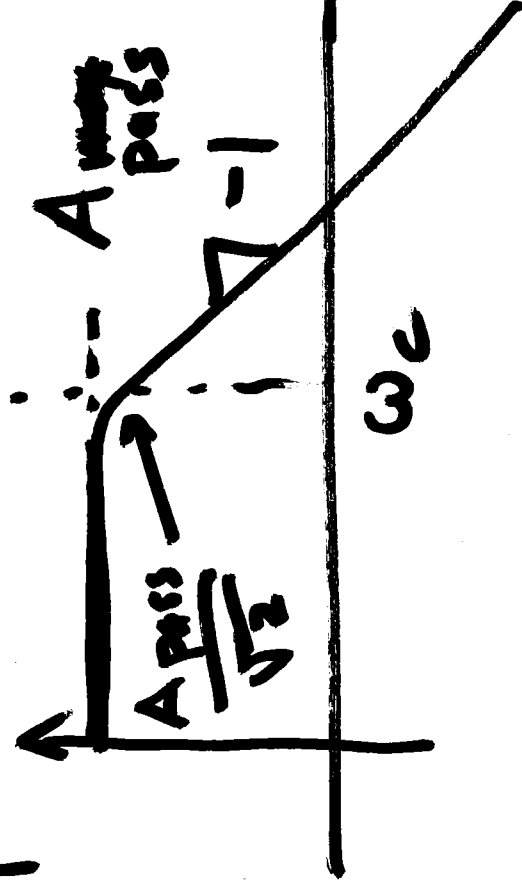

$$20 \log_{10} |A| \Rightarrow \text{dB}$$

$$\frac{1}{j\omega + \omega_c}$$

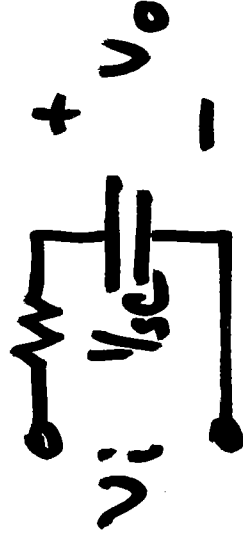

$$V_o = \frac{1/s_c}{R + 1/s_c} V_i$$

$$= \frac{1}{sRc + 1} = \frac{1}{Rc} \left(\frac{1}{s + \frac{1}{Rc}} \right)$$

$$= \frac{1}{Rc} \left[\frac{1}{\frac{1}{Rc} + j\omega} \right]$$


$$\frac{1}{Rc} = \omega_c$$

$\theta(j\omega)$

$$\omega_c = 500 \text{ MHz} = \frac{1}{RC}$$

$$2\pi \times 5 \times 10^8 \text{ Hz}$$
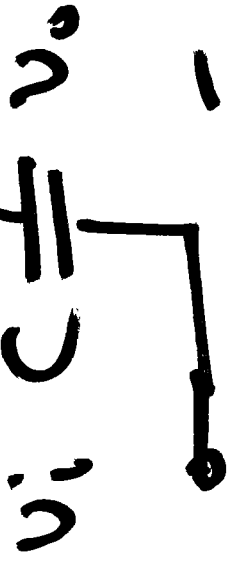
$$R + \frac{3.14 \times 10^9 \text{ rad}}{s} = \frac{1}{RC}$$



$$C = 22 \text{ pF}$$

$$R = \frac{1}{3 \times 10^9 + C} = \frac{1}{\omega_c C}$$

$$= \frac{1}{(3 \times 10^9)(2 \times 10^{-11})}$$

$$= \frac{1}{6 \times 10^{-2}} = \frac{100}{6} = 17.5 \Omega$$

$$\omega < \frac{1}{RC}$$

$$\frac{V_o}{V_i}$$

$$= \frac{1}{RC} \left(\frac{1}{\frac{1}{RC} + j\omega} \right)$$

$$= \frac{1}{RC} \left(\frac{1}{\frac{1}{RC}} \right) = 1$$


$$\omega > \frac{1}{RC} = \omega_c$$


$$= \frac{1}{RC} \left[\frac{1}{j\omega} \right] = \frac{1}{j\omega RC}$$

$$= \frac{1}{j\omega RC} = -\frac{j}{\omega RC}$$

for slope -1
log-log

20 dB/decade

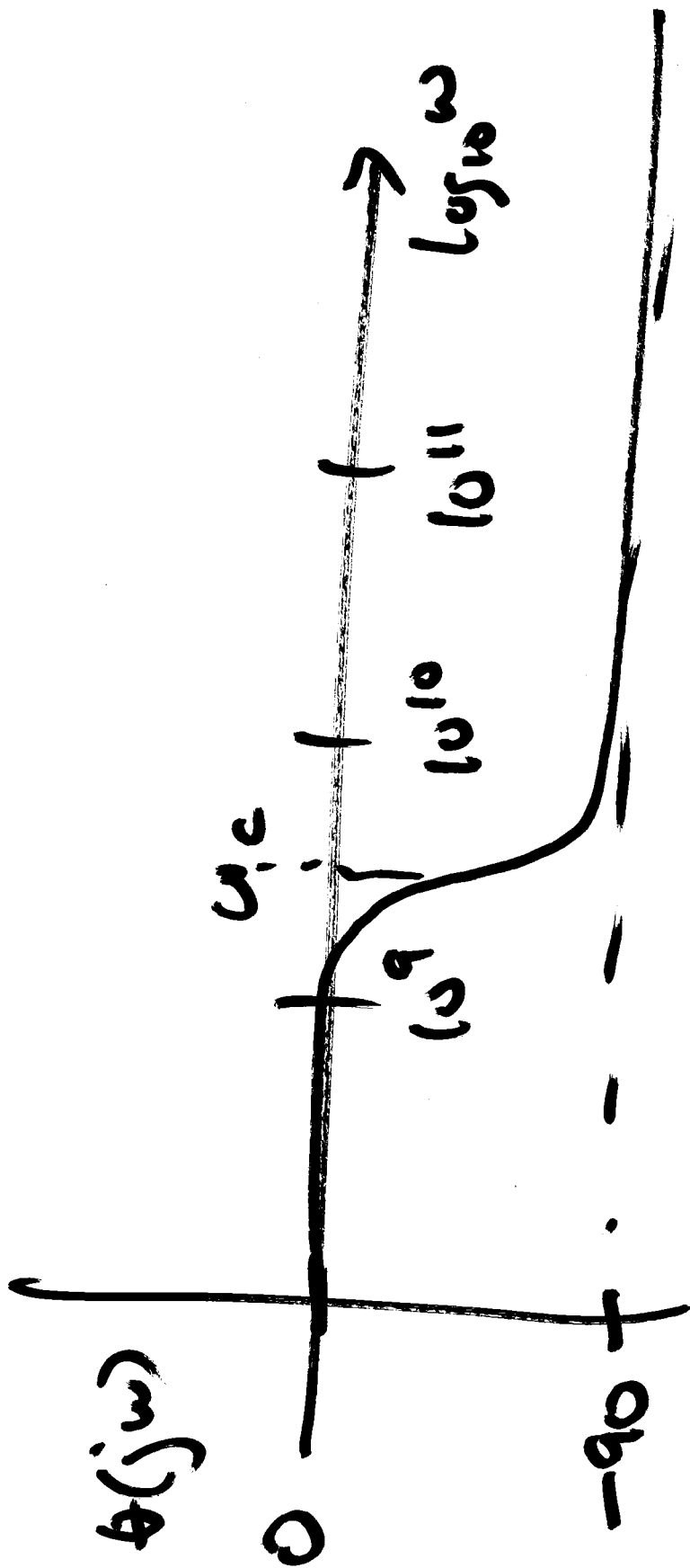

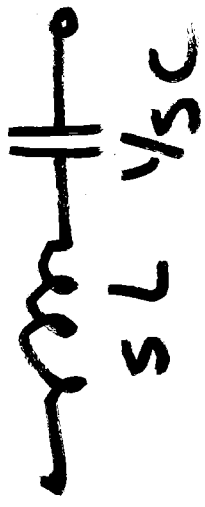

$$Z = sL + \frac{1}{sC}$$

$$= \frac{s^2 L + 1}{s}$$



$$Z \rightarrow 0$$



$$\omega \rightarrow \frac{1}{LC}$$


$$\omega_0 \rightarrow \sqrt{1/LC}$$

$$Z(j\omega) = \frac{-\omega^2 LC + 1}{j\omega C}$$



$$= \frac{1 - \omega^2 LC}{j\omega C}$$

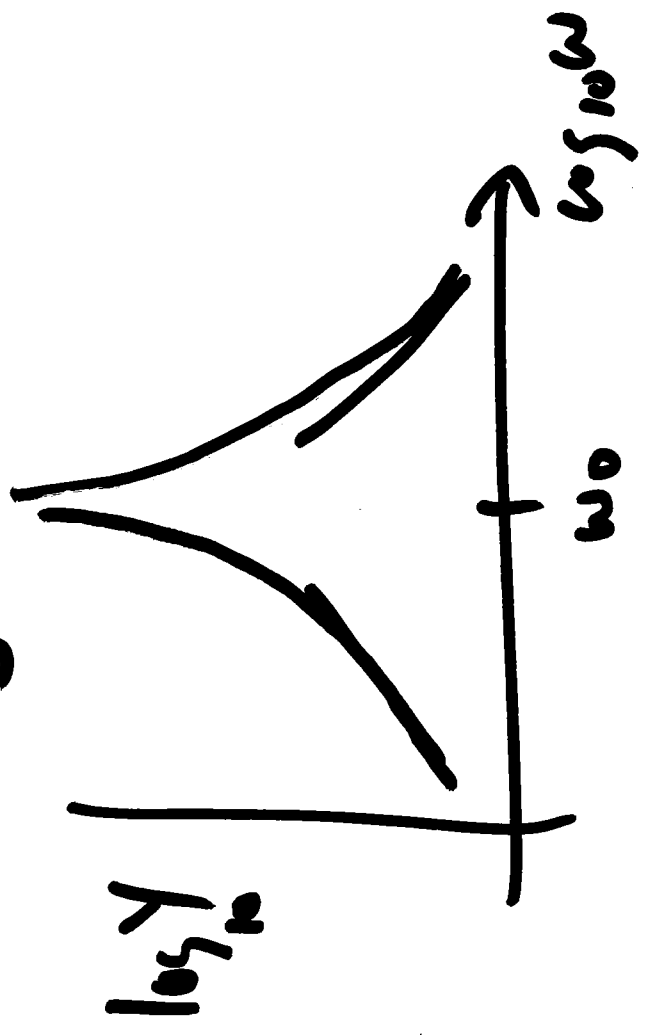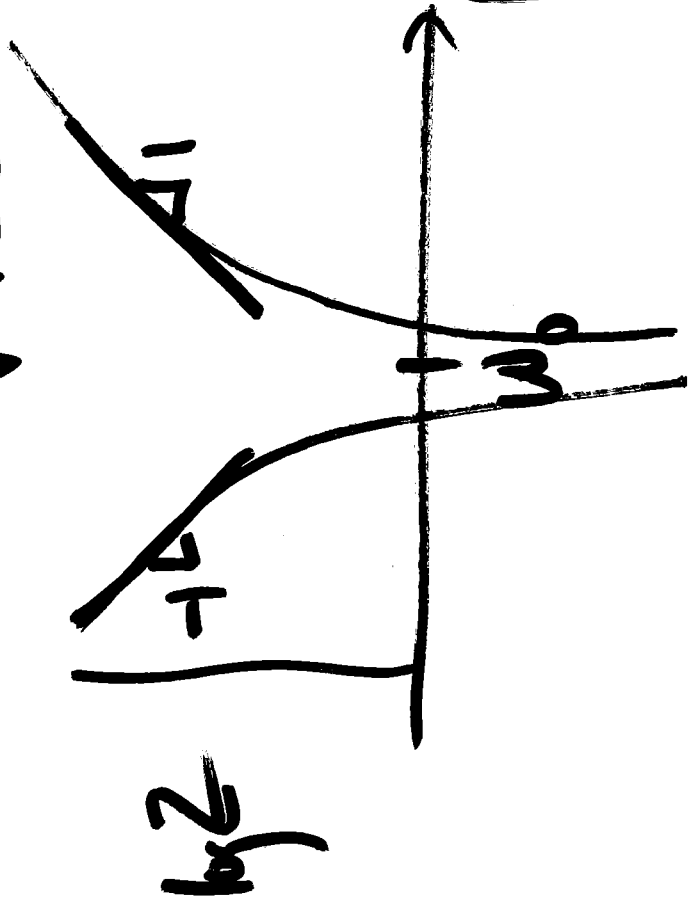

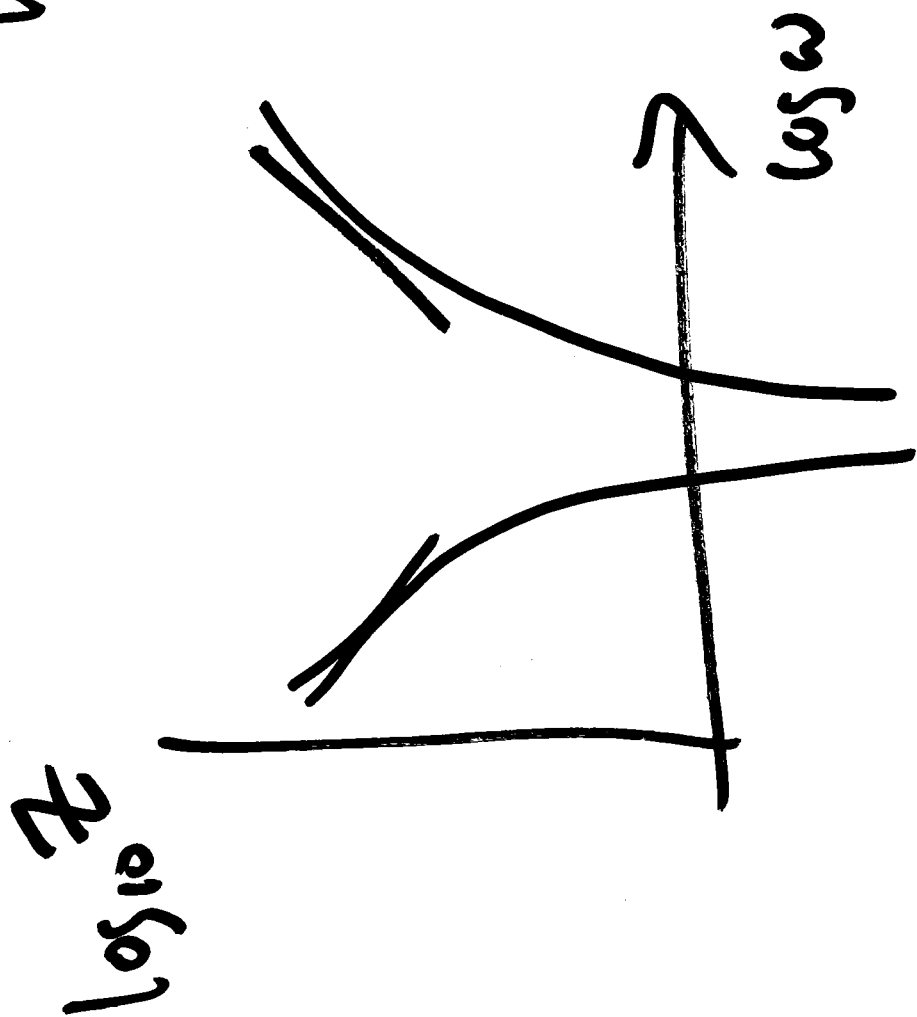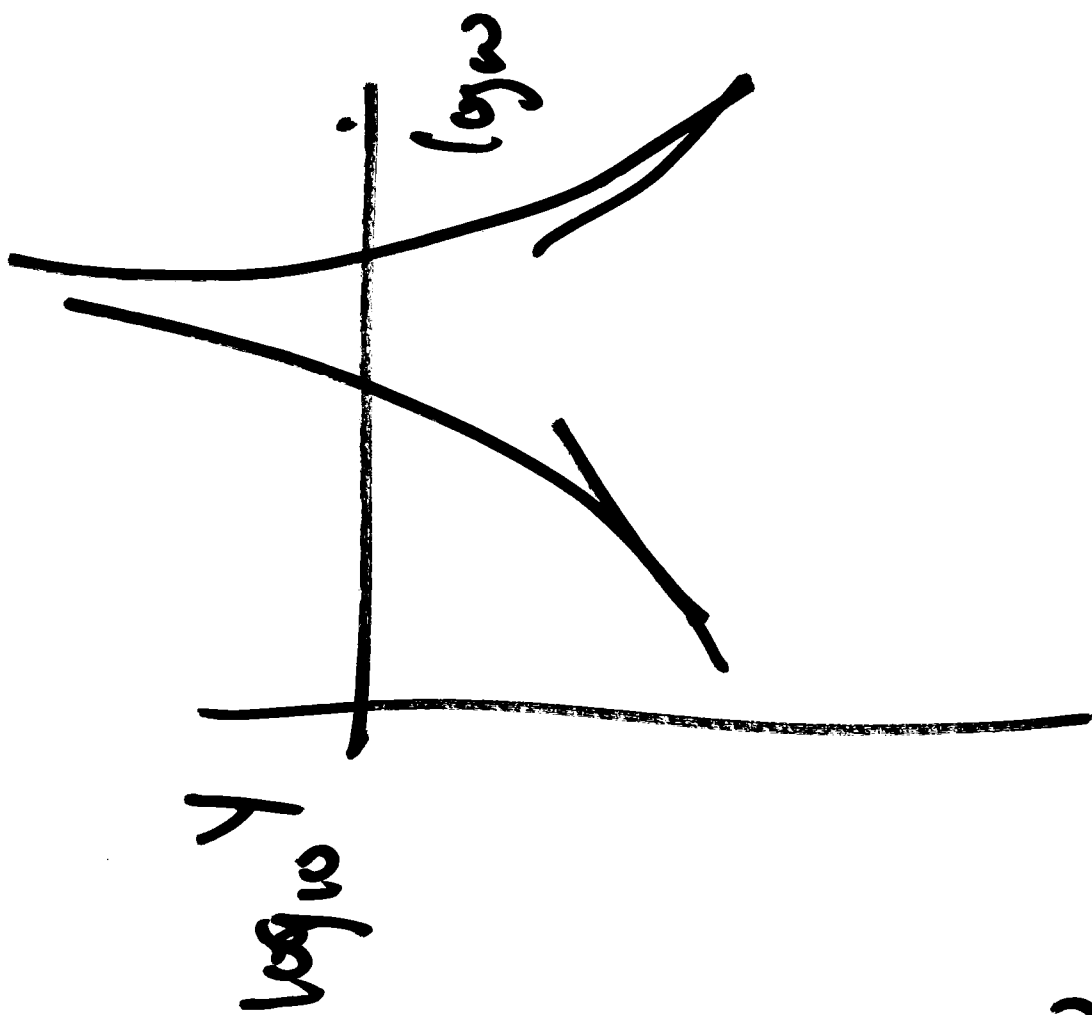

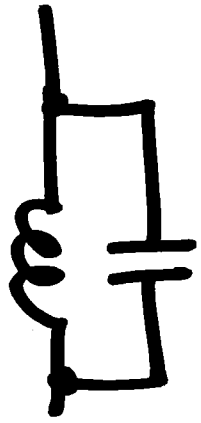
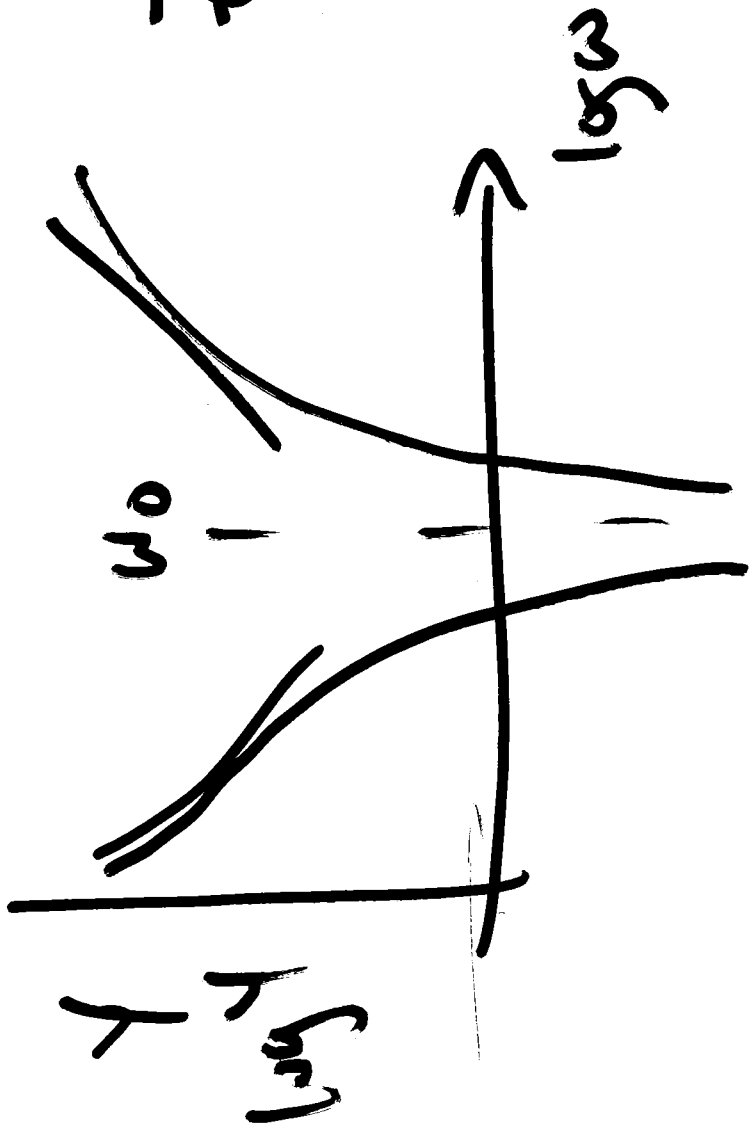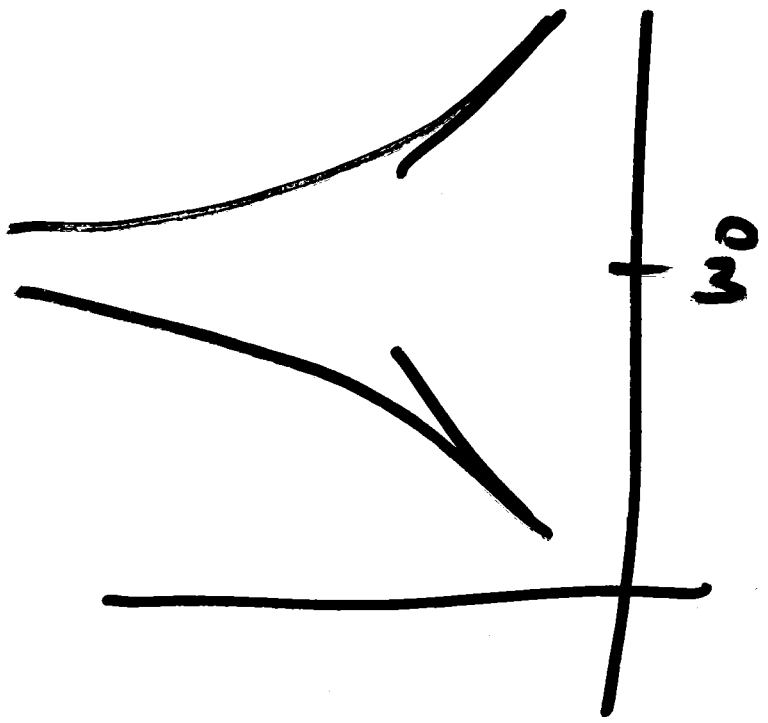
$$Y = sC + \frac{1}{sL} = \frac{1 - \omega^2 LC}{j\omega L}$$




$$\omega_c = R/L$$

$$\omega_c = RC$$

Band pass Filter

R, L, C

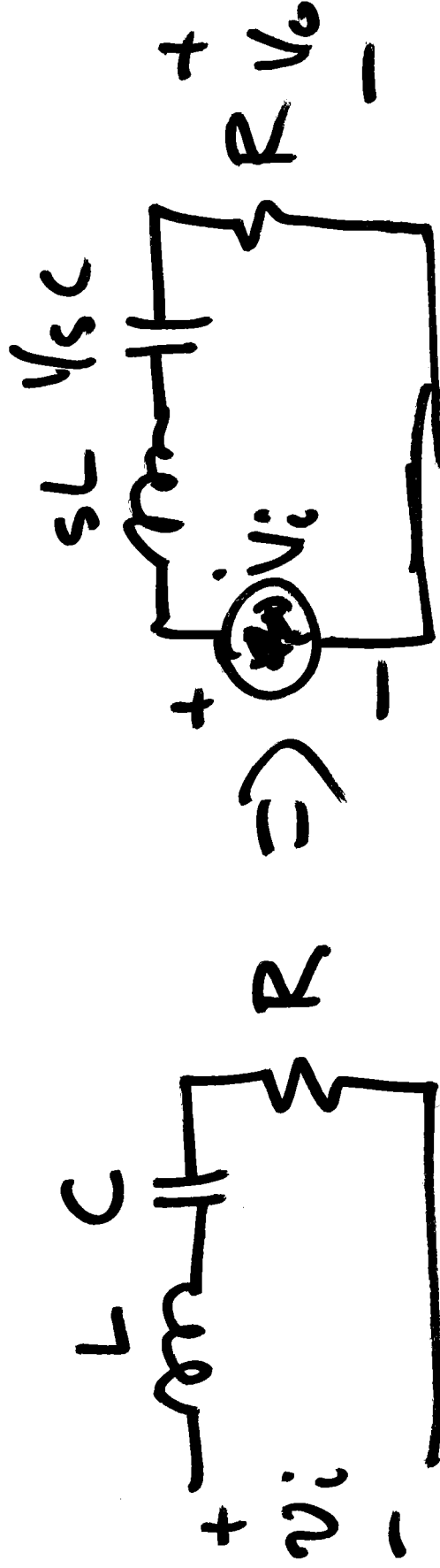

$$V_o(s) = \frac{R V_i(s)}{sL + 1/sC + R} = \frac{s(R/L) V_i(s)}{s^2 + s(R/L) + (1/LC)}$$


$$H(j\omega) = \frac{V_o(j\omega)}{V_i(j\omega)} = \frac{j\omega(R/L)}{-\omega^2 + j\omega(R/L) + (1/LC)}$$

Maximum of $H(j\omega)$

$$1/LC - \omega^2 = 0$$

$$\omega = \omega_0 = \sqrt{1/LC}$$

↑ center frequency

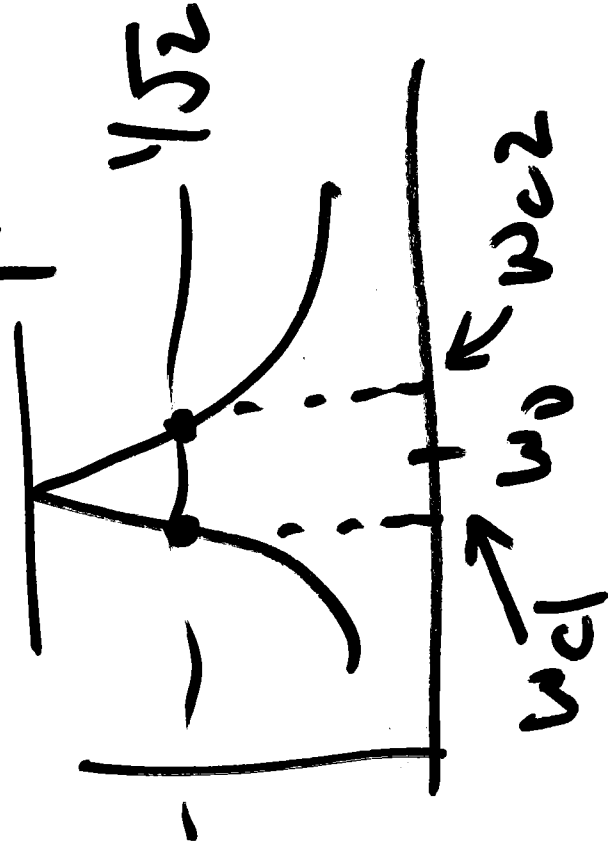

$$|H(j\omega)| = \frac{\omega R/L}{\sqrt{(\frac{\omega R}{L})^2 + (\frac{1}{LC} - \omega^2)^2}}$$

$$= \frac{1}{\sqrt{1 + \underbrace{\left[\frac{(\frac{1}{LC} - \omega^2)^2}{(\frac{\omega R}{L})^2} \right]}_{\neq 1}}} = \frac{1}{\sqrt{2}}$$

$$\frac{1}{LC} - \omega^2 = \pm \frac{\omega R}{L}$$

$$\omega^2 \pm \frac{\omega R}{L} - \frac{1}{LC} = 0$$

$$\omega = \frac{\pm \frac{R}{L} \pm \sqrt{\left(\frac{R}{L}\right)^2 + 4\left(\frac{1}{LC}\right)}}{2}$$


$$\omega_c = \pm \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \left(\frac{1}{LC}\right)}$$

$$\omega_{c1} = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

$$\sqrt{\omega_{c1}\omega_{c2}} = \sqrt{\left(\frac{R}{2L}\right)^2 + \left(\frac{1}{2L}\right)^2} - \left(\frac{R}{2L}\right)^2$$

$$\omega_0 = \sqrt{\frac{1}{LC}}$$
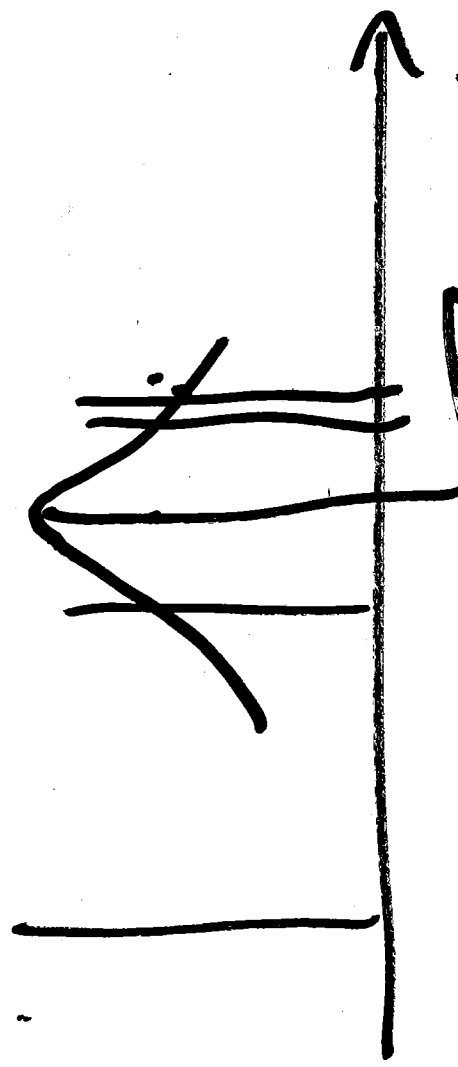
$$\frac{\omega_0}{\omega_{c1}} = \frac{\omega_{c2}}{\omega_0}$$




β = Bandwidth

$$= BW$$

$$= \omega_{c2} - \omega_{c1}$$

$$= R/L$$

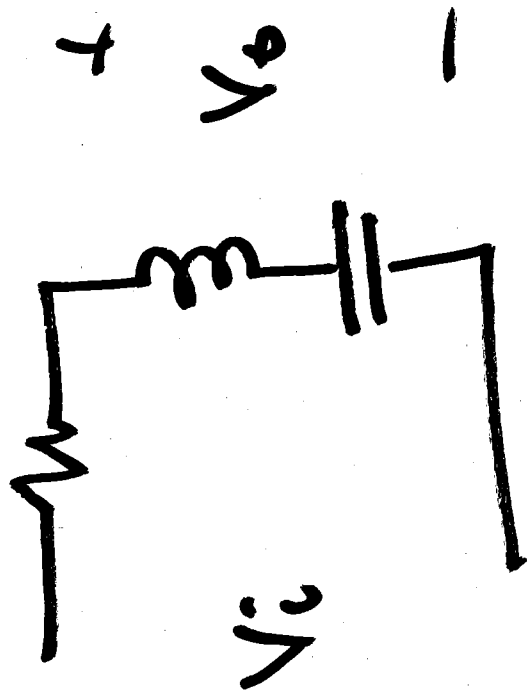
$$Q = \frac{\omega_0}{\beta} = \frac{\sqrt{1/LC}}{R/L} = \sqrt{\frac{L}{RC}} = \frac{1}{R} \sqrt{\frac{L}{C}}$$




$$H(s) = \frac{s^2 + (1/LC)}{s^2 + s(R/L) + (1/LC)}$$

Notch or

Band-reject
Filter

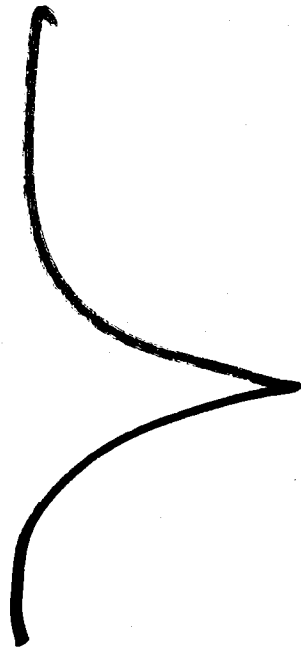

Band Reject Filter

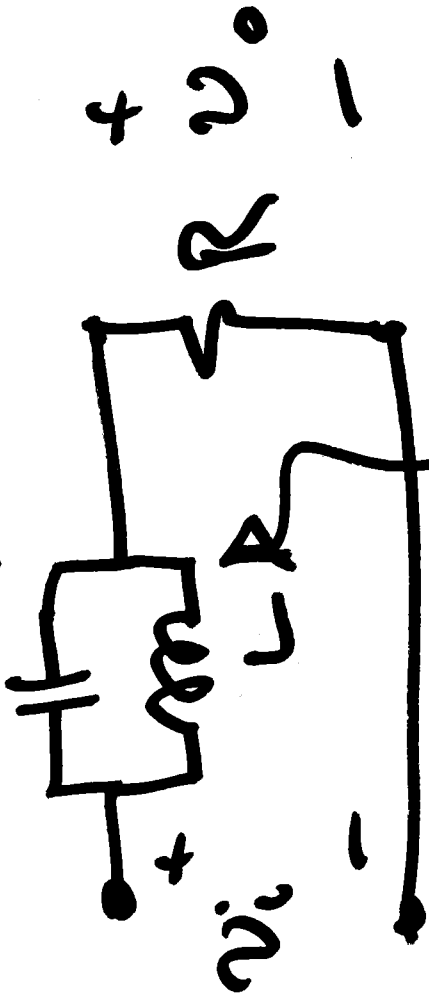

Band Pass

$$Z_{LC} = \frac{j\omega L}{j\omega L + 1/C} = \frac{j\omega L}{j\omega L + 1/C}$$

$$H(s) = \frac{V_o(s)}{V_i(s)}$$

$$= \frac{R}{R + sL + \frac{1}{sC}}$$

$$= \frac{R(sL + 1/C)}{R(sL + 1/C) + sL}$$


$$H(s) = \frac{R(s^2 LC + 1)}{R(s^2 LC + 1) + sL} = \frac{s^2 RLC + R}{s^2 RLC + R + sL}$$

$$= \frac{s^2 + 1/LC}{s^2 + s/RC + 1/LC}$$

$$H(j\omega) = \frac{-\omega^2 + 1/LC}{-\omega^2 + j\omega/R_C + 1/LC}$$

$$= \frac{1/LC - \omega^2}{1/LC - \omega^2 + j\omega/R_C}$$

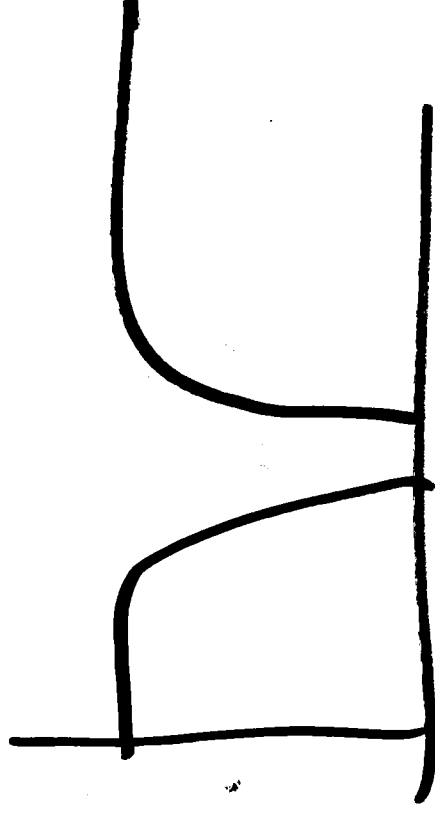
$$\omega = \omega_0 = \sqrt{1/LC} \Rightarrow H(j\omega) = 0$$



$$Q = \omega_0 R_C$$

$$= \frac{R_C}{\sqrt{1/LC}} = R\sqrt{C/L}$$

Loaded Passive Filter

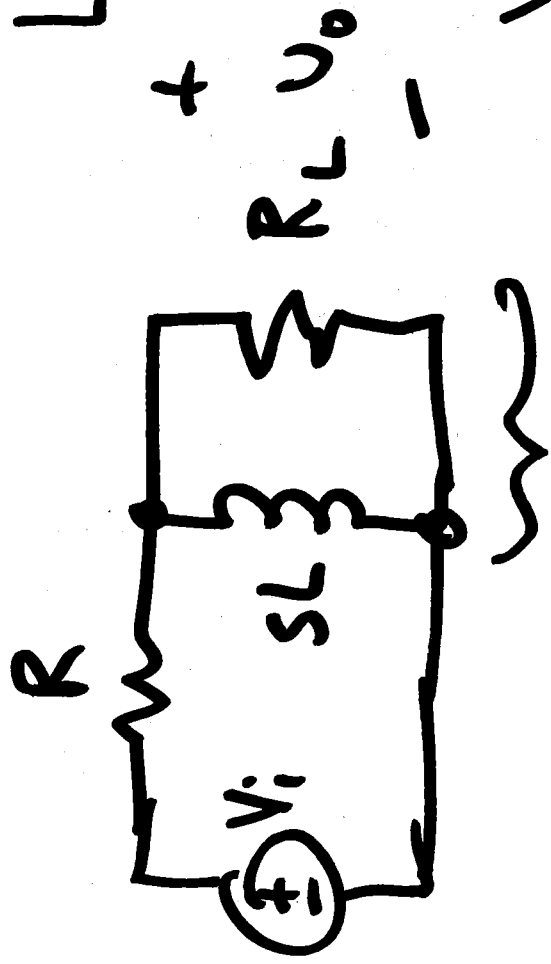

$$Z = \left(\frac{R_L sL}{R_L + sL} \right) \quad \frac{V_o}{V_i} = \frac{R_L Z}{Z + R}$$

$$= \frac{R_L sL}{R_L + sL} = \frac{R + \frac{R_L sL}{R_L + sL}}{R + \frac{R_L sL}{R_L + sL}}$$

~~$$s \left(\frac{R_L}{R_L + sL} \right)$$~~

$$= \frac{R_L sL}{R(R_L + sL) + R_L sL} = \frac{s(R_L)}{s(R_L + R_L) + R R_L}$$

$$= \frac{s \left(\frac{R_L Y}{R_Y + R_L Y} \right)}{s + \frac{R R_L}{R_L + R_L L}} = \frac{s \left(\frac{R_L}{R + R_L} \right)}{s + \frac{R}{L} \left(\frac{R_L}{R + R_L} \right)}$$

$$K = R_L / (R + R_L)$$

$$K = 1 \text{ unloaded}$$

$$K < 1 \text{ loaded}$$

$$H(s) = \frac{K s}{s + K \frac{R}{L}}$$

$$\text{peak gain} = K$$

$$\omega_c: K \frac{R}{L} = \omega_c$$

$$H(j\omega) = \frac{j\omega K}{j\omega + K \frac{R}{L}}$$


$$H(s) = K \frac{s^m + a_1 s^{m-1} + \dots + a_m s^0}{s^n + b_1 s^{n-1} + \dots + b_n s^0}$$

$$\lim_{s \rightarrow \infty} H(s) = K s^{m-n} \quad m > n$$

$s \rightarrow \infty$ $\swarrow$ non-zero

$$\lim_{\substack{s \rightarrow 0 \\ \omega \rightarrow 0}} H(j\omega) = K \frac{a_m}{b_n} \quad m = n$$

$$m < n$$

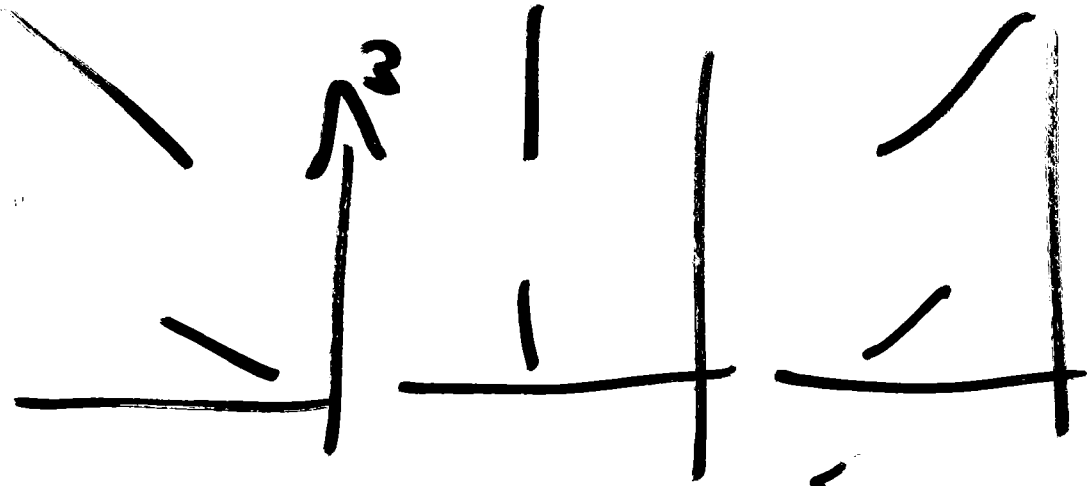

$$H(s) = \frac{K(s+z_1)(s+z_2) \dots}{(s+p_1)(s+p_2)}$$

1 Real pole $s = -a$


$$H(s) = \frac{Ka}{s+a}$$

$\rightarrow K$ $|H(j\omega)|_{\text{corner}}$

$$H(j\omega) = \frac{Ka}{j\omega + a}$$

$$a = \omega$$
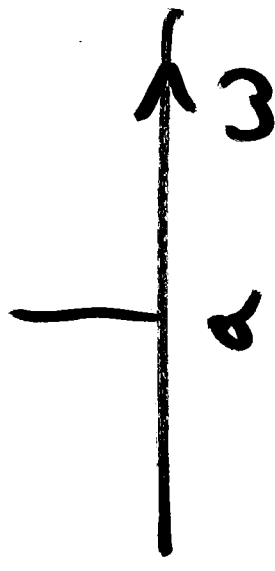
$$H(j\omega) = K \left(\frac{a}{a(1+j)} \right)$$



$$|H(ja)| = K/\sqrt{2} = 0.707K$$

dB often used for magnitude of gain

$$\left| \frac{V_o}{V_i} \right| \equiv \text{gain}$$

$$|H(j\omega)| = 1 \quad 0\text{dB}$$


$$= 0.1 \quad -20\text{dB}$$

$$= 10 \quad +20\text{dB}$$

$$= 0.707 \quad -3\text{dB}$$

$$\text{dB} = 20 \log_{10} |H(j\omega)|$$

$$\frac{K a}{a + j\omega}$$

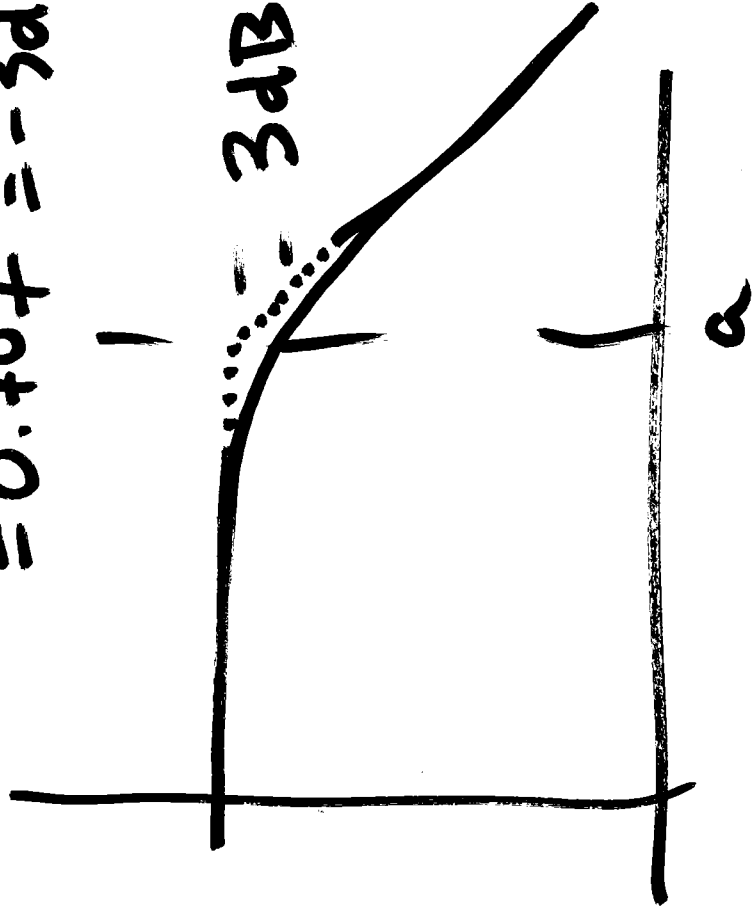

$$\Rightarrow -6\text{dB}$$

$$-10\text{dB}$$

$$+20-6 = 14\text{dB}$$

$$6+6+6 = 18\text{dB}$$

"

$$\frac{1}{2} \quad \frac{1}{\sqrt{10}}$$

$$5$$

$$8 \\ = 2^3$$

$$K \frac{s+a}{a}$$

K

= 3dB

$$K \left(\frac{s+a}{a} \right) \left(\frac{b}{s+b} \right)$$

log K

3dB

a

a

Zero

b


3dB

-1

-1


$$\frac{a}{s+a}$$

Bode Plot

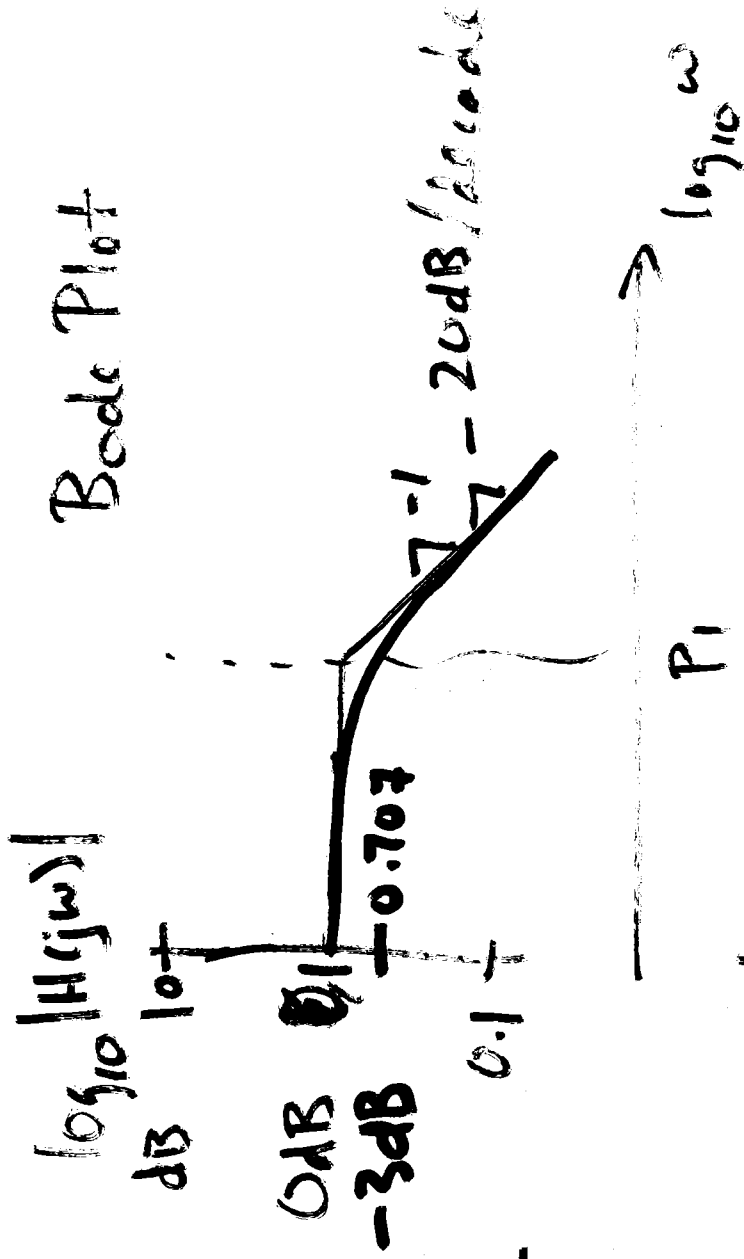

$$\frac{P_1}{s + P_1}$$

$$\frac{P_1}{s + j\omega + P_1}$$

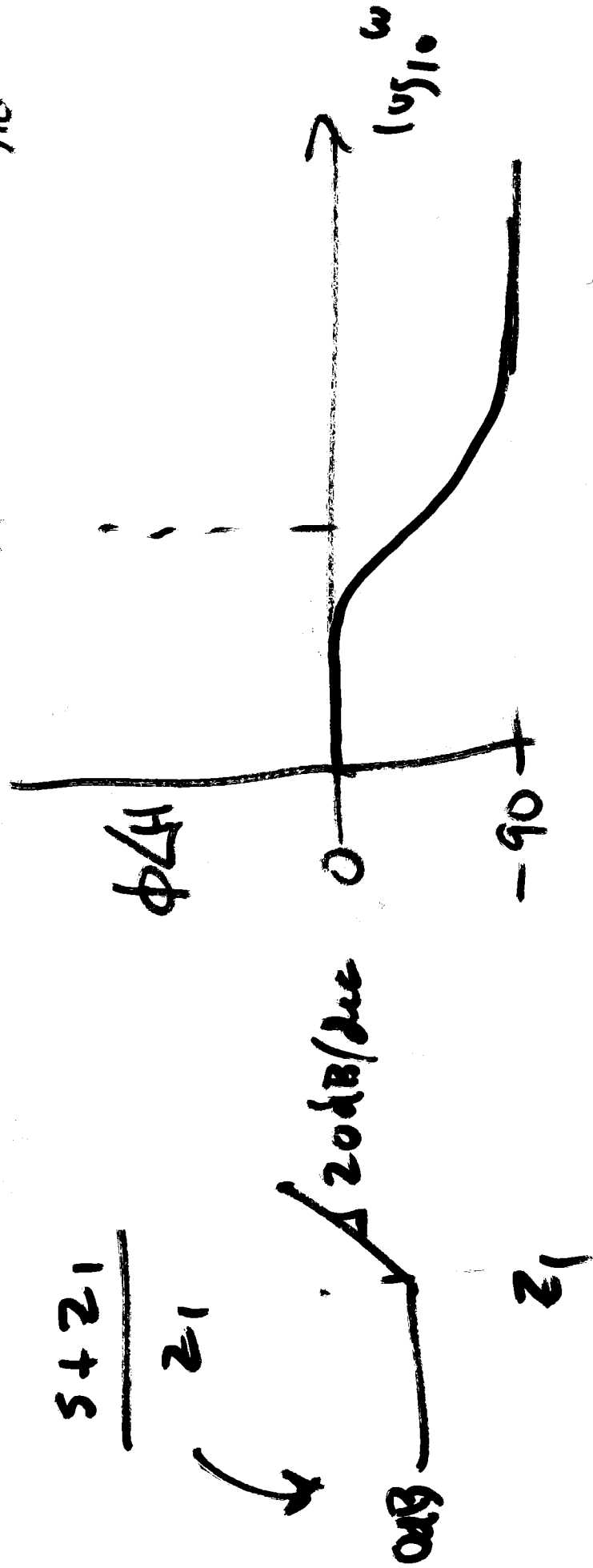

$$\frac{s + z_1}{s + z_2}$$

$$H(s) = \frac{s(s+10^7)100}{(s+100)(s+10^4)(s+10^5)}$$


Zeros @ $0, 10^7$ rad/s

Poles @ $100, 10^4, 10^5$ rad/s

$$\approx \frac{\cancel{(j\omega)} \cancel{10^7} 10^2}{\cancel{(j\omega)} \cancel{10^4} 10^5} \approx \frac{1}{j\omega} \approx 10^{-7} \text{ rad/s}$$

$$\omega \rightarrow \infty$$

$$\frac{100(j\omega)^2}{(j\omega)^3}$$

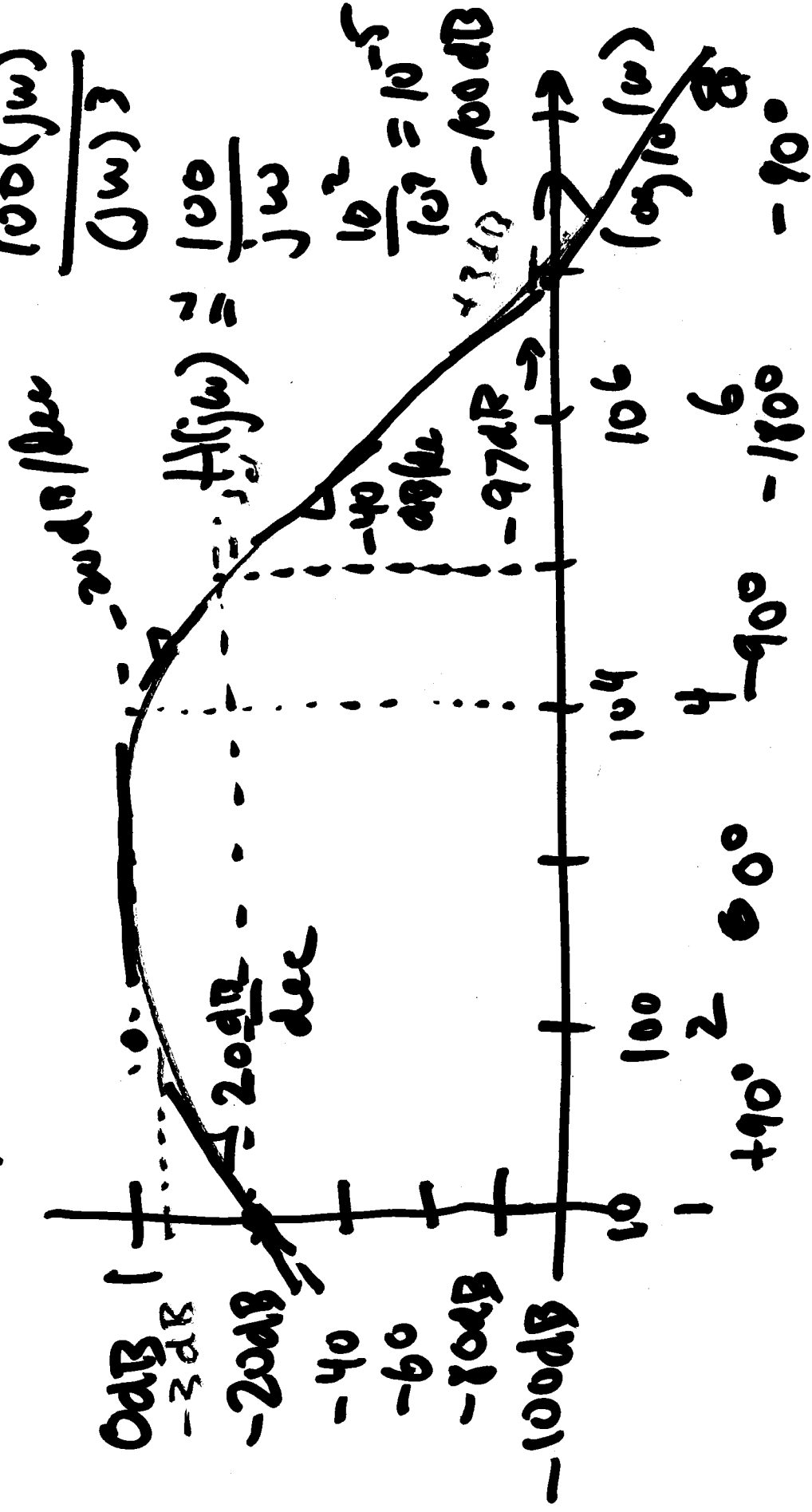

$$s^2 + 2\alpha s + \omega_0^2$$

$$s^2 + \underset{\uparrow}{b}s + \omega_0^2$$

bandwidth

$$-\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$\omega_0^2 = \alpha^2 + \beta^2$$


$$-\alpha \pm j\beta$$


$$2|K|e^{-\alpha t} \cos(\beta t + \theta)$$

$$s^2 + \frac{\omega_0}{Q}s + \omega_0^2 \quad \log |H(j\omega)|$$


$$H(j\omega) = \frac{-\omega^2 + j\omega\omega_0 + \omega_0^2}{\omega_0^2}$$

$$@ \omega = \omega_0 \quad |H(j\omega)| = \frac{j\omega_0}{Q\omega_0^2} = \frac{1}{Q} \frac{\omega_0}{\omega_0}$$

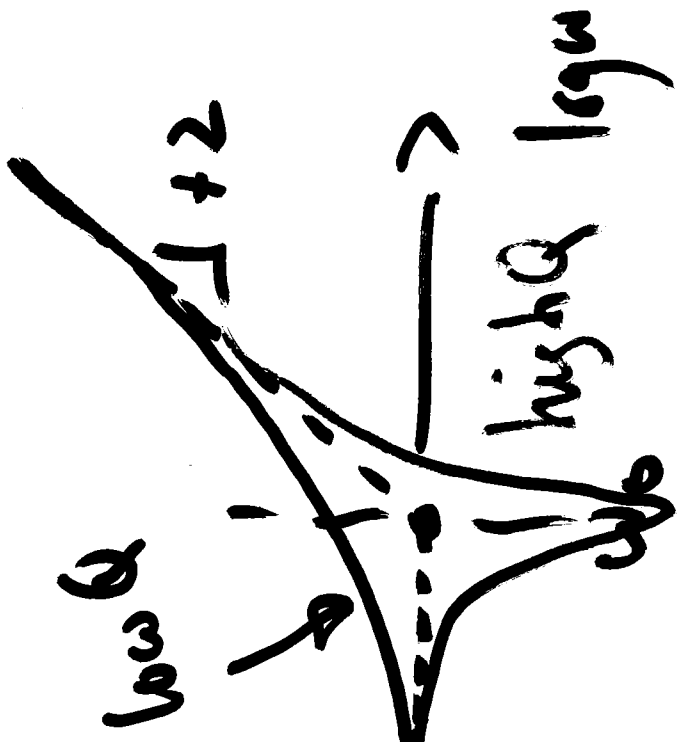

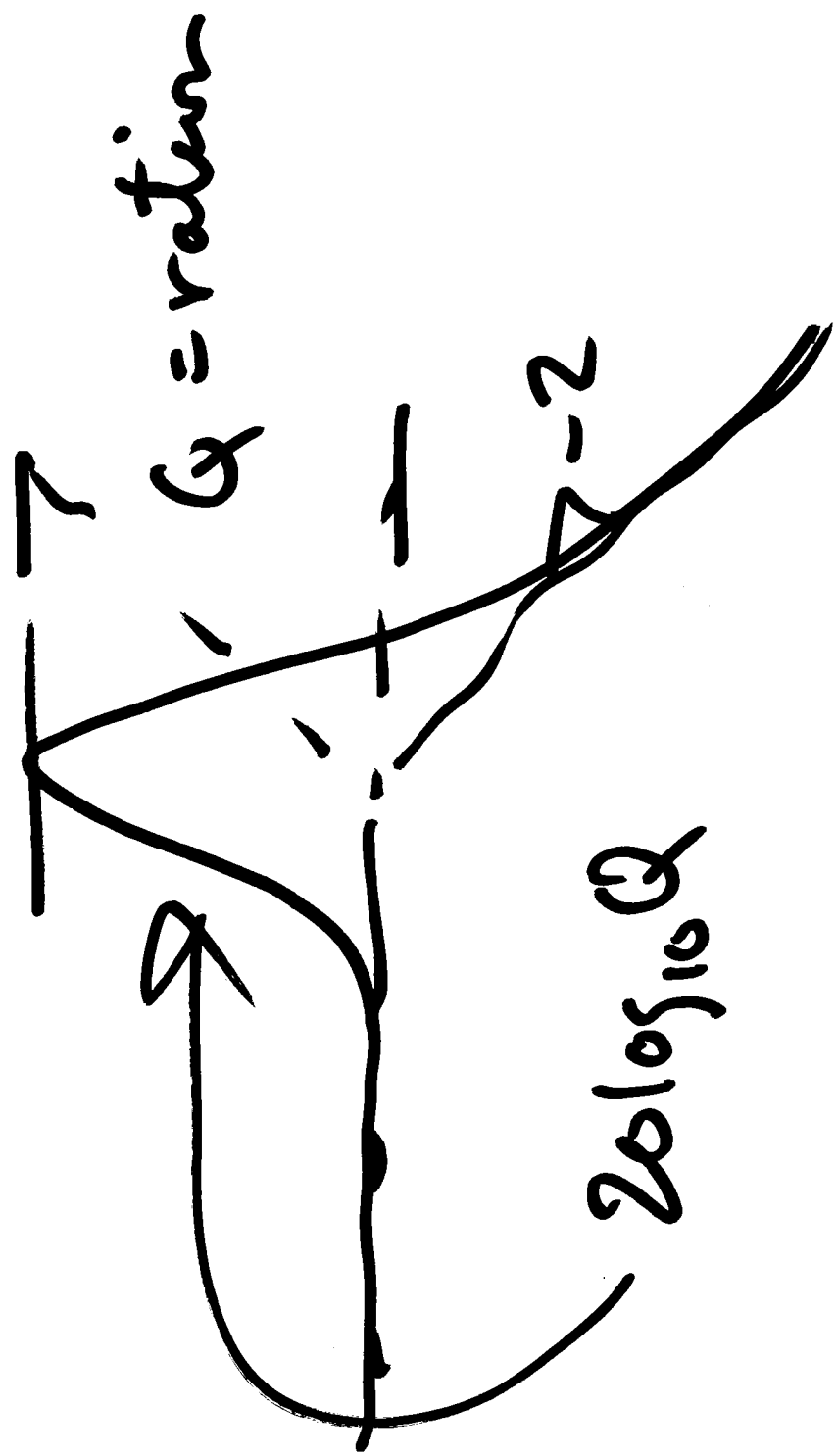
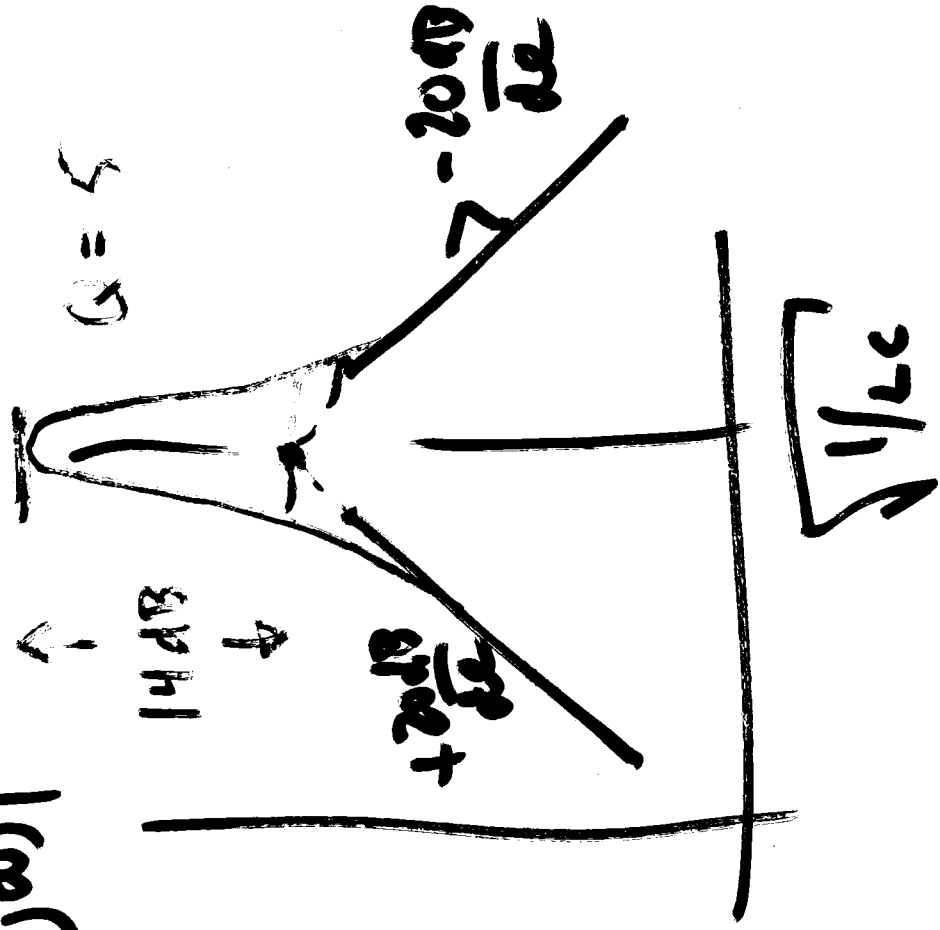
$$H(s) = \frac{K/s}{s^2 + \frac{K}{J}s + \frac{1}{J}}$$



$$\omega_0^2 = \frac{1}{J}$$

$$\frac{\omega_0}{\alpha} = \frac{K}{J}$$