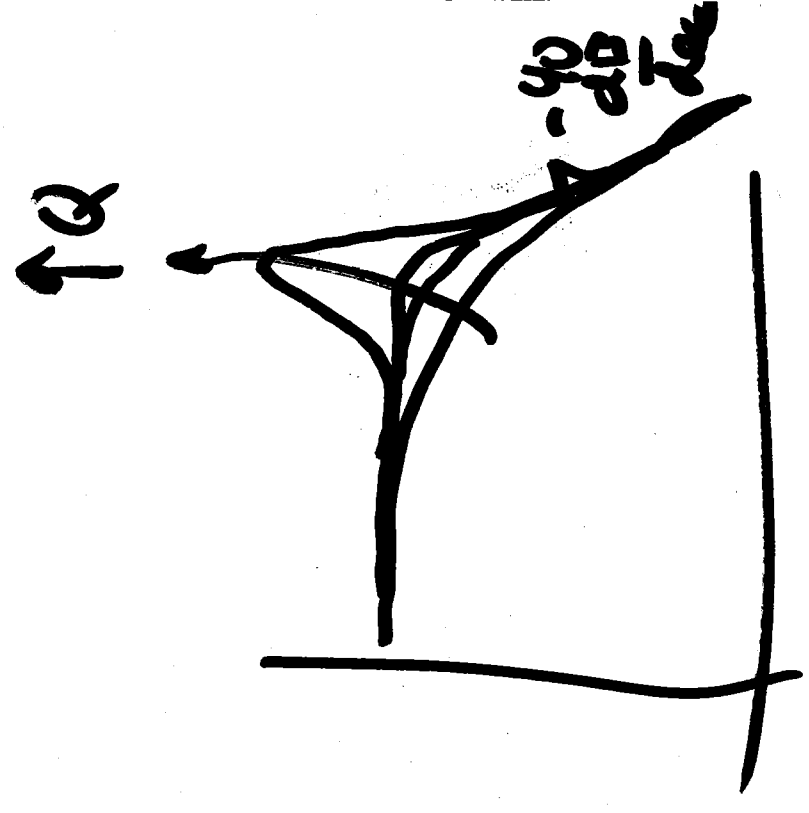


1. Phasors, SSS $\leftarrow$
2. Laplace, transient $\rightarrow$
3. Filters, design $\rightarrow$
- 4.

$$\frac{\omega_0^2}{s^2 + \frac{\omega_0}{Q}s + \omega_0^2}$$

low $Q < 1/2 \Rightarrow 2 \text{ real roots}$

$$\frac{\omega_0^2}{(s + \omega_{c1})(s + \omega_{c2})} \quad \omega_{c1}, \omega_{c2} = \omega_0^2$$



Transient response


impulse response

$$H(s) = \frac{K_1}{s + \omega_{c1}} + \frac{K_2}{s + \omega_{c2}}$$

$$K_1 e^{-\omega_{c1} t} + K_2 e^{-\omega_{c2} t}$$

$\cos(\omega t)$
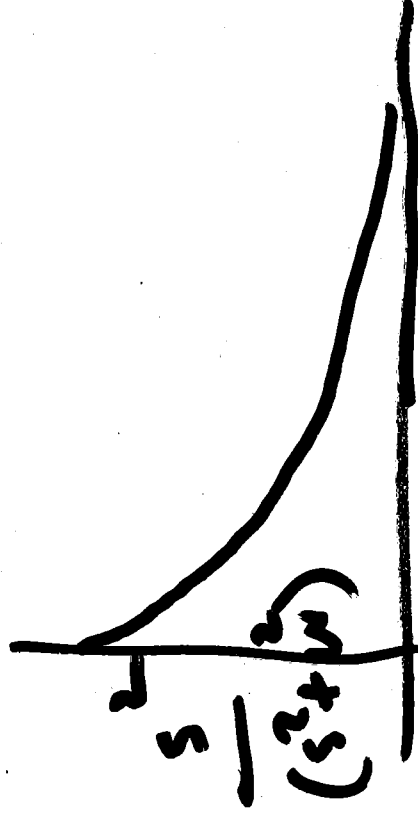
$$H(s) = \frac{\omega_0^2}{s^2 + \frac{\omega_0}{Q}s + \omega_0^2}$$




$Q_1 > 1 \Rightarrow$ complex conj pair of roots

$$H(s) = \frac{\omega_0^2}{s^2 + \frac{\omega_0}{Q}s + \omega_0^2}$$


Impulse response

$$H(s) = \frac{k_1}{s - \alpha + \beta j} + \frac{k^*}{s - \alpha - \beta j}$$
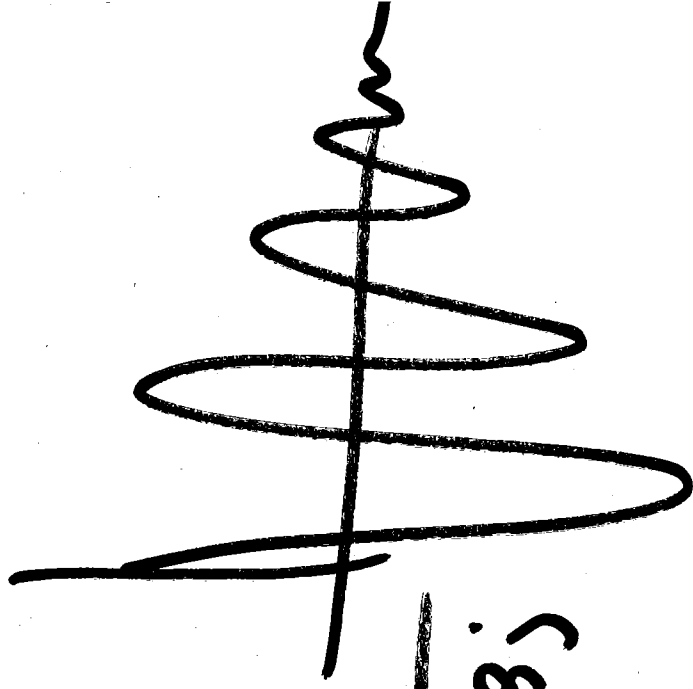
$$h(t) = e^{-\alpha t} \cos(\beta t + \phi)$$




Two ports

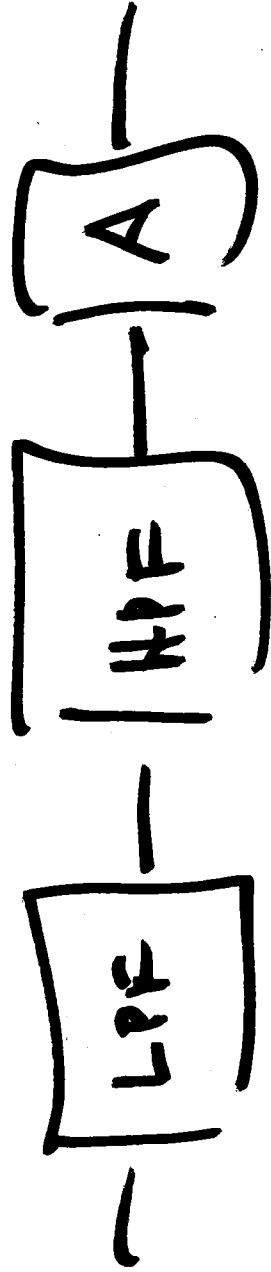


Active op-amp circuit

had

$$Z_{out} = 0$$

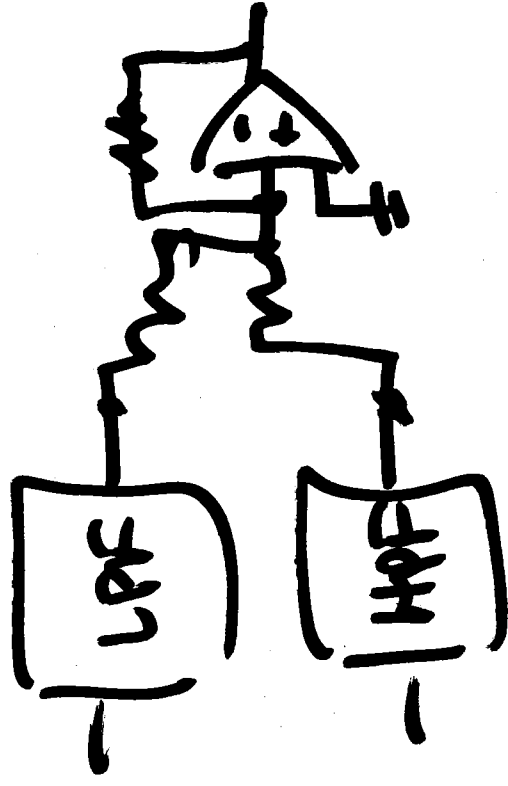

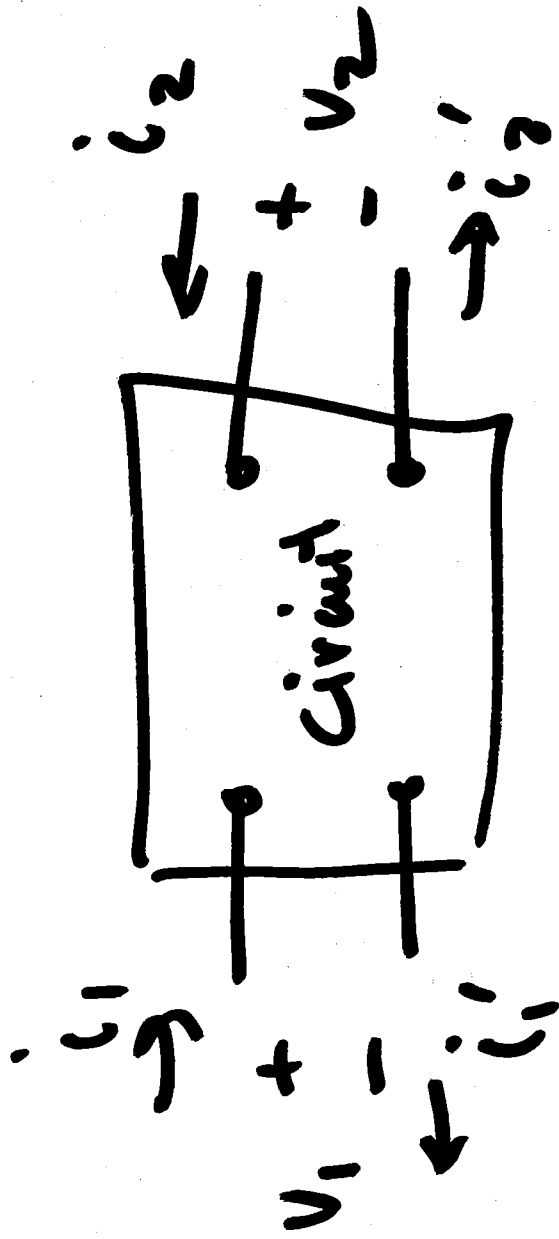

Know any 2 $\Rightarrow$ Calculate the other 2

$$V_1 = \underline{z_{11}} I_1 + \underline{z_{12}} I_2$$

$$V_2 = \underline{z_{21}} I_1 + \underline{z_{22}} I_2$$

$$I_2 = 0 \Rightarrow \underline{z_{11}} = \frac{V_1}{I_1} \quad \underline{z_{21}} = \frac{V_2}{I_1}$$

$$I_1 = 0 \Rightarrow \underline{z_{12}} = \frac{V_1}{I_2}$$

$$\underline{z_{22}} = \frac{V_2}{I_2}$$

r terminal variables, only two are independent. Thus for we specify two of the variables, we can find the two owns. For example, knowing V_1 and V_2 and the circuit we can determine I_1 and I_2 . Thus we can describe a two- h just two simultaneous equations. However, there are six which to combine the four variables:

$$\begin{aligned} I_1 &= y_{11}V_1 + y_{12}V_2, \\ I_2 &= y_{21}V_1 + y_{22}V_2; \end{aligned} \quad \hat{\mathbf{I}} = \hat{\mathbf{Y}}\hat{\mathbf{V}} \quad (18.2)$$

$$\begin{aligned} V_1 &= a_{11}V_2 - a_{12}I_2, \\ I_1 &= a_{21}V_2 - a_{22}I_2; \end{aligned} \quad \text{transmission} \quad (18.3)$$


$$\begin{aligned} V_2 &= b_{11}V_1 - b_{12}I_1, \\ I_2 &= b_{21}V_1 - b_{22}I_1; \end{aligned}$$

$$\begin{cases} V_1 = h_{11}I_1 + h_{12}V_2, \\ I_2 = h_{21}I_1 + h_{22}V_2; \end{cases} \quad \text{hybrid} \quad (18.5)$$


$$\left. \begin{aligned} I_1 &= g_{11}V_1 + g_{12}I_2, \\ V_2 &= g_{21}V_1 + g_{22}I_2. \end{aligned} \right\} \quad (18.6)$$

sets of equations may also be considered as three pairs of relations. The first set, Eqs. 18.1, gives the input and output functions of the input and output currents. The second set, Eqs. 18.2, gives the input and output voltages in terms of the input and output currents, that is, the input and output cur-

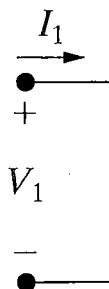Therefore the inductance L can be measured by first opening the switch S to measure V_2/I_1 , and then opening the switch S_1 to measure V_2/I_2 . Example 18.1 illustrates this procedure in a representative circuit.



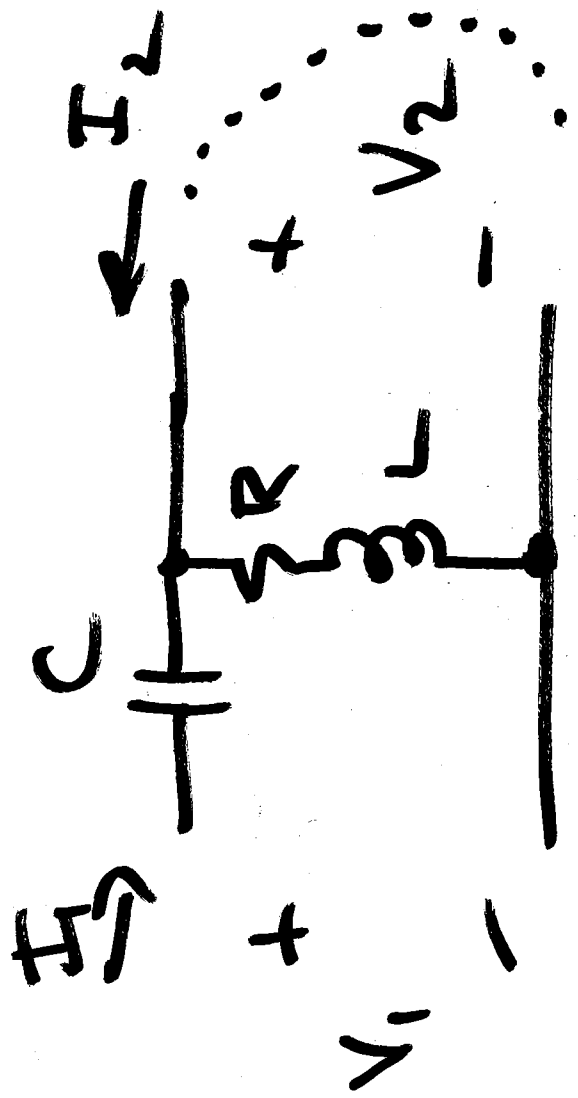The circuit is purely resistive, so the average power in the circuit is also purely resistive. Since $I_2 = 0$, the resistance of the $20\ \Omega$ resistor in parallel with the $5\ \Omega$ and $15\ \Omega$ resistors is



Calculate

H-parameters

$$h_{11}, h_{21} \Rightarrow V_2 = 0 \quad h_{11} = \frac{V_1}{I_1} \bigg|_{V_2=0} = \frac{1}{sC}$$

$$h_{12}, h_{22} \Rightarrow I_1 = 0 \quad h_{21} = \frac{I_2}{I_1} \bigg|_{V_2=0} = -1$$

$$h_{12} = \frac{V_1}{V_2} \bigg|_{I_1=0} = 1$$

$$h_{22} = \frac{I_2}{V_2} \bigg|_{I_1=0} = \frac{1}{R+sL}$$

$$a_{11} = - \frac{\Delta h}{h_{21}} = \frac{-(h_{11}h_{22} - h_{12}h_{21})}{h_{21}}$$


$$= - \left[\frac{\frac{1}{sC(R+sL)} + 1}{-1} \right] = \frac{sC(R+sL)+1}{sC(R+sL)}$$


a_{12}

a_{21}

a_{22}

$Z:$

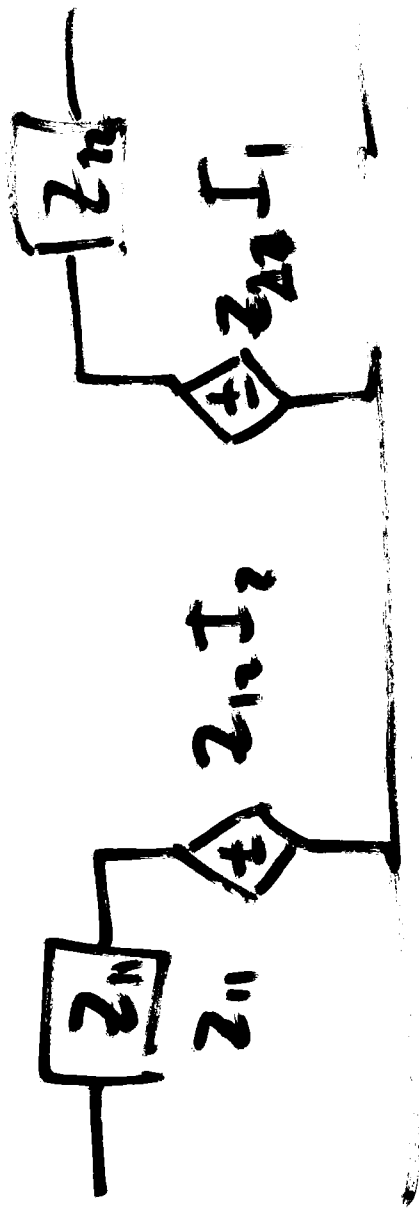


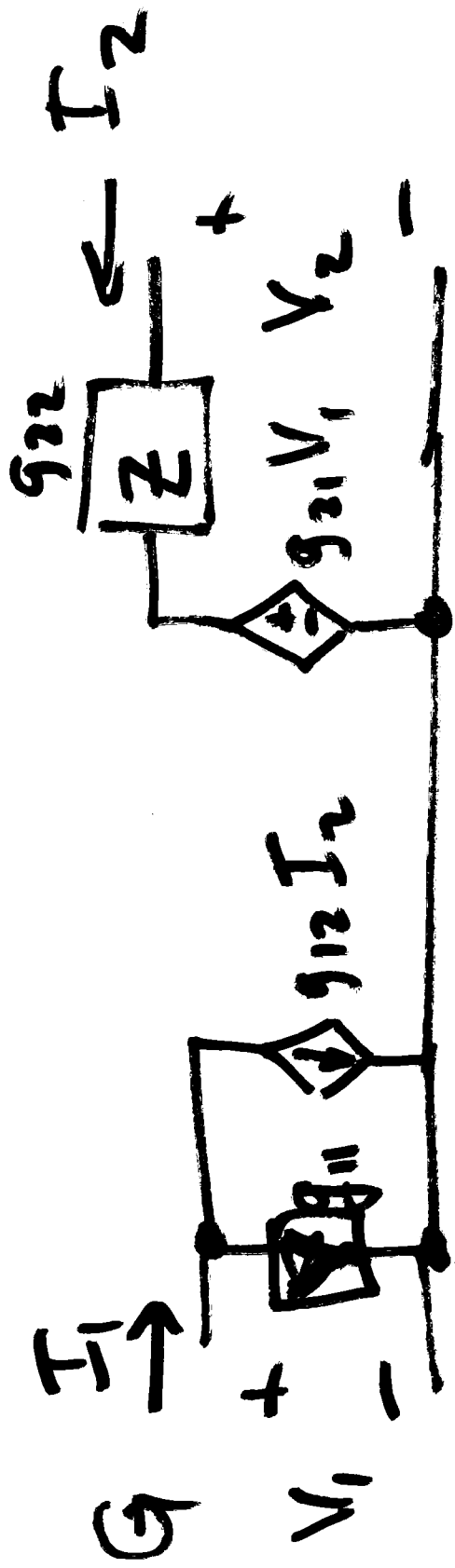

$$I_1 = V_1 g_{11} + g_{12} I_2$$

$$V_2 = g_{21} V_1 + g_{22} I_2$$
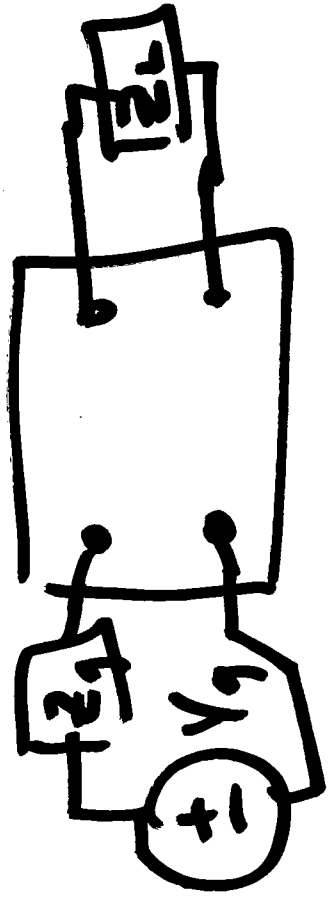
$$= G \begin{bmatrix} V_1 \\ I_2 \end{bmatrix}$$



$$Z_{in} = \frac{V_1}{\text{output } I_1 \text{ current } I_2}$$

~~output current I_2~~

$$V_{th}, Z_{th}$$

$$I_2 / I_1$$

$$V_2 / V_1$$

$$V_2 / V_g$$

TABLE 18.2 Terminated Two-Port Equations

z Parameters

$$Z_{in} = z_{11} - \frac{z_{12}z_{21}}{z_{22} + Z_L}$$

$$I_2 = \frac{-z_{21}V_g}{(z_{11} + Z_g)(z_{22} + Z_L) - z_{12}z_{21}}$$

$$V_{Th} = \frac{z_{21}}{z_{11} + Z_g}V_g$$

$$Z_{Th} = z_{22} - \frac{z_{12}z_{21}}{z_{11} + Z_g}$$

$$\frac{I_2}{I_1} = \frac{-z_{21}}{z_{22} + Z_L}$$

$$\frac{V_2}{V_1} = \frac{z_{21}Z_L}{z_{11}Z_L + \Delta z}$$

$$\frac{V_2}{V_g} = \frac{z_{21}Z_L}{(z_{11} + Z_g)(z_{22} + Z_L) - z_{12}z_{21}}$$

a Parameters

$$Z_{in} = \frac{a_{11}Z_L + a_{12}}{a_{21}Z_L + a_{22}}$$

$$I_2 = \frac{-V_g}{a_{11}Z_L + a_{12} + a_{21}Z_gZ_L + a_{22}Z_g}$$

$$V_{Th} = \frac{V_g}{a_{11} + a_{21}Z_g}$$

$$Z_{Th} = \frac{a_{12} + a_{22}Z_g}{a_{11} + a_{21}Z_g}$$

$$\frac{I_2}{I_1} = \frac{-1}{a_{21}Z_L + a_{22}}$$

$$\frac{V_2}{V_1} = \frac{Z_L}{a_{11}Z_L + a_{12}}$$

$$\frac{V_2}{V_g} = \frac{Z_L}{(a_{11} + a_{21}Z_g)Z_L + a_{12} + a_{22}Z_g}$$

h Parameters

$$Z_{in} = h_{11} - \frac{h_{12}h_{21}Z_L}{1 + h_{22}Z_L}$$

$$I_2 = \frac{h_{21}V_g}{(1 + h_{22}Z_L)(h_{11} + Z_g) - h_{12}h_{21}Z_L}$$

$$V_{Th} = \frac{-h_{21}V_g}{h_{22}Z_g + \Delta h}$$

$$Z_{Th} = \frac{Z_g + h_{11}}{h_{22}Z_g + \Delta h}$$

$$\frac{I_2}{I_1} = \frac{h_{21}}{1 + h_{22}Z_L}$$

$$\frac{V_2}{V_1} = \frac{-h_{21}Z_L}{\Delta hZ_L + h_{11}}$$

$$\frac{V_2}{V_g} = \frac{-h_{21}Z_L}{(h_{11} + Z_g)(1 + h_{22}Z_L) - h_{12}h_{21}Z_L}$$

y Parameters

$$Y_{in} = y_{11} - \frac{y_{12}y_{21}Z_L}{1 + y_{22}Z_L}$$

$$I_2 = \frac{y_{21}V_g}{1 + y_{22}Z_L + y_{11}Z_g + \Delta yZ_gZ_L}$$

$$V_{Th} = \frac{-y_{21}V_g}{y_{22} + \Delta yZ_g}$$

$$Z_{Th} = \frac{1 + y_{11}Z_g}{y_{22} + \Delta yZ_g}$$

$$\frac{I_2}{I_1} = \frac{y_{21}}{y_{11} + \Delta yZ_L}$$

$$\frac{V_2}{V_1} = \frac{-y_{21}Z_L}{1 + y_{22}Z_L}$$

$$\frac{V_2}{V_g} = \frac{y_{21}Z_L}{y_{12}y_{21}Z_gZ_L - (1 + y_{11}Z_g)(1 + y_{22}Z_L)}$$

b Parameters

$$Z_{in} = \frac{b_{22}Z_L + b_{12}}{b_{21}Z_L + b_{11}}$$

$$I_2 = \frac{-V_g\Delta b}{b_{11}Z_g + b_{21}Z_gZ_L + b_{22}Z_L + b_{12}}$$

$$V_{Th} = \frac{V_g\Delta b}{b_{22} + b_{21}Z_g}$$

$$Z_{Th} = \frac{b_{11}Z_g + b_{12}}{b_{21}Z_g + b_{22}}$$

$$\frac{I_2}{I_1} = \frac{-\Delta b}{b_{11} + b_{21}Z_L}$$

$$\frac{V_2}{V_1} = \frac{\Delta bZ_L}{b_{12} + b_{22}Z_L}$$

$$\frac{V_2}{V_g} = \frac{\Delta bZ_L}{b_{12} + b_{11}Z_g + b_{22}Z_L + b_{21}Z_gZ_L}$$

g Parameters

$$Y_{in} = g_{11} - \frac{g_{12}g_{21}}{g_{22} + Z_L}$$

$$I_2 = \frac{-g_{21}V_g}{(1 + g_{11}Z_g)(g_{22} + Z_L) - g_{12}g_{21}Z_g}$$

$$V_{Th} = \frac{g_{21}V_g}{1 + g_{11}Z_g}$$

$$Z_{Th} = g_{22} - \frac{g_{12}g_{21}Z_g}{1 + g_{11}Z_g}$$


$$\frac{I_2}{I_1} = \frac{-g_{21}}{g_{11}Z_L + \Delta g}$$

$$\frac{V_2}{V_1} = \frac{g_{21}Z_L}{g_{22} + Z_L}$$

$$\frac{V_2}{V_g} = \frac{g_{21}Z_L}{(1 + g_{11}Z_g)(g_{22} + Z_L) - g_{12}g_{21}Z_g}$$

4 eq = 4 unknowns

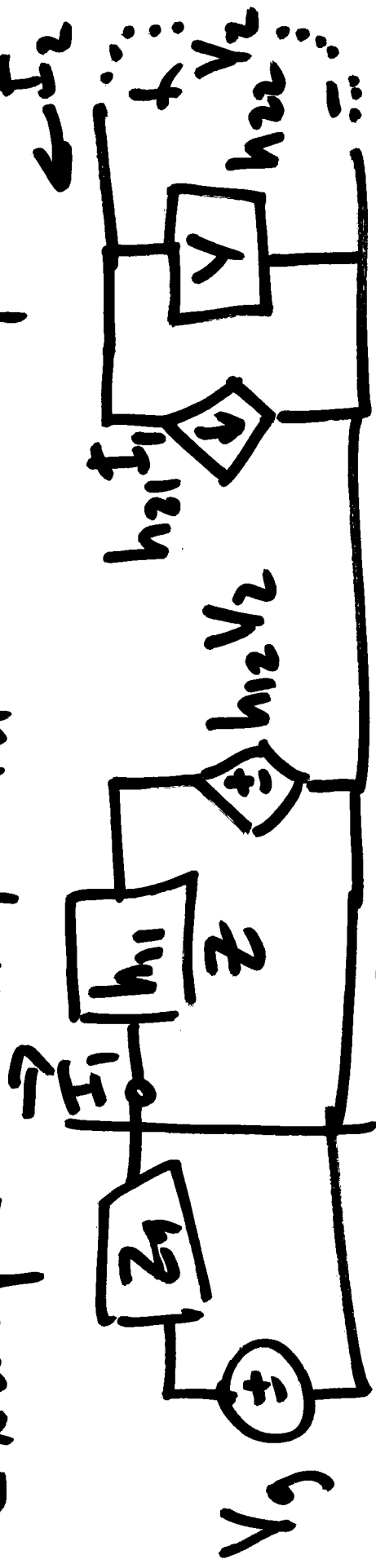Example: V_{th} , Z_{th} from h-parameters



$$\underline{I_{sc}}, \underline{V_{oc}} \equiv I_1 = \frac{V_g}{Z_g + h_{11}} \Rightarrow I_2 = +h_{21}I_1$$

$$I_{sc} = -I_2 = \frac{-h_{21}V_g}{Z_g + h_{11}}$$

$$oc: V_2 = -\frac{h_{21}I_1}{h_{22}}$$

$$I_1 = \frac{V_g - h_{12}V_2}{Z_g + h_{11}}$$

$$V_2 = \frac{-h_{21}h_{12}(V_g - h_{12}V_2)}{Z_g + h_{11}}$$

$$V_{oc} = V_2 = V_{th} + \frac{V_2(Z_g + h_{11} - \frac{h_{12}h_{21}}{h_{22}})}{h_{22}}$$

$$V_{oc} = V_2 = V_{th} + \frac{-h_{21}V_g}{h_{22}Z_g + h_{11}h_{22} - h_{12}h_{21}} = -\frac{h_{21}V_g}{h_{22}} = -\frac{h_{21}V_g}{Ch_{22}Z_g + \Delta h}$$

Cascade

A or B

$$A = A_1 A_2, \quad B = B_2 B_1$$

Series

$$Z = Z_1 + Z_2$$

Parallel

$$Y = Y_1 + Y_2$$

Hybrid: was complicated

$$V_1 = V_1^A = V_1^B$$

$$I_1 = I_1^A + I_1^B$$


$$I_2 = I_2^A + I_2^B$$

$$V_2 = V_2^A = V_2^B$$

$$Y = Y^A + Y^B$$

$$I_1 = V_1 (Y_{11}^A + Y_{11}^B)$$

$$+ V_2 (Y_{12}^A + Y_{12}^B)$$

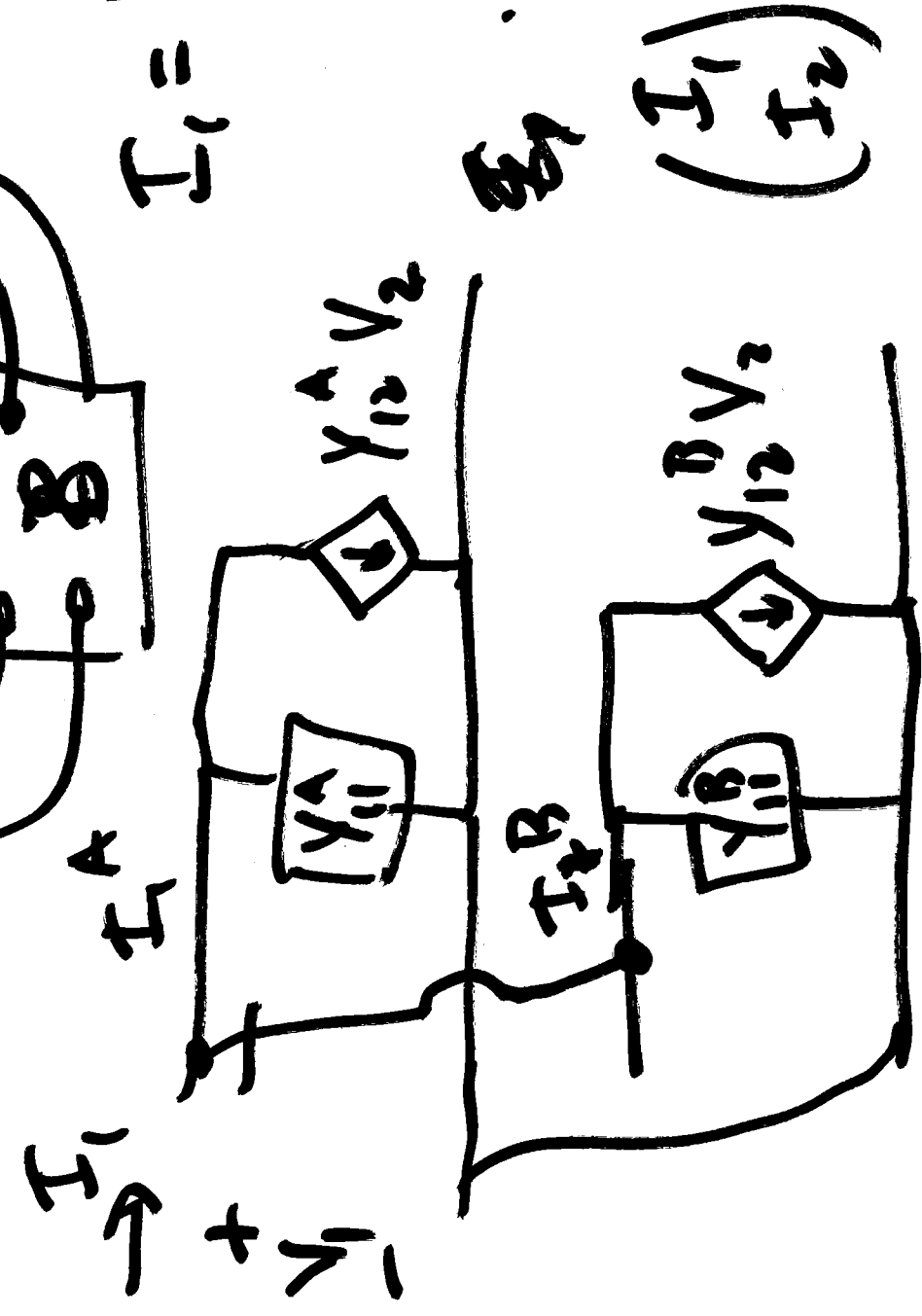


$$\begin{pmatrix} I_1 \\ I_2 \end{pmatrix} = (Y_A + Y_B) \begin{pmatrix} V_1 \\ V_2 \end{pmatrix}$$

3. A filter has the transfer function


$$H(s) = \frac{-\left(\frac{1}{R_2 C_1}\right)s}{s^2 + \frac{s}{R_1 C_1} + \frac{1}{R_1 R_2 C_1 C_2}}$$

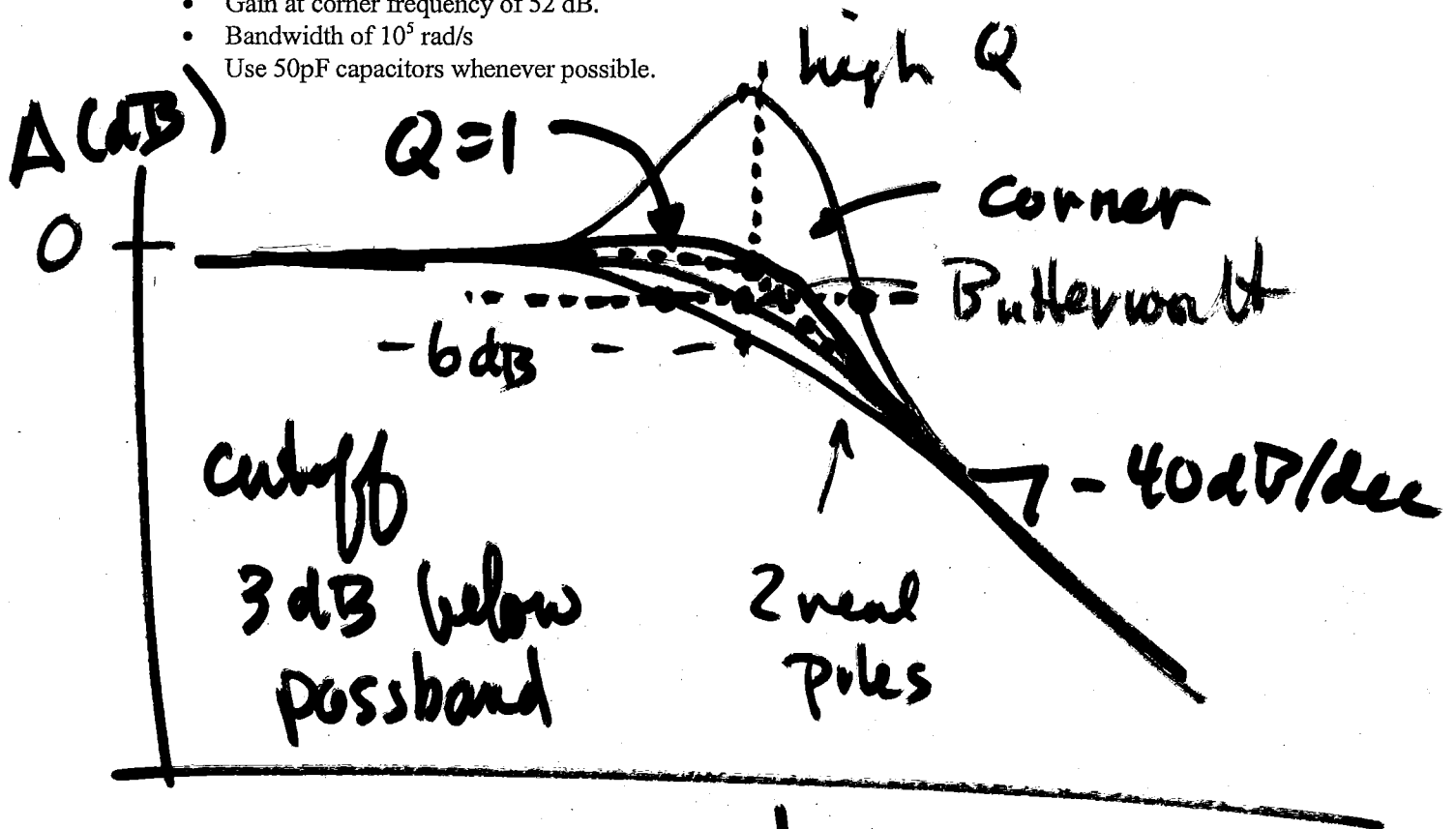(a) Choose values for R_1 , R_2 , C_1 and C_2 to satisfy the following conditions: (12)

- Center frequency of 2×10^6 rad/s.
- Gain at corner frequency of 52 dB.
- Bandwidth of 10^5 rad/s
- Use 50pF capacitors whenever possible.




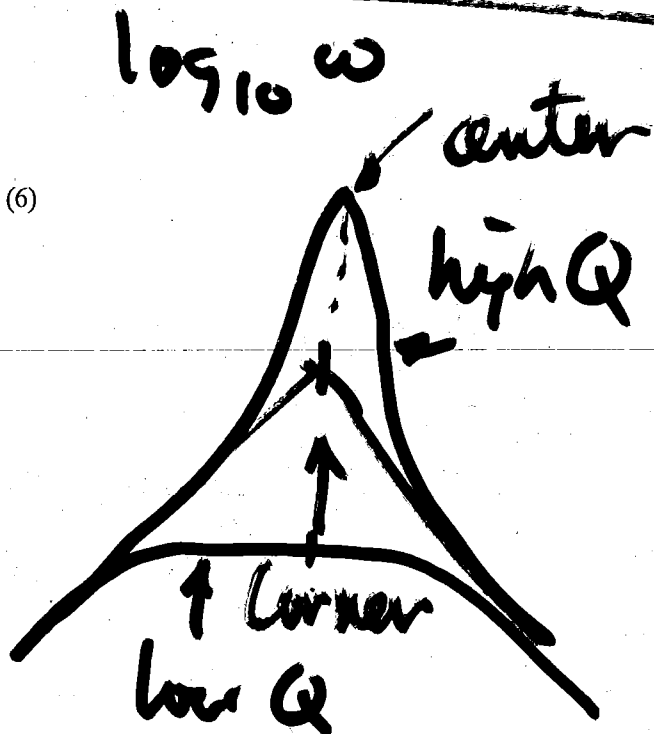(b) Calculate the cutoff frequency or frequencies? (6)



End of Exam

GENERATOR

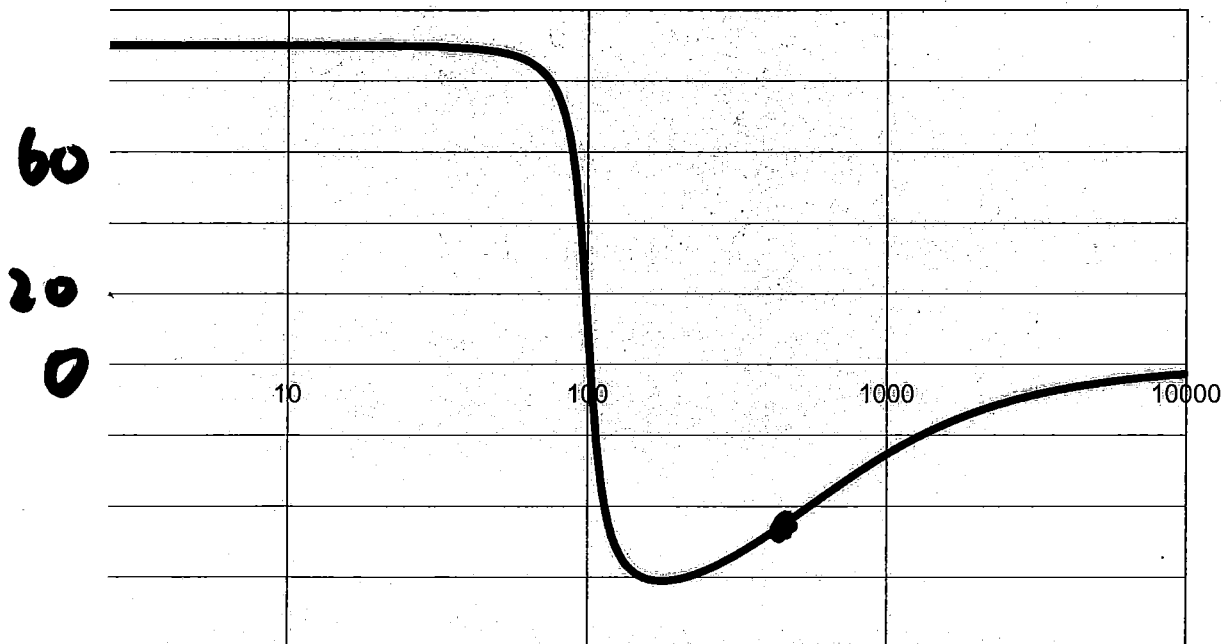

1) Phasor transform and SSS

- Working with complex impedances & ~~sources~~ currents/voltages

2) Complex power:

- Calculating & optimizing power transfer

3) Laplace transform

- General method for $DE_s \Rightarrow AE_s$

- Functional & Operational Transforms

- Use for circuits (s-domain models of R, L, C, etc.)

- Inverse Laplace transform (partial fractions)

- Impulse response and convolution transfer function

4) Filters and $H(j\omega)$ from $H(s)$

- Loading of passive filters


- Designing passive and active filters

- Multistage filters

- Bode plots mag plot $\Leftrightarrow H(s)$

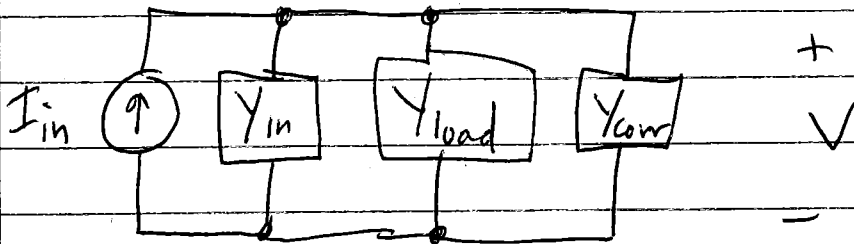5) Two ports

$$S = \underline{I_{rms}^* V_{rms}} = \frac{I_m^* V_m}{2}$$



$$I_{load} = \frac{Y_{load} V}{Y_{in} + Y_{load} + Y_{corr}}, \quad V = \frac{I_{in}}{Y_{in} + Y_{load} + Y_{corr}}$$

$$I_{load}^* V = Y_{load}^* V^* V = Y_{load}^* |V|^2$$

$$|V|^2 = \frac{|I_{in}|^2}{|Y_{in} + Y_{load} + Y_{corr}|^2}$$

$$= \frac{|I_{in}|^2}{[(G_{in} + G_{load} + G_{corr})^2 + (B_{in} + B_{load} + B_{corr})^2]}$$

Maximum when $B_{in} + B_{load} + B_{corr} = 0$

$$B_{corr} = -(B_{in} + B_{load})$$

$$G_{corr} = 0$$

$$S = Y_{load}^* |V|^2$$

$$= \frac{(G_{in} + G_{load}) |I_{in}|^2}{(G_{in} + G_{load})^2} \Rightarrow S = \frac{G_{load} = G_{in}}{(G_{in} + G_{load})^2}$$