

Analyze & Design Circuits to Maximize Power Delivery

Dunham/Soma 1

Learning goals

- Physical meaning of power
- Compute power delivered to a component
 - Given circuit diagram and component values
 - Compute power (analysis step)
- Design circuits to maximize power delivery to a component
 - Given circuit diagram
 - Determine component values

Dunham/Soma 2

Physical meaning

- Home electricity bill
 - Bring a bill to class
- Power to run desktop vs. laptop computers
 - Which consumes more?
 - Find how much power a Pentium CPU needs
- Maximizing power: why?
 - Reduce power waste
 - Get better radio reception (more power received)
 - Make speakers sound louder
 - Find speaker input impedance as an exercise

Dunham/Soma 3

Procedure to compute power

- Compute using general definitions
 - Valid in ALL cases
 - Instantaneous power $p(t)$
 - Function of time
 - $p(t) = v(t) i(t)$
 - Average power P_{av}
 - Average value of $p(t)$ over a time interval T (e.g. average power use at home in one month)
 - NOT a function of time

$$P_{ave} = \frac{1}{T} \int_0^T p(t) dt$$

Dunham/Soma 4

In-class exercises

- Compute average power in components with sinusoidal signals
 - Given $V(t) = V_m \cos(\omega t + \phi)$
 - Average power consumed by R
 - Average power consumed by L
 - Average power consumed by C
- Observations
 - Why $P_{av}=0$ for L and C?
 - Faster way to compute average power for specific case of sinusoidal signals?

Dunham/Soma 5

P_{av} consumed by R

- DC case
 - $P = V I = V^2/R = R I^2$
- Sinusoidal case from previous calculation
 - $P_{av} = V_m I_m / 2 = V_m^2 / (2R) = R(I_m^2 / 2)$
- One 'general formula' for both cases?
 - Use a Root-Mean-Square value for $v(t)$ and $i(t)$
 - RMS definition for any signal $v(t)$

$$V_{RMS} = \sqrt{\frac{1}{T} \int_0^T v^2(t) dt}$$

Dunham/Soma 6

In-class exercises

- Compute V_{RMS} for
 - $V(t) = V_m \cos(\omega t + \phi)$
- Sinusoidal case with amplitude V_m and I_m

$$V_{RMS} = V_m / \sqrt{2}$$

$$I_{RMS} = I_m / \sqrt{2}$$

Dunham/Soma 7

Revisit P_{av} by R

- DC case
 - $P = VI = V^2/R = RI^2$
- Sinusoidal case from previous calculation
 - $P_{av} = V_m I_m / 2 = V_m^2 / (2R) = R(I_m^2 / 2)$
- Use RMS value
 - $P_{av} = V_m I_m / 2 = V_m^2 / (2R) = (V_{RMS}^2) / R = R I_{RMS}^2$
- Same 'general form' using DC value and RMS value

Dunham/Soma 8

Superposition note

- Apply 2 or more sources to a component
 - For each source, calculate $v(t)$ and $i(t)$ for the component
 - Sum all $v(t)$ to get total $V(t)$ across the component
 - Sum all $i(t)$ to get total $I(t)$ into the component
 - $P(t) = V(t) I(t)$. Calculate P_{av} from $P(t)$.
- Do NOT calculate $p(t)$ for each source and sum to get $P(t)$!!!

Dunham/Soma 9

Maximum power transfer

- Circuit with sinusoidal signals
 - Thevenin equivalent: $V_t, Z_t = R_t + jX_t$
 - Load: $Z_L = R_L + jX_L$
- Design the load Z_L to maximize power delivered to the load
 - $Z_L = Z_t^*$ or $[R_L = R_t, X_L = -X_t]$
 - Calculate maximum power for this case

Dunham/Soma 10

Design problem

- $R = 800 \Omega, L = 1.6H$

Dunham/Soma 11