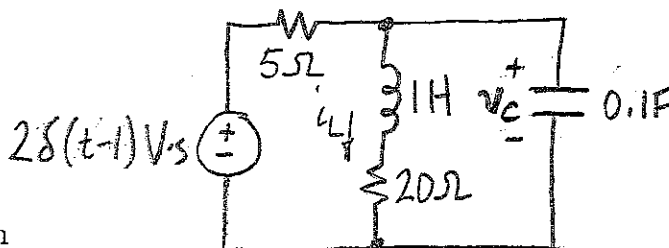


Final Exam — EE 233
Fall 2006

The test is closed book, with two sheets of 8.5 by 11 inch notes and standard (non-graphing) calculators allowed. Show all work. Be sure to state all assumptions made and **check** them when possible. The number of points per problem are indicated in parentheses. Total of 150 points in 6 problems on 6 pages. A table of Laplace transform pairs are attached as page 7.


1. In the circuit to the right,
 $v_C = 3\text{ V}$ and $i_L = 0.1\text{ A}$ at
 $t = 0^-$.

Draw the s -domain circuit
valid for $t > 0$ and determine
 $V_C(s)$. Check your result with
the Initial Value Theorem. (25)



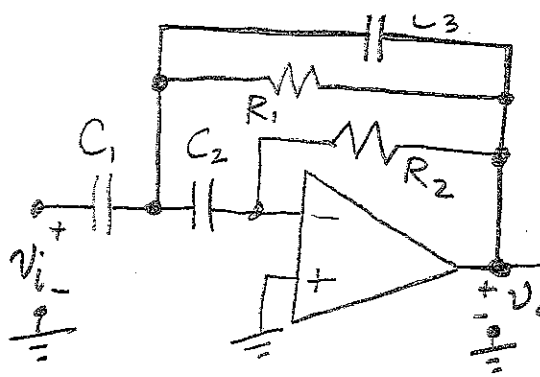2. A filter is constructed using the circuit at the right.

Find the transfer function $H(s)$ in terms of R_1 , R_2 , C_1 , C_2 , and C_3 . What kind of filter is it? (25)




3. Design the s -domain transfer function for a low-pass filter with a corner frequency of 10^4 rad/s, a pass-band gain of 50, a gain at the corner frequency of 37 dB, and a gain less than 0.5 at 8×10^4 rad/s. (25)


4. Find the time-domain behavior of the following s -domain functions:

(a) $V_1(s) = \frac{2s+1}{s+3}$ (10)

(b) $V_2(s) = \frac{10s+5}{s^2+9s+13}$. (15)

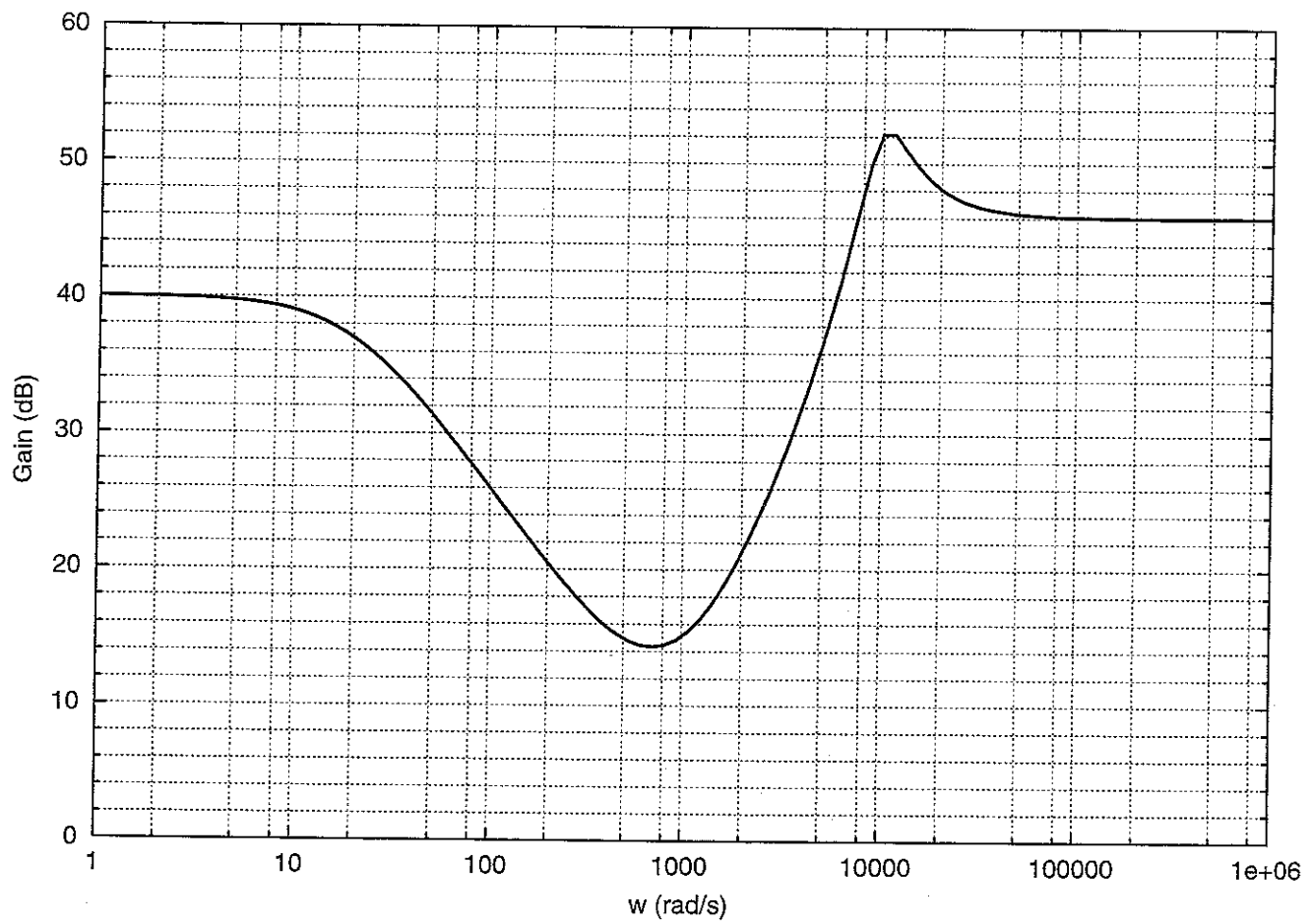5. Determine the s -domain transfer function associated with Bode magnitude plot below. Show your work on the plot and in workspace. (25)



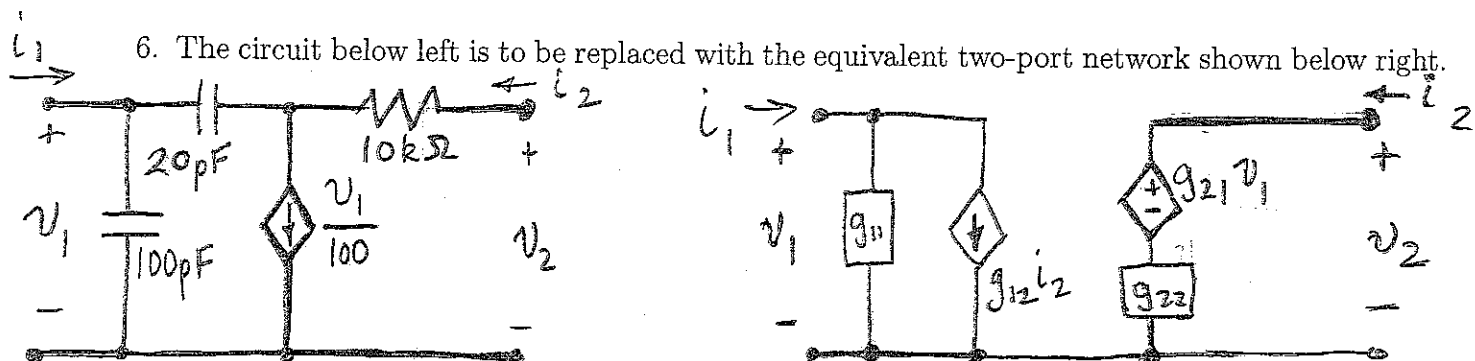

- (a) Calculate the two-port parameters g_{12} and g_{22} in the frequency domain (as function of ω).
(15)

- (b) For $v_1(t) = 2 \exp(-10^6 t) \text{V}$, calculate the complex power delivered to a load connected across v_2 consisting of a $10 \text{k}\Omega$ resistor in series with a 100pF capacitor. (10)

End Of Exam