


Final Exam — EE 233

Fall 2006

The test is closed book, with two sheets of 8.5 by 11 inch notes and standard (non-graphing) calculators allowed. Show all work. Be sure to state all assumptions made and **check** them when possible. The number of points per problem are indicated in parentheses. Total of 150 points in 6 problems on 6 pages. A table of Laplace transform pairs are attached as page 7.

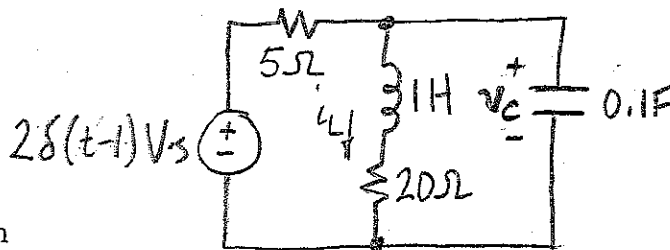
1. In the circuit to the right,
 $v_C = 3\text{ V}$ and $i_L = 0.1\text{ A}$ at
 $t = 0^-$.

Draw the s-domain circuit
 valid for $t > 0$ and determine
 $V_C(s)$. Check your result with
 the Initial Value Theorem. (25)



$$\mathcal{L}\{2\delta(t-1)\} = 2e^{-s}$$
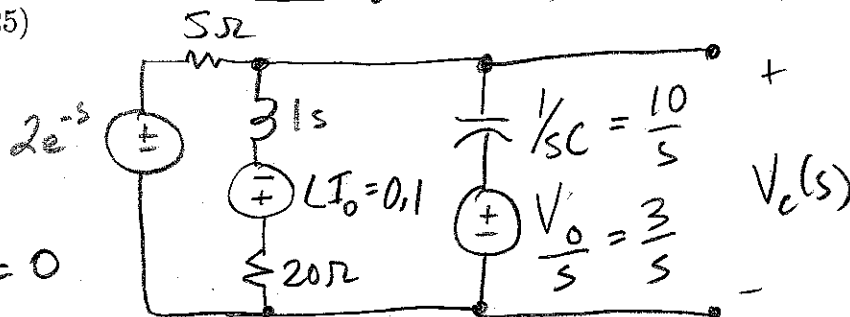
$$\frac{V_C - 2e^{-s}}{s} + \frac{V_C + 0.1}{s+20} + \frac{V_C - 3/s}{10/s} = 0$$



$$\frac{(V_C - 2e^{-s})(s+20)(2) + 10(V_C + 0.1) + (sV_C - 3)(s+20)}{10(s+20)} = 0$$


$$V_C [2s + 40 + 10 + s^2 + 20s] = (4s + 80)e^{-s} - 1 + 3s + 60$$

$$V_C = \frac{(4s + 80)e^{-s} + 3s + 59}{s^2 + 22s + 50}$$

$$\lim_{s \rightarrow \infty} sV_C(s) = \lim_{s \rightarrow \infty} \left[\frac{(4s^2 + 80s)e^{-s} + 3s^2 + 59s}{s^2 + 22s + 50} \right] = \frac{3s^2}{s^2} = 3 \quad \text{checks}$$

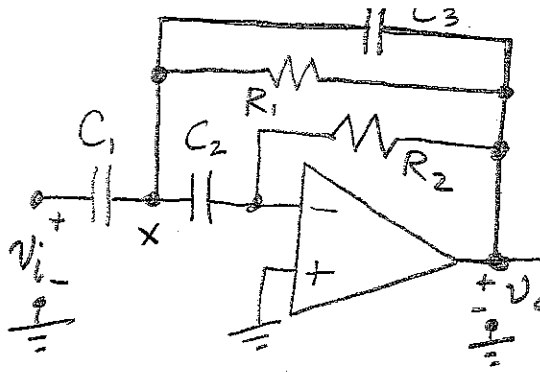2. A filter is constructed using the circuit at the right.

Find the transfer function $H(s)$ in terms of R_1 , R_2 , C_1 , C_2 , and C_3 . What kind of filter is it? (25)



Node x:

$$(V_i - V_x) s C_1 = V_x (s C_2) + (V_x - V_o) \left(s C_3 + \frac{1}{R_1} \right)$$

Node V-

$$V_x (s C_2) = -V_o / R_2 \Rightarrow V_x = -\frac{V_o}{s R_2 C_2}$$

substitute:

$$\begin{aligned} V_i (s C_1) &= V_x \left(s C_1 + s C_2 + s C_3 + \frac{1}{R_1} \right) - V_o \left(s C_3 + \frac{1}{R_1} \right) \\ &= -\frac{V_o}{s R_2 C_2} \left[s (C_1 + C_2 + C_3) + \frac{1}{R_1} \right] - V_o \left(s C_3 + \frac{1}{R_1} \right) \end{aligned}$$

$$\begin{aligned} \frac{V_o}{V_i} &= \frac{-s C_1 (s R_2 C_2)}{s (C_1 + C_2 + C_3) + \frac{1}{R_1} + s R_2 C_2 (s C_3 + \frac{1}{R_1})} \\ &= -\frac{s^2 R_2 C_1 C_2}{s^2 R_2 C_2 C_3 + s \left(C_1 + C_2 + C_3 + \frac{R_2}{R_1} C_2 \right) + \frac{1}{R_1}} \\ &= -\frac{C_1}{C_3} \left[\frac{s^2}{s^2 + \left[\frac{C_1 + C_2 + C_3}{R_2 C_2 C_3} + \frac{1}{R_1 C_3} \right] s + \frac{1}{R_1 R_2 C_2 C_3}} \right] \end{aligned}$$

2nd order High Pass Filter

3. Design the s-domain transfer function for a low-pass filter with a corner frequency of 10^4 rad/s, a pass-band gain of 50, a gain at the corner frequency of 37 dB, and a gain less than 0.5 at 8×10^4 rad/s. (25)

LPF $\omega_c = 10^4 \frac{\text{rad}}{\text{s}}$

$$20 \log_{10}(0.5) = -6 \text{ dB}, 20 \log_{10} 50 = 34 \text{ dB}$$

$$H(s) = \frac{A}{(s+10^4)(s^2 + \frac{10^4}{Q}s + 10^8)}$$

Need drop of $34 - (-6) = 40 \text{ dB}$

over $\log_{10} 8 = 0.9$ decades

$$\frac{40 \text{ dB}}{0.9 \text{ dec}} = 44.4 \text{ dB/dec} > 40 \text{ dB}$$

need 3rd order LPF

At corner real pole gives drop of 3 dB, but need increase of 3 dB = $37 \text{ dB} - 34 \text{ dB}$ from passband, so

$$Q = 2 \quad (20 \log_{10} 2 = 6 \text{ dB})$$

In passband ($\omega \ll 10^4$) $H(s) \approx \frac{A}{10^{12}}$, so $A = 5 \times 10^{13}$

$$H(s) = \frac{5 \times 10^{13}}{(s+10^4)(s^2 + 5000s + 10^8)}$$

4. Find the time-domain behavior of the following s-domain functions:

(a) $V_1(s) = \frac{2s+1}{s+3}$ (10)

$$\frac{2s+1}{s+3} = 2 - \frac{5}{s+3}$$

$$\mathcal{L}^{-1}\left(2 - \frac{5}{s+3}\right) = 2\delta(t) - 5e^{-3t}u(t) = v_1(t)$$

(b) $V_2(s) = \frac{10s+5}{s^2+9s+13}$ (15)

roots of $s^2+9s+13$ are $\frac{-9 \pm \sqrt{9^2 - 4(13)}}{2}$
 $= -\frac{9}{2} \pm \frac{\sqrt{29}}{2} = -1.81, -7.19$

$$V_2(s) = \frac{K_1}{s+1.81} + \frac{K_2}{s+7.19}$$

$$K_1 = \frac{10s+5}{s^2+9s+13} (s+1.81) \Big|_{s=-1.81} = \frac{10s+5}{s+7.19} \Big|_{s=-1.81}$$

$$= \frac{-18.1+5}{-1.81+7.19} = -2.43$$

Check: $s=0$


$$K_2 = \frac{10s+5}{s+1.81} \Big|_{s=-7.19} = \frac{-71.9+5}{-7.19+1.81} = 12.43$$

$$\frac{-2.43}{1.81} + \frac{12.43}{7.19} = 0.38 = \frac{5}{13}$$

$$v_2(t) = -2.43e^{-1.81t} + 12.43e^{-7.19t}$$

Check w/ IFT: $\lim_{s \rightarrow \infty} sV_2(s) = 10 = v_2(0) \checkmark$

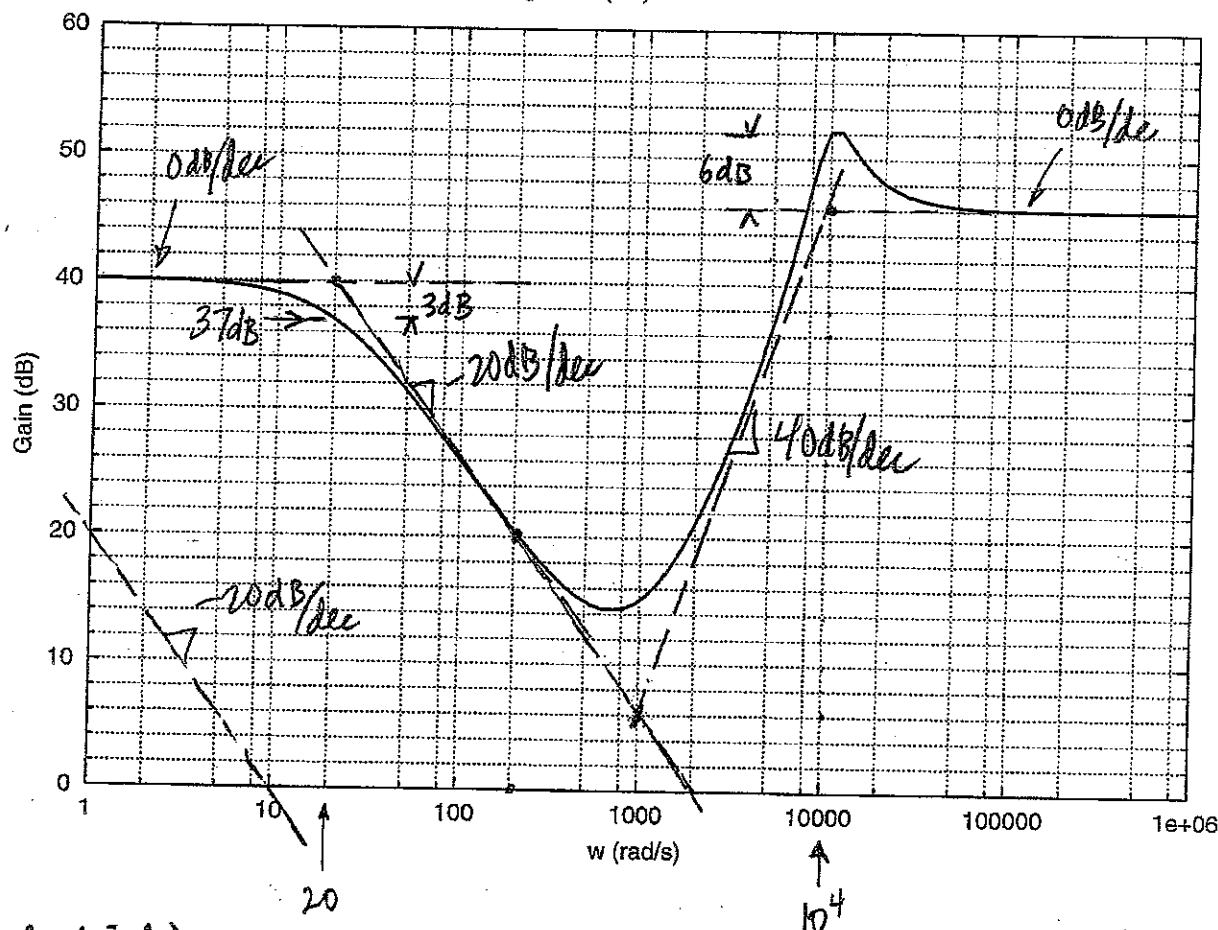5. Determine the s-domain transfer function associated with Bode magnitude plot below. Show your work on the plot and in workspace. (25)



pole (single) at ~ 20 rad/s
 triple zero at ~ 1000 rad/s
 double pole at $\sim 10^4$ rad/s

$$H(s) = \frac{A(s+1000)(s^2 + \frac{1000}{Q_z}s + 10^6)}{(s+20)(s^2 + \frac{10^4}{Q_p}s + 10^8)}$$

$$Q_p = 2 \quad 20 \log_{10} Q_p = 6 \text{ dB at upper corner frequency}$$

Gain at 1000 3 dB above corner due to 1st order term

Additional 6 dB due to 2nd order term $\Rightarrow Q_z = \frac{1}{2}$ ← pair of real zeroes $(s+10^4)^2$

For low frequency $|H(j\omega)| = \frac{A(10^9)}{2 \times 10^9} = 100 \Rightarrow |A| = 200$

$$H(s) = \frac{200(s+1000)^3}{(s+20)(s^2 + 5000s + 10^8)}$$

Check: at very high frequency
 $|H(j\omega)| = \frac{200s^3}{s^3} = 200 \Rightarrow 46 \text{ dB}$