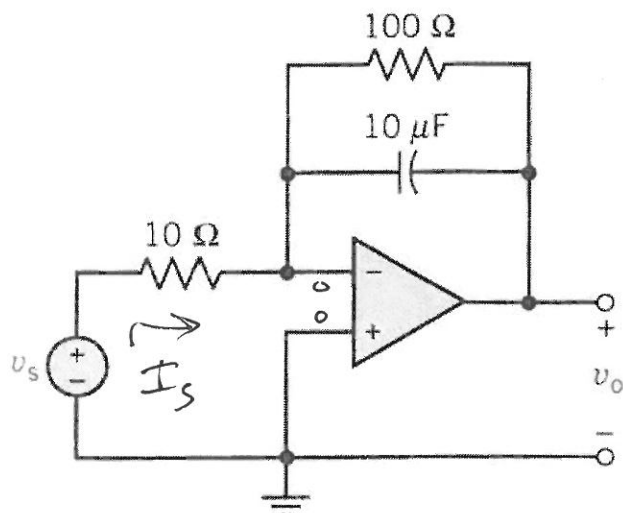


Exam 1 — EE 233
Spring 2010

Mean = 31
Median = 33
Std. Dev = 9.5

The test is closed book, with one sheet of notes and standard calculators (no communications) allowed. Show all work. Be sure to state all assumptions made and **check** them when possible. The number of points per problem are indicated in parentheses. Total of 50 points in 3 problems on 3 pages.

1. If $v_s(t) = 2 \cos(1000t - 60^\circ)$, find $v_o(t)$. (15)



$$V_s = 2 \angle -60^\circ \text{ V}$$

$$\begin{aligned} \omega = 1000, \text{ so } Z_c &= -\frac{j}{\omega C} \\ &= -\frac{j}{10^3 \cdot 10^{-5}} \\ &= -j100 \Omega \end{aligned}$$

$$V^- = V^+ = 0, \text{ so}$$

$$I_s = \frac{V_s}{10 \Omega} = 0.2 \angle -60^\circ \text{ A}$$

$$V_o = -I_s Z_{RC}, \text{ where } Z_{RC} = 100 \Omega \parallel Z_c = \frac{(100)(-j100)}{100 - j100}$$

$$= -(0.2 \angle -60^\circ)(50\sqrt{2} \angle -45^\circ)$$

$$= -10\sqrt{2} \angle -105^\circ$$

$$= 10\sqrt{2} \angle 180 - 105$$

$$= 10\sqrt{2} \angle 75^\circ$$

$$= 100 \frac{-j}{1-j} = 100 \frac{1 \angle -90}{\sqrt{2} \angle -45}$$

$$= \frac{100}{\sqrt{2}} \angle -45 = 50\sqrt{2} \angle -45$$



$$= 50 - j50 \Omega$$

$$v_o(t) = 10\sqrt{2} \cos(1000t + 75^\circ)$$

$$= 14.14 \cos(1000t + 75^\circ) \text{ V}$$

Two (of many) approaches shown (left & right)

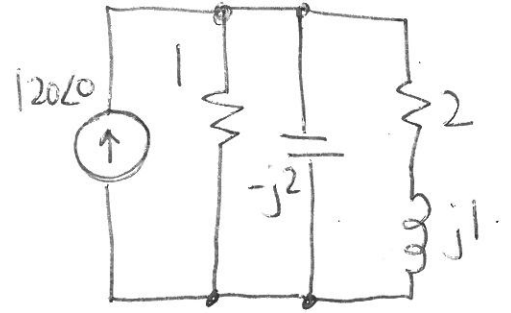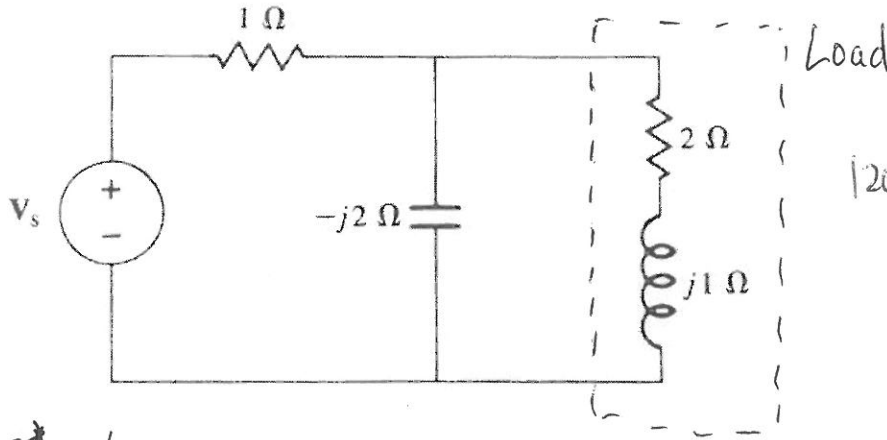2. If $V_s = 120 \angle 0^\circ \text{ V (rms)}$, what is the complex power delivered to RL series load? (15)



$$S = I_{rms}^* V_{rms}$$

$$S_L = I_L^* V_L = \left(\frac{V_L}{Z_L} \right)^* V_L = \frac{|V_L|^2}{Z_L^*}$$

$$Z_L = 2 + j; Z_L^* = 2 - j$$

$$V_L = \frac{Z_C \parallel Z_L}{1 + Z_C \parallel Z_L} V_s$$

$$Z_C \parallel Z_L = \frac{Z_C Z_L}{Z_C + Z_L} = \frac{(-j2)(2+j)}{-j2+2+j}$$

$$= \frac{-j4+2}{2-j} = \frac{(2-j4)(2+j)}{2^2+1^2}$$

$$= \frac{4+j2-j8+4}{5} = \frac{8-j6}{5}$$

$$\frac{V_L}{V_s} = \frac{(8-j6)/5}{1+(8-j6)/5} = \frac{8-j6}{13-j6}$$

$$\frac{|V_L|^2}{|V_s|^2} = \frac{8^2+6^2}{13^2+6^2} = 0.488$$

$$|V_L|^2 = 0.488(120)^2 = 7024.4$$

$$S_L = \frac{7024.4}{2-j} = \frac{7024.4}{2^2+1^2} (2+j)$$

$$= 1404.9(2+j) = \underline{\underline{2810 + j1405 \text{ VA}}}$$

$$I_L = I_{total} \frac{Y_L}{Y_{total}}$$

$$Y_L = \frac{1}{Z_L} = \frac{1}{2+j} = \frac{2-j}{2^2+1^2} = \frac{2-j}{5}$$

$$Y_{total} = 1 + \frac{1}{-j2} + \frac{2-j}{5}$$

$$= \frac{1}{5} [5 + j2.5 + 2 - j]$$

$$= \frac{1}{5} [7 + j1.5] \text{ S}$$

$$I_L = 120 \angle 0 \frac{2-j}{7+j1.5} = 120 \frac{(2-j)(7-j1.5)}{7^2+1.5^2}$$

$$= \frac{120}{51.25} [14 - j3 - j7 - 1.5]$$

$$= 2.34 [12.5 - j10]$$

$$S_L = I_L^* V_L = I_L^* (I_L Z_L) = |I_L|^2 Z_L$$

$$|I_L|^2 = (2.34)^2 (12.5^2 + 10^2) = 1400$$


$$S_L = 1400(2+j) = 2800 + j1400 \text{ VA}$$

$$P = 2800 \text{ W}$$

$$Q = 1400 \text{ VAR}$$

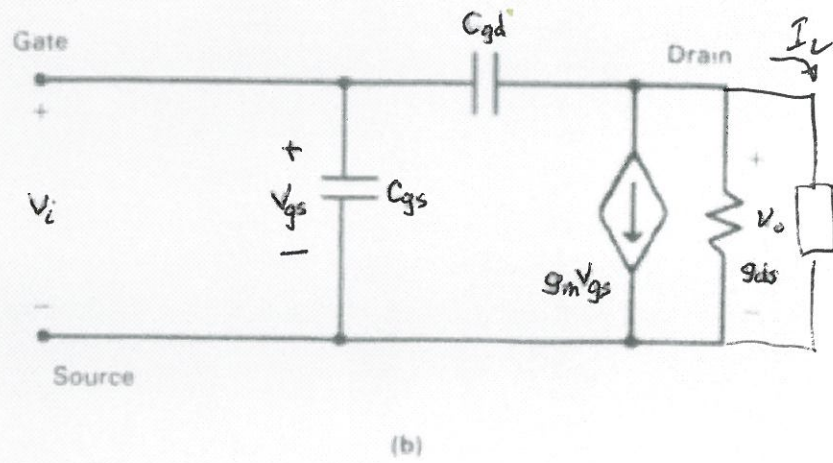3. For the circuit to the right, $C_{gs} = 100 \text{ pF}$, $C_{gd} = 20 \text{ pF}$, $g_m = 0.1 \text{ S}$, and $g_{ds} = 10 \text{ mS}$.

If the input voltage is $v_i(t) = 20 \cos(10^9 t) \text{ mV}$, what load admittance $Y_L = G_L + jB_L$ placed in parallel to g_{ds} (across v_o) would maximize power transfer to the load? (20)



We can reduce this circuit to its Thevenin or Norton equivalent and power is maximized by making $Z_L = Z_{th}^*$ or $Y_L = Y_N^* = 1/Z_{th}^*$

$$I_{sc} = V_i (j\omega C_{gd}) - g_m V_i = V_i (j\omega C_{gd} - g_m)$$

$$= 20 \angle 0 \text{ mV} (j20 - 100 \text{ mS})$$

$$= \underline{\underline{-2 + j0.4 \text{ mA}}}$$

For V_{oc} , use node voltage equation

$$(V_{oc} - V_{gs})(j\omega C_{gd}) + g_m V_{gs} + V_{oc} g_{ds} = 0$$

$$V_{oc}(j\omega C_{gd} + g_{ds}) = V_{gs}(j\omega C_{gd} - g_m)$$

$$V_{oc} = V_{gs} \left(\frac{j\omega C_{gd} - g_m}{j\omega C_{gd} + g_{ds}} \right) = V_i \left(\frac{j\omega C_{gd} - g_m}{j\omega C_{gd} + g_{ds}} \right) = 20 \angle 0 \text{ mV} \left[\frac{j20 - 100 \text{ mS}}{j20 + 10 \text{ mS}} \right]$$

$$Y_N = \frac{I_{sc}}{V_{oc}} = \frac{V_i (j\omega C_{gd} - g_m)}{V_i \left(\frac{j\omega C_{gd} - g_m}{j\omega C_{gd} + g_{ds}} \right)} = j\omega C_{gd} + g_{ds}$$

$$= 10 + j20 \text{ mS}$$

$$= \underline{\underline{-24 + j88 \text{ mV}}}$$

Maximum Power Transfer for $Y_L = Y_N^* = g_{ds} - j\omega C_{gd}$


$$= 10 \times 10^{-3} - j(10^9)(20 \times 10^{-12})$$

$$Z_L^{MPT} = \frac{1}{Y_L} = \frac{1000 \Omega}{10 - j20} = \frac{100(1+j2)\Omega}{1^2 + 2^2} = 20 + j40 \Omega$$

$$= \underline{\underline{10 - j20 \text{ mS}}}$$

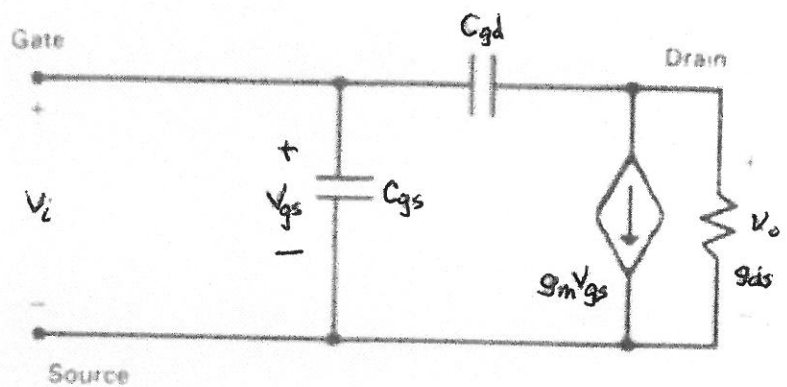3. For the circuit to the right, $C_{gs} = 100 \text{ pF}$, $C_{gd} = 20 \text{ pF}$, $g_m = 0.1 \text{ S}$, and $g_{ds} = 10 \text{ mS}$.


If the input voltage is $v_i(t) = 20 \cos(10^9 t) \text{ mV}$, what load admittance $Y_L = G_L + jB_L$ placed in parallel to g_{ds} (across v_o) would maximize power transfer to the load? (20)




(b)

There is an easier alternate method.

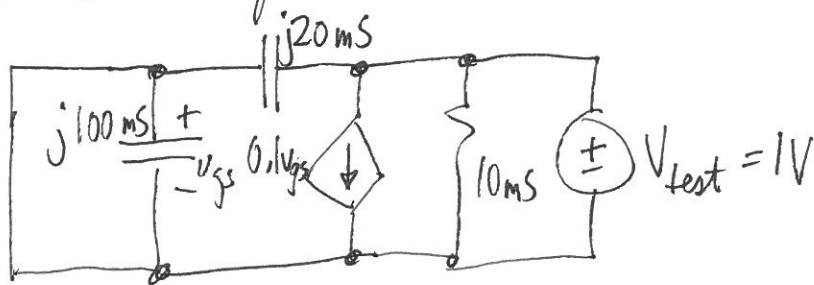Since only Y_N is needed, just use a test output voltage and zero input



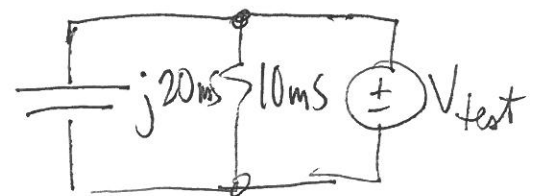$V_{gs} = 0$ &
 C_{gs} is shorted, so
 can reduce to:



$$Y_N = 10 \text{ mS} + j20 \text{ mS}$$

$$Y_L^{\text{MPT}} = Y_N^* = \underline{\underline{10 - j20 \text{ mS}}}$$

Note: This circuit is a high frequency model for an MOS transistor (note labels of gate, drain and source).