

Exam 2 — EE 233
Spring 2010Mean = 65.4
Median = 69
Std. Dev = 16.4

The test is closed book, with two sheets of notes and calculators allowed. Show all work. Be sure to state all assumptions made and **check** them when possible. The number of points per problem are indicated in parentheses. Total of 100 points in 3 problems on 3 pages (4th page has Laplace transform pairs).

1. The Laplace transform of an output voltage is:

$$V(s) = \frac{5e^{-s}}{(s+1)^2} + \frac{2s+2}{s^2+6s+10}$$

- (a) Find $v(t)$ for $t > 0^-$. (20)

$$\mathcal{L}^{-1}\left\{\frac{5}{(s+1)^2}\right\} = 5te^{-t}u(t), \text{ so } \mathcal{L}^{-1}\left\{\frac{5e^{-s}}{(s+1)^2}\right\} = 5(t-1)e^{-(t-1)}u(t-1)$$

$$s^2+6s+10 = (s+3)^2+1 = (s+3-j)(s+3+j), \quad \frac{-6 \pm \sqrt{6^2-4(10)}}{2} = -3 \pm j$$

$$\frac{2s+2}{s^2+6s+10} = \frac{K}{s+3-j} + \frac{K^*}{s+3+j}$$

$$K = \left[\frac{(2s+2)(s+3+j)}{(s+3-j)(s+3+j)} \right]_{s=-3+j} = \frac{2s+2}{s+3+j} \bigg|_{s=-3+j} = \frac{2(-3+j)+2}{-j+j+1} = \frac{-4+j}{1} = -4+j$$

$$= \frac{-4+j}{j^2} = 1 + \frac{-2}{j} = 1 + j2 = \sqrt{1+4} \angle \tan^{-1}(2) = \sqrt{5} \angle 63.4^\circ$$

$$v(t) = 5(t-1)e^{-(t-1)}u(t-1) + 2\sqrt{5}e^{-3t} \cos(t + 63.4^\circ)$$


$\uparrow$ $|K|$ $\uparrow$ θ_K
 $\alpha = -3$ $\beta = 1$

- (b) Use the Initial and Final Value Theorems to check your results. (10)


$$\lim_{s \rightarrow \infty} (sV(s)) = \lim_{s \rightarrow \infty} \frac{2s^2+2s}{s^2+6s+10} = 2, \quad \lim_{t \rightarrow 0} v(t) = 0 + 2\sqrt{5} \cos(63.4^\circ) = 2.0 \checkmark$$

$$\lim_{s \rightarrow 0} (sV(s)) = \lim_{s \rightarrow 0} \frac{2s^2+2s}{s^2+6s+10} = 0, \quad \lim_{t \rightarrow \infty} v(t) = 0 \begin{cases} te^{-(t-1)} \rightarrow 0 \\ e^{-3t} \rightarrow 0 \end{cases} \checkmark$$

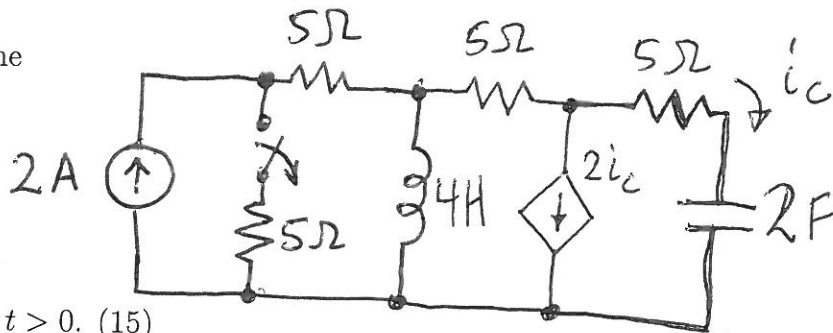2. For the circuit to the right, note that the switch opens at $t = 0$,



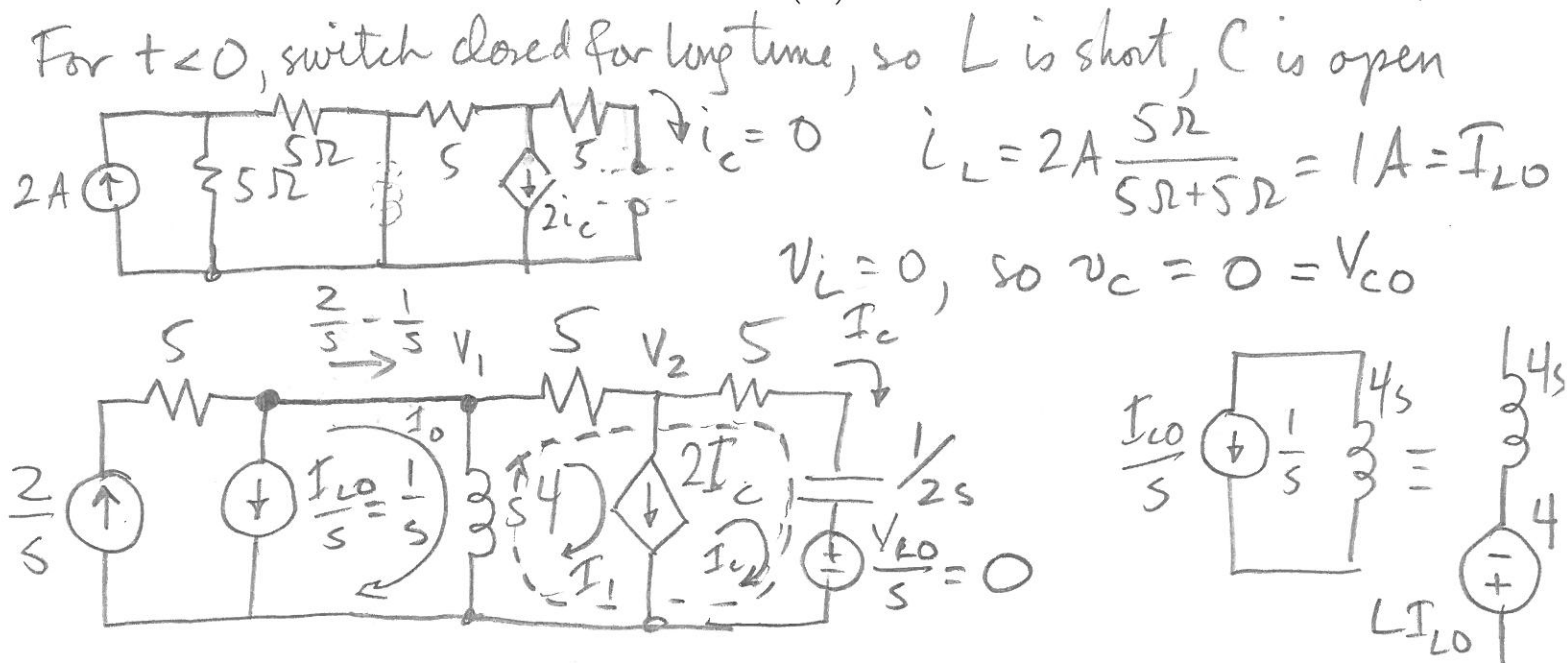- (a) Draw the s -domain circuit valid for $t > 0$. (15)



- (b) Find $I_c(s)$ (Laplace transform of capacitor current). (15)

Super Mesh (see above): $4s(I_1 - I_0) + 5I_1 + (5 + \frac{1}{2s})I_c = 0$

$$I_0 = \frac{2}{s} - \frac{1}{s} = \frac{1}{s}, \quad I_1 - I_c = 2I_c, \quad \text{so } I_1 = 3I_c$$

$$4s(3I_c - \frac{1}{s}) + 5(3I_c) + (5 + \frac{1}{2s})I_c = 0$$

$$I_c(12s + 15 + 5 + \frac{1}{2s}) = 4 \Rightarrow$$

$$I_c = \frac{4}{12s + 20 + \frac{1}{2s}} = \frac{1}{3} \left[\frac{s}{s^2 + \frac{5s}{3} + \frac{1}{24}} \right]$$



Can also use node voltage:

$$V_1: -\frac{2}{s} + \frac{1}{s} + \frac{V_1}{4s} + \frac{V_1 - V_2}{5} = 0$$

$$V_2: \frac{V_2 - V_1}{5} + 2I_c + \frac{V_2}{5 + 1/2s} = 0 \quad \text{where } I_c = \frac{V_2}{5 + 1/2s}$$

solve 2×2 to get same answer

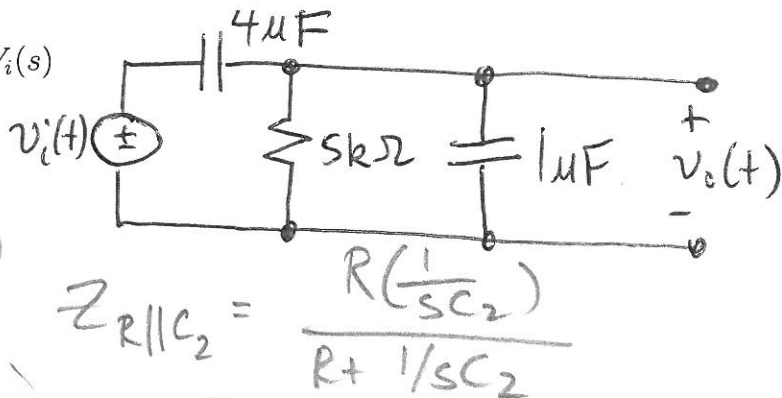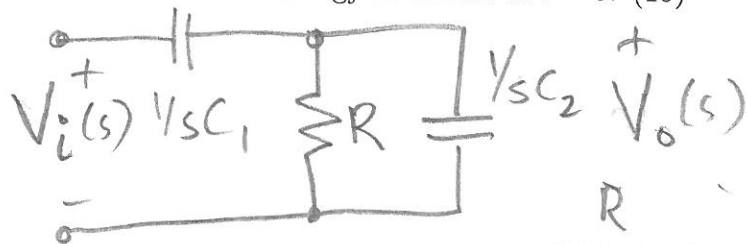3. (a) Find the transfer function $H(s) = V_o(s)/V_i(s)$ for the circuit to the right. Assume no stored energy in circuit at $t = 0$. (15)



$$\begin{aligned} \frac{V_o(s)}{V_i(s)} = H(s) &= \frac{Z_{R||C_2}}{Z_{C_1} + Z_{R||C_2}} = \frac{\frac{R}{sRC_2 + 1}}{\frac{1}{sC_1} + \frac{R}{sRC_2 + 1}} = \frac{R}{sRC_2 + 1} \\ &= \frac{sRC_1}{sRC_2 + 1 + sRC_1} = \frac{sRC_1}{sR(C_1 + C_2) + 1} \\ &= \frac{0.02s}{0.025s + 1} = \frac{0.8s}{s + 40} \end{aligned}$$

$$\begin{aligned} RC_1 &= (5 \times 10^3)(4 \times 10^{-6}) \\ &= 20 \times 10^{-3} \\ &= 0.02 \\ RC_2 &= 5 \times 10^{-3} \\ &= 0.005 \end{aligned}$$

- (b) Calculate the impulse response for this circuit. (10)

$$h(t) = \mathcal{L}^{-1}\{H(s)\}$$

$$= \mathcal{L}^{-1}\left\{0.8 - \frac{32}{s+40}\right\}$$

$$= 0.8\delta(t) - 32e^{-40t}u(t)$$

$$\begin{aligned} H(s) &= \frac{0.8s}{s+40} \quad \text{improper} \\ &= \frac{0.8(s+40) - 32}{s+40} \\ &= 0.8 - \frac{32}{s+40} \end{aligned}$$

- (c) If $v_i(t) = u(t) - u(t - 50)$, calculate and sketch $v_o(t)$ versus time (seconds). (15)

$$\text{Option 1: } V_o(s) = V_i(s)H(s) = \left(\frac{1}{s} - \frac{e^{-50s}}{s}\right)\left(\frac{0.8s}{s+40}\right) = \frac{0.8(1-e^{-50s})}{s+40}$$

$$v_o(t) = \mathcal{L}^{-1}\left\{\frac{0.8(1-e^{-50s})}{s+40}\right\} = \mathcal{L}^{-1}\left\{\frac{0.8}{s+40} - \frac{0.8e^{-50s}}{s+40}\right\} =$$

$$\text{Option 2: } v_o(t) = v_i(t) * h(t) = 0.8e^{-40t}u(t) - 0.8e^{-40(t-50)}u(t-50)$$

$$= \int_{-\infty}^{\infty} v_i(\lambda - t)h(\lambda) d\lambda$$

$$\begin{aligned} &= \int_0^t [0.8\delta(\lambda) - 32e^{-40\lambda}] d\lambda = 0.8 - \frac{32}{40}e^{-40t} \quad 0 < t < 50 \\ &= \int_{t-50}^t h(\lambda) d\lambda = \frac{32}{40}e^{-40\lambda} \Big|_{t-50}^t \quad t > 50 \end{aligned}$$

End Of Exam

