


Final Exam — EE 233

Fall 2006

The test is closed book, with two sheets of 8.5 by 11 inch notes and standard (non-graphing) calculators allowed. Show all work. Be sure to state all assumptions made and **check** them when possible. The number of points per problem are indicated in parentheses. Total of 150 points in 6 problems on 6 pages. A table of Laplace transform pairs are attached as page 7.

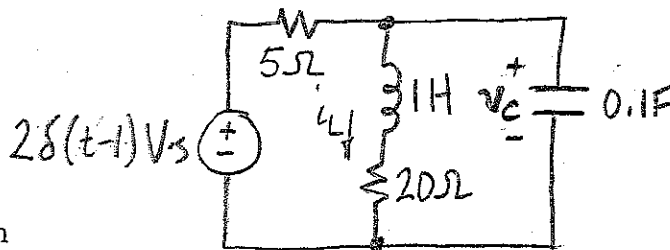
1. In the circuit to the right,
 $v_C = 3\text{ V}$ and $i_L = 0.1\text{ A}$ at
 $t = 0^-$.

Draw the s-domain circuit
 valid for $t > 0$ and determine
 $V_C(s)$. Check your result with
 the Initial Value Theorem. (25)



$$\mathcal{L}\{28(t-1)\} = 2e^{-s}$$
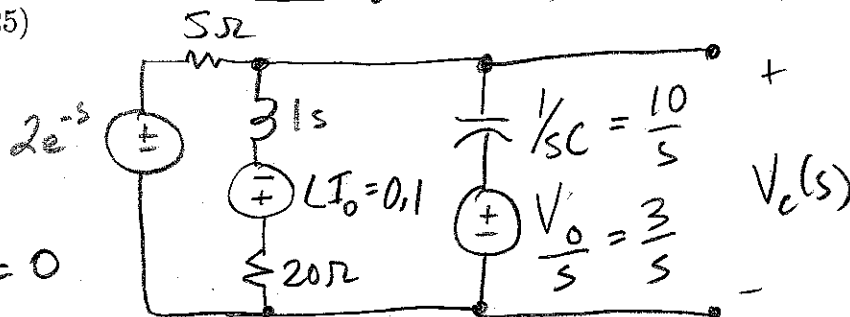
$$\frac{V_C - 2e^{-s}}{s} + \frac{V_C + 0.1}{s+20} + \frac{V_C - 3/s}{10/s} = 0$$



$$\frac{(V_C - 2e^{-s})(s+20)(2) + 10(V_C + 0.1) + (sV_C - 3)(s+20)}{10(s+20)} = 0$$

$$V_C [2s + 40 + 10 + s^2 + 20s] = (4s + 80)e^{-s} - 1 + 3s + 60$$

$$V_C = \frac{(4s + 80)e^{-s} + 3s + 59}{s^2 + 22s + 50}$$

$$\lim_{s \rightarrow \infty} sV_C(s) = \lim_{s \rightarrow \infty} \left[\frac{(4s^2 + 80s)e^{-s} + 3s^2 + 59s}{s^2 + 22s + 50} \right] = \frac{3s^2}{s^2} = 3 \quad \text{checks}$$

4. Find the time-domain behavior of the following s-domain functions:

(a) $V_1(s) = \frac{2s+1}{s+3}$ (10)

$$\frac{2s+1}{s+3} = 2 - \frac{5}{s+3}$$

$$\mathcal{L}^{-1}\left(2 - \frac{5}{s+3}\right) = 2\delta(t) - 5e^{-3t}u(t) = v_1(t)$$

(b) $V_2(s) = \frac{10s+5}{s^2+9s+13}$ (15)

roots of $s^2+9s+13$ are $\frac{-9 \pm \sqrt{9^2 - 4(13)}}{2}$
 $= -\frac{9}{2} \pm \frac{\sqrt{29}}{2} = -1.81, -7.19$

$$V_2(s) = \frac{K_1}{s+1.81} + \frac{K_2}{s+7.19}$$

$$K_1 = \frac{10s+5}{s^2+9s+13} (s+1.81) \Big|_{s=-1.81} = \frac{10s+5}{s+7.19} \Big|_{s=-1.81}$$

$$= \frac{-18.1+5}{-1.81+7.19} = -2.43$$

Check: $s=0$

$$K_2 = \frac{10s+5}{s+1.81} \Big|_{s=-7.19} = \frac{-71.9+5}{-7.19+1.81} = 12.43$$

$$\frac{-2.43}{1.81} + \frac{12.43}{7.19} = 0.38 = \frac{5}{13}$$

$$v_2(t) = -2.43e^{-1.81t} + 12.43e^{-7.19t}$$

Check w/ IFT: $\lim_{s \rightarrow \infty} sV_2(s) = 10 = v_2(0) \checkmark$