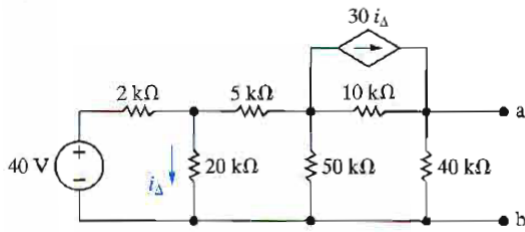


4.72 Find the Thévenin equivalent with respect to the terminals a,b for the circuit seen in Fig. P4.72.


Figure P4.72



5.14 The $330\text{ k}\Omega$ feedback resistor in the circuit in Fig. P5.13 is replaced by a variable resistor R_f . The voltages $v_a - v_d$ have the same values as given in Problem 5.13(a).

- What value of R_f will cause the op amp to saturate? Note that $0 \leq R_f \leq \infty$.
- When R_f has the value found in (a), what is the current (in microamperes) into the output terminal of the op amp?


Figure P5.13

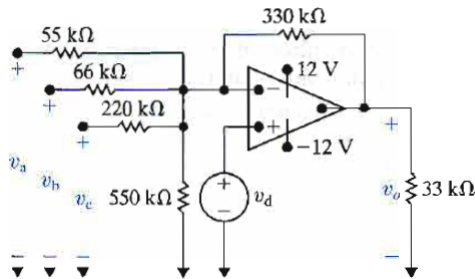

6.17 The current shown in Fig. P6.17 is applied to a $0.25\text{ }\mu\text{F}$ capacitor. The initial voltage on the capacitor is zero.

- Find the charge on the capacitor at $t = 30\text{ }\mu\text{s}$.
- Find the voltage on the capacitor at $t = 50\text{ }\mu\text{s}$.
- How much energy is stored in the capacitor by this current?


Figure P6.17

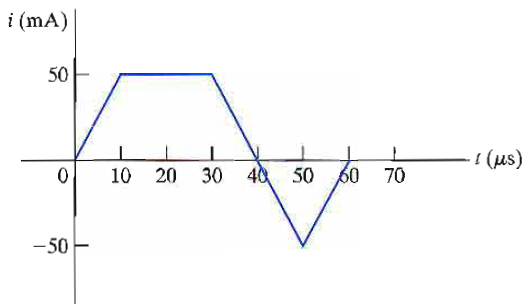

7.25 Both switches in the circuit in Fig. P7.25 have been closed for a long time. At $t = 0$, both switches open simultaneously.

- Find $i_o(t)$ for $t \geq 0^+$.
- Find $v_o(t)$ for $t \geq 0$.
- Calculate the energy (in microjoules) trapped in the circuit.


Figure P7.25

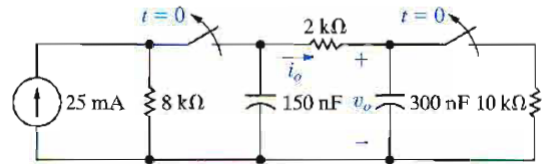

8.51 The switch in the circuit of Fig. P8.51 has been in position a for a long time. At $t = 0$ the switch moves instantaneously to position b. Find


- $v_o(0^+)$
- $dv_o(0^+)/dt$
- $v_o(t)$ for $t \geq 0$.

Figure P8.51

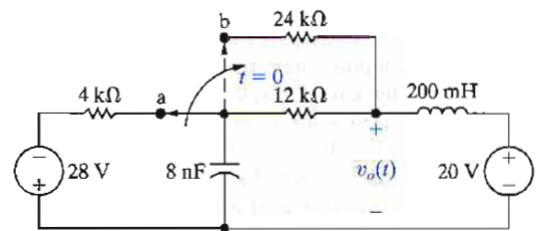

Calculate the following complex number: $(1+3j)+(2-2j)/(2+j)$. Give answer in both Cartesian and angular (magnitude and phase) form.

P.4.72

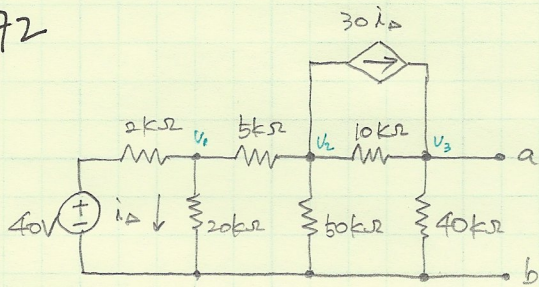

$$\leftarrow V_{ab} = V_{Th} = V_3.$$

$$i_{\Delta} = \frac{V_1}{20000}$$

$$\begin{aligned} \text{at } V_1 \text{ node. } & \frac{V_1 - 40}{2000} + \frac{V_1}{20000} + \frac{V_1 - V_2}{5000} = 0 \\ \text{at } V_2 \text{ node. } & \frac{V_2 - V_1}{5000} + \frac{V_2}{50000} + \frac{V_2 - V_3}{10000} + 30 \cdot \frac{V_1}{20000} = 0 \\ \text{at } V_3 \text{ node. } & \frac{V_3 - V_2}{10000} + \frac{V_3}{40000} - 30 \cdot \frac{V_1}{20000} = 0 \end{aligned}$$

$$\begin{cases} V_1 \left(-\frac{1}{2000} + \frac{1}{20000} + \frac{1}{5000} \right) + V_2 \left(-\frac{1}{5000} \right) + V_3 (0) = \frac{40}{2000} \\ V_1 \left(-\frac{1}{5000} + \frac{30}{20000} \right) + V_2 \left(\frac{1}{5000} + \frac{1}{50000} + \frac{1}{10000} \right) + V_3 \left(-\frac{1}{10000} \right) = 0 \\ V_1 \left(-\frac{30}{20000} \right) + V_2 \left(-\frac{1}{10000} \right) + V_3 \left(\frac{1}{10000} + \frac{1}{40000} \right) = 0 \end{cases}$$

$$\begin{cases} V_1 (10 + 1 + 4) + V_2 (-4) + V_3 (0) = 400 \\ V_1 (-10 + 75) + V_2 (10 + 1 + 5) + V_3 (-5) = 0 \\ V_1 (-60) + V_2 (-4) + V_3 (4 + 1) = 0 \end{cases}$$

$$V_1 (15) + V_2 (-4) + V_3 (0) = 400 \quad \text{--- ①}$$

$$V_1 (65) + V_2 (16) + V_3 (-5) = 0 \quad \text{--- ②}$$

$$V_1 (-60) + V_2 (-4) + V_3 (5) = 0 \quad \text{--- ③}$$

$$\text{①} - \text{②} \quad ; V_1 (75) + V_3 (-5) = 400 \quad \text{--- ④}$$


$$\text{①} \times 4 + \text{③} \quad ; V_1 (125) + V_3 (-5) = 1600 \quad \text{--- ⑤}$$

$$\text{④} - \text{⑤} \quad ; V_1 (-50) = -1200 \rightarrow V_1 = 24 \text{ V.}$$

$$\text{from ①, } V_2 = (400 - 15 \times 24) / (-4) = -10 \text{ V.}$$

$$\text{from ④, } V_3 = (400 - 75 \times 24) / (-5) = 280 \text{ V.}$$
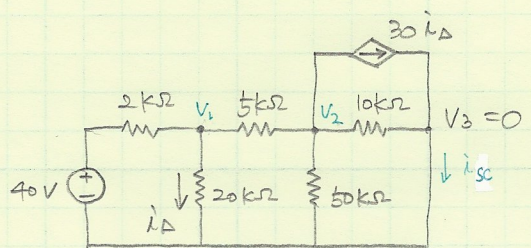
$$\therefore \underline{V_{Th} = V_3 = 280 \text{ V.}} \quad (*)$$



if $V_3 = 0$

$$\begin{cases} V_1 \left(\frac{1}{2000} + \frac{1}{20000} + \frac{1}{5000} \right) + V_2 \left(-\frac{1}{5000} \right) = \frac{40}{2000} \\ V_1 \left(-\frac{1}{5000} + \frac{30}{20000} \right) + V_2 \left(\frac{1}{5000} + \frac{1}{50000} + \frac{1}{10000} \right) = 0 \end{cases}$$

$$V_1 (15) + V_2 (-4) = 400 \quad \text{--- ①'}$$

$$V_1 (65) + V_2 (16) = 0 \quad \text{--- ②'}$$

$$\text{①'} \times 4 + \text{②} \quad ; \quad V_1 (125) = 1600 \quad \therefore V_1 = 1600/125 = 12.8 \text{ V}$$


$$\text{from ②'} \quad ; \quad V_2 = -V_1 \times 65/16 = -52 \text{ V}$$

$$\therefore i_{\Delta} = V_1 / 20000 = 0.64 \text{ mA}$$


$$\begin{aligned} \therefore i_{sc} &= 30 i_{\Delta} + \frac{V_2}{10000} = 30 \times 0.64 \times 10^{-3} + \frac{-52}{10000} \\ &= \underline{14 \text{ mA.}} \quad (**) \end{aligned}$$

From (*) and (**)
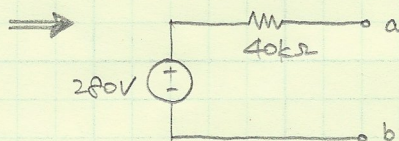
$$R_{Th} = \frac{280 \text{ V}}{14 \text{ mA}} = \underline{20 \text{ k}\Omega}$$



5.14

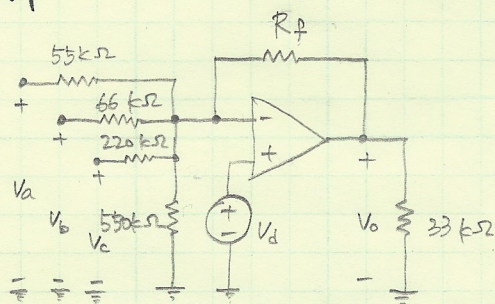

$$\begin{aligned} V_a &= 16V \\ V_b &= 12V \\ V_c &= -6V \\ V_d &= 10V \end{aligned}$$

- a) Assuming ① $V(+) = V(-) = V_d$
 ② No current into Op-Amp.

$$\rightarrow \frac{V_a - V_d}{55000} + \frac{V_b - V_d}{66000} + \frac{V_c - V_d}{220000} - \frac{V_d}{550000} = \frac{V_d - V_o}{R_f}$$

$$12(V_a - V_d) + 10(V_b - V_d) + 3(V_c - V_d) - 1.2V_d = 660000(V_d - V_o)/R_f$$

$$12(16 - 10) + 10(12 - 10) + 3(-6 - 10) - 1.2(10) = 660000(10 - V_o)/R_f$$

$$72 + 20 - 48 - 12 = 660000(10 - V_o)/R_f$$


$$32 R_f = 660000(10 - V_o)$$

When saturated, $V_o = \pm 12V$.

i) $V_o = 12 \rightarrow R_f < 0$

ii) $V_o = -12 \rightarrow R_f = 660000(10 + 12)/32 = \underline{\underline{453.75 k\Omega}}$

b) $V_o = -12V$

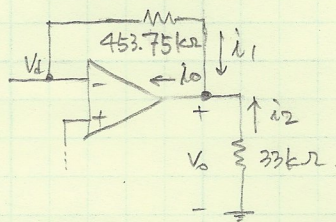

$$I_o = i_1 + i_2$$

$$\therefore I_o = \frac{V_d - V_o}{453750} + \frac{-V_o}{33000}$$

$$= \frac{10 - (-12)}{453750} + \frac{-12}{33000}$$


$$= \underline{\underline{412.121 \mu A}}$$

6.17

$$C = 0.25 \mu\text{F}$$

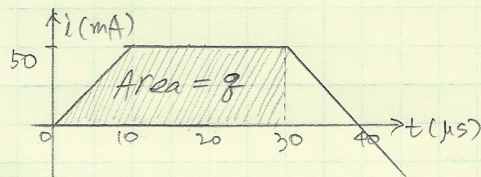a) the charge on the capacitor at $t = 30 \mu\text{s}$?

$$\begin{cases} 0 \leq t \leq 10 \mu\text{s} & i = \frac{50 \times 10^{-3}}{10 \times 10^{-6}} t = 5 \times 10^3 t \text{ A} \\ 10 \mu\text{s} < t < 30 \mu\text{s} & i = 50 \times 10^{-3} \text{ A} \end{cases}$$



from $i = dq/dt$

$$\begin{aligned} q &= \int i dt = \int_0^{10 \mu} 5 \times 10^3 t dt + \int_{10 \mu}^{30 \mu} 50 \times 10^{-3} dt \\ &= 5 \times 10^3 \cdot \frac{t^2}{2} \Big|_0^{10 \mu} + 50 \times 10^{-3} t \Big|_{10 \mu}^{30 \mu} \\ &= 5 \times 10^3 \cdot (10^{-10}/2) + 50 \times 10^{-3} (20 \times 10^{-6}) \end{aligned}$$

$$= 1.25 \mu\text{C} \leftarrow \text{the same as the area above.}$$

b) the voltage on the capacitor at $t = 50 \mu\text{s}$?

$$30 \mu\text{s} \leq t \leq 50 \mu\text{s} \quad i = 200 \times 10^{-3} - 5 \times 10^3 t \text{ A}$$

$$\therefore q = \int i dt + q_0 \quad (q_0 = 1.25 \mu\text{C} \text{ from (a)})$$

$$\begin{aligned} &= \int_{30 \mu}^{50 \mu} 200 \times 10^{-3} dt - \int_{30 \mu}^{50 \mu} 5 \times 10^3 t dt + q_0 \\ &= 200 \times 10^{-3} (20 \times 10^{-6}) - 5 \times 10^3 \times \frac{1}{2} (2500 - 900) \times 10^{-12} + q_0 \\ &= 4 \mu\text{C} - 4 \mu\text{C} + 1.25 \mu\text{C} \\ &= \underline{1.25 \mu\text{C}} \end{aligned}$$

$$\text{from } q = CV \rightarrow V = q/C = 1.25/0.25 = \underline{5 \text{ V}}$$

c) Stored energy?

the charge at $t = 60 \mu\text{s}$

$$50 \mu\text{s} \leq t \leq 60 \mu\text{s} \rightarrow i = -300 \times 10^{-3} + 5 \times 10^3 t$$

$$\begin{aligned} \therefore q &= \int_{50 \mu}^{60 \mu} -300 \times 10^{-3} dt + \int_{50 \mu}^{60 \mu} 5 \times 10^3 t dt + q_0 \\ &= -300 \times 10^{-3} (10 \times 10^{-6}) + 5 \times 10^3 \times \frac{1}{2} (3600 - 2500) \times 10^{-12} + q_0 \\ &= -3 \mu\text{C} + 2.75 \mu\text{C} + 1.25 \mu\text{C} \\ &= \underline{1 \mu\text{C}} \end{aligned}$$


We need to use the equation: $W = \frac{1}{2} CV^2$

$$\text{from } Q = CV \rightarrow V = Q/C = 1/0.25 = 4V$$

$$\therefore W = \frac{1}{2} (0.25 \times 10^{-6}) (4^2) = \underline{\underline{2 \mu J}}$$

7.25

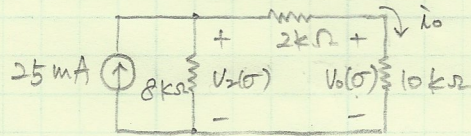a) When $t < 0$; No current through capacitors. as system is in steady state.



(so $C \frac{dV}{dt} = 0$)


$$i_o(0^-) = \frac{(25 \times 10^{-3}) \cdot 8}{8 + 12} = 10 \times 10^{-3} = \underline{10 \text{ mA}}$$

$$V_o(0^-) = i_o(0^-) \times 10000 = \underline{100 \text{ V}}$$

$$V_z(0^-) = \{25 \times 10^{-3} - i_o(0^-)\} \times 8000$$


$$= 15 \times 10^{-3} \times 8 \times 10^3 = \underline{120 \text{ V}}$$

When $t > 0$

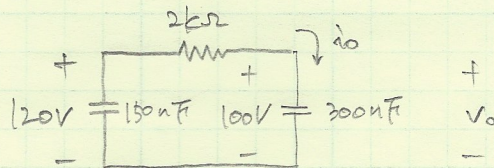

$$C_{\text{tot}} = \left(\frac{1}{150 \times 10^{-9}} + \frac{1}{300 \times 10^{-9}} \right)^{-1} = \frac{300 \times 150 \times 10^{-18}}{(300 + 150) \times 10^{-9}}$$

$$= 0.1 \mu\text{F}$$

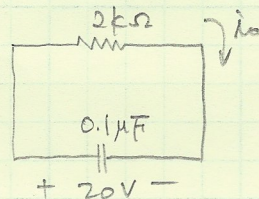

$$\tau = RC = 0.2 \text{ ms}$$

$$\therefore i_o(t) = \frac{20}{2000} e^{-t/\tau}$$

$$= 10 e^{-t/0.2 \times 10^{-3}} \text{ mA}$$

$$= \underline{10 e^{-5000t} \text{ mA}}$$

b) $q = CV$

$$\therefore V = \frac{1}{C} q = \frac{1}{C} \int i dt$$


$$V_o = \frac{1}{300 \times 10^{-9}} \int_0^t 10 \times 10^{-3} \cdot e^{-5000t} dt + V_o$$

$$= \frac{10^9}{300} \times 10^{-2} \times \left(\frac{1}{-5000} \right) e^{-5000t} \Big|_0^t + 100$$

$$= -\frac{20}{3} \cdot (e^{-5000t} - 1) + 100 \quad \left(\frac{20}{3} + 100 = \frac{320}{3} \right)$$

$$= \underline{-\frac{20}{3} e^{-5000t} + \frac{320}{3} \text{ V} \quad (t \geq 0)}$$

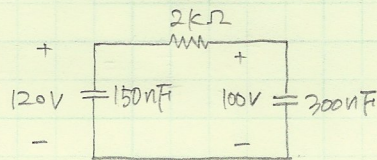c) The energy (in μJ) trapped in the circuit.



from $W = \frac{1}{2} CV_0^2$

&


$$V_0(t) = -\frac{20}{3} e^{-5000t} + \frac{320}{3} \rightarrow \text{The final voltage}$$

$$V_0(\infty) = 320/3$$

$$\begin{aligned} \therefore W_{\text{trapped}} &= \frac{1}{2} (150 \times 10^{-9}) \left(\frac{320}{3} \right)^2 + \frac{1}{2} (300 \times 10^{-9}) \left(\frac{320}{3} \right)^2 \\ &= \underline{\underline{2560 \mu\text{J}}} \end{aligned}$$

8.51

a) when $t < 0$

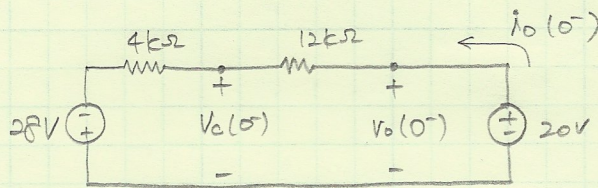


$$i_o(t^-) = [20 - (-28)] / 16000 = 3 \text{ mA}$$


$$V_o(t^-) - V_c(t^-) = 12000 \times 3 \times 10^{-3} = 36 \text{ V}$$

$$\therefore V_c(t^-) = V_o(t^-) - 36 \text{ V} = 20 - 36 = -16 \text{ V}$$

when $t = 0^+$

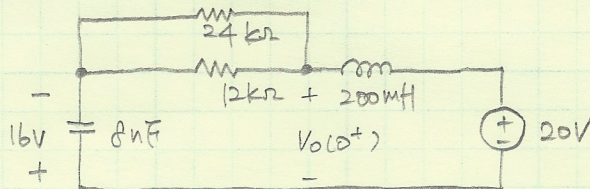
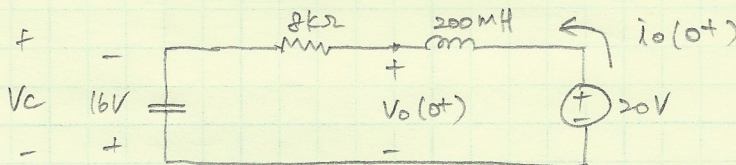
$$24 \text{ k}\Omega \parallel 12 \text{ k}\Omega = \left(\frac{1}{24} + \frac{1}{12} \right)^{-1} = 8 \text{ k}\Omega$$



$$i_o(t^+) = \frac{V_o(t^+) - (-16)}{8000} = 3 \times 10^{-3}$$

$$\therefore V_o(t^+) = 24 - 16 = \underline{\underline{8 \text{ V}}}$$

b) $V_o(t^+) = 8000 i_o(t^+) + V_c(t^+)$

$$\frac{dV_o(t^+)}{dt} = 8000 \frac{di_o(t^+)}{dt} + \frac{dV_c(t^+)}{dt}$$

① from $V_L(t^+) = L \cdot \frac{di_o(t^+)}{dt} \rightsquigarrow \frac{di_o(t^+)}{dt} = V_L(t^+) / L$
 $= (20 - 8) / 0.2 = 60 \text{ A/s}$

② from $i_o(t^+) = C \cdot \frac{dV_c(t^+)}{dt} \rightsquigarrow \frac{dV_c(t^+)}{dt} = \frac{3 \times 10^{-3}}{8 \times 10^{-9}} = 375000$

CV = fast.

$$\therefore \frac{dV_o(t^+)}{dt} = 8000(60) + 375000 = \underline{\underline{855000 \text{ V/s}}}$$

c) $V_o(t)$ for $t \geq 0$.

For a series RLC circuit with voltage source V

$$\frac{d^2 V_o}{dt^2} + \frac{R}{L} \frac{dV_o}{dt} + \frac{V_o}{RL} = \frac{V}{LC}$$

$$\omega_0^2 = 1/LC = 625 \times 10^6 \rightarrow \omega_0 = 25000 \text{ rad/s}$$

$$\alpha = R/2L = 20000 \text{ rad/s} \rightarrow \alpha^2 = 400 \times 10^6$$

$$\alpha^2 - \omega_0^2 = -225 \times 10^6 < 0 \therefore \text{Underdamped.}$$

$$\begin{aligned} s_1, s_2 &= -20000 \pm j\sqrt{225 \times 10^6} \\ &= -20000 \pm j15000 \text{ rad/s} \end{aligned}$$

For underdamped RLC circuits,

$$V_o(t) = V_f + B_1' e^{-\alpha t} \cos \omega_d t + B_2' e^{-\alpha t} \sin \omega_d t$$

$$V_f = V_o(\infty) = 20V$$

At $t = 0^+$,

$$V_o(0^+) = 8V \quad \text{----- } \textcircled{1}$$

$$\frac{dV_o(0^+)}{dt} = 855000 \text{ V/s} \quad \text{----- } \textcircled{2}$$

$$\text{from } \textcircled{1}, \quad 8 = 20 + B_1' \rightarrow B_1' = -12$$

$$\text{from } \textcircled{2}, \quad 855000 = B_1'(-\alpha) + B_2' \omega_d$$

$$\therefore B_2 = \frac{855000 + 20000(-12)}{15000} = 41$$

$$\begin{aligned} \therefore \frac{dV_o(t)}{dt} &= 0 + B_1'(-\alpha)e^{-\alpha t} \cos \omega_d t + B_1'(\omega_d)e^{-\alpha t} (-\sin \omega_d t) \\ &\quad + B_2'(-\alpha)e^{-\alpha t} \sin \omega_d t + B_2'(\omega_d)e^{-\alpha t} \cos \omega_d t \end{aligned}$$

$$\therefore V_o(t) = 20 - 12e^{-20000t} \cos 25000t + 41e^{-20000t} \sin 25000t$$

6.

$$\begin{aligned}
 (1+3j) + \frac{2-2j}{2+j} &= \frac{(1+3j)(2+j) + (2-2j)}{2+j} \\
 &= \frac{2+7j-3+2-2j}{2+j} \\
 &= \frac{1+5j}{2+j} = \frac{(1+5j)(2-j)}{(2+j)(2-j)} \\
 &= \frac{2+10j-j+5}{5} \\
 &= \frac{7+9j}{5} = 1.4 + 1.8j \quad (\text{Cartesian form}) \\
 &= \sqrt{1.4^2 + 1.8^2} \angle \tan^{-1}(1.8/1.4) \\
 &= 2.28 \angle 52.125^\circ \quad (\text{polar form})
 \end{aligned}$$

OR,

$$\begin{aligned}
 \frac{1+5j}{2+j} &= \frac{\sqrt{1^2+5^2} \angle \tan^{-1}(5/1)}{\sqrt{2^2+1^2} \angle \tan^{-1}(1/2)} \\
 &= \frac{\sqrt{26} \angle 78.690^\circ}{\sqrt{5} \angle 26.565^\circ} \\
 &= 2.28 \angle (78.690^\circ - 26.565^\circ) \\
 &= 2.28 \angle 52.125^\circ
 \end{aligned}$$