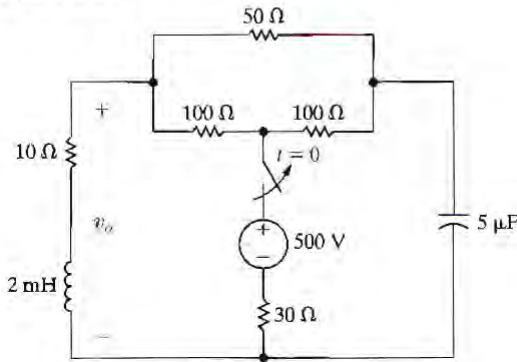



- 13.13** The switch in the circuit in Fig. P13.13 has been closed for a long time before opening at  $t = 0$ .  
PSPICE  
 a) Construct the  $s$ -domain equivalent circuit for  $t > 0$ .  
 b) Find  $V_o$ .  
 c) Find  $v_o$  for  $t \geq 0$ .  
 d) Check your answer to (c) with PSpice.

Figure P13.13




- 13.19** The switch in the circuit in Fig. P13.19 has been closed for a long time. At  $t = 0$ , the switch is opened.  
PSPICE  
 a) Find  $v_o(t)$  for  $t \geq 0$ .  
 b) Find  $i_o(t)$  for  $t \geq 0$ .

Figure P13.19

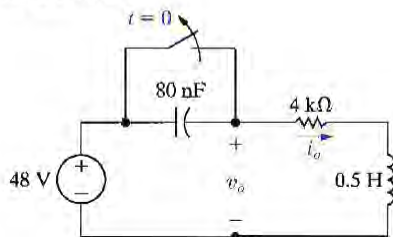


- 13.32** There is no energy stored in the circuit in Fig. P13.32 at the time the current source turns on. Given that  $i_g = 100u(t)$  A:  
PSPICE  
 a) Find  $I_o(s)$ .  
 b) Use the initial- and final-value theorems to find  $i_o(0^+)$  and  $i_o(\infty)$ .  
 c) Determine if the results obtained in (b) agree with known circuit behavior.  
 d) Find  $i_o(t)$ .

Figure P13.32

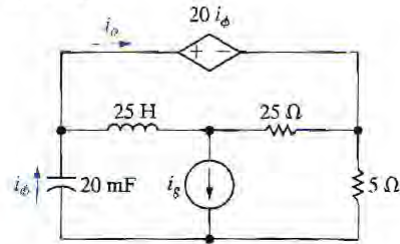


- 13.44** Find  $v_o(t)$  in the circuit shown in Fig. P13.44 if the ideal op amp operates within its linear range and  $v_g = 400u(t)$  mV.  
PSPICE

Figure P13.44

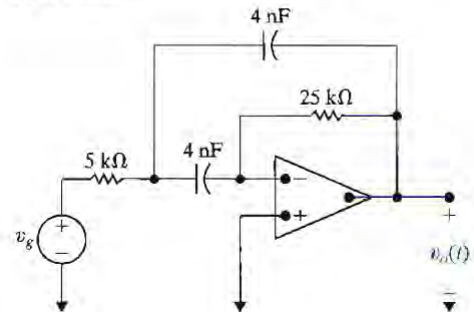


- 13.56** a) Find the transfer function  $I_o/I_g$  as a function of  $\mu$  for the circuit seen in Fig. P13.56.  
PSPICE  
 b) Find the largest value of  $\mu$  that will produce a bounded output signal for a bounded input signal.  
 c) Find  $i_o$  for  $\mu = -0.5, 0, 1, 1.5$ , and 2 if  $i_g = 10u(t)$  A.

Figure P13.56

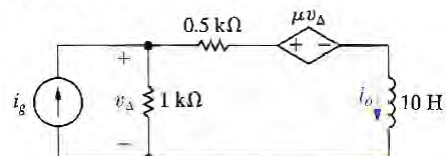

13.13

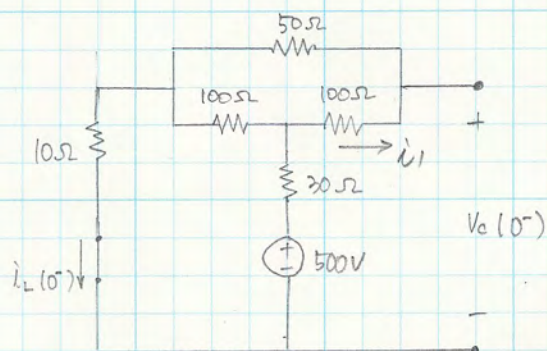
(a) For  $t < 0$ ,

$$100 \parallel (100 + 50) = \frac{100 \times 150}{100 + 150} = 60 \Omega$$

$$\therefore i_1(0^-) = \frac{500}{30 + 60 + 10} = 5 \text{ A}$$


$$i_1 = 5 \times \frac{100}{100 + 150} = 2 \text{ A}$$

$$\begin{aligned} \rightarrow V_0(0^-) &= 500 - 30 \cdot i_1(0^-) - 100 i_1 \\ &= 500 - 150 - 200 \\ &= \underline{\underline{150 \text{ V}}} \end{aligned}$$

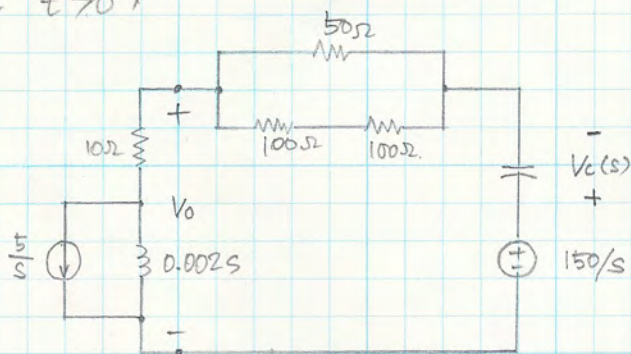For  $t > 0$ ,

$$50 \parallel (100 + 100) = \frac{50 \times 200}{50 + 200} = 40 \Omega$$

Via source transform.

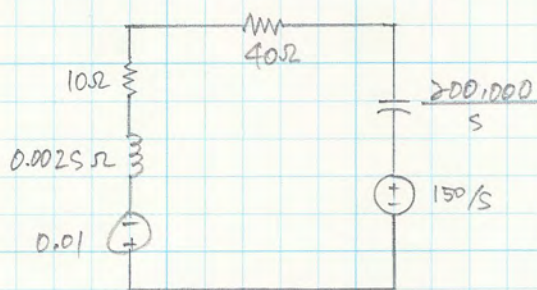



$$(b) \frac{V_0 + 0.01}{10 + 0.002s} + \frac{V_0 - 150/s}{40 + \frac{200,000}{s}} = 0$$

$$V_0 \left[ \frac{1}{10 + 0.002s} + \frac{1}{40 + \frac{200,000}{s}} \right] = \frac{150/s}{40 + \frac{200,000}{s}} - \frac{0.01}{10 + 0.002s}$$



$$V_0 \left[ \frac{500}{s + 5000} + \frac{s}{40(s + 5000)} \right] = \frac{150}{40(s + 5000)} - \frac{50}{s + 5000}$$

$$V_0 [500 \times 40 + s] = 150 - 50 \times 40 = -50.$$


$$\therefore V_0 = \frac{-50.}{s + 20000}$$

$$(c) \underline{v_0(t) = -50 \cdot e^{-20000t} \cdot u(t) \text{ V}}$$


(d) check next page

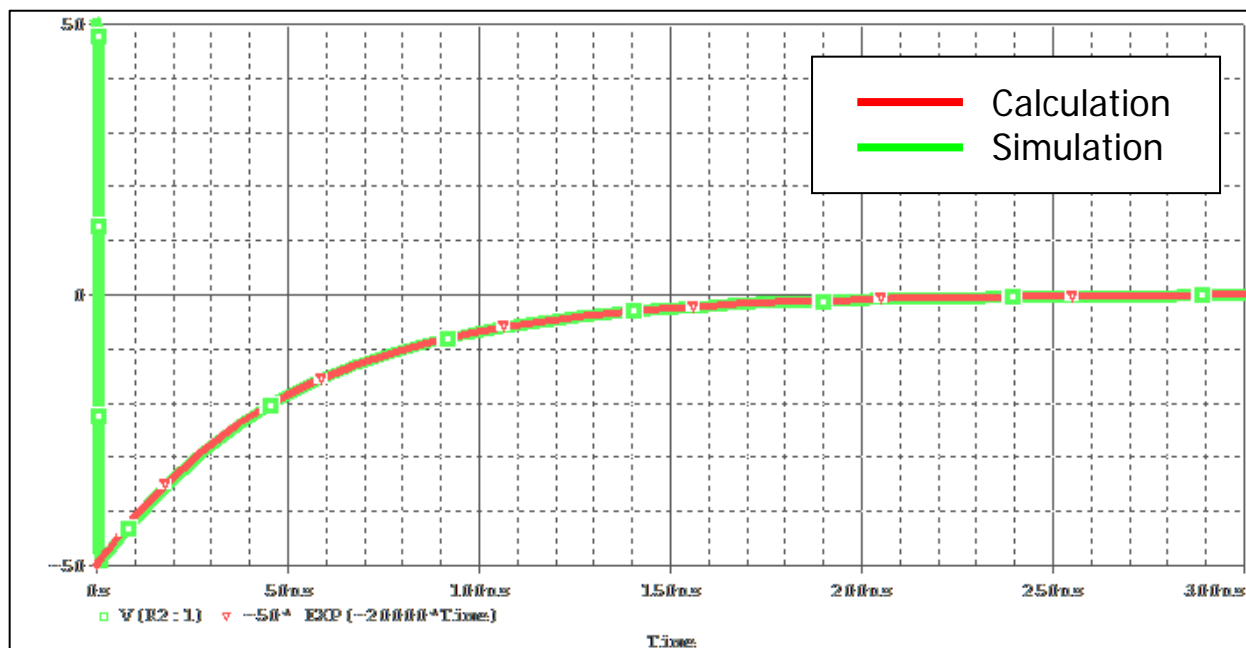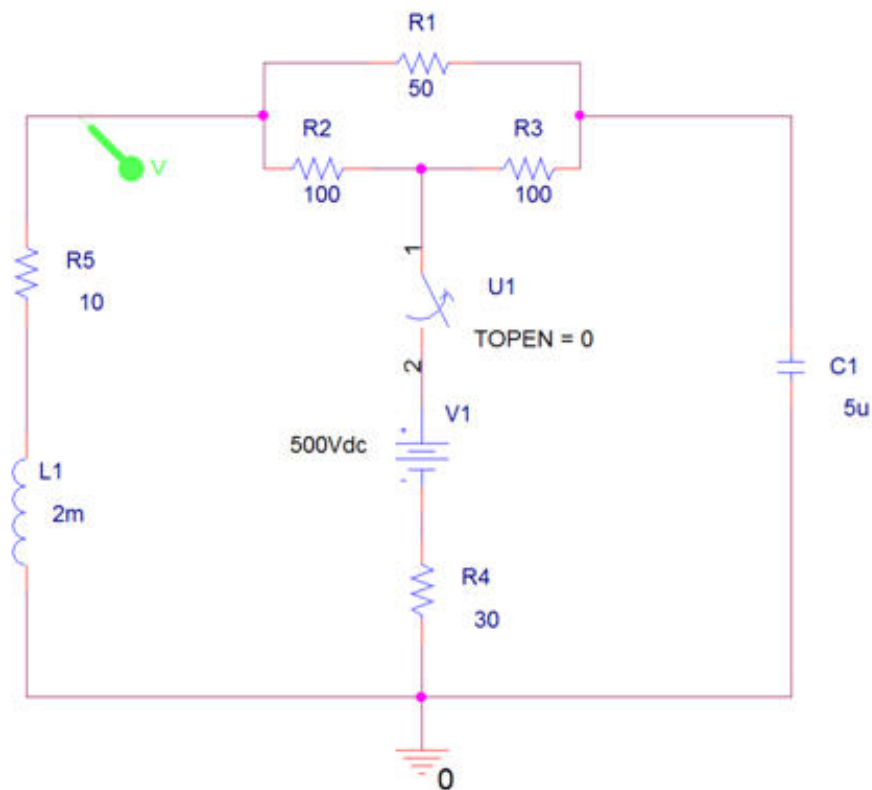


13.19

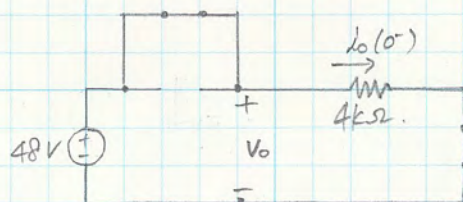(a) Find  $V_o(t)$  for  $t \geq 0$ .for  $t < 0$ .

$$i_o(0^-) = 48/4k = 12 \text{ mA}$$

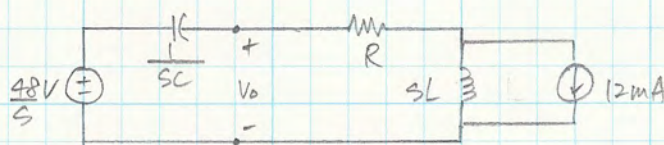for  $t \geq 0$ 

Via Source transform

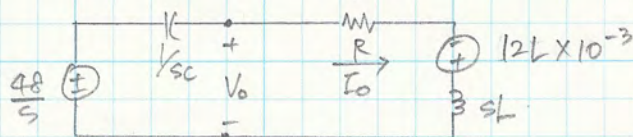

$$\frac{V_o - 48/s}{1k} + \frac{V_o + 12L \times 10^{-3}}{R + sL} = 0$$

$$(sC V_o - 48C)(R + sL) + V_o + 12L \times 10^{-3} = 0$$

$$V_o(sRC + s^2LC + 1) = s48LC + 48RC - 12L \times 10^{-3}$$

$$\therefore V_o = \frac{s48LC + 48RC - 12L \times 10^{-3}}{s^2LC + sRC + 1}$$

$$= \frac{48(s + R/L) - 12 \times 10^{-3}/C}{s^2 + s(R/L) + (1/LC)}$$

$$R/L = 8000$$

$$1/LC = 2.5 \times 10^7$$

$$= \frac{48s + 48 \times 8000 - 150 \times 10^3}{s^2 + 8000s + 2.5 \times 10^7}$$

$$= \frac{48(s + 4875)}{s^2 + 8000s + 2.5 \times 10^7}$$

$$s = -4000 \pm j 3000$$

C



$$\therefore V_o = \frac{k_1}{s+4000-j3000} + \frac{k_2}{s+4000+j3000}$$

$$48(s+4875) = k_1(s+4000+j3000) + k_2(s+4000-j3000)$$

$$s = -4000 + j3000$$

$$48(-4000+j3000+4875) = k_1(j6000)$$

$$\therefore k_1 = \frac{48(875+j3000)}{j6000}$$

$$= \frac{48 \times 3125 \angle 73.74^\circ}{6000 \angle 90^\circ}$$

$$= 25 \angle (73.74^\circ - 90^\circ)$$

$$= 25 \angle -16.26^\circ$$

$$k_2 = k_1^* = 25 \angle 16.26^\circ$$

$$\sqrt{875^2 + 3000^2} = 3125$$

$$\tan^{-1}(3000/875) = 73.74^\circ$$

$$\Rightarrow V_o = \frac{25 \angle -16.26^\circ}{s+4000-j3000} + \frac{25 \angle 16.26^\circ}{s+4000+j3000}$$

$$\hookrightarrow V_o(t) = \underline{2 \times 25 e^{-4000t} \cos(3000t - 16.26^\circ) \text{ u(t) V.}}$$

(b) Find  $i_o(t)$  for  $t \geq 0$

$$I_o = \frac{48/s + 12L \times 10^{-3}}{1/sC + R + sL} = \frac{48C + sC \cdot 12L \times 10^{-3}}{s^2 LC + sRC + 1}$$

$$= \frac{48/L + s \cdot 12 \times 10^{-3}}{s^2 + 8000s + 2.5 \times 10^7}$$

$$= \frac{12 \times 10^{-3}(s+8000)}{(s+4000-j3000)(s+4000+j3000)}$$

$$= \frac{k_1}{s+4000-j3000} + \frac{k_2}{s+4000+j3000}$$

$$12 \times 10^{-3}(s+8000) = k_1(s+4000+j3000) + k_2(s+4000-j3000)$$

$$s = -4000 + j3000 \rightarrow 12 \times 10^{-3}(-4000 + j3000 + 8000) = k_1(j6000)$$

$$\therefore k_1 = \frac{12 \times 10^{-3}(4000 + j3000)}{j6000}$$

CL



$$k_1 = \frac{12 \times 10^{-3} \times 5000 \angle 36.87^\circ}{6000 \angle 90^\circ} = 10 \times 10^{-3} \angle -53.13^\circ$$



$$\therefore k_2 = k_1^* = 10 \times 10^{-3} \angle 53.13^\circ$$

$$I_0 = \frac{10 \times 10^{-3} \angle -53.13^\circ}{s + 4000 - j3000} + \frac{10 \times 10^{-3} \angle 53.13^\circ}{s + 4000 + j3000}$$

$$\begin{aligned} \hookrightarrow i_0(t) &= 2 \times 10 \times 10^{-3} e^{-4000t} \cos(3000t - 53.13^\circ) \text{ A} \\ &= \underline{\underline{20 \cdot e^{-4000t} \cos(3000t - 53.13^\circ) \text{ mA}}} \end{aligned}$$

13.32

(a)

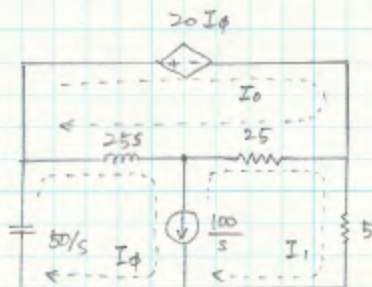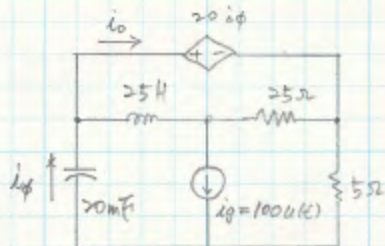

$$20 I_\phi + 25(I_0 - I_1) + 25s(I_0 - I_\phi) = 0 \quad \text{----- ①}$$

$$\frac{50}{s} I_\phi + 25s(I_\phi - I_0) + 25(I_1 - I_0) + 5I_1 = 0 \quad \text{----- ②}$$

$$I_\phi - I_1 = 100/s \quad \text{----- ③}$$

from ① + ②,

$$20 I_\phi + 5 I_1 + 50/s I_\phi = 0$$



using ③

$$20 I_\phi + 5 \left( I_\phi - \frac{100}{s} \right) + \frac{50}{s} I_\phi = 0$$

$$I_\phi \left( 20 + 5 + \frac{50}{s} \right) = \frac{500}{s}$$

$$\therefore I_\phi = \frac{500}{25s + 50} = \frac{20}{s+2}$$

$$\rightarrow I_1 = I_\phi - \frac{100}{s} = \frac{20}{s+2} - \frac{100}{s}$$

$\therefore$  equation ① becomes

$$I_0(25 + 25s) = I_\phi(25s - 20) + 25 I_1$$

$$I_0 = I_\phi \frac{5s - 4}{5(s+1)} + I_1 \cdot \frac{1}{s+1}$$

$$= \frac{20}{s+2} \cdot \frac{5s-4}{5(s+1)} + \left( \frac{20}{s+2} - \frac{100}{s} \right) \frac{1}{s+1}$$

$$= \frac{20s - 16}{(s+1)(s+2)} + \frac{20}{(s+1)(s+2)} - \frac{100}{s(s+1)}$$

$$= \frac{20s^2 - 16s + 20s - 100s - 200}{s(s+1)(s+2)}$$

$$= \frac{20s^2 - 96s - 200}{s(s+1)(s+2)}$$

~~~~~

(b)  $\lim_{t \rightarrow 0^+} f(t) = \lim_{s \rightarrow \infty} s F(s)$  (if  $f(t)$  contains no impulse function)

$$= \lim_{s \rightarrow \infty} \frac{20s^2 - 96s - 200}{(s+1)(s+2)} = \underline{\underline{20 \text{ A}}}$$


$$\lim_{t \rightarrow \infty} f(t) = \lim_{s \rightarrow 0} s F(s)$$

(if the poles of  $F(s)$ , except for a first-order pole at the origin lie in the left half of the  $s$  plane)

$$= \lim_{s \rightarrow 0} \frac{20s^2 - 96s - 200}{(s+1)(s+2)} = \frac{-200}{2} = \underline{\underline{-100 \text{ A}}}$$



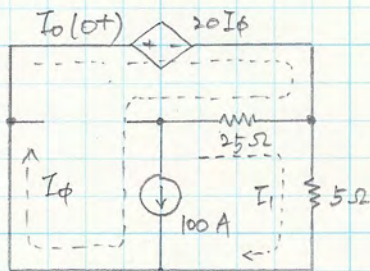(c) at  $t = 0^+$  (inductor  $\rightarrow$  open)



$$20 I_{\phi} + 5 I_1 = 0.$$



$$I_{\phi} - I_1 = 100.$$

$$\therefore 20 I_{\phi} + 5(I_{\phi} - 100) = 0$$


$$25 I_{\phi} = 500.$$

$$\therefore \underline{I_{\phi} = 20 \text{ A.} = I_0(0^+)}$$

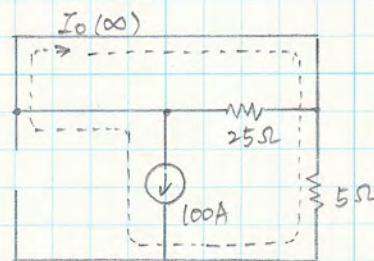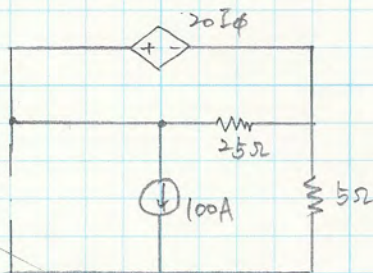at  $t \rightarrow +\infty$  (capacitor open,  $I_{\phi} = 0$ )



$\equiv$

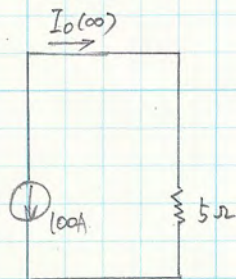

$$\underline{I_0(\infty) = -100 \text{ A}}$$

$$(d) \quad I_0 = \frac{20s^2 - 96s - 200}{s(s+1)(s+2)} = \frac{k_1}{s} + \frac{k_2}{s+1} + \frac{k_3}{s+2}$$

$$20s^2 - 96s - 200 = k_1(s+1)(s+2) + k_2 s(s+2) + k_3 \cdot s(s+1)$$

$$s=0. \quad -200 = 2k_1 \rightarrow k_1 = -100$$

$$s=-1. \quad 20 + 96 - 200 = k_2(-1) \rightarrow k_2 = 84.$$

$$s=-2. \quad 80 + 192 - 200 = k_3(2) \rightarrow k_3 = 36$$

$$\therefore I_0(s) = \frac{-100}{s} + \frac{84}{s+1} + \frac{36}{s+2}$$


$$\hookrightarrow \underline{i_0(t) = [-100 + 84e^{-t} + 36e^{-2t}] u(t) \text{ A.}}$$

$$\text{check) ZVT } i_0(0^+) = -100 + 84 + 36 = \underline{20 \text{ A.}}$$

$$\text{FVT } i_0(\infty) = \underline{-100 \text{ A.}}$$



13.44

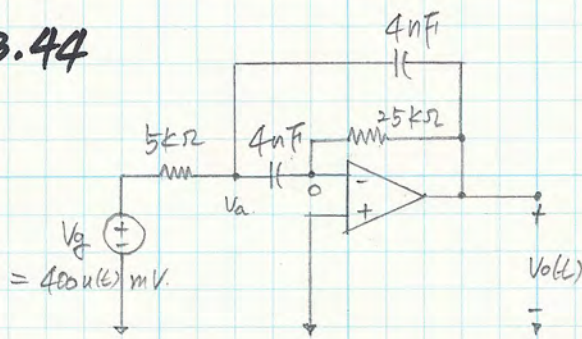Find  $V_o(t)$ 

$$\frac{1}{sC} = 250 \times 10^6 / s$$

$$\text{KCL at } V_a \text{ node} \rightarrow \frac{V_a - 0.4/s}{5000} + \frac{V_a - V_o}{250 \times 10^6 / s} + \frac{V_a}{250 \times 10^6 / s} = 0 \dots (1)$$

$$\text{KCL at inverting input} \rightarrow \frac{0 - V_a}{250 \times 10^6 / s} + \frac{0 - V_o}{25000} = 0 \dots (2)$$

$$V_a = -\frac{V_o}{25000} \times \frac{250 \times 10^6}{s} = \frac{-10^4 V_o}{s}$$

equation (1)

$$50000 (V_a - 0.4/s) + s(V_a - V_o) + s V_a = 0$$

$$50000 \left( -\frac{10^4 V_o}{s} - \frac{0.4}{s} \right) + s \left( \frac{-10^4 V_o}{s} - V_o \right) + s \left( -\frac{10^4 V_o}{s} \right) = 0$$

$$V_o \left( \frac{-50000 \times 10^4}{s} - 10^4 - s - 10^4 \right) = \frac{20000}{s}$$

$$V_o (-5 \times 10^8 - 2 \times 10^4 s - s^2) = 2 \times 10^4$$

$$\therefore V_o = \frac{-2 \times 10^4}{s^2 + 2 \times 10^4 s + 5 \times 10^8} \quad \leftarrow s = -10000 \pm j20000$$

$$= \frac{k_1}{s + 10000 - j20000} + \frac{k_2}{s + 10000 + j20000}$$

$$-2 \times 10^4 = k_1 (s + 10000 + j20000) + k_2 (s + 10000 - j20000)$$

$$s = -10000 + j20000$$

$$\rightarrow -20000 = k_1 (j40000) \quad \therefore k_1 = j0.5 = 0.5 \angle 90^\circ$$


$$k_2 = k_1^* = 0.5 \angle -90^\circ$$

$$V_o = \frac{0.5 \angle 90^\circ}{s + 10000 - j20000} + \frac{0.5 \angle -90^\circ}{s + 10000 + j20000}$$

$$\begin{aligned} \hookrightarrow V_o(t) &= 2 \times 0.5 e^{-10000t} \cos(20000t + 90^\circ) \cdot u(t) \text{ V} \\ &= \underline{\underline{e^{-10000t} \sin(20000t) \cdot u(t) \text{ V}}} \end{aligned}$$



13.56

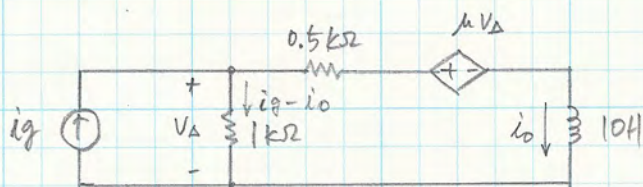

(a) Find the transfer function  $I_o/I_g$

$$1000(I_g - I_o) = V_\Delta \quad \text{--- (1)}$$

$$V_\Delta = 500 I_o + \mu V_\Delta + 10s I_o \quad \text{--- (2)}$$

from (1) and (2)

$$1000(I_g - I_o) = 500 I_o + \mu \cdot 1000(I_g - I_o) + 10s I_o$$

$$I_g(1000 - 1000\mu) = I_o(1000 + 500 - 1000\mu + 10s)$$

$$\therefore \frac{I_o}{I_g} = \frac{1000(1-\mu)}{10s + 1500 - 1000\mu} = \frac{100(1-\mu)}{s + 100(1.5-\mu)}$$

(b) Bounded output: Poles should be in the left half of the  $s$ -plane. (except for a first order pole at the origin)

$$\therefore 1.5 - \mu > 0.$$

(c) Find  $i_o(t)$  for  $\mu = -0.5, 0, 1, 1.5$  and  $2$ .

$$(i_g(t) = 10\text{ u}(t)\text{ A})$$

$$I_o = I_g \cdot \frac{100(1-\mu)}{s + 100(1.5-\mu)} = \frac{1000(1-\mu)}{s[s + 100(1.5-\mu)]}$$

$$1) \mu = -0.5 \quad I_o = \frac{1500}{s(s+200)} = \frac{7.5}{s} - \frac{7.5}{s+200}$$

$$i_o(t) = [7.5 - 7.5e^{-200t}] \text{ u}(t) \text{ A}$$



$$2) \mu = 0$$

$$I_0 = \frac{1000}{s(s+150)} = \frac{6.666}{s} - \frac{6.666}{s+150}$$

$$\underline{i_0(t) = [6.666 - 6.666 e^{-150t}] u(t) \text{ A}}$$

$$3) \mu = 1$$

$$I_0 = 0$$

$$i_0(t) = 0$$

$$4) \mu = 1.5$$

$$I_0 = \frac{-500}{s^2}$$

$$\underline{i_0(t) = -500t \cdot u(t) \text{ A}}$$

$$5) \mu = 2$$

$$I_0 = \frac{-1000}{s(s-50)} = \frac{20}{s} - \frac{20}{s-50}$$

$$\underline{i_0(t) = [20 - 20 e^{50t}] u(t) \text{ A}}$$