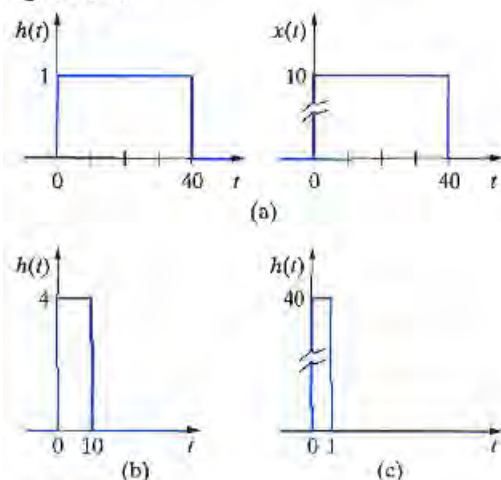


- 13.60** a) Given $y(t) = h(t) * x(t)$, find $y(t)$ when $h(t)$ and $x(t)$ are the rectangular pulses shown in Fig. P13.60(a).
 b) Repeat (a) when $h(t)$ changes to the rectangular pulse shown in Fig. P13.60(b).
 c) Repeat (a) when $h(t)$ changes to the rectangular pulse shown in Fig. P13.60(c).
 d) Sketch $y(t)$ versus t for (a)–(c) on a single graph.
 e) Do the sketches in (d) make sense? Explain.

Figure P13.60




- 13.71** The input voltage in the circuit seen in Fig. P13.71 is

$$v_i = 10[u(t) - u(t - 0.1)] \text{ V.}$$

- a) Use the convolution integral to find v_o .
 b) Sketch v_o for $0 \leq t \leq 1$ s.

Figure P13.71

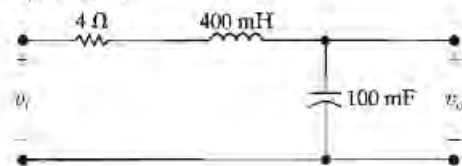


- 13.76** The op amp in the circuit seen in Fig. P13.78 is ideal.

PSpice

- a) Find the transfer function V_o/V_g .
 b) Find v_o if $v_g = 10u(t)$ V.
 c) Find the steady-state expression for v_o if $v_g = 8 \cos 2000t$ V.
 d) Check your answer to (c) with PSpice.


Figure P13.76

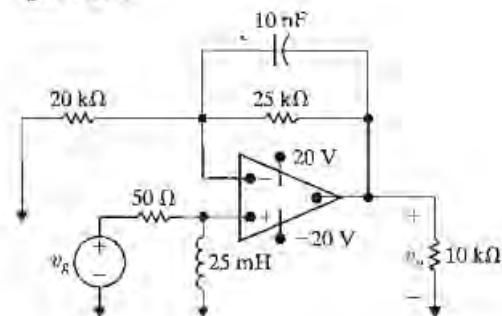

- 13.79** The parallel combination of R_2 and C_2 in the circuit shown in Fig. P13.79 represents the input circuit to a cathode-ray oscilloscope (CRO). The parallel combination of R_1 and C_1 is a circuit model of a compensating lead that is used to connect the CRO to the source. There is no energy stored in C_1 or C_2 at the time when the 10 V source is connected to the CRO via the compensating lead. The circuit values are $C_1 = 5$ pF, $C_2 = 20$ pF, $R_1 = 1$ MOhm, and $R_2 = 4$ MOhm.

- a) Find v_o .
 b) Find i_o .
 c) Repeat (a) and (b) given C_1 is changed to 80 pF.


Figure P13.79

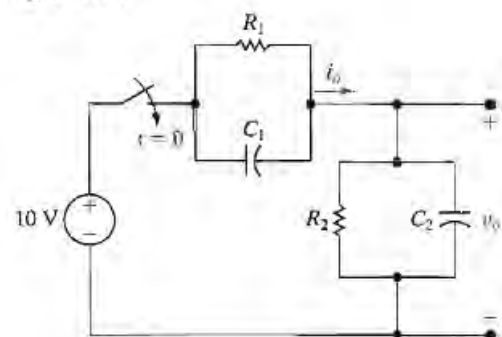

13.85 There is no energy stored in the circuit in Fig. P13.85 at the time the impulsive voltage is applied.

- Find $v_o(t)$ for $t \geq 0$.
- Does your solution make sense in terms of known circuit behavior? Explain.

Figure P13.85

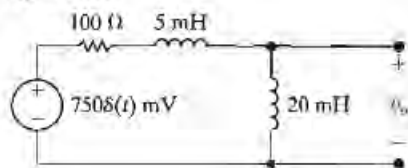

14.5 A resistor denoted as R_L is connected in parallel with the capacitor in the circuit in Fig. 14.7. The loaded low-pass filter circuit is shown in Fig. P14.5.

- Derive the expression for the voltage transfer function V_o/V_i .
- At what frequency will the magnitude of $H(j\omega)$ be maximum?
- What is the maximum value of the magnitude of $H(j\omega)$?
- At what frequency will the magnitude of $H(j\omega)$ equal its maximum value divided by $\sqrt{2}$?
- Assume a resistance of $300 \text{ k}\Omega$ is added in parallel with the 4 nF capacitor in the circuit in Fig. P14.4. Find ω_c , $H(j0)$, $H(j\omega_c)$, $H(j0.2\omega_c)$, and $H(j8\omega_c)$.

Figure P14.5


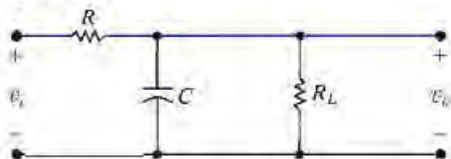


Figure P14.4



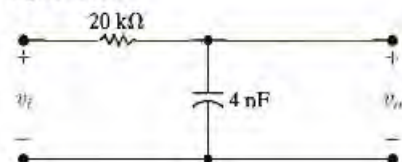


14.13 Using a 25 mH inductor, design a high-pass, RL , passive filter with a cutoff frequency of 160 krad/s .


DESIGN
PROBLEM
PSICE

- Specify the value of the resistance.
- Assume the filter is connected to a pure resistive load. The cutoff frequency is not to drop below 150 krad/s . What is the smallest load resistor that can be connected across the output terminals of the filter?

13.60

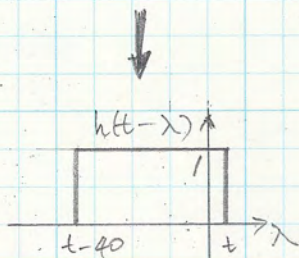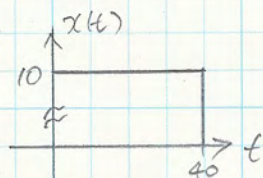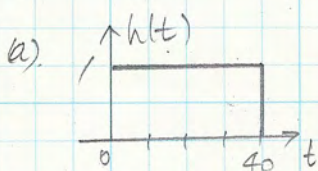


① $0 \leq t \leq 40$; Area increases.

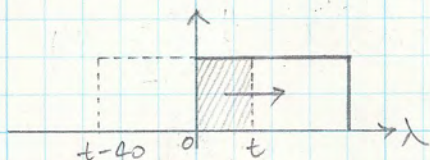

$$\begin{aligned}
 y &= \int_0^t h(t-\lambda) x(\lambda) d\lambda \\
 &= \int_0^t 1 \times 10 d\lambda \\
 &= 10\lambda \Big|_0^t = \underline{10t}
 \end{aligned}$$

② $40 \leq t \leq 80$; Area decreases.


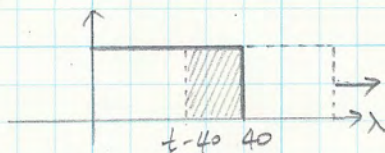


$$\begin{aligned}
 y &= \int_{t-40}^{40} h(t-\lambda) x(\lambda) d\lambda \\
 &= 40\lambda \Big|_{t-40}^{40} \\
 &= 40[40 - (t-40)] \\
 &= \underline{40(80-t)}
 \end{aligned}$$


③ $40 \leq t$; Area = 0

$$y = \underline{0}$$


(b)

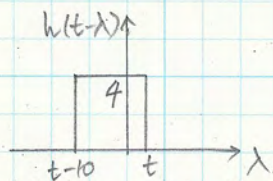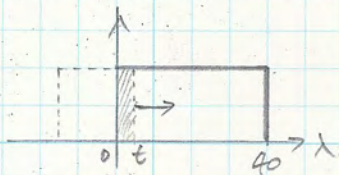① $0 \leq t \leq 10$; Area increases


$$\begin{aligned}
 y &= \int_0^t h(t-\lambda) x(\lambda) d\lambda \\
 &= 4 \times 10 \lambda \Big|_0^t \\
 &= \underline{40t}
 \end{aligned}$$

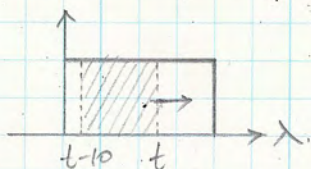② $10 \leq t \leq 40$; Area constant

$$\begin{aligned}
 y &= \int_{t-10}^t h(t-\lambda) x(\lambda) d\lambda \\
 &= 40 \lambda \Big|_{t-10}^t \\
 &= 40(t - (t-10)) \\
 &= \underline{400}
 \end{aligned}$$


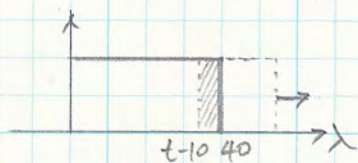
③ $40 \leq t \leq 50$; Area decreases

$$\begin{aligned}
 y &= \int_{t-10}^{40} h(t-\lambda) x(\lambda) d\lambda \\
 &= 40 \lambda \Big|_{t-10}^{40} \\
 &= 40(40 - (t-10)) \\
 &= \underline{40(50-t)}
 \end{aligned}$$

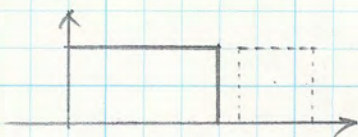④ $50 \leq t$; Area = 0


$$y = \underline{0}$$

(c)

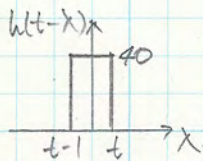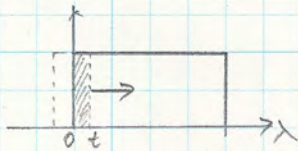① $0 \leq t \leq 1$: Area increases

$$y = \int_0^t h(t-x)x(\lambda) d\lambda$$


$$= \underline{400t}$$

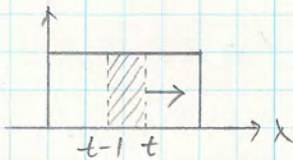② $1 \leq t \leq 40$: Area constant

$$y = \int_{t-1}^t h(t-x)x(\lambda) d\lambda$$

$$= 400[t - (t-1)]$$

$$= \underline{400}$$

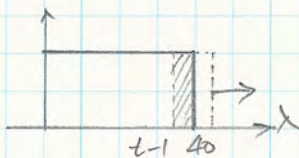③ $40 \leq t \leq 41$: Area decreases


$$y = \int_{t-1}^{40} h(t-x)x(\lambda) d\lambda$$

$$= 400[40 - (t-1)]$$

$$= 400(41-t)$$

④ $41 \leq t$: Area = 0

$$y = \underline{0}$$

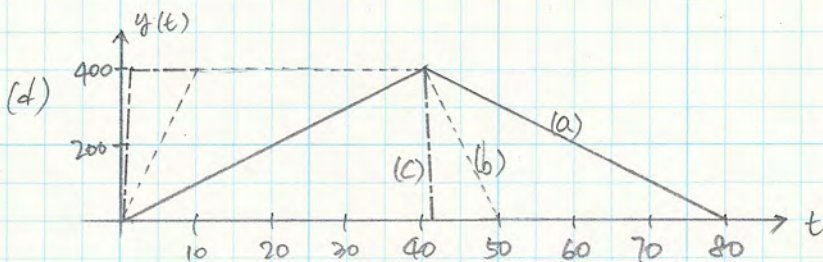



(e) Yes, when $h(t)$ is approaching $40\delta(t)$, $y(t)$ must approach $40x(t)$.
 (a) \rightarrow (c)

$$y(t) = \int_0^t h(t-x)x(\lambda) d\lambda \rightarrow \int_0^t 40\delta(t-x)x(\lambda) d\lambda \rightarrow 40x(t)$$

This can be seen in plot (c). $y(t) \approx 40x(t)$

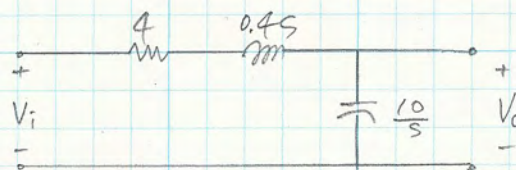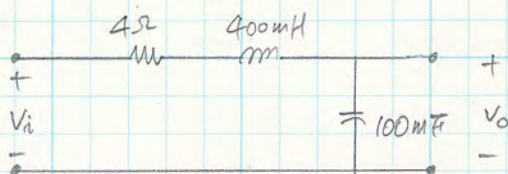
13.71

$$V_i = 10 [u(t) - u(t - 0.1)] \text{ V}$$




$$\begin{aligned} \text{(a)} \quad H(s) &= \frac{V_o}{V_i} = \frac{10/s}{4 + 0.4s + 10/s} \\ &= \frac{10}{0.4s^2 + 4s + 10} \\ &= \frac{25}{s^2 + 10s + 25} \\ &= \frac{25}{(s + 5)^2} \end{aligned}$$
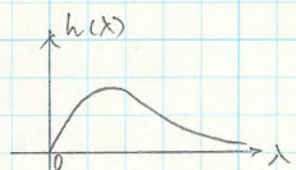
$$\therefore h(\lambda) = 25\lambda e^{-5\lambda} u(\lambda) \implies$$



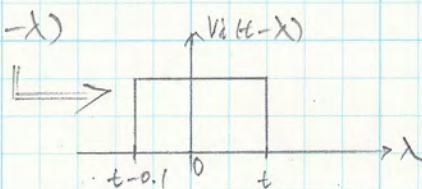For convolution, we need $V_i(t - \lambda)$



i) $0 \leq t \leq 0.1$: Area increasing.

$$V_o = \int_0^t (25\lambda e^{-5\lambda}) \cdot 10 \, d\lambda$$

$$= 250 \int_0^t \underbrace{\lambda}_{f} \underbrace{e^{-5\lambda}}_{g'} \, d\lambda = 250 \left[-\frac{1}{5} t e^{-5t} - \frac{1}{25} e^{-5t} + \frac{1}{25} \right]$$

$$\begin{aligned} (fg)' &= f'g + fg' \\ fg &= (fg)' - f'g \end{aligned}$$

$$= -10e^{-5t}(1 + 5t) + 10.$$

* let $f = \lambda$, $g' = e^{-5\lambda}$.

$$\rightarrow f' = 1, \quad g = -\frac{1}{5} e^{-5\lambda}$$

from $(f \cdot g)' = f'g + fg'$

$$fg' = (fg)' - f'g$$

$$\int_0^t fg' \, d\lambda = [fg]_0^t - \int_0^t f'g \, d\lambda.$$

$$= \left[\lambda \left(-\frac{1}{5} e^{-5\lambda} \right) \right]_0^t - \int_0^t \left(-\frac{1}{5} \right) e^{-5\lambda} \, d\lambda$$

$$= \left[-\frac{1}{5} \lambda e^{-5\lambda} - \frac{1}{25} e^{-5\lambda} \right]_0^t$$

ii) $0.1 \leq t \leq \infty$

$$V_o = \int_{t-0.1}^t (25\lambda e^{-5\lambda}) 10 d\lambda$$

$$= \left[-\frac{1}{5}\lambda e^{-5\lambda} - \frac{1}{25} e^{-5\lambda} \right]_{t-0.1}^t \times 250$$

$$= \frac{-1}{25} \left[e^{-5\lambda} + 5\lambda e^{-5\lambda} \right]_{t-0.1}^t \times 250$$


$$= -10 \left[\underbrace{e^{-5t} + 5te^{-5t}} - \underbrace{e^{-5t+0.5} - 5(t-0.1)e^{-5t+0.5}} \right]$$

$$= -10 e^{-5t} \left[1+5t + e^{0.5} (-1-5t+0.5) \right]$$


$$= -10 e^{-5t} \left[1+5t - e^{0.5} (5t+0.5) \right]$$

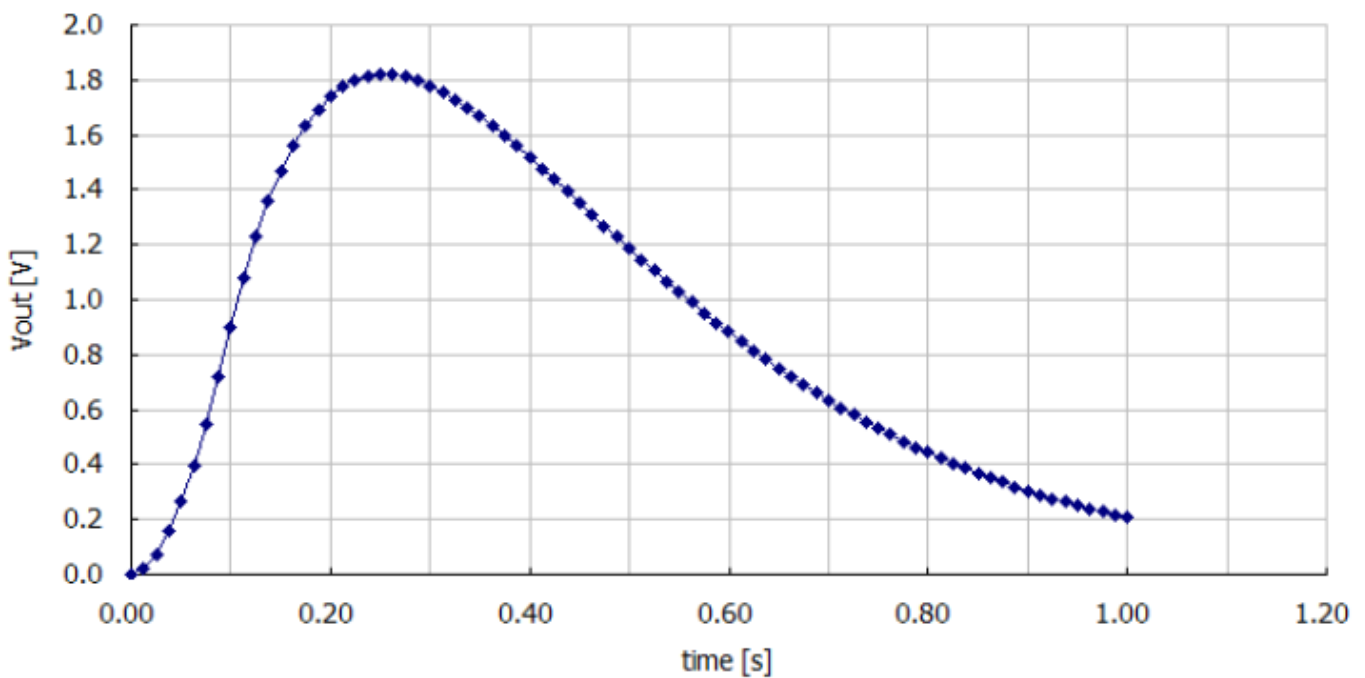(b) sketch.

$$0 \leq t \leq 1 \rightarrow \begin{array}{ll} 0 \leq t \leq 0.1 & ; -10e^{-5t} (1+5t) + 10 \\ 0.1 \leq t \leq 1.0 & ; -10e^{-5t} (1+5t) - e^{0.5} (5t+0.5) \end{array}$$



13.76

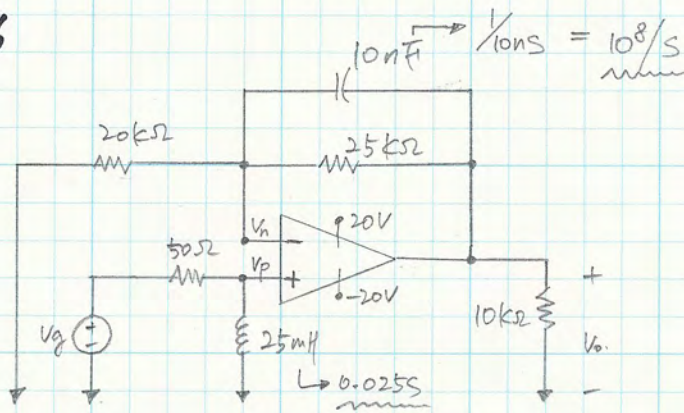

$$(a) \quad V_p = V_n = V_g \cdot \left(\frac{0.025S}{50 + 0.025S} \right) = \frac{S}{S + 2000} V_g$$

KCL at V_n node,

$$\frac{V_n}{20 \times 10^3} + \frac{V_n - V_o}{25 \times 10^3} + \frac{V_n - V_o}{10^8/S} = 0$$

$$V_n \left(\frac{1}{20} + \frac{1}{25} + \frac{S}{10^5} \right) = V_o \left(\frac{1}{25} + \frac{S}{10^5} \right)$$

$$V_n (5000 + 4000 + S) = V_o (4000 + S)$$

$$\frac{S}{(S+2000)} (9000 + S) V_g = V_o (S + 4000) \rightarrow \frac{V_o}{V_g} = \frac{S(S+9000)}{(S+2000)(S+4000)} = H(s)$$

$$(b) \quad V_g = 10 u(t) \rightarrow V_g = 10/s$$

$$\therefore V_o = \frac{S(S+9000)}{(S+2000)(S+4000)} \cdot \frac{10}{S} = \frac{10(S+9000)}{(S+2000)(S+4000)}$$

$$= \frac{k_1}{S+2000} + \frac{k_2}{S+4000}$$

$$k_1 = \frac{10(S+9000)}{(S+4000)} \Big|_{S=-2000} = \frac{10(7000)}{2000} = 35$$

$$k_2 = \frac{10(S+9000)}{(S+2000)} \Big|_{S=-4000} = \frac{10(5000)}{-2000} = -25$$


$$\therefore \underline{V_o(t) = [35 e^{-2000t} - 25 e^{-4000t}] u(t)}$$

$$(c) \quad V_g = 8 \cos 2000t$$

$$S = j\omega = j2000$$

$$\begin{aligned} H(j\omega) &= \frac{j2000(9000 + j2000)}{(2000 + j2000)(4000 + j2000)} = \frac{j2(9 + j2)}{(2 + j2)(4 + j2)} \\ &= \frac{(2 \angle 90^\circ) \sqrt{9^2 + 2^2} \angle 12.521^\circ}{(\sqrt{2^2 + 2^2} \angle 45^\circ)(\sqrt{4^2 + 2^2} \angle 26.565^\circ)} \\ &= 1.458 \angle (90^\circ + 12.521^\circ - 45^\circ - 26.565^\circ) \\ &= 1.458 \angle 30.956^\circ \end{aligned}$$
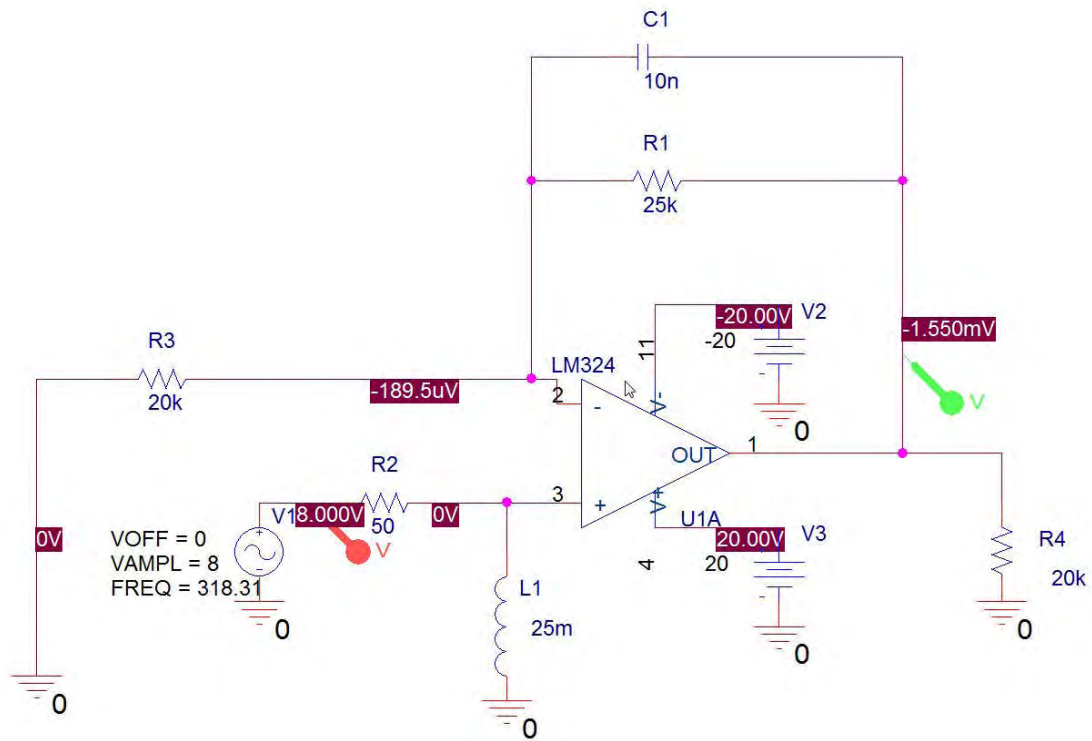
$$\begin{aligned} \therefore V_o - \text{steady state} &= 8 \times 1.456 \cos(2000t + 30.956^\circ) \\ &= \underline{\underline{11.68 \cos(2000t + 30.956^\circ)}} \end{aligned}$$




Property Editor


New Column... Apply Display... Delete Property Filter PSpice Help

| | Reference | Value | AC | DC | DF | FREQ | PHASE | TD | VAMPL | VOFF |
|---|---------------------|-------|------|----|----|------|-------|----|-------|------|
| 1 | SCHEMATIC1:PAGE1:V2 | V2 | VSIN | | | 0 | 100 | 90 | 1 | 0 |

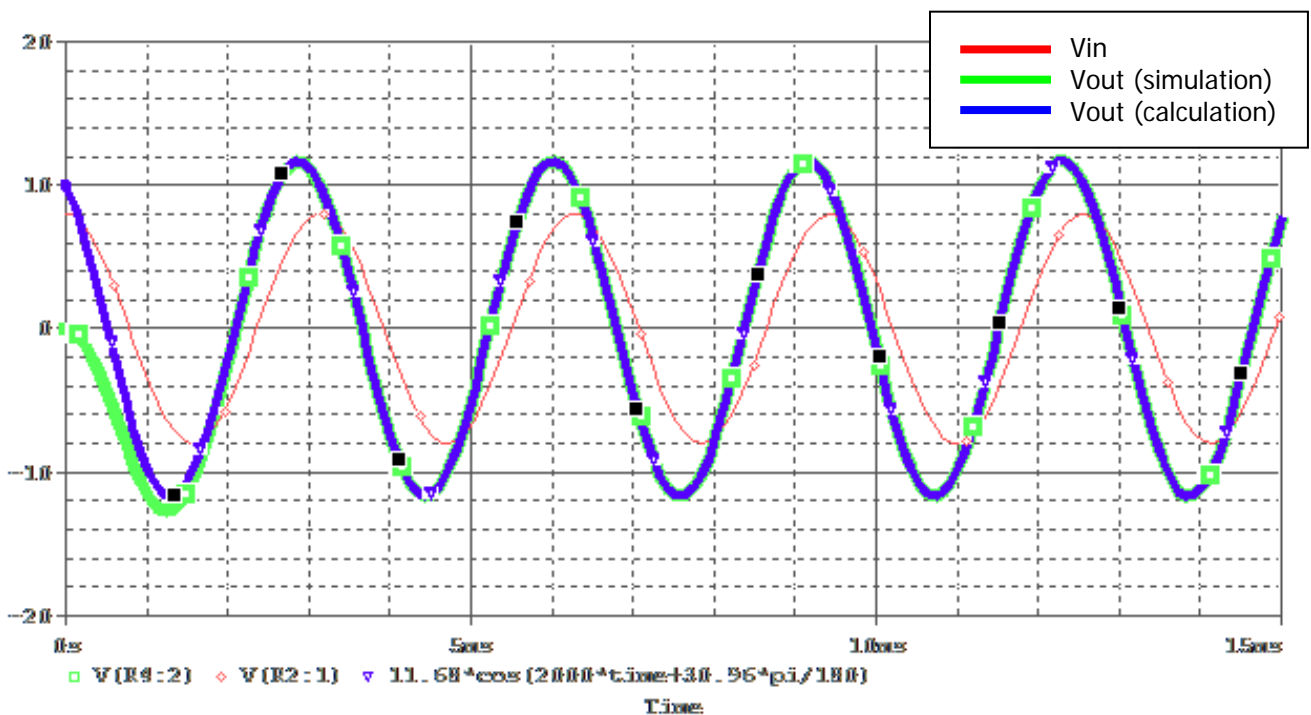Parts Schematic Nets Pins Title Blocks Globals



13.79

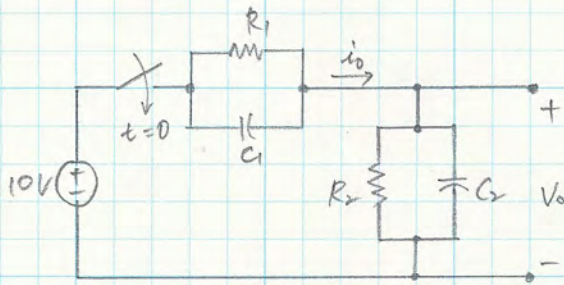

$$\begin{aligned} R_1 &= 1 \text{ M}\Omega \\ R_2 &= 4 \text{ M}\Omega \\ C_1 &= 5 \text{ pF} \\ C_2 &= 20 \text{ pF} \end{aligned}$$

no energy stored in C_1, C_2 at $t=0$.

(a)

$$\begin{aligned} \text{let } Z_1 &= R_1 \parallel C_1 \\ Z_2 &= R_2 \parallel C_2 \end{aligned}$$

$$Z_1 = \frac{R_1 / sC_1}{R_1 + 1/sC_1} = \frac{1/C_1}{s + 1/R_1 C_1} = \frac{20 \times 10^{10}}{s + 20 \times 10^4} \Omega$$

$$Z_2 = \frac{1/C_2}{s + 1/R_2 C_2} = \frac{5 \times 10^{10}}{s + 12500} \Omega$$

$$\therefore V_0 = \frac{10}{s} \frac{Z_2}{Z_1 + Z_2} = \frac{10 \cdot \frac{5 \times 10^{10}}{s + 12500}}{\left(\frac{20 \times 10^{10}}{s + 20 \times 10^4} + \frac{5 \times 10^{10}}{s + 12500} \right) s}$$

$$= \frac{50(s + 20 \times 10^4)}{[20(s + 12500) + 5(s + 20 \times 10^4)]s}$$

$$= \frac{50(s + 20 \times 10^4)}{s(25s + 125000)} = \frac{2(s + 20 \times 10^4)}{s(s + 5 \times 10^4)}$$

$$= \frac{k_1}{s} + \frac{k_2}{s + 5 \times 10^4}$$

$$k_1 = \frac{2(s + 20 \times 10^4)}{s + 5 \times 10^4} \Big|_{s=0} = \frac{40 \times 10^4}{5 \times 10^4} = 8$$

$$k_2 = \frac{2(s + 20 \times 10^4)}{s} \Big|_{s=-5 \times 10^4} = \frac{2(15 \times 10^4)}{-5 \times 10^4} = -6$$

$$\therefore V_0 = \underline{[8 - 6e^{-50000t}] \text{ u(t)} \text{ V}}$$

$$(b) \quad I_0 = \frac{V_0}{Z_2} = \frac{2(s + 20 \times 10^4)}{s(s + 5 \times 10^4)} \times \frac{s + 12500}{5 \times 10^{10}} = \frac{2}{5 \times 10^{10}} \left[\frac{s^2 + 2(12500)s + 25 \times 10^8}{s^2 + 50000s} \right]$$

$$= 4 \times 10^{-11} \left[1 + \frac{162500s + 25 \times 10^8}{s^2 + 50000s} \right]$$

$$= 4 \times 10^{-11} \left[1 + \frac{162500s + 25 \times 10^8}{s(s + 50000)} \right]$$

$$= 40 \times 10^{-12} \left(1 + \frac{k_1}{s} + \frac{k_2}{s + 50000} \right)$$

Ca 10p

$$k_1 = \frac{162500s + 25 \times 10^8}{s + 50000} \bigg|_{s=0} = \frac{25 \times 10^8}{5000} = \underline{50000}$$

$$k_2 = \frac{162500s + 25 \times 10^8}{s} \bigg|_{s=-50000} = \frac{5625 \times 10^6}{50000} = \underline{112500}$$

$$\therefore i_0 = \underline{[40 \delta(t) + 2 \times 10^6 + 4.5 \times 10^6 e^{-50000t}] \mu(t) \text{ pA}}$$

(c) Repeat (a), (b) if $C_1 = 80 \text{ pF}$.

$$Z_1 = \frac{R_1 / sC_1}{R_1 + 1/sC_1} = \frac{1/sC_1}{s + 1/R_1C_1} = \frac{125 \times 10^8}{s + 12500} \Omega$$


$$\begin{aligned} V_0 &= \frac{10}{s} \cdot \frac{Z_2}{Z_1 + Z_2} = \frac{10 \cdot \frac{5 \times 10^{10}}{s + 12500}}{\left(\frac{125 \times 10^8}{s + 12500} + \frac{5 \times 10^{10}}{s + 12500} \right) s} \\ &= \frac{50 \times 10^{10}}{s(125 \times 10^8 + 5 \times 10^6)} \\ &= \frac{8}{s} \end{aligned}$$

$$\therefore \underline{V_0 = 8 \mu(t) \text{ V}}$$

$$\begin{aligned} I_0 &= \frac{V_0}{Z_2} = \frac{8}{s} \cdot \frac{s + 12500}{5 \times 10^{10}} = 160 \times 10^{-12} \left(\frac{s + 12500}{s} \right) \\ &= 160 \times 10^{-12} \left(1 + \frac{12500}{s} \right) \end{aligned}$$

$$\begin{aligned} \therefore i_0 &= 160 \delta(t) + 160 \times 12500 \mu(t) \text{ pA} \\ &= \underline{160 \delta(t) + 2 \times 10^6 \mu(t) \text{ pA}} \end{aligned}$$

13.85

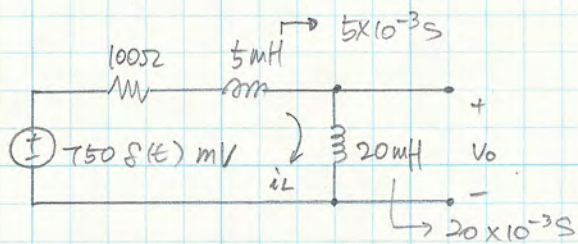

$$\begin{aligned}
 (a) \quad V_o &= \frac{20 \times 10^{-3} \text{ S}}{100 + 5 \times 10^{-3} \text{ S} + 20 \times 10^{-3} \text{ S}} \times 750 \times 10^{-3} \\
 &= \frac{15000 \times 10^{-6} \text{ S}}{100 + 25 \times 10^{-3} \text{ S}} = \frac{0.6 \text{ S}}{\text{S} + 4000} = 0.6 + \frac{-2400}{\text{S} + 4000} \\
 \therefore V_o &= 0.6 \delta(t) - 2400 e^{-4000t} \text{ u}(t) \text{ V.}
 \end{aligned}$$

$$V = L \frac{di}{dt}$$

(b) At $t=0$, the impulsive voltage establishes a current in the inductors.

$$\begin{aligned}
 i_L(0) &= \frac{1}{(5+20) \times 10^{-3}} \int_{0^-}^{0^+} 0.75 \delta(t) dt \quad (\leftarrow \text{from } V_L = L \frac{di}{dt}) \\
 &= 400 \times 0.75 = 30 \text{ A.}
 \end{aligned}$$

$$\rightarrow \frac{di_L(0)}{dt} = 30 \delta(t)$$

$$\therefore V_o(0) = (20 \times 10^{-3}) (30 \delta(t)) = 0.6 \delta(t) \text{ V}$$

This agrees with the solution to (b). //

At $t=0^+$

$$\frac{V}{R+SL} = V \frac{1}{\text{S} + R/L} \Rightarrow V \cdot e^{-R/L t}$$

For RL circuit,

$$i_L(t) = i_L(0) \cdot e^{-(R/L)t} \quad \left(\leftarrow \frac{V}{R+SL} = \frac{V/L}{\text{S} + R/L} \rightarrow \frac{V}{L} e^{-(R/L)t} \right)$$

$$R = 100 \Omega, \quad L = (20+5) \times 10^{-3} \text{ H.}$$

$$\therefore R/L = 4000$$


$$\rightarrow i_L(t) = 30 \cdot e^{-4000t} \text{ A.} \quad (t \geq 0^+)$$

$$\frac{di_L(t)}{dt} = -120000 e^{-4000t}$$

$$\begin{aligned}
 \therefore V_o(t) &= (20 \times 10^{-3}) (-120000 e^{-4000t}) \\
 &= -2400 e^{-4000t} \text{ V.}
 \end{aligned}$$

This agrees with the solution to (b). //

14.5

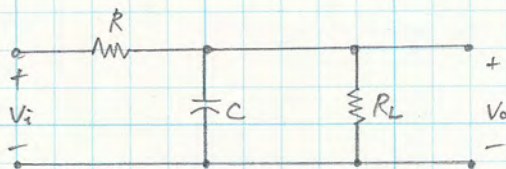

(a)

$$V_o = \frac{V_{SC} \parallel R_L}{R + V_{SC} \parallel R_L} V_i$$

$$V_{SC} \parallel R_L = \frac{\frac{R_L}{sC}}{\frac{1}{sC} + R_L} = \frac{R_L}{1 + sR_L C}$$

$$\frac{V_o}{V_i} = \frac{\frac{R_L}{1 + sR_L C}}{R + \frac{R_L}{1 + sR_L C}} = \frac{R_L}{R_L + R + sR_L C}$$

$$= \frac{V_{RC}}{s + V_{RC} + V_{RLC}}$$

(b)

$$|H(j\omega)| = \frac{V_{RC}}{\sqrt{\omega^2 + (V_{RC} + V_{RLC})^2}}$$

(c)

at $\omega = 0 \rightarrow |H(j\omega)|$ is maximum.

$$\therefore |H(j\omega)|_{\max} = \frac{V_{RC}}{V_{RC} + V_{RLC}} = \frac{R_L}{R_L + R}$$

(d)

at $\omega = \omega_c \rightarrow |H(j\omega_c)| = |H(j\omega)|_{\max} / \sqrt{2}$


$$\frac{V_{RC}}{\sqrt{\omega_c^2 + (V_{RC} + V_{RLC})^2}} = \frac{V_{RC}}{V_{RC} + V_{RLC}} \cdot \frac{1}{\sqrt{2}}$$

$$\therefore \omega_c^2 + (V_{RC} + V_{RLC})^2 = (V_{RC} + V_{RLC})^2 \cdot 2$$

$$\omega_c^2 = \left(\frac{1}{RC} + \frac{1}{R_L C} \right)^2 = \left(\frac{R + R_L}{R R_L C} \right)^2 = \left(\frac{1}{RC} \left(1 + \frac{R}{R_L} \right) \right)^2$$

$$\therefore \omega_c = \frac{1}{RC} \left(1 + \frac{R}{R_L} \right)$$

(e)

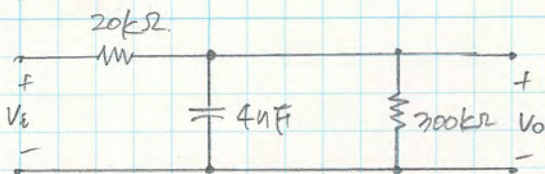

$$\omega_c = \frac{1}{RC} \left(1 + \frac{R}{R_L} \right) = \frac{1}{2500} \left(1 + \frac{20}{200} \right) = 13.333 \text{ krad/s}$$

$$H(j0) = \frac{200}{20 + 200} = 0.9375$$

ce
hp

$$H(j\omega_c) = \frac{1/R_C}{s + \frac{R+R_L}{R R_L C}} \bigg|_{s=j\omega_c = j13333.33}$$

$$= \frac{1.25 \times 10^4}{j13333.333 + 13333.333}$$

$$= \frac{1.25 \times 10^4}{1.8856 \angle 45^\circ} = \underline{0.6629 \angle -45^\circ}$$

$$H(j0.2\omega_c) = \frac{1.25 \times 10^4}{j0.2 \times 13333.333 + 13333.333}$$

$$= \frac{1.25 \times 10^4}{13.579 \times 10^4 \angle 11.31^\circ} = \underline{0.9193 \angle -11.31^\circ}$$


$$H(j0.8\omega_c) = \frac{1.25 \times 10^4}{j0.8 \times 13333.333 + 13333.333}$$

$$= \frac{1.25 \times 10^4}{10.750 \times 10^4 \angle 82.875^\circ} = \underline{0.1163 \angle -82.875^\circ}$$

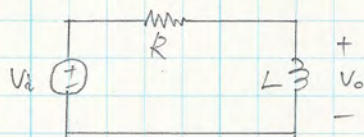14.13

Design a high-pass, RL passive filter.


Cutoff frequency = 160 krad/s. $L = 25 \text{ mH}$



$$H(s) = \frac{sL}{R + sL} = \frac{s}{s + R/L}$$

(a) $\omega_c = R/L \quad \therefore R = \omega_c L = 160 \times 10^3 \times 25 \times 10^{-3} = 4000 = \underline{4 \text{ k}\Omega}$

(b) with R_L

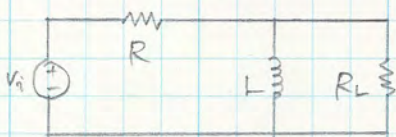

$$H(s) = \frac{sL \parallel R}{R + sL \parallel R} = \frac{\frac{sLR}{sL + R}}{R + \frac{sLR}{sL + R}}$$

$$= \frac{sLR}{sLR + RR_L + sLRL} = \frac{sLR}{s(LR + LRL) + RR_L}$$

$$\therefore \frac{RR_L}{LR + LRL} = 150 \times 10^3$$

$$RR_L = 150 \times 10^3 (LR + LRL)$$

$$R_L (R - 150 \times 10^3 L) = 150 \times 10^3 LR$$

$$\therefore R_L = \frac{150 \times 10^3 \times 100}{2500}$$

$$= \underline{60 \text{ k}\Omega}$$