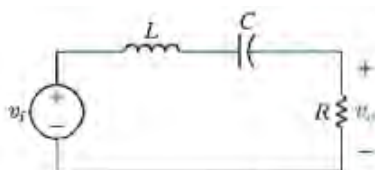


- 14.18** Calculate the center frequency, the bandwidth, and the quality factor of a bandpass filter that has an upper cutoff frequency of 200 krad/s and a lower cutoff frequency of 180 krad/s.

- 14.25** Design a series  $RLC$  bandpass filter (see Fig. 14.19[a]) with a quality of 5 and a center frequency of 20 krad/s, using a  $0.05 \mu\text{F}$  capacitor.

- Draw your circuit, labeling the component values and output voltage.
- For the filter in part (a), calculate the bandwidth and the values of the two cutoff frequencies.



- Plot the asymptotic Bode plot for this filter and compare to computer calculation.


- 14.40** The parameters in the circuit in Fig. P14.39 are  $R = 5 \text{ k}\Omega$ ,  $L = 400 \text{ mH}$ ,  $C = 250 \text{ pF}$ , and  $R_L = 20 \text{ k}\Omega$ .

- Find  $\omega_o$ ,  $\beta$  (in kilohertz), and  $Q$ .
- Find  $H(j0)$  and  $H(j\infty)$ .
- Find  $f_{c2}$  and  $f_{c1}$ .
- Show that if  $R_L$  is expressed in kilohms the  $Q$  of the circuit is

$$Q = 8[1 + (5/R_L)].$$

- Plot  $Q$  versus  $R_L$  for  $2 \text{ k}\Omega \leq R_L \leq 50 \text{ k}\Omega$ .

Figure P14.39

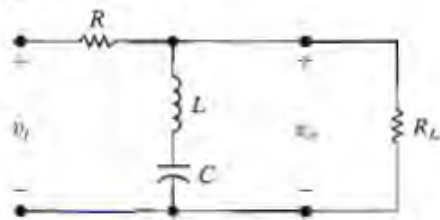


- 15.5** Design an op amp-based low pass filter with a cut-off frequency of 500 Hz and a passband gain of 10 using a  $50 \text{ nF}$  capacitor.

- Draw your circuit, labeling the component values and output voltage.
- If the value of the feedback resistor in the filter is changed but the value of the resistor in the forward path is unchanged, what characteristic of the filter is changed?

- 15.13**
- Specify the component values for the prototype passive bandpass filter described in Problem 15.12 if the quality factor of the filter is 25.
  - Specify the component values for the bandpass filter described in Problem 15.12 if the quality factor is 25; the center, or resonant, frequency is 100 krad/s; and the impedance at resonance is  $3.6 \text{ k}\Omega$ .
  - Draw a circuit diagram of the scaled filter and label all the components.

Figure P15.12

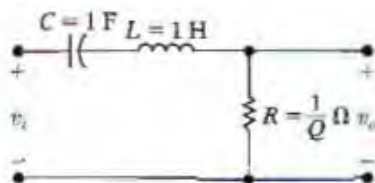

- 15.27**
- Using  $5 \text{ nF}$  capacitors, design an active broadband first-order bandreject filter with a lower cutoff frequency of 1000 Hz, an upper cutoff frequency of 5000 Hz, and a passband gain of 10 dB. Use the prototype filter circuits introduced in Problems 15.24 and 15.25 in the design process.

- Draw the circuit diagram of the filter and label all the components.
- What is the transfer function of the scaled filter?
- Evaluate the transfer function derived in (c) at the center frequency of the filter.
- What is the gain (in decibels) at the center frequency?
- Using a computer program of your choice, make a Bode magnitude plot of the filter transfer function.

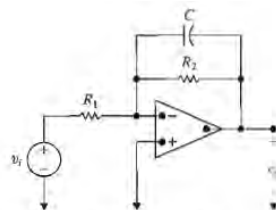


Figure 15.1 A first-order low-pass filter.

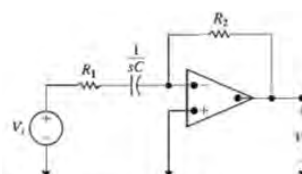


Figure 15.4 A first-order high-pass filter.

14.18

$$\omega_0 = \sqrt{\omega_{c1} \cdot \omega_{c2}} = \sqrt{180 \cdot 200} = 189.74 \text{ krad/s.}$$


$$\therefore f_0 = \omega_0 / 2\pi = \underline{\underline{30.2 \text{ kHz}}}$$

$$\beta = \omega_{c2} - \omega_{c1} = 200 - 180 = \underline{\underline{20 \text{ krad/s}}}$$

$$Q = \frac{\omega_0}{\beta} = \frac{189.74}{20} = \underline{\underline{9.49}}$$

14.25

RLC BPF.

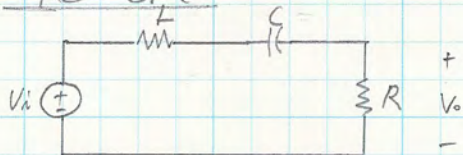

$$Q = 5$$

$$\omega_0 = 20 \text{ krad/s}$$

$$C = 0.05 \mu\text{F}$$

$$(a) \quad \omega_0 = 1/\sqrt{LC} \rightarrow L = 1/\omega_0^2 C = \underline{\underline{50 \text{ mH}}}$$

$$Q = \frac{\omega_0}{\beta} = 5 \quad \& \quad \beta = \frac{R}{L} \rightarrow Q = \omega_0 \cdot \frac{L}{R} = 5$$

$$\therefore R = \frac{\omega_0 L}{5} = \underline{\underline{200 \Omega}} \quad (\beta = 4000)$$


$$(b) \quad \omega_{c1,2} = \pm \frac{\beta}{2} + \sqrt{\left(\frac{\beta}{2}\right)^2 + \omega_0^2} = \pm \frac{4000}{2} + \sqrt{\left(\frac{4000}{2}\right)^2 + (20000)^2}$$

$$= \pm 2000 + 20099.75$$


$$\left\{ \begin{array}{l} \omega_{c1} = 18099.75 \text{ rad/s} \\ \omega_{c2} = 22099.75 \text{ rad/s} \end{array} \right\}$$

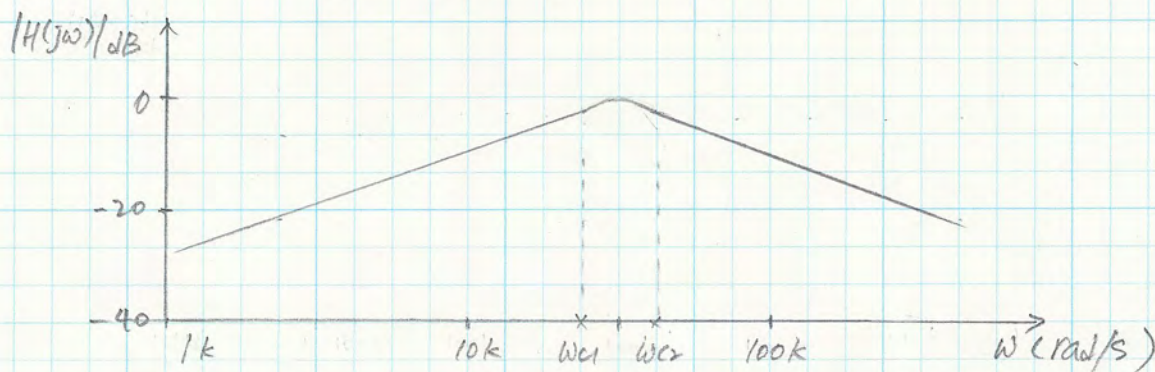(c) Asymptotic bode plot

$$H(s) = \frac{R}{sL + 1/sC + R} = \frac{sRC}{s^2 LC + sRC + 1} = \frac{s(R/L)}{s^2 + s(R/L) + 1/LC}$$




Bode Diagram

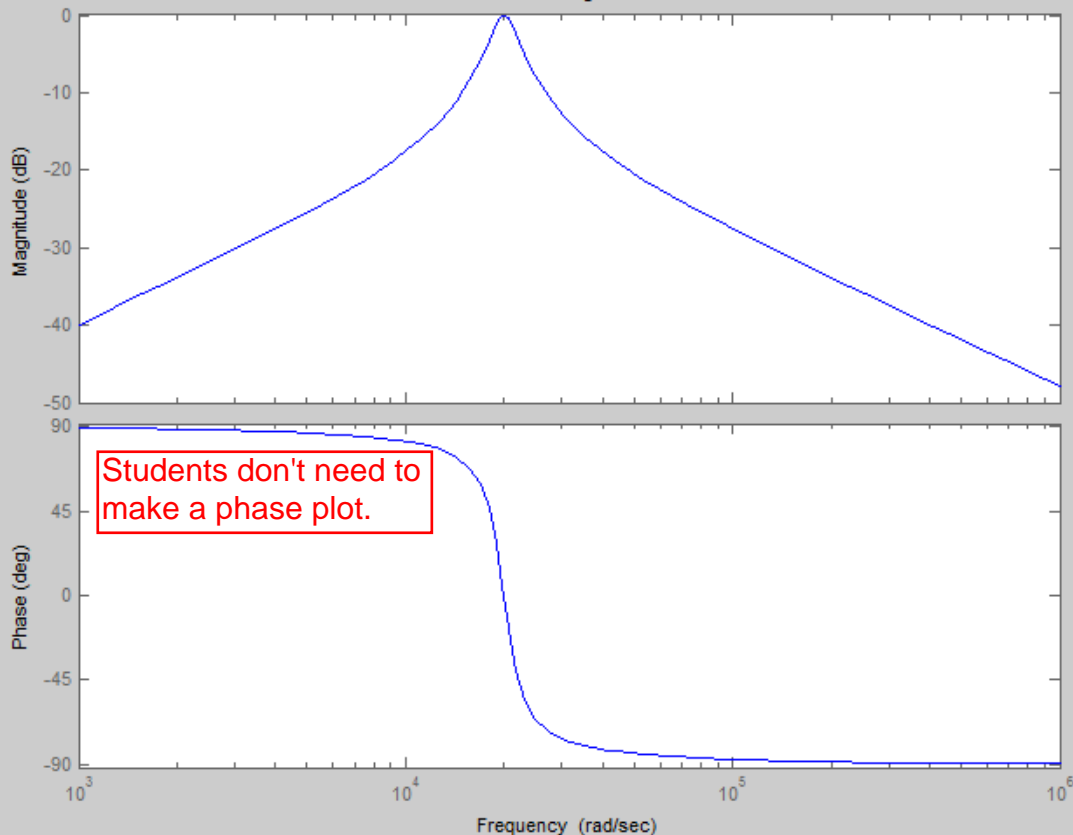



14.39

14.40

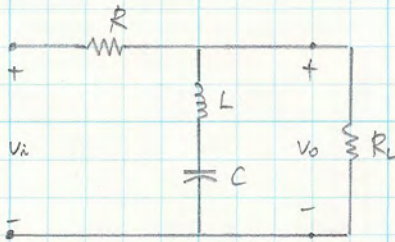

$$\begin{aligned}
 R &= 5 \text{ k}\Omega \\
 L &= 400 \text{ mH} \\
 C &= 250 \text{ pF} \\
 R_L &= 20 \text{ k}\Omega
 \end{aligned}$$

(a) let  $Z = (sL + 1/sC) \parallel R_L$

$$= \frac{R_L(sL + 1/sC)}{sL + 1/sC + R_L} = \frac{R_L(s^2LC + 1)}{s^2LC + sR_LC + 1}$$

$$\therefore H(s) = \frac{Z}{R + Z}$$

$$= \frac{\frac{R_L(s^2LC + 1)}{s^2LC + sR_LC + 1}}{R + \frac{R_L(s^2LC + 1)}{s^2LC + sR_LC + 1}} = \frac{R_L(s^2LC + 1)}{s^2RLC + sRR_LC + R + s^2R_LLC + R_L}$$

$$= \frac{R_L(s^2LC + 1)}{s^2LC(R + R_L) + sRR_LC + (R + R_L)}$$

$$= \frac{R_L(s^2LC + 1)}{LC(R + R_L)} \cdot \frac{1}{s^2 + s \underbrace{\frac{RR_L}{(R + R_L) \cdot L}}_{\beta} + \underbrace{\frac{1}{LC}}_{\omega_0^2}}$$

$$= \frac{R_L}{R + R_L} \cdot \frac{(s^2 + \underbrace{1/LC}_{\omega_0^2})}{s^2 + s\beta + \omega_0^2}$$

$$\rightarrow \omega_0^2 = 1/LC \rightarrow \omega_0 = \sqrt{1/LC} = 100 \text{ rad/s} = \underline{15.915 \text{ kHz}}$$

$$\beta = \frac{RR_L}{(R + R_L) \cdot L} = 10^4 \text{ rad/s} = \underline{1.591 \text{ kHz}}$$

$$Q = \frac{\omega_0}{\beta} = \underline{10}$$

(b)  $H(j\omega) = \frac{R_L}{R + R_L} \cdot \frac{\omega_0^2}{0 + 0 + \omega_0^2} = \frac{R_L}{R + R_L} = \frac{20}{5 + 20} = \underline{0.8}$

$$H(j\infty) = \frac{R_L}{R + R_L} \cdot \frac{s^2}{s^2} \Big|_{s=j\omega} = \frac{R_L}{R + R_L} = \underline{0.8}$$



(c) Denominator,  $D(s) = s^2 + \beta s + \omega_0^2$

$$\omega_{c1,2} = \pm \frac{\beta}{2} + \sqrt{\left(\frac{\beta}{2}\right)^2 + \omega_0^2}$$

$$\beta = 10^4 = 10 \text{ krad/s}$$

$$\omega_0 = 100 \text{ krad/s}$$

$$= \pm \frac{10}{2} + \sqrt{\left(\frac{10}{2}\right)^2 + (100)^2}$$

$$= \pm 5 + 100.1249 \text{ krad/s.}$$

$$\omega_{c1} = 95.1249 \text{ krad/s} = \underline{15.14 \text{ kHz}}$$

$$\omega_{c2} = 105.1249 \text{ krad/s} = \underline{16.73 \text{ kHz}}$$

(x-check)

$$\beta = \omega_{c2} - \omega_{c1} = 1.591 \text{ kHz}$$


$$(d) Q = \frac{\omega_0}{\beta} = \frac{10^5}{\frac{R R_L}{(R_L + R) \cdot L}} = \frac{10^5 \cdot L \cdot (R_L + R)}{R R_L} = 10^5 \cdot L \cdot \left( \frac{1}{R} + \frac{1}{R_L} \right)$$

$$= 0.4 \times 10^5 \left( \frac{1}{5000} + \frac{1}{R_L} \right) = 0.4 \times 10^5 \times \frac{1}{5000} \left( 1 + \frac{5000}{R_L} \right)$$

$$= 8 \left( 1 + \frac{5000}{R_L} \right) \quad ; R_L \text{ in } \Omega$$

$$= \underline{8 \left( 1 + \frac{5}{R_L} \right)} \quad ; R_L \text{ in k}\Omega$$

(e)

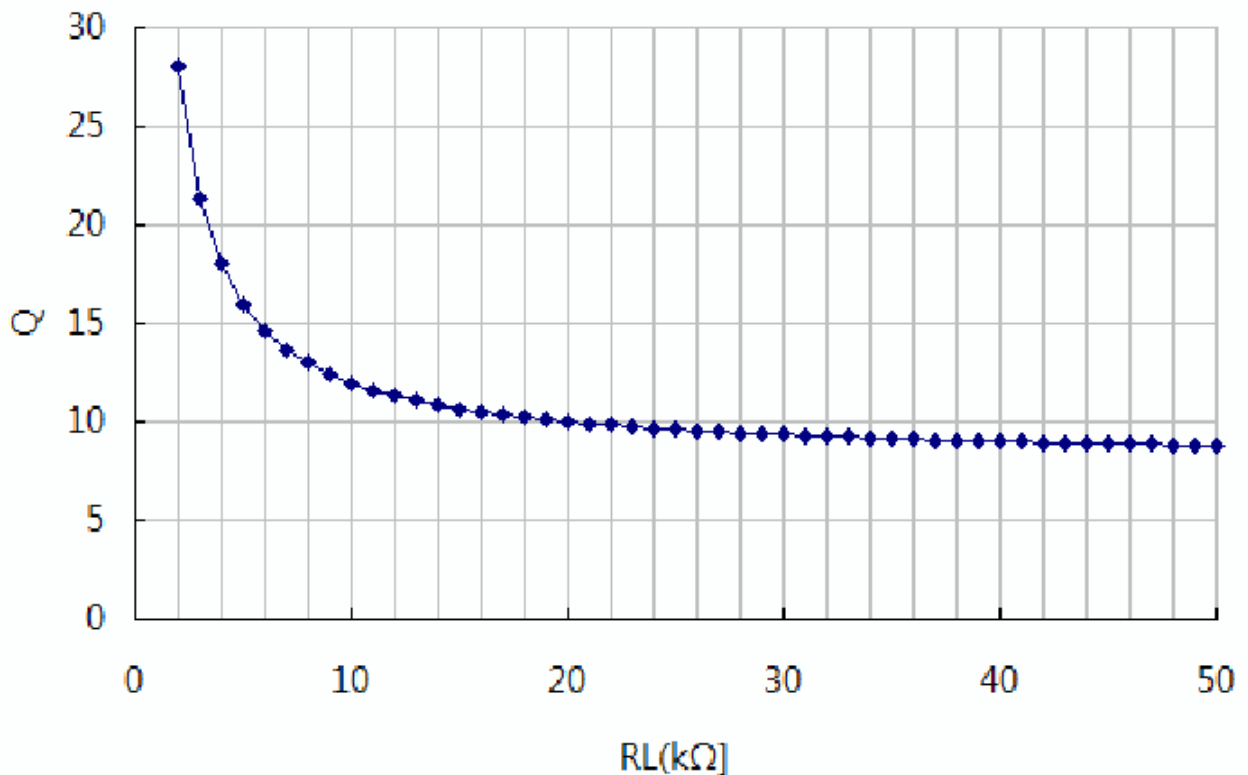




14.40

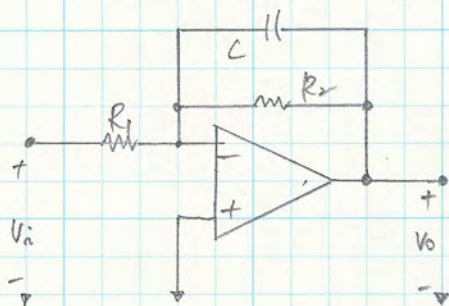15.5

op-amp - based LPF

$$f_c = 500 \text{ Hz} \quad \text{gain} = 10 \quad C = 50 \text{ nF}$$




$$(a) \quad \omega_c = 1/R_2 C \quad \therefore R_2 = \frac{1}{\omega_c C} = \frac{1}{(2\pi \cdot 500)(50 \times 10^{-9})} = \underline{6366.2 \Omega}$$

gain. k

$$k = \frac{R_2}{R_1} = 10 \quad \therefore R_1 = \underline{636.6 \Omega}$$

(b) ( Gain is changed,  
Cutoff frequency is changed )

15.13.

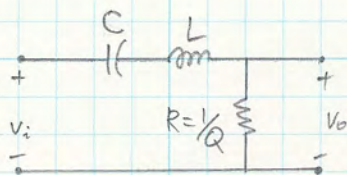

$$Q = 25$$

$$(a) \quad \underline{C = 1 \text{ F}} \quad \underline{L = 1 \text{ H}} \quad , \quad Q = 25 \Rightarrow \underline{R = 1/Q = 0.04 \Omega}$$

$$(b) \quad H(s) = \frac{R}{1/sC + sL + R} = \frac{sRC}{s^2 LC + sRC + 1} = \frac{s(R/L)}{s^2 + s(R/L) + (1/LC)}$$

$$= \frac{\beta s}{s^2 + \beta s + \omega_0^2}$$

$$(1) \quad Q = 25 \rightarrow \frac{\omega_0}{\beta} = 25 \quad \omega_0 = 1/\sqrt{LC} \quad , \quad \beta = R/L$$

$$\beta = \frac{\omega_0}{25} = \frac{100 \times 10^3}{25} = 4 \times 10^3 = \frac{R}{L}$$

$$\text{from } \underline{R = 3.6 \text{ k}\Omega} \rightarrow \underline{L = \frac{R}{4 \times 10^3} = 0.9 \text{ H}}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} \rightarrow \underline{C = \frac{1}{L \omega_0^2} = 0.111 \text{ nF}}$$

$$(c) \quad \begin{aligned} C &= 0.111 \text{ nF} \\ L &= 0.9 \text{ H} \\ R &= 3.6 \text{ k}\Omega \end{aligned}$$



15.27

5

First-order bandreject filter.

$$f_{c1} = 1000 \text{ Hz}, \quad f_{c2} = 5000 \text{ Hz}$$

$$g_{aru} = 10 \text{ dB}$$

x. Bandreject filter

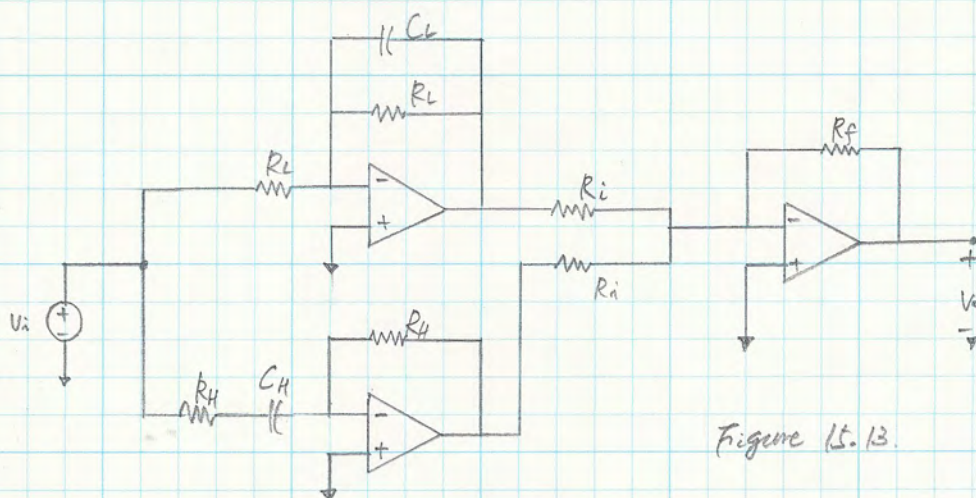
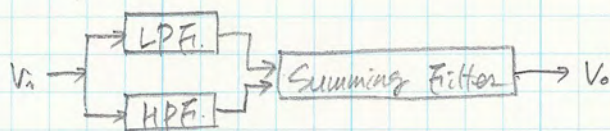


Figure 15.13.

$$(a) \quad \omega_{c1} = \frac{1}{R_L C_L} \quad C = 5 \text{ nF}. \quad \therefore R_L = \frac{1}{\omega_{c1} C_L} = \frac{1}{2\pi(1000)(5 \times 10^{-9})} = \underline{31.83 \text{ k}\Omega}$$

$$\omega_{c2} = \frac{1}{R_H C_H} \quad \therefore R_H = \frac{1}{\omega_{c2} C_H} = \frac{1}{2\pi(5000)(5 \times 10^{-9})} = \underline{6.37 \text{ k}\Omega}$$

$$\text{gain } 20 \log_{10} \left( \frac{R_F}{R_i} \right) = 10. \quad \therefore R_F = \sqrt{10} R_i$$

$$\text{choose } R_i = 31.83 \text{ k}\Omega \quad (\leftarrow \text{Any value for } R_i \text{ is ok})$$

$$\rightarrow R_F = \underline{100.66 \text{ k}\Omega}$$

(b) The circuit diagram is shown above.

$$\begin{aligned} R_L &= 31.83 \text{ k}\Omega & C_L &= 5 \text{ nF} \\ R_H &= 6.37 \text{ k}\Omega & C_H &= 5 \text{ nF} \\ R_i &= 31.83 \text{ k}\Omega \\ R_F &= 100.66 \text{ k}\Omega \end{aligned}$$



(c) i) LPF

$$H_L(s) = -\frac{Z_L}{R_L} \quad \left( Z_L = R_L \parallel \frac{1}{sC} = \frac{R_L/sC}{R_L + 1/sC} = \frac{R_L}{1+sR_LC} \right)$$

$$= -\frac{1}{R_L} \left( \frac{R_L}{1+sR_LC} \right)$$

$$= -\frac{1}{1+sR_LC} = \frac{-\omega_{c1}}{s + \omega_{c1}} \quad (\omega_{c1} = \frac{1}{R_L C_L})$$

HPF

$$H_H(s) = -\frac{R_H}{Z_H} \quad \left( Z_H = \frac{1}{sC_H} + R_H \right)$$

$$= -\frac{R_H}{\frac{1}{sC_H} + R_H} = -\frac{sR_H C_H}{1+sR_H C_H} = \frac{s}{s + \omega_{c2}}$$

Summing filter

$$H_s(s) = -\frac{R_f}{R_i} = -\sqrt{10}$$

$$\therefore H(s) = (H_L(s) + H_H(s)) \cdot H_s(s)$$

$$= \left( \frac{2000\pi}{s+2000\pi} + \frac{s}{s+10000\pi} \right) \cdot \sqrt{10}$$

$$= \sqrt{10} \left( \frac{s^2 + 4000\pi s + 20 \times 10^6 \pi^2}{(s+2000\pi)(s+10000\pi)} \right)$$

(d)  $\omega_0 = \sqrt{\omega_{c1} \omega_{c2}} = \sqrt{(2000\pi)(10000\pi)} = 2000\pi\sqrt{5} \text{ rad/s.}$

$$H(j\omega_0) = \sqrt{10} \frac{-4 \times 10^6 \pi^2 \times 5 + 4000\pi(j2000\pi\sqrt{5}) + 20 \times 10^6 \pi^2}{(2000\pi + j2000\pi\sqrt{5})(10000\pi + 2000\pi\sqrt{5})}$$

$$= \sqrt{10} \frac{(2000\pi)^2 \times 2 \times j\sqrt{5}}{2000\pi(1+j\sqrt{5}) \times 2000\pi(5+j\sqrt{5})}$$

$$= \frac{\sqrt{10} \times 2 \times j\sqrt{5}}{(1+j\sqrt{5})(5+j\sqrt{5})} = \frac{j2\sqrt{5}\sqrt{10}}{5+j6\sqrt{5}-5}$$

$$= \frac{2\sqrt{10}}{6} = \underline{\underline{1.054}}$$



(e) from (d) gain = 1.05

$$\therefore 20 \log_{10} 1.05 = \underline{\underline{0.46 \text{ dB}}}$$

(f) Bode plot

