


Ideal Op-amp

($A \rightarrow \infty, i_p, i_n \approx 0$)

If $V^- < V^+ < V^+$,

then $V_p \approx V_n$

Assume true, then check.

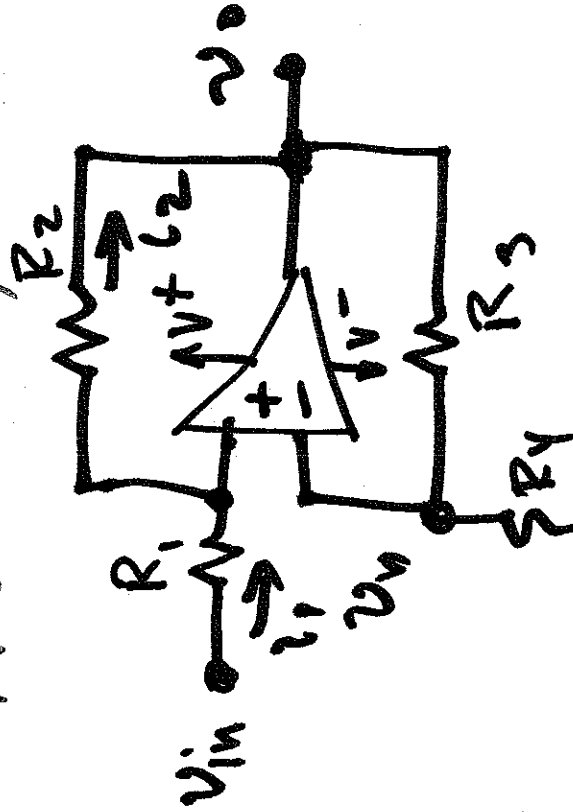

$$v_{in} = v_p + i_1 R_1$$

$$= \frac{R_4 v_o}{R_3 + R_4} - \frac{R_1 R_3 v_o}{R_2 (R_3 + R_4)}$$

Slope = A

$$v_n = \frac{R_4}{R_3 + R_4} v_o = v_p$$

$$i_1 = i_2 = \frac{v_p - v_o}{R_1}$$

$$= \frac{R_4 v_o / (R_3 + R_4) - v_o}{R_1}$$

$$i_1 = i_2 = \frac{-R_3}{R_2 (R_3 + R_4)} v_o$$

$$v_{in} = \frac{R_2 R_4 - R_1 R_3}{R_2 (R_3 + R_4)} \cdot v_{out}$$

$$v_{out} = \left[\frac{R_2 (R_3 + R_4)}{R_2 R_4 - R_1 R_3} \right] v_{in}$$

$$R_2 = 2\Omega, R_3 = 3\Omega$$

$$R_4 = 4, R_1 = 1$$


$$v_{out} = \left[\frac{2(3+4)}{8-3} \right] v_{in} = \frac{14}{5} v_{in}$$

$$V^+ = 7V$$

$$V_{in} = 5V$$

max(v_{in}) 2.5V
w/o sat

$$A_{v1} = 14V$$

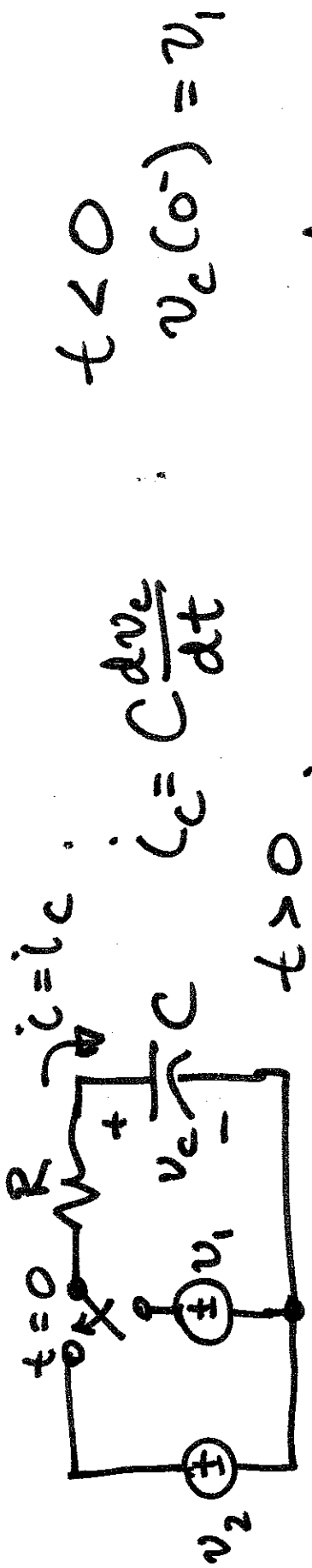

$t < 0$
 $v_c(0^-) = v_1$

$i_c = C \frac{dv_c}{dt}$

$i = \frac{v_2 - v_c}{R} = C \frac{dv_c}{dt}$

dependent on v_c

$C \frac{dv_c}{dt} + \frac{v_c}{R} = \frac{v_2}{R}$

General Sol'n to linear DE

- 1) Gen'l Sol'n to homogeneous eqn.
- 2) Specific solution to full eqn.

$C \frac{dv_c}{dt} + \frac{v_c}{R} = 0$

Characteristic eqn. $Cs + \frac{1}{R} = 0 \Rightarrow s = -\frac{1}{RC}$

$v_c^{GH} = A e^{-t/RC}$

Specific sol'n to full: $v_c^{ss} = \text{cst} \text{ constant} = B$

$C(0) + \frac{B}{R} = \frac{v_2}{R}$

$\Rightarrow B = v_2$

$$v_c(t) = A e^{-t/RC} + v_2$$


$$v_c^{GH} + v_c^{SS}$$

$$v_c(0^+) = v_c(0^-) = v_1 = v_2 + A e^{-0/RC}$$

$$A = v_1 - v_2$$

$$v_c(t) = v_2 + (v_1 - v_2) e^{-t/RC}$$

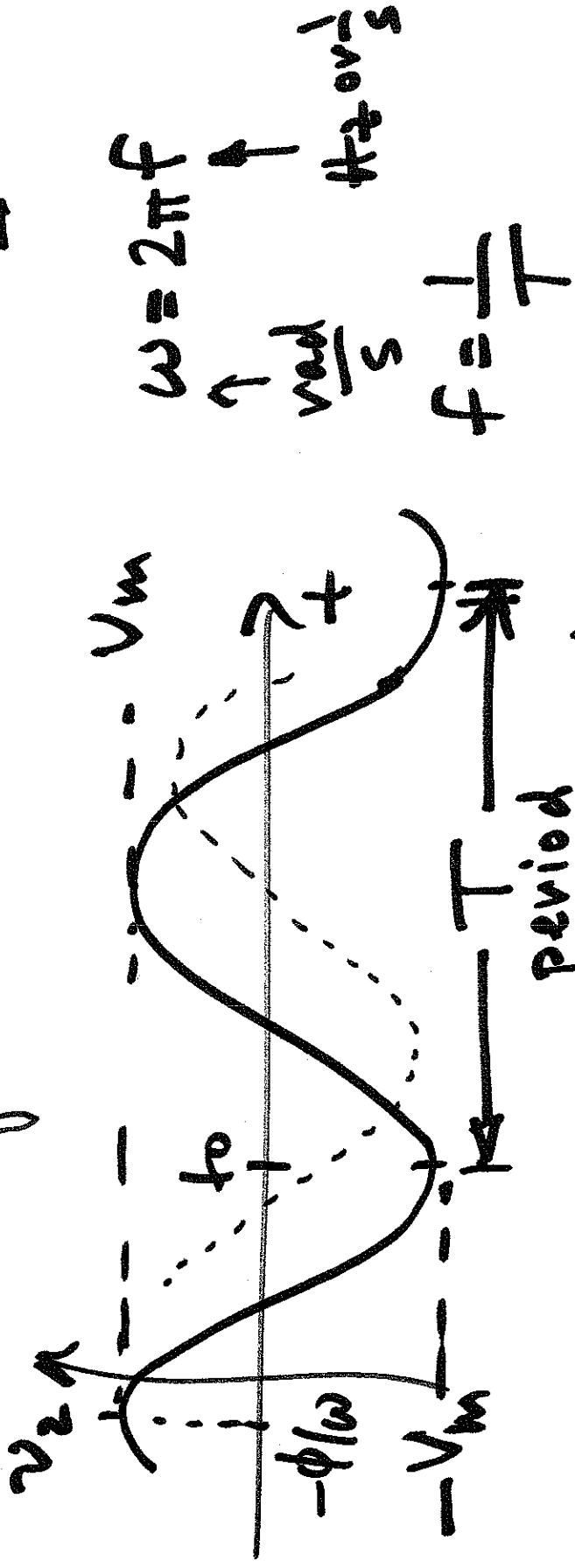Now ... what if $v_2 = v_2(t) = V_m \cos(\omega t + \phi)$



$\phi > 0$ shifts to left $\phi = \text{phase angle}$

ϕ in radians ($0 \rightarrow 2\pi$)

or degrees ($0 \rightarrow 360^\circ$)

$$V_{\text{rms}} = \sqrt{\frac{1}{T} \int_{t_0}^{t_0+T} V_m^2 \cos^2(\omega t + \phi) dt}$$

$$v_c^{GH} = A e^{-t/RC}$$

Specific Solution:

$$B \cos(\omega t + \delta)$$

$$F \cos(\omega t) + G \sin(\omega t)$$

$$\text{Page 817: } \cos(\alpha \pm \beta) = \cos \alpha \cos \beta \mp \sin \alpha \sin \beta$$

$$F = B \cos \phi$$

redefine $t = t' - \phi/\omega$

$$v_2 = V_m \cos(\omega t')$$

$$C \frac{dv_c}{dt'} + \frac{v_c}{R} = \frac{V_m}{R} \cos(\omega t')$$

$$v_c^{ss} = F \cos(\omega t') + G \sin(\omega t')$$

$$C \left[-\underline{F \omega} \sin(\omega t') + \underline{G \omega \cos(\omega t')} \right] + \frac{1}{R} \left[\underline{F \cos(\omega t')} + \underline{G \sin(\omega t')} \right] = \frac{V_m}{R} \underline{\underline{\cos(\omega t')}}$$

$$\sin: -C\omega + \frac{G}{R} = 0 \Rightarrow G = C\omega R$$

$$\cos: C\omega + \frac{F}{R} = \frac{V_m}{R} \Rightarrow C^2\omega^2 + \frac{F}{R} = \frac{V_m}{R}$$

$$F = \frac{V_m}{R^2C^2\omega^2 + 1}; G = \frac{\omega RC V_m}{\omega^2 R^2 C^2 + 1}$$

$$v_c^{ss} = \frac{V_m}{1 + (\omega RC)^2} \left[\cos(\omega t') + \omega RC \sin(\omega t') \right]$$

(note) $\rightarrow$

$$= B \cos(\omega t' + \delta)$$

$$\tan \delta = \omega RC$$

$$\delta = \arctan(\omega RC)$$

$$\tan^{-1}(\omega RC)$$

$$B = \frac{V_m}{1 + (\omega RC)^2} \left[1 + (\omega RC)^2 \right]^{1/2}$$

$$(B \cos \delta)^2 + (B \sin \delta)^2 = B^2$$

Whew! That was hard!!

Step I skipped:

$$\begin{aligned} B \cos(\omega t' + \delta) &= B \left[\cos(\omega t') \cos(\delta) - \sin(\omega t') \sin(\delta) \right] \\ &= \frac{V_m}{1 + (\omega RC)^2} \left[\cos(\omega t') + \omega RC \sin(\omega t') \right] \end{aligned}$$

$$B \cos \delta = \frac{V_m}{1 + (\omega RC)^2}; \quad B \sin \delta = \frac{-\omega RC V_m}{1 + (\omega RC)^2}$$

$$\frac{B \sin \delta}{B \cos \delta} = \tan \delta = -\omega RC \rightarrow \delta = \tan^{-1}(-\omega RC)$$

$$\begin{aligned} (B \cos \delta)^2 + (B \sin \delta)^2 &= \left[\frac{V_m}{1 + (\omega RC)^2} \right]^2 (1 + (\omega RC)^2) \\ B^2 (\cos^2 \delta + \sin^2 \delta) &= \frac{V_m^2}{[1 + (\omega RC)^2]} \Rightarrow B = \frac{V_m}{[1 + (\omega RC)^2]^{1/2}} \end{aligned}$$