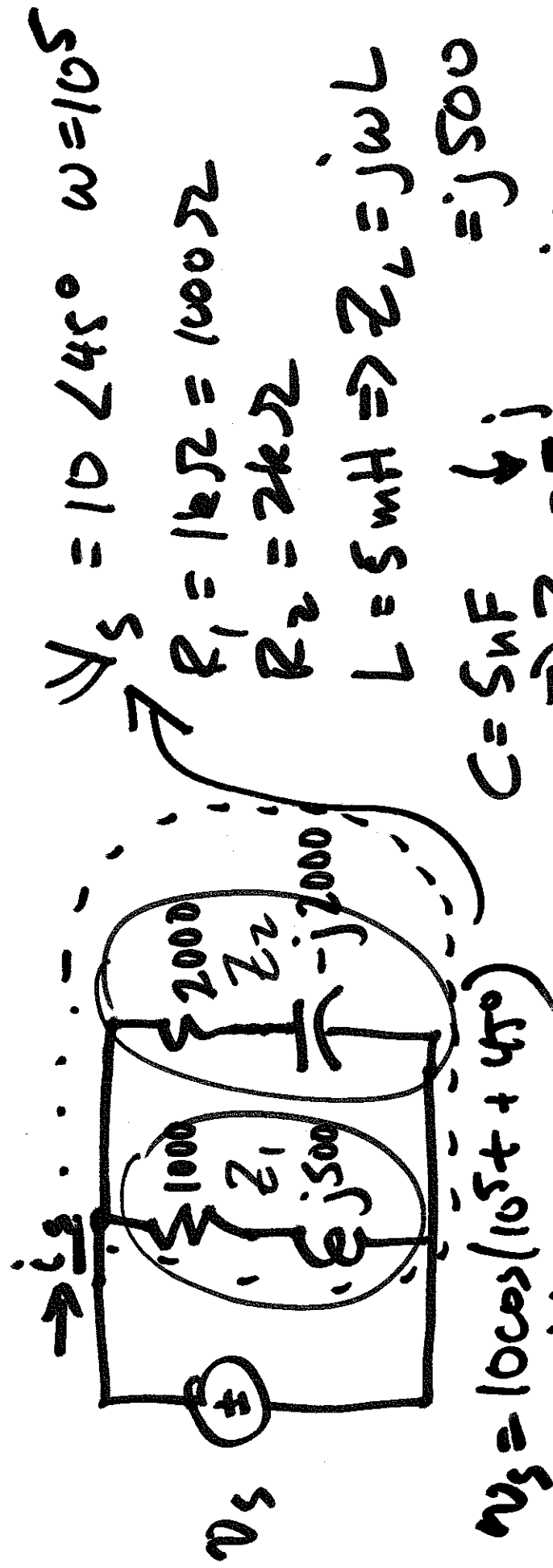




$$C = 5 \mu F \rightarrow j = j500$$

$$\Rightarrow Z_C = \frac{-j}{\omega C} = -j2000$$

$$(10^5)(5 \times 10^{-6}) = 5 \times 10^{-1}$$

$$I_s = \frac{v_s}{Z_{total}}$$

$$Z_{total} = \frac{Z_1 Z_2}{Z_1 + Z_2}$$

$$Z_1 = 1000 + j500$$

$$Z_2 = 2000 - j2000$$

$$= \frac{(1000 + j500)(2000 - j2000)}{3000 - j1500}$$


Z_{total}

$$= \frac{(1000)(1000)}{1000}$$

$$[1000 + j500] (2000 - j2000)$$

$$= 1000 \left[\frac{(1 + j0.5)(2 - j2)}{3 - j1.5} \right]$$
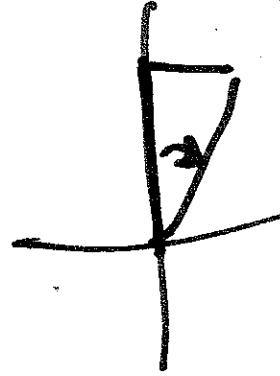
$$= 1000 \left[\frac{2 + j - j2 + 1}{3 - j1.5} \right] = 1000 \frac{3 - j}{3 - 1.5j}$$



$$e^{j\theta} = e^{j(\theta + \phi)}$$

$$= 1000 \frac{3.16 \angle -18.4^\circ}{3.35 \angle -26.6^\circ} \leftarrow \text{negative}$$

$$Z_{total} = 943 \angle 8.2^\circ \leftarrow -18.4^\circ - (-26.6^\circ)$$

$$I_s = \frac{V_s}{Z_{total}} = \frac{10 \angle 45^\circ V}{943 \angle 8.2^\circ} = 0.0106 \angle 36.8^\circ A$$

$$= 10.6 \angle 36.8^\circ mA$$

$$7\angle 25^\circ + 3\angle 62^\circ \quad \cancel{10\angle 87^\circ}$$

$$\downarrow P \rightarrow R \quad \downarrow P \rightarrow R$$

$$6.34 + j2.96 + 1.41 + j2.65 = 7.45 + j5.61 = 9.33\angle 37.0^\circ$$

$$I_S = 10.6 \cos(105^\circ + \frac{\pi}{2} 36.8^\circ) \text{ mA}$$

$$Y = \frac{1}{Z} \quad I_S = Y_{\text{total}} V_S \quad Y_{\text{total}} = 1.06\angle -8.2^\circ \text{ mS}$$

$$Y = Y_1 + Y_2 = \frac{1}{1000 + j500} + \frac{1}{2000 - j2000}$$

$$= \frac{1000 - j500}{1000^2 + (500)^2} + \frac{2000 + j2000}{(2000)^2 + (2000)^2}$$

$$= \frac{1}{1000} \left[\frac{1 - 0.5j}{1.25} + \frac{2 + j2}{8} \right]$$




$$= \frac{1}{1000} [0.8 - 0.4j + 0.25 + 0.25j]$$

Answer ✓

$$= \frac{1}{1000} [1.05 - j0.15] = 1.06 \times 10^{-3} \angle -8.1^\circ \text{ A}$$

$$= 1.06 \angle -8.1^\circ \text{ mA}$$

Thevenin / Norton

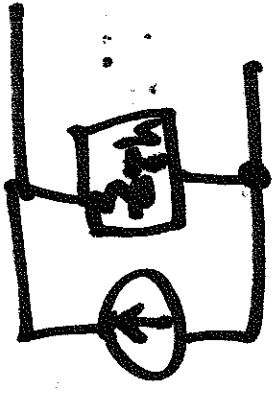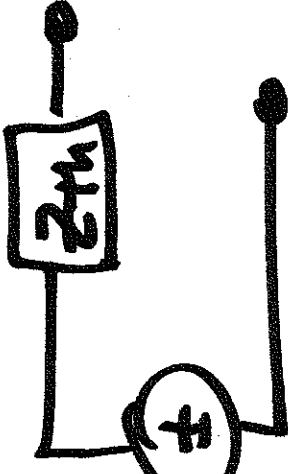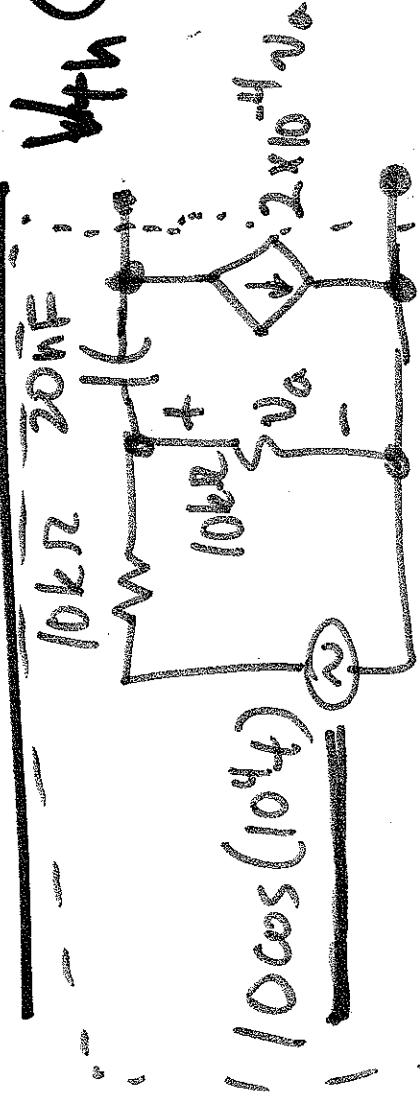


$$Z_N = Z_{th}$$


$$Z_C = -\frac{j}{\omega C} = -\frac{j}{10^4 (2 \times 10^{-8})}$$

$$= -\frac{j}{2 \times 10^{-4}}$$

$$= -j5000$$

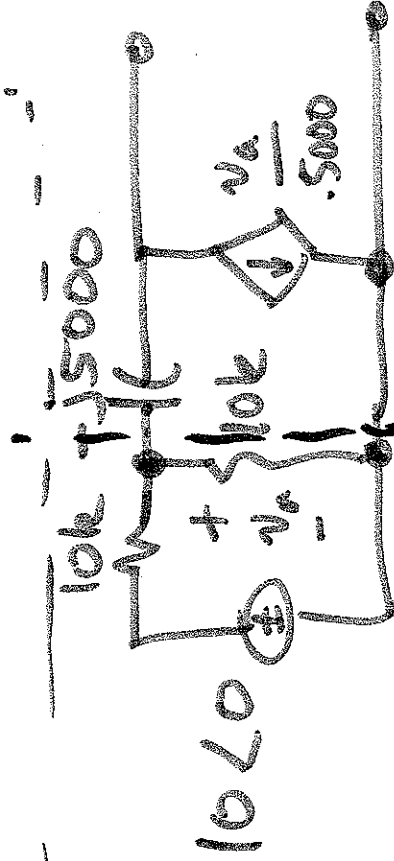

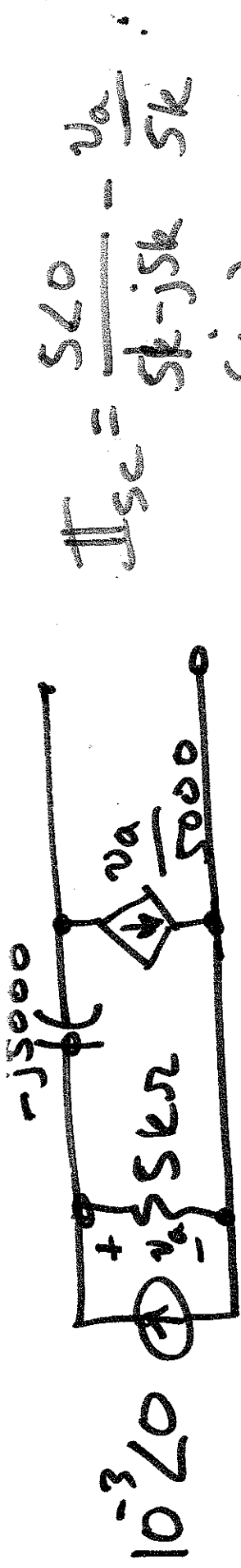
$$10^3 \angle 0^\circ \text{ A} \parallel 10k\Omega \parallel 10k\Omega \Rightarrow 10^3 \angle 0^\circ \text{ A} \parallel 5k\Omega \Rightarrow V_a$$



$$I_{sc} = \frac{5\angle 0}{5k - j5k} - \frac{v_a}{5k}$$

(i)

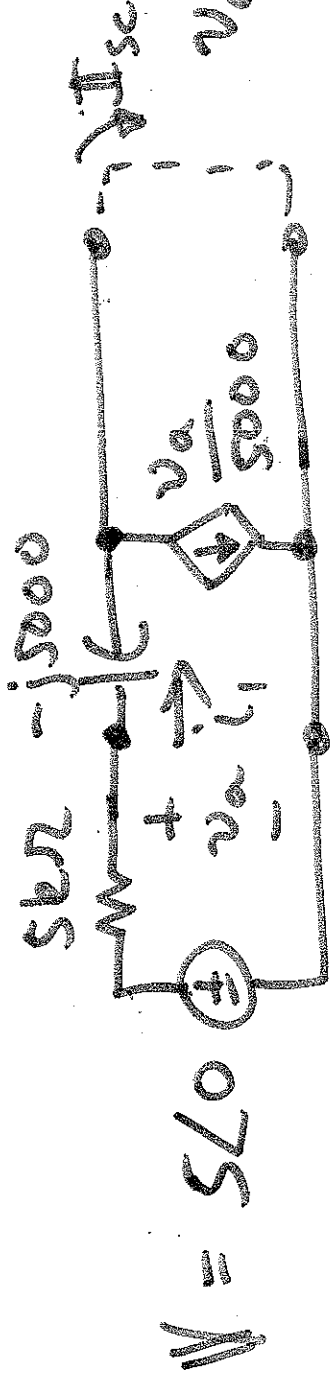

$$v_a = \frac{-j5k \cdot 5\angle 0}{5k - j5k}$$

(voltage divider)

$$I_{sc} = \frac{5}{5k - j5k} + \frac{j5k \cdot 5\angle 0}{(5k - j5k)(5k)}$$

$$= \frac{5}{5k - j5k} + \frac{j5k \cdot 5}{(5k - j5k)(5k)} = \frac{5 + j5}{5k - j5k}$$

$$45^\circ - (-45^\circ) = 90^\circ$$

$$= \frac{5\sqrt{2} \angle 45^\circ}{5\sqrt{2} \angle -45^\circ} V$$

$$= 1mA \angle 90^\circ$$

$$V_{oc} = 5\angle 0 - \frac{v_a(5k - j5k)}{5k\cancel{5k}}$$

$$\frac{5\angle 0 - v_a}{5k\cancel{5k}} = \frac{v_a}{5k\cancel{5k}}$$

$$v_a = \frac{5\angle 0}{2} = 2.5\angle 0 \text{ V}$$

$$V_{oc} = 5\angle 0 - \frac{(2.5\angle 0)(5k - j5k)}{5k}$$

$$= 5\cancel{5k} - 2.5(1 - j) = 2.5 + j2.5$$

$$Z_{Th} = Z_N = \frac{V_{Th}}{I_N} = \frac{2.5\sqrt{2}\angle 45^\circ}{10^{-3}\angle 90^\circ} = 2.5\sqrt{2}\angle 45^\circ$$

$$= 3.53\angle -45^\circ \text{ k}\Omega$$

