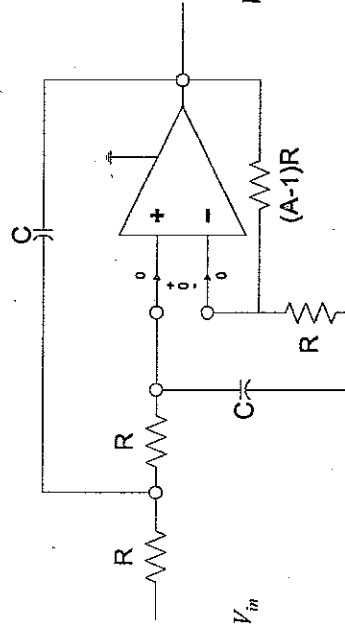


Second-Order Sallen-Key Filters

S.K. Low-Pass Filter




$$\omega_c = \frac{1}{RC},$$

$$A_v = A,$$

$$Q = \frac{1}{3-A}$$

S.K. High-Pass Filter

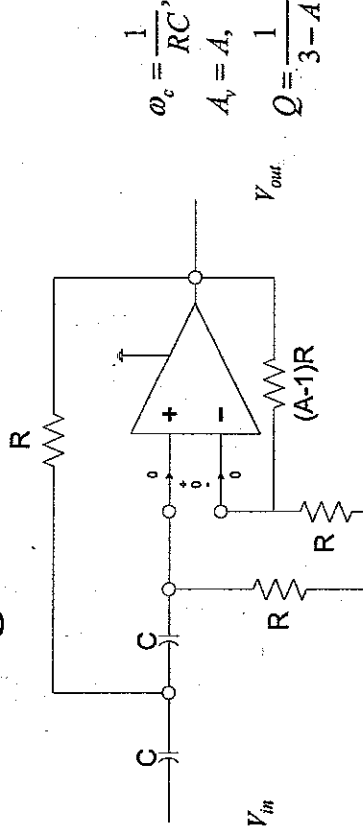


$$\omega_c = \frac{1}{RC},$$

$$A_v = A,$$

$$Q = \frac{1}{3-A}$$

S.K. Band-Pass Filter

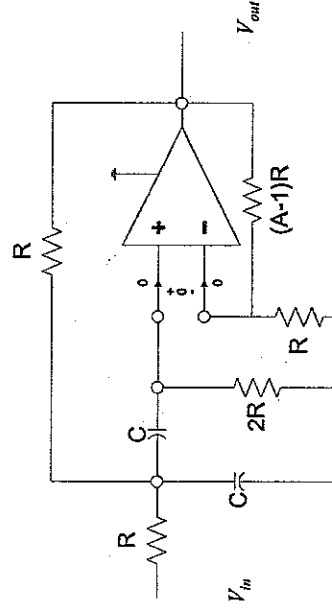


$$\omega_o = \frac{1}{RC}$$

$$Q = \frac{1}{3-A}$$

$$A_v = AQ$$

S.K. Band-Reject Filter

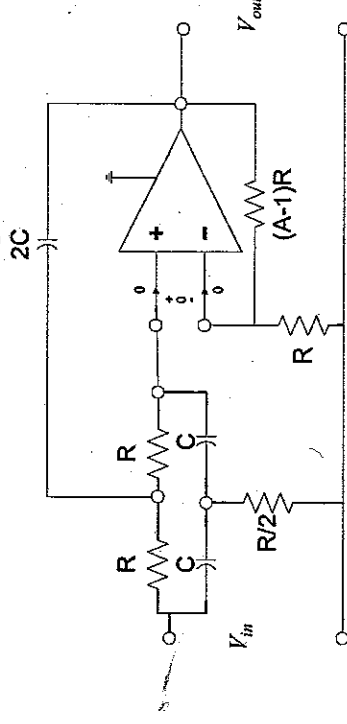

$$\omega_o = \frac{1}{RC}$$

$$Q = \frac{1}{4-2A}$$

$$A_v = A$$


Properties of Sallen-Key Filters:

1. Simplicity of the design
2. Non-Inverting Amplifier (positive Gain)
3. Replication of elements

Limitations of Sallen-Key Filters:

1. The Gain and Q are related
2. Q must be $> \frac{1}{2}$, since A must be > 1

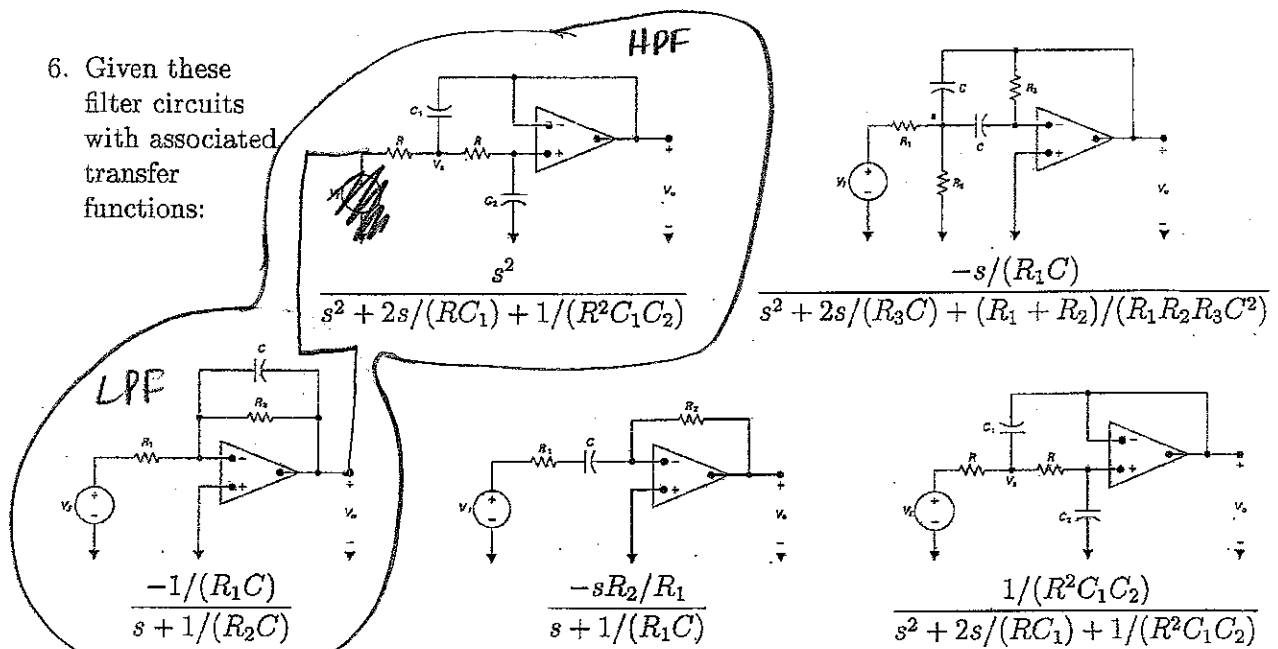6. Given these filter circuits with associated transfer functions:



Using the above active filter blocks, design a broadband bandpass filter with corner frequencies of $\omega_{c1} = 2000$ rad/s and $\omega_{c2} = 10^5$ rad/s and a pass-band gain of 200 (46dB). At high frequencies, a drop-off of -20dB/decade is sufficient. However, for low frequencies, the gain must be below 0dB for frequencies below 100 rad/s. Also, the gain at the lower corner frequency (ω_{c1}) should be 160. Choose all component values. (30)

$$\frac{\omega_{c1}}{\omega_s} = \frac{2000}{100} = 20 = 10^{1.3} \quad \frac{46\text{dB}}{1.3 \text{ decades}} = 37 \frac{\text{dB}}{\text{decade}} \quad n \geq 2 \quad \text{For HPF}$$

Thus can use 2nd order HPF w/ $\omega_{c1} = 2000 \frac{\text{rad}}{\text{s}}$ & $Q = \frac{160}{200} = 0.8$
and 1st order LPF w/ $\omega_{c2} = 10^5$ and gain of 200

$$\text{For HPF, } \omega_{c1}^2 = (2000)^2 = \frac{1}{R^2C_1C_2} \quad \text{and} \quad \frac{\omega_{c1}}{Q} = \frac{2000}{0.8} = \frac{2}{RC_1}$$

$$\text{Take } R = 10\text{k}\Omega = 10^4, \text{ then } C_1 = \frac{2(0.8)}{2000(10^4)} = 8 \times 10^{-8} \text{F} = 80\text{nF}$$

$$C_2 = \frac{1}{(2000)^2(10^4)^2 8 \times 10^{-8}} = \frac{1}{32 \times 10^6} = 3.1 \times 10^{-8} = 31\text{nF}$$

$$\text{For LPF, } \omega_{c2} = 10^5 = 1/R_2C, \quad |A_{pb}| = 200 = \frac{R_2}{R_1}$$

$$\text{Use } R_2 = 200\text{k}\Omega \\ R_1 = 1\text{k}\Omega$$

$$C = \frac{1}{(2 \times 10^5)(10^5)} \\ = 5 \times 10^{-11} \text{F} \\ = 50\text{pF}$$

End Of Exam