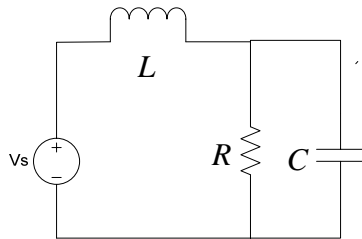
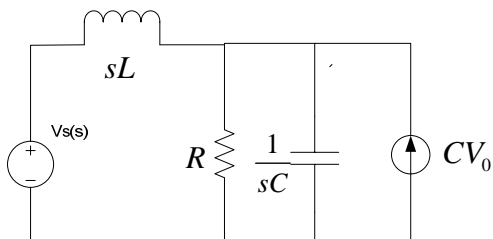


3. Determine $V_c(s)$ for the following circuit with $v_s(t) = 2t u(t)$. Include initial conditions for the capacitor, but assume that the inductor has no stored energy at $t=0^-$. (25)



Transform the circuit into the Laplace domain:



KCL @ V_c

$$\frac{V_c - V_s}{sL} + \frac{V_c}{R} + \frac{V_c}{1/sC} - CV_0 = 0$$

$$\left(\frac{1}{sL} + \frac{1}{R} + sC \right) V_c - \frac{1}{sL} V_s - CV_0 = 0$$

$$V_c = \frac{\frac{1}{sL} V_s + CV_0}{\left(\frac{1}{sL} + \frac{1}{R} + sC \right)}$$

$$v_s(t) = 2t \cdot u(t) \leftrightarrow V_s(s) = \frac{2}{s^2}$$

$$V_c = \frac{\frac{2}{s^3} + CV_0}{\left(\frac{1}{sL} + \frac{1}{R} + sC \right)} = \frac{\frac{2}{s^2 LC} + sV_0}{\left(s^2 + s \frac{1}{RC} + \frac{1}{LC} \right)}$$

3b) Find the inverse Laplace transform of $\frac{3s+4}{s^2+2s+2}$:

First perform the partial fraction expansion by factoring the denominator into its roots, in this case complex roots. Next solve for the coefficients A and A*. Perform the inverse transform by inspection with the aid of a Laplace transform table.

$$F(s) = \frac{3s+4}{s^2+2s+2} = \frac{3s+4}{(s+1-j)(s+1+j)} = \frac{A}{(s+1-j)} + \frac{A^*}{(s+1+j)}$$

$$3s+4 = A(s+1+j) + A^*(s+1-j)$$

if $s=-1+j$

$$3(-1+j) + 4 = A(-1+j+1+j)$$

$$1+j3 = Aj2$$

$$A = \frac{1+j3}{j2} = 1.5 - j0.5 = 1.58 \angle -18.43^\circ$$

$$\therefore \frac{3s+4}{s^2+2s+2} = \frac{1.5-j0.5}{(s+1-j)} + \frac{1.5+j0.5}{(s+1+j)}$$

By table lookup:

$$\begin{aligned} f(t) &= \left[(1.5-j0.5)e^{-(1-j)t} + (1.5+j0.5)e^{-(1+j)t} \right] u(t) \\ &= \left[3.16e^{-t} \cos(1t-18.43^\circ) \right] u(t) \end{aligned}$$

Be careful that the phase sign comes from the “positive” pole, marked in red.