Spring 2012

Version A

Name:\_\_\_\_\_

Student Number:\_\_\_\_

## Useful units and constants

Definition of electron volt:  $1 \text{ eV} = 1.6 \times 10^{-19} \text{ J}$ Electronic charge:  $q = 1.6 \times 10^{-19} \text{ C}$ Boltzmann constant:  $k = 8.62 \times 10^{-5} \text{ eV/K} = 1.38 \times 10^{-23} \text{ J/K}$ Thermal voltage at room temperature: kT / q = 0.0259 VRelative permittivity of silicon:  $\varepsilon_r = 11.7$ Permittivity of free space:  $\varepsilon_0 = 8.854 \times 10^{-14} \text{ F/cm}$ Silicon intrinsic carrier density at room temperature:  $n_i = 10^{10}/\text{cm}^3$ Band gap for silicon:  $E_G = 1.12 \text{ eV}$ Carrier density constant for silicon:  $B = 2.23 \times 10^{31} \text{ K}^{-3} \text{ cm}^{-6}$ 



1. A silicon pn junction has uniform doping concentrations of  $N_A = 2 \times 10^{18}$ /cm<sup>3</sup> and  $N_D = 10^{16}$ /cm<sup>3</sup> on the two sides of the junction, respectively. The widths of the undepleted regions are W<sub>p</sub>'=100 nm and W<sub>n</sub>'=500 µm. The minority carrier lifetimes are  $\tau n_p = 0.1$  µs and  $\tau p_n = 2$  µs The diode has a cross sectional area of 20 µm×100 µm. (40)

- a) Is the n side of the device short base or long base?
- b) Calculate the reverse leakage current I<sub>S</sub> (you can assume p-side is short base).
- c) What is the resistance of the undepleted n-region?
- d) If a current of 1 mA was passed through this diode, what would be the voltage measured (including neutral n-region)?

2. In the circuit below, use the constant voltage diode model for D1 and D2 with a threshold (turn-on) voltage of 0.70 V. The reverse breakdown voltage of the Zener diode (DZ) is -5V and the series resistance is  $250 \Omega$ . (30)

- a) Assume that D1 is on, D2 is off and DZ is in reverse breakdown. Calculate the voltage across and current through each diode.
- b) Check the each of the assumptions made in (a). Which mode is each diode actually in (on, off, breakdown)?



3. For the power supply circuit shown below, the rms value of  $v_S$  is 10 V, the operating frequency is 50 Hz, C = 2000  $\mu$ F, and the on-voltage of the diode is 0.70 V. The load sinks up to 5 mA. State your assumptions clearly and check them if possible. (40)

- (a) What is the dc output voltage  $V_O$  if the ripple voltage is small?
- (b) What is the maximum value of the ripple voltage at  $V_0$ ?
- (c) What is the minimum PIV rating for the diode?
- (d) What is the maximum current through the diode during start-up transient ( $v_c = 0$ )?

