

1. a) $\phi_j = V_T \ln \left(\frac{N_A N_D}{n_i^2} \right)$, $V_T = \frac{kT}{q} = 0.0259 \text{ V}$ (given on cover page)

$$= 0.0259 \cdot \ln \left(\frac{(2 \times 10^{18}) \times (10^{19})}{(10^{10})^2} \right) \approx \boxed{1.03 \text{ V}}$$

see lecture #8 → b) $I_s = q A n_i^2 \left(\frac{D_n}{N_A L_n} + \frac{D_p}{N_D L_p} \right) = q A n_i^2 \left(\frac{D_n}{N_A \sqrt{D_n \tau_{np}}} + \frac{D_p}{N_D \sqrt{D_p \tau_{pn}}} \right)$

$$= q A n_i^2 \left(\frac{\sqrt{D_n}}{N_A \sqrt{\tau_{np}}} + \frac{\sqrt{D_p}}{N_D \sqrt{\tau_{pn}}} \right)$$

Find approx μ_n, μ_p on chart on cover page

$$= q A n_i^2 \left(\frac{\sqrt{V_T \mu_n}}{N_A \sqrt{\tau_{np}}} + \frac{\sqrt{V_T \mu_p}}{N_D \sqrt{\tau_{pn}}} \right)$$

note: $L = \sqrt{D \tau}$
 $\frac{D}{\mu} = \frac{kT}{q} = V_T$

$$= (1.6 \times 10^{-19}) ((50 \times 10^{-7}) \times (100 \times 10^{-7}) ((10^{10})^2) \left(\dots \right)$$

$$\left(\frac{\sqrt{0.0259 \times 207}}{2 \times 10^{18} \sqrt{100 \times 10^{-9}}} + \frac{\sqrt{0.0259 \times 70}}{10^{19} \sqrt{20 \times 10^{-9}}} \right)$$

$$= \boxed{3.69 \times 10^{-24} \text{ A}}$$

$\mu_n \approx 207$
 $\mu_p \approx 70$

c) $I_D = I_s (e^{V_D/V_T} - 1) \rightarrow \ln \left(\frac{I_D}{I_s} + 1 \right) V_T = V_D$

$$\ln \left(\frac{1 \times 10^{-9}}{3.69 \times 10^{-24}} + 1 \right) 0.0259 = \boxed{0.86 \text{ V}}$$

see lecture #6 → d) $C_j = \frac{dQ_D}{dV_D}$, $C_{j0} = \frac{\epsilon_s A}{x_{do}} = \frac{11.7 \times 8.854 \times 10^{-14} \times 50 \times 10^{-7} \times 100 \times 10^{-7}}{2.83 \times 10^{-6}} = 1.83 \times 10^{-17}$

$$x_{do} = \sqrt{\frac{2 \epsilon_s \phi_j}{q} \left(\frac{1}{N_D} + \frac{1}{N_A} \right)} = \sqrt{\frac{2 \times 11.7 \times 8.854 \times 10^{-14} \times 1.03}{1.6 \times 10^{-19}} \left(\frac{1}{2 \times 10^{18}} + \frac{1}{10^{19}} \right)}$$

$$= 2.83 \times 10^{-6}$$

$$C_j = C_{j0} \left(\frac{x_{do}}{x_0} \right) = C_{j0} \sqrt{\frac{\phi_j}{\phi_j - V_D}} = (1.83 \times 10^{-17}) \sqrt{\frac{1.03}{1.03 - 0.6}}$$

$$= \boxed{2.83 \times 10^{-17} \text{ F}}$$

2. In the circuit below, use the constant voltage model for all diodes with a turn-on voltage of 0.6 V and reverse breakdown voltage of -5 V ($V_Z = 5$ V). (30)

a) What is the minimum value of V_{IN} at which D_1 turns on?

What is the associated V_O ?

When D_1 first turns on, $V_{D1} = V_{on} = 0.6$ V and $I_{D1} = 0$.

Using KCL at V_1 assuming D_2 and D_3 are ON:

$$\frac{10 \text{ V} - 2 * 0.6 \text{ V} - V_1}{200 \Omega} = \frac{V_1 - (-5 \text{ V})}{1000 \Omega}$$

Solving, $V_1 = 6.5$ V, so $V_{IN} = V_1 + 0.6 \text{ V} = 7.1$ V and

$V_O = V_1 + 2 * 0.6 \text{ V} = 7.7$ V.

Checking, V_O is less than +10V, so current through D_2 and D_3 is positive, confirming that they are ON.


b) If $V_{IN} = 10$ V, what is the value of V_O ? Specify what mode each of the diodes is in and check any assumptions made.

Assume that D_1 , D_2 and D_3 are all on. KCL at V_1 gives:


$$\frac{10 \text{ V} - 0.6 \text{ V} - V_1}{500 \Omega} + \frac{10 \text{ V} - 2 * 0.6 \text{ V} - V_1}{200 \Omega} = \frac{V_1 - (-5 \text{ V})}{1000 \Omega}$$

Solving, $V_1 = 7.225$ V, so $V_O = V_1 + 2 * 0.6 \text{ V} = 8.425$ V. Checking, V_O is less than +10V, so current through D_2 and D_3 is positive, confirming that they are ON. $V_1 + 0.6 \text{ V}$ is less than V_{IN} , D_1 is also ON.

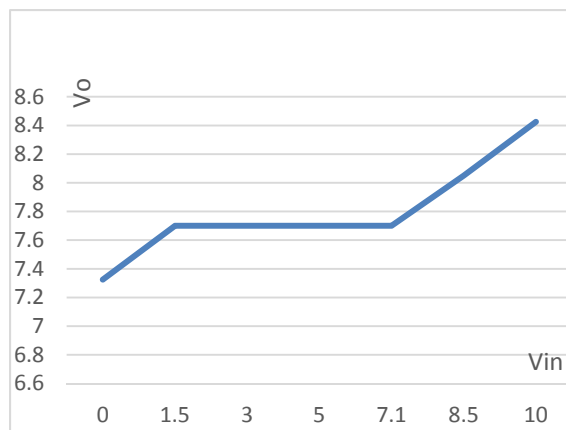
c) Sketch plot of the output voltage V_O versus input voltage for $0 \text{ V} < V_{IN} < 10 \text{ V}$. Specify voltages at inflection points.



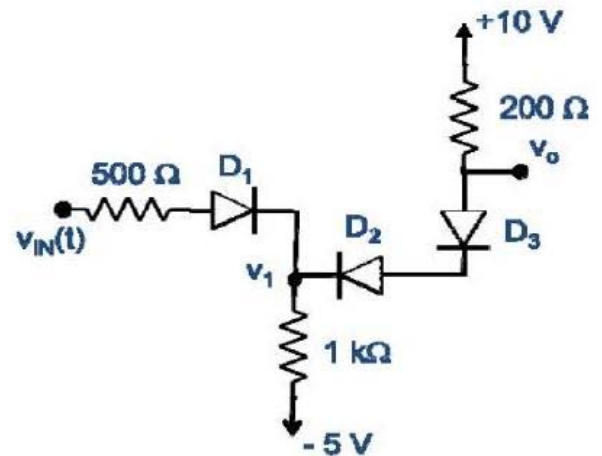For a given mode for all the diodes, the circuit is linear. For $V_{IN} < 7.1$ V, D_1 turns off, so V_O stay the same (7.7 V). D_1 remains off as V_{IN} is reduced until it breaks down when $V_{D1} = -5$ V, which occurs for $V_{IN} = V_1 - 5 \text{ V} = 1.5$ V. For $V_{IN} = 0$ V, can solve KCL at V_1 again using same equation as (b), getting $V_1 = 6.125$ V and $V_O = 7.325$ V.



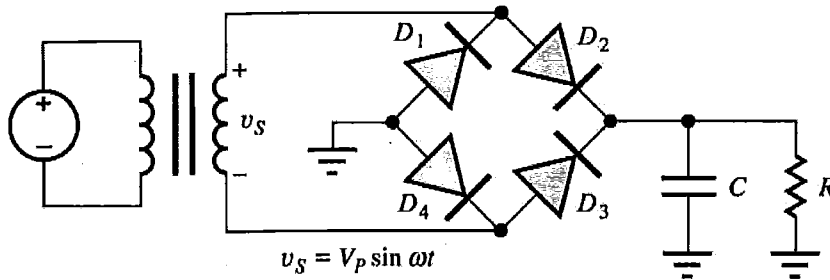3. For the power supply circuit shown below, the peak value of v_S is 14 V, the operating frequency is 50 Hz, and the on-voltages of the diodes are 0.60 V. State your assumptions clearly and check them if possible. (35)



Solution :

(a) What is the dc output voltage across R if the ripple voltage is small?(8)

$$V_{dc} = V_P - 2V_{on} = 12.8 \text{ V}$$

(b) What is the required minimum reverse breakdown voltage for the diodes?(5)

$$PIV = V_P = 14 \text{ V}$$

(c) If $R = 2 \text{ k}\Omega$, what is the minimum value of capacitance C to ensure that the output voltage remains above 12 V?(12)

$$V_r = 12.8 - 12 = 0.8 \text{ V}$$

$$C_{min} = \frac{V_P - 2V_{on}}{V_r} \frac{T}{2R} = \frac{V_P - 2V_{on}}{fV_r} \frac{1}{2R} = 80 \mu\text{F}$$

(d) What fraction of a period is each diode conducting?(10)

$$\Delta T = \frac{1}{\omega} \sqrt{\frac{2V_r}{V_p}} = \frac{0.338}{100\pi} = 1.07 \text{ ms}$$

$$T = \frac{1}{50} = 20 \text{ ms}$$

$$\text{Fraction of conducting period} = \frac{\Delta T}{T} = 0.053$$