Spring 2014

٦

Exam 2 Version A

Q 0.25 ∖

by the point of the problem, use
$$V_{TN} = 0.8 V$$
 and $K_n' = 200 \mu \Lambda/V^2$ (40 points).
(i) Identify and label the Drain (D), Source (S), Gate (O), and Bulk/Body (B) (20) $\frac{1.6V}{9}$ $\frac{1}{9}$ $\frac{1}{9}$

so assumption checks

Problem 2.
Redraw circuit:
$$R = R_1 : R_2 :: R_0 \neq V_0$$

 $\downarrow V = \frac{1}{2} V_0 = \frac{1}{2} V_0 = \frac{1}{2} V_0$
 $\downarrow V = \frac{1}{2} V_0 =$

·

42.031 00 NEETS SYGEASSE' - 5 SOUARES 42.032 000 NEETS SYGEASSE' - 5 SOUARES 42.032 000 NEETS SYGEASSE' - 5 SOUARES 42.039 200 SHEETS SYGEASSE' - 5 SOUARES

N. (

(;

(

EE 331 - Midlem 2

b)
$$KVL: Vpp - IpRp - VpS - IpRs = 0$$

(1) $\frac{Vop - VpS}{Fp} = Rp + Rs \rightarrow \frac{3 - 1V}{2syA} = 80 KD$
From a) $Vqs = 1.3 V_{2} V6 = Vpp/2 = 1.5 V$
 $Vqs = Vq - Vs = Vq - IpRs$
 $\rightarrow Rs = \frac{Vq - Vqs}{Tp} = \frac{1.5 - 1.3 V}{2syA} = \frac{0.2 V}{2syA} = \frac{8 KSL}{2syA} = \frac{8 KSL}{2syA} = \frac{72 k Q}{2syA} = \frac{72 k$

42.031 50 SHEETS EYE-ASE7.5 SOUNDES 42.031 50 SHEETS EYE-ASE7.5 SOUNDES 42.032 100 SHEETS EYE-ASE7.5 SOUNDES 42.039 200 SHEETS EYE-ASE7.5 SOUNDES 42.031 50 SHEETS EYE-ASE7.5 SOUNDES 42.031 50 SHEETS EYE-ASE7.5 SOUNDES 42.031 50 SHEETS EYE-ASE7.5 SOUNDES 42.032 100 SHEETS EYE-ASE7.5 SOUNDES 43.032 100 SHEETS EYE-ASE7.5 SOUNDES 45.032 100 SHEETS EYE-ASE7.5 SOUNDES 45.032 100 SHEETS EYE-ASE7.5 SOUNDES 45.032 100 SHEETS EYES 45.032 100 SHEETS EYES 45.032 100 SHEETS EYES 45.

•

(

3. (30 pts) An NMOS linear load inverter design is shown in the figure to the right. Use the following parameters for both devices: $V_{TO} = 0.8 \text{ V}$, $K_n' = 200 \text{ }\mu\text{A/V}^2$.

(a) Find V_H and V_L . Ignore channel length modulation and body effect. [15]

$$V_H = V_{DD} = 3.3$$
V:

When $v_I = V_H$ and v_O is low (v_L), Ms and M_L are both in the triode region and the i_D values are given by:

$$i_{DSS} = K'_n \left(\frac{W}{L}\right)_s \left(v_{GSS} - V_{TNS} - \frac{v_{DSS}}{2}\right) v_{DSS}$$
$$i_{DSL} = K'_n \left(\frac{W}{L}\right)_L \left(v_{GSL} - V_{TNL} - \frac{v_{DSL}}{2}\right) v_{DSL}$$



$$\left(\frac{1}{2}\right)\left(5.0 - v_L - 0.8 - \frac{3.3 - v_L}{2}\right)(3.3 - v_L) = 5\left(3.3 - 0.8 - \frac{v_L}{2}\right)v_L$$

Solving for v_L gives $v_L = 0.305V$

(b) If body effect exists ($\gamma > 0$), will V_H increase/decrease/stay the same? How about V_L ? Explain. [5]

Only the load device has body effect. V_H is unaffected by the body effect unless V_{TNL} becomes larger than 1.7 V so that M_L is off when v_0 equals V_{DD} . This would require an extremely large value of the body effect coefficient, since V_{TNL0} is just 0.8 V. Thus no change is expected.

The body effect will cause an increase in V_{TNL} and thus a decrease in i_{DSL} which makes V_L decrease to match currents. However, the change is expected to be small as $V_{SBL}=V_L$ is small.

(c) Design a gate to perform function $\overline{A \cdot (B + C)}$ based on this inverter with the same V_L and V_H and noise margins and performance. Sketch your design and specify W/L ratios for all transistors. [10]

Load is unchanged. W/L ratios for switching (pull-down) transistors are chosen based on worst case. Weakest pull-down is when B or C and A are on. Conducting path to ground is via B and A or C and A, so these transistors need double width to compensate for double length. Thus W/L values should be 10/1.



