
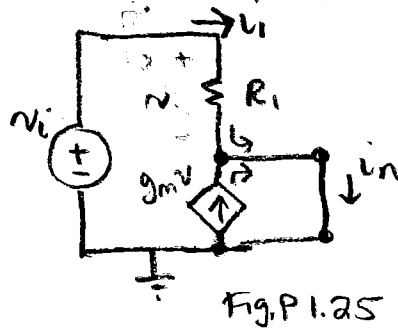


EE 331 Spring 2014 Homework #0 solutions

1.24)

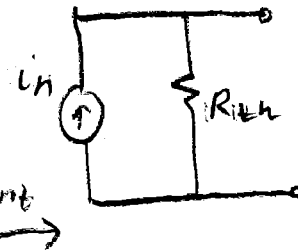

want
Norton
Equivalent




Kinda Like Example 1.2, do lots of KCL/KVL:

$$i_n = i_1 + g_m v, \quad v_i = G_1 v_i$$

$$i_n = v_i (G_1 + g_m) = \left(\frac{1}{10k} + 0.002 \right) v_i = 0.0021 v_i$$

R_{th} :

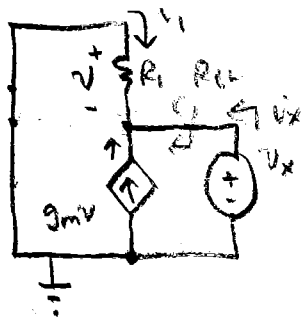

$$R_{th} = \frac{v_x}{i_x}$$

KCL again:

$$-i_1 - g_m v - i_x = 0$$

$$i_x = -\left(\frac{v}{R_i}\right) - g_m(-v_x) \quad \left\{ \begin{array}{l} v_x = -v \end{array} \right.$$


$$i_x = v_x \left(\frac{1}{R_i} + g_m \right)$$

$$\therefore \frac{v_x}{i_x} = R_{th} = \frac{1}{\left(\frac{1}{R_i} + g_m\right)} = \frac{1}{\left(\frac{1}{10k} + 0.002\right)}$$


$$\approx 476 \Omega$$

∴ solution

$$i_n = (2.1 \times 10^{-3}) v_s$$

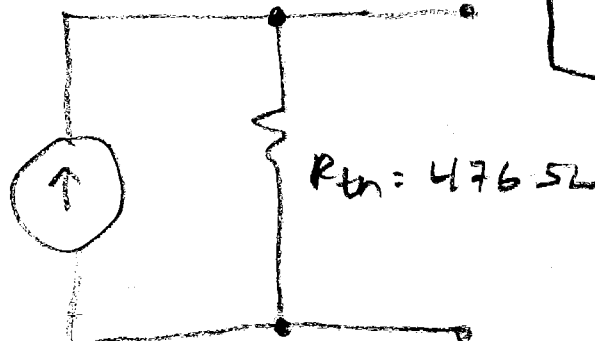

1.29)

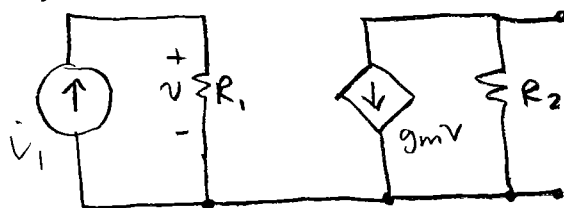


$$g_m = 0.0025 \text{ S}$$

$$R_1 = 200 \text{ k}\Omega$$

$$R_2 = 1.5 \text{ M}\Omega$$

Find R_{th} :


$$R_{th} = \frac{v_x}{i_x}$$

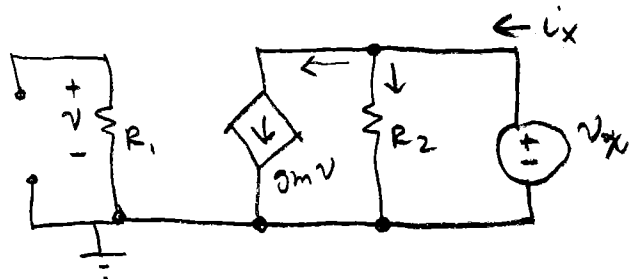

KCL @ v_x : $-i_x + \frac{v_x}{R_2} + g_m v = 0$ (Note: $v = 0 \text{ V}$ is indicated)

$$\therefore \frac{v_x}{i_x} = R_{th} = R_2 = 1.5 \text{ M}\Omega$$

short output to find i_n :

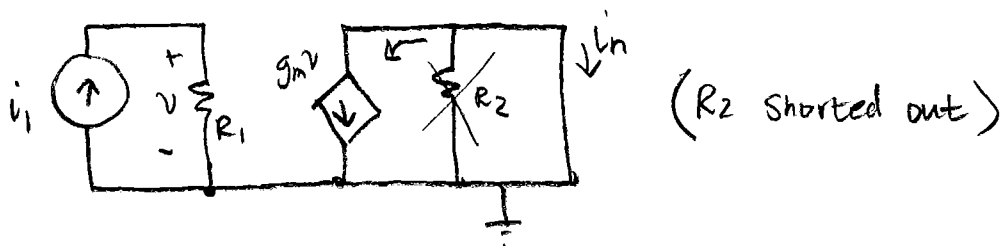

KCL: $i_n = -g_m v$

$$i_n = -g_m R_1 i_1$$

$v = i_1 R_1$
(substitute)

$$\therefore v_{th} = i_n R_{th} = (-g_m R_1 i_1) (R_{th})$$

$$= -(0.0025)(1.5 \text{ M}) (v_s) (1.5 \text{ M})$$

$$= -3750 v_s$$


Solution

$$v_{th} =$$

$$-3750$$

$$v_s$$

$$v_{th}$$

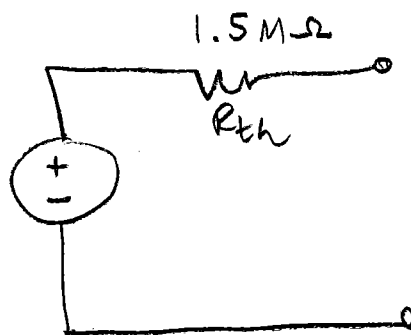

Problem 1

problem 1B2 here have wrong HWS
but use other methods to solve FYI



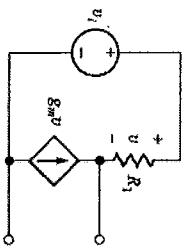


Figure P1.25

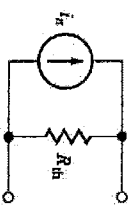

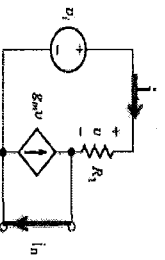i_n represents the current when output circuit is short.



$$\begin{aligned} i_1 + g_m(i_1 R_1) &= i_n \\ i_1 &= v_1 / R_1 \\ \Rightarrow i_n &= (1 + g_m R_1) i_1 = \frac{(1 + g_m R_1)}{R_1} v_1 = \frac{251}{10 \text{ k}\Omega} \text{ V} \end{aligned}$$


R_{th} represents the equivalent resistance present at the output terminals with all independent sources set at zero.

There are three methods to solve R_{th} .

Method 1: open circuit voltage divided by short circuit current


$$R_{th} = \frac{V_{oc}}{I_{sc}}$$

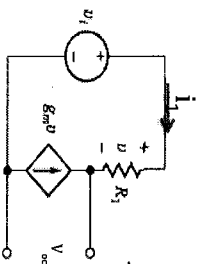I_{sc} is the output current when output circuit is short, same with i_n
 V_{oc} is the output voltage when output circuit is open.




$$\begin{aligned} i_1 &= -g_m(i_1 R_1) \Rightarrow i_1 = 0, V_{oc} = v_1 \\ R_{th} &= \frac{V_{oc}}{I_{sc}} = \frac{v_1}{\frac{v_1}{(1 + g_m R_1) R_1}} = \frac{R_1}{1 + g_m R_1} = 39.84 \Omega \end{aligned}$$

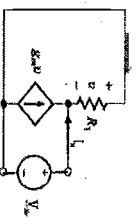Method 2: Set voltage source to zero, add an external voltage source at the output port



$$\begin{aligned} R_{th} &= \frac{V_x}{i_x}, i_x = -(1 + g_m R_1) i_1, V_x = -i_1 R_1 \\ \Rightarrow R_{th} &= \frac{R_1}{1 + g_m R_1} = 39.84 \Omega \end{aligned}$$

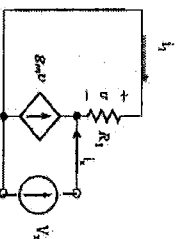Method 3: Set voltage source to zero, add an external current source at the output port



$$\begin{aligned} i_1 &= -(1 + g_m R_1) i_x, V_x = -i_1 R_1 \\ R_{th} &= \frac{V_x}{i_x} = \frac{-i_1 R_1}{-(1 + g_m R_1) i_x} = \frac{R_1}{1 + g_m R_1} = 39.84 \Omega \end{aligned}$$

Problem 2:


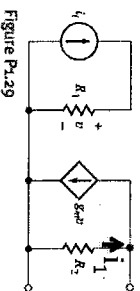


Figure P1.29

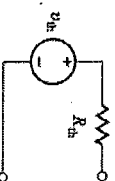

$\Rightarrow$

v_h represents the equivalent voltage when output is open.


$$\begin{aligned} v &= i_1 R_1 \\ i_1 &= g_m v = i_1 R_1 \\ v_h &= i_1 R_2 = R_1 R_2 g_m i_1 \end{aligned}$$

R_h represents the equivalent resistance when all independent sources are zero.

Three ways to solve R_h


Method 1: open circuit voltage divided by short circuit current
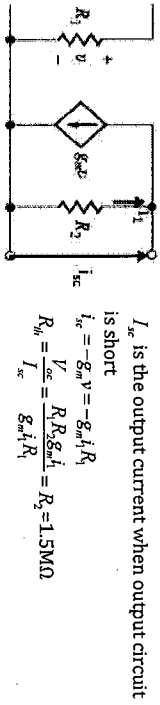
$$\begin{aligned} R_h &= \frac{V_{oc}}{I_{sc}} \\ V_{oc} &= v_h = R_1 R_2 g_m i_1 \end{aligned}$$




$$\begin{aligned} I_{sc} &\text{ is the output current when output circuit is short} \\ i_{sc} &= -g_m v = -g_m i_1 R_1 \\ R_h &= \frac{V_{oc}}{I_{sc}} = \frac{R_1 R_2 g_m i_1}{g_m i_1 R_1} = R_2 = 1.5 \text{ M}\Omega \end{aligned}$$

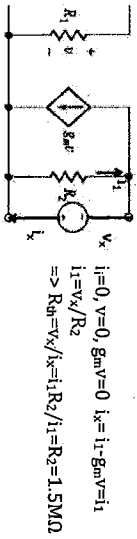Method 2: Set current source to zero, add an external voltage source at output



$$\begin{aligned} i_1 &= 0, v = 0, g_m v = 0 \quad i_x = i_1 - g_m v = i_1 \\ i_1 &= v_x / R_2 \\ \Rightarrow R_h &= v_x / i_x = i_1 R_2 / i_1 = R_2 = 1.5 \text{ M}\Omega \end{aligned}$$

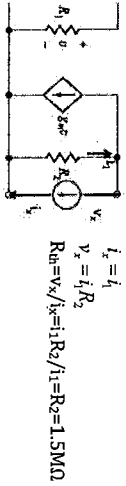Method 3: set current source to zero, add an external current source at output



$$\begin{aligned} i_x &= i_1 \\ v_x &= i_1 R_2 \\ R_h &= v_x / i_x = i_1 R_2 / i_1 = R_2 = 1.5 \text{ M}\Omega \end{aligned}$$

Problem 3

Expressions for V_1 , I_2 and I_3 are given by:

Nominal values are:

$$\begin{aligned} V_1 &= \frac{V}{1 + \left(\frac{1}{R_3 + \frac{1}{R_2}} \right) \frac{1}{R_1}} \\ I_2 &= \frac{V - V_1}{R_2} \\ I_3 &= \frac{V - V_1}{R_3} \end{aligned}$$

$$\begin{aligned} V_1^{nom} &= \frac{1}{1 + \left(\frac{1}{11k + \frac{1}{30k}} \right) \frac{1}{24k}} \approx 0.75V \\ I_2^{nom} &= \frac{1 - 0.7489}{30k} \approx 8.37 \mu A \end{aligned}$$

$$I_3^{nom} = \frac{1 - 0.7489}{11k} \approx 22.83 \mu A$$

According to the expression of V_1 , the max and minimum values of V_1 are:

$$V_1^{max} = \frac{1}{1 + \frac{1}{11k \times 0.9 + \frac{1}{30k \times 0.9}} \frac{1}{24k \times 1.1}} \approx 0.82V$$

$$V_1^{min} = \frac{1 \times 0.95}{1 + \frac{1}{11k \times 1.1 + \frac{1}{30k \times 1.1}} \frac{1}{24k \times 0.9}} \approx 0.67V$$

Worst-case values of I_2 and I_3 are:

$$I_2^{max} = \frac{V - V_1^{min}}{R_2} = \frac{1 - 0.67}{30k \times 0.9} = 12.22 \mu A$$


$$I_2^{min} = \frac{V - V_1^{max}}{R_2} = \frac{1 - 0.82}{30k \times 1.1} = 5.45 \mu A$$

$$I_3^{max} = \frac{V - V_1^{min}}{R_3} = \frac{1 - 0.67}{11k \times 0.9} = 33.33 \mu A$$


$$I_3^{min} = \frac{V - V_1^{max}}{R_3} = \frac{1 - 0.82}{11k \times 1.1} = 14.88 \mu A$$

Problem 4 Solution


a) and b)

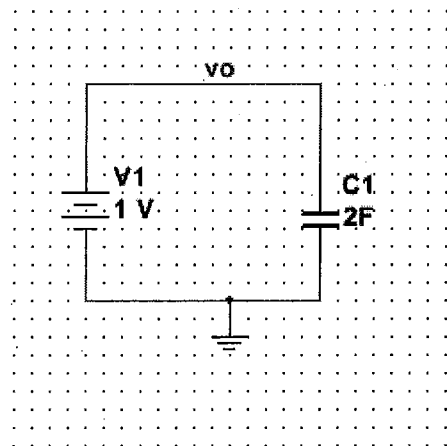


4ab Transient Analysis

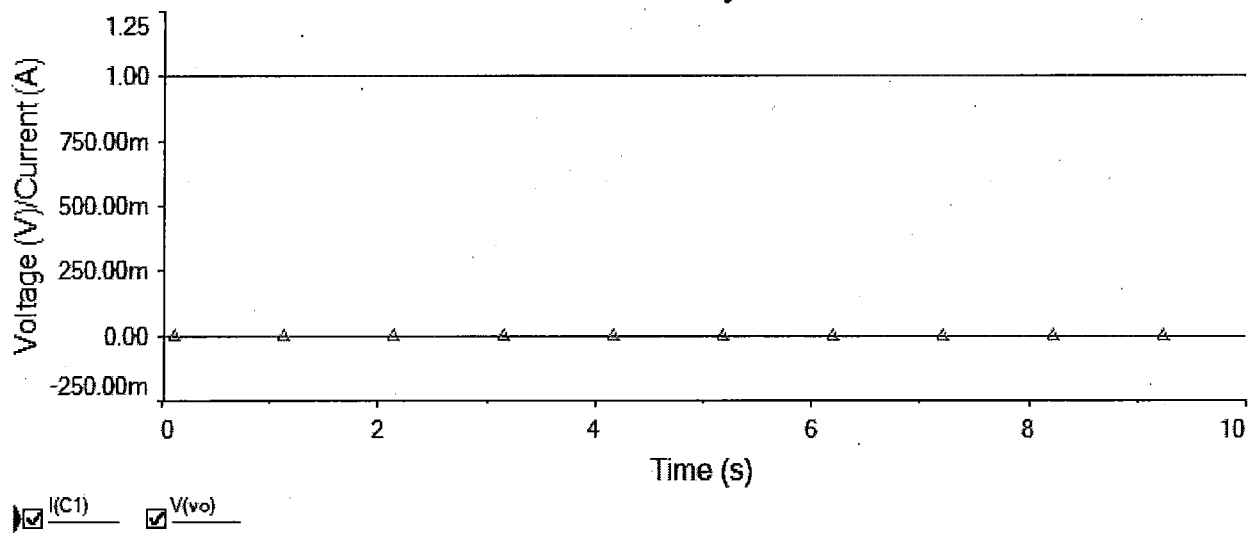

c) and d)

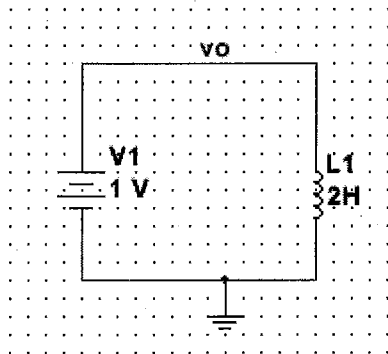

4cd Transient Analysis

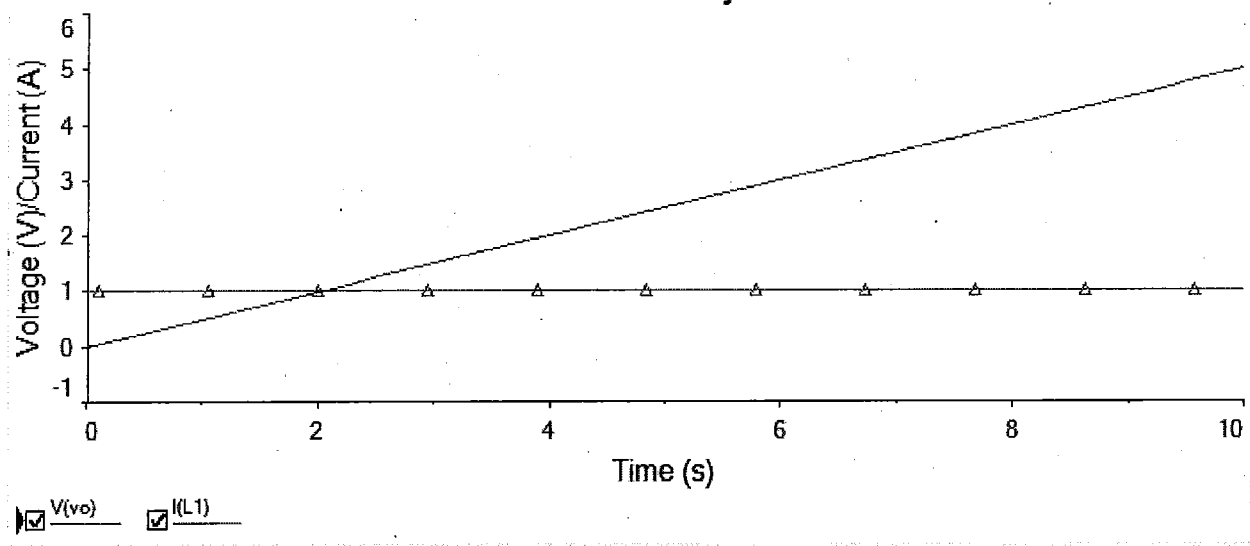

Problem 5

a) The first step in finding the transfer function is to construct the s-domain equivalent circuit. By definition, the transfer function is the ratio of V_o/V_s which can be computed from a single node-voltage equation. Summing the currents away from the upper node generates

$$\frac{V_o - V_o}{1000} + \frac{V_o}{250 + 0.05s} + \frac{V_o s}{10^6} = 0$$

Solve V_o ,

$$V_o = \frac{1000(s + 5000)V_o}{s^2 + 6000s + 25 \times 10^6}$$

Hence the transfer function is

$$H(s) = \frac{V_o}{V_s} = \frac{1000(s + 5000)}{s^2 + 6000s + 25 \times 10^6}$$

The poles of $H(s)$ are the roots of the denominator polynomial. Therefore

$$\begin{aligned} -p_1 &= -3000 - j4000 \\ -p_2 &= -3000 + j4000 \end{aligned}$$

The zeros of $H(s)$ are the roots of the numerator polynomial; thus

$$-z_1 = -5000$$

For the impulse response, let

$$\begin{aligned} V_o &= \frac{1000(s + 5000)}{s^2 + 6000s + 25 \times 10^6} = \frac{K_1}{s + 3000 - j4000} + \frac{K_1^*}{s + 3000 + j4000} \\ K_1 &= 500 - j250 = 559.017 \angle -26.57^\circ \\ K_1^* &= 500 + j250 = 559.017 \angle 26.57^\circ \end{aligned}$$

Test the solutions with the zero of $H(s)$

$$H(-5000) = \frac{500 - j250}{-5000 + 3000 - j4000} + \frac{500 + j250}{-5000 + 3000 + j4000} = 0$$

Then, transform back to time domain,

$$y(t) = h(t) = 1118e^{-3000t} \cos(4000t - 26.57^\circ) u(t)$$

For the response of the input source, let

$$V_o = \frac{15000(s + 5000)}{s(s^2 + 6000s + 25 \times 10^6)} = \frac{K_2}{s} + \frac{K_3}{s + 3000 - j4000} + \frac{K_3^*}{s + 3000 + j4000}$$

$$\begin{aligned} K_2 &= 3 \\ K_3 &= -1.5 - j0.75 = 1.6771 \angle -153.44^\circ \\ K_3^* &= -1.5 + j0.75 = 1.6771 \angle 153.44^\circ \end{aligned}$$

Test the root of zero


$$\frac{3}{-5000} + \frac{-1.5 - j0.75}{-5000 + 3000 - j4000} + \frac{-1.5 + j0.75}{-5000 + 3000 + j4000} = 0$$

Then the response due to the input is

$$y(t) = [3 + 3.35e^{-3000t} \cos(4000t - 153.44^\circ)] u(t)$$

We can see the response includes a DC which is 3 V and a fast decaying cosine wave.

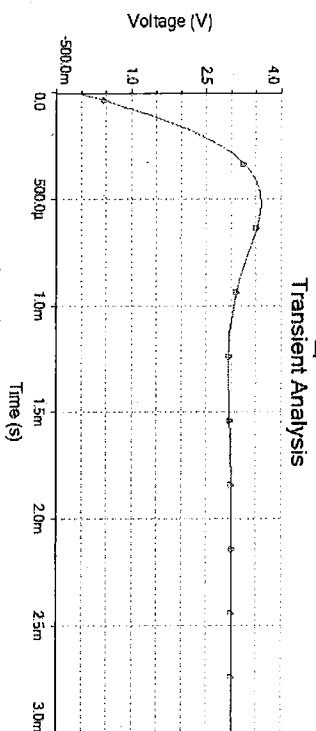b) Multisim simulation result is shown below:



The steady state voltage is 3V, consistent with solution in part a).

Problem 6

Applying superposition, $V_o = V_{oDC} + V_{oAC}$. V_{oDC} is the response of the DC source V_{ac} and V_{oAC} is the response of the AC source v_{ac} . Then in s-domain, we have

$$V_o = \frac{1000(s + 5000)(V_o + V_s)}{s^2 + 6000s + 25 \times 10^6} = V_{oAC} + V_{oDC}$$

We have got V_{oDC} in the last problem and

$$V_{oAC} = \frac{1000(s + 5000)V_o}{s^2 + 6000s + 25 \times 10^6}$$

To verify the phase value, the steady output waveform in red is compared with a reference waveform of $3+0.005\cos(10^4t-60^\circ)$ in green. As can be seen, they are completely overlapped in steady state.

$$H(j10^6) = \frac{1000(j10^6 + 5000)}{(j10^6)^2 + 6000(j10^6) + 25 \times 10^6} \approx 0.001\angle -90^\circ$$

$$v_{\text{vac}} = 0.005 \cos(10^6 t - 60^\circ) u(t)$$
$$\begin{aligned} v_o &= v_{odc} + v_{vac} \\ &= [3 + 0.005 \cos(10^6 t - 60^\circ) \\ &\quad + 1.6771e^{-3000t} \cos(4000t - 153.44^\circ)]u(t) \end{aligned}$$
$$v_{o_steady} = [3 + 0.005 \cos(10^6 t - 60^\circ)] u(t)$$

Transient Analysis

Voltage (V)

Time (s)

Case	V (output)
V1	4.2339m
V2	3.9951
V3	4.2339m
V4	3.0048
V5	-3.0048
V6	-3.0058m
V7	5.8190m
V8	-3.1542K
V9	-3.1542K
V10	-3.1542K

$$\text{Frequency } f = \frac{1}{2\pi} = \frac{1}{2 \times 3.086 \times 10^{-6}} = 1.62 \times 10^5, \quad 2\pi f \approx 10^6$$


Central voltage level is $(2.9951+3.0049)/2 \approx 3 \text{ V}$

Amplitude is $dy/2=9.8\text{mV}/2\approx5\text{mV}$


Homework #0

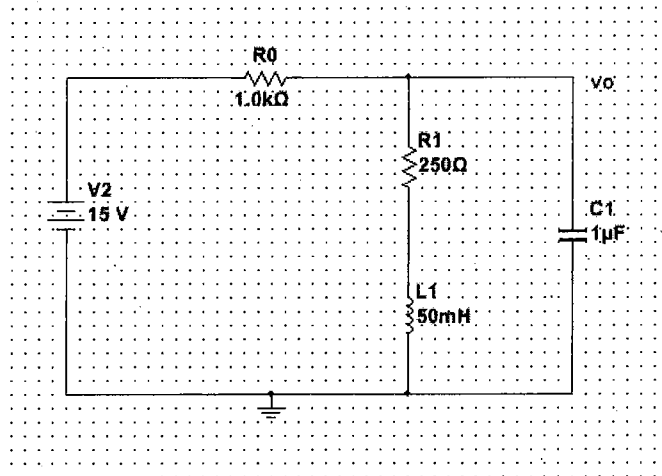Problem 5. b) solution


Using Multisim, put together the following circuit. I labeled the node vO for convenience:




Next, run a Transient Analysis:

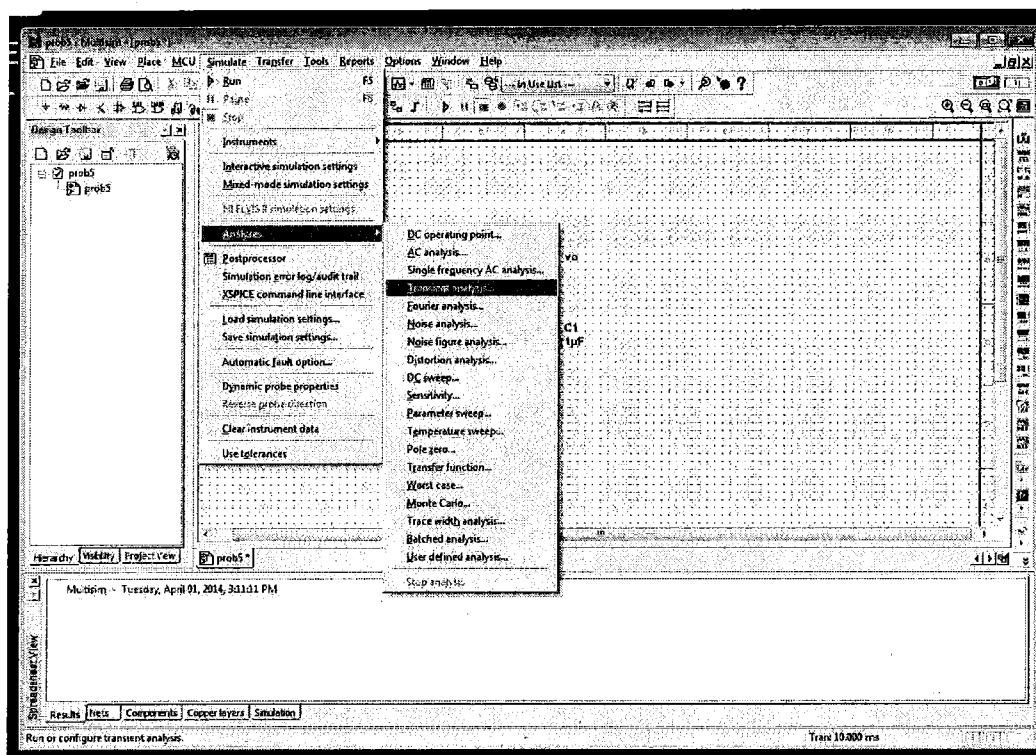

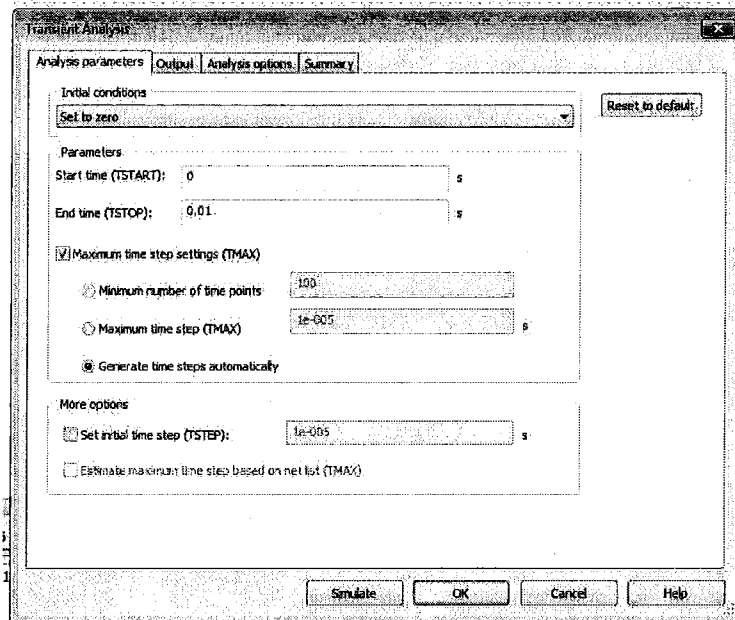
I set the stop time (TSTOP) to 10 mS, but you can pick whatever amount of time makes a good-looking plot. I kept everything else set to default:



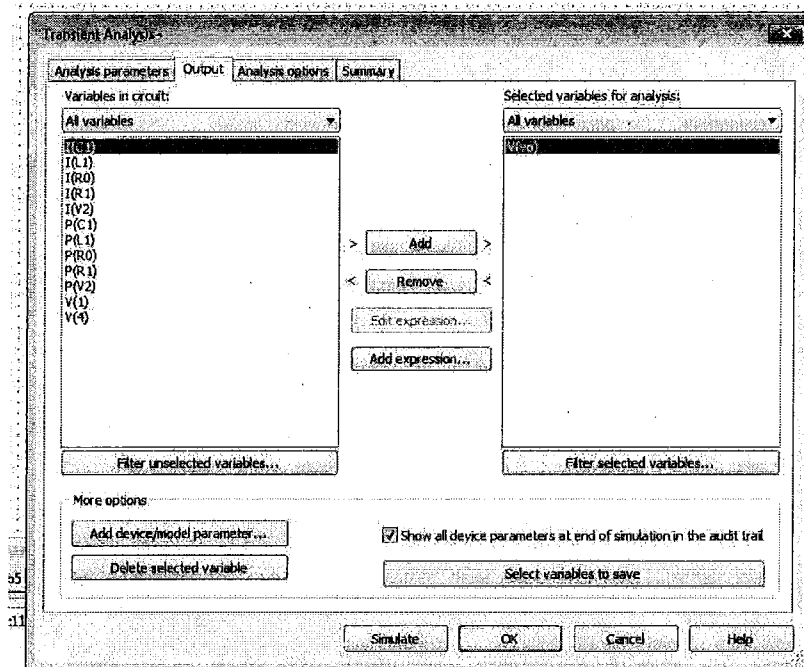Next, I went to the Output tab and selected V(vo) so the graph will display the output voltage we want for this problem:



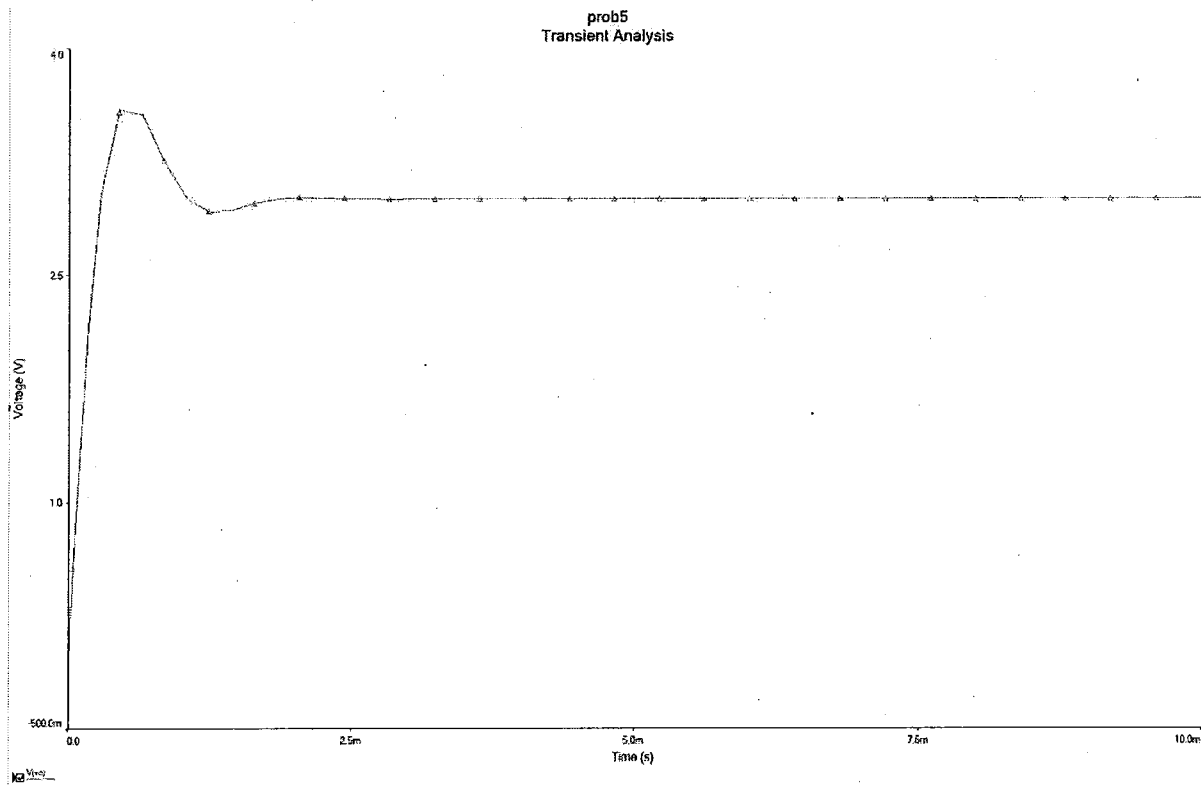Last, hit the "Simulate" button at the bottom of the Transient Analysis dialog, and a graph like this should appear showing the Transient Response at the node vo:



Homework #0

Problem 6. b) solution

Solution is similar to Problem 5. b), but notice that the sinusoidal voltage input for Multisim requires RMS voltage = $V_{\text{amplitude}}/1.41 = 5/1.41 = 3.54 \text{ V}$, and 10^6 rad/sec frequency is converted to kHz.

