

EE331 Devices and Circuits 1

Spring 2014

Homework 8

Due in class on Friday, May 30 2014.

1. Jaeger & Blalock Problem 7.19.
2. Jaeger & Blalock Problem 7.22.
3. Jaeger & Blalock Problem 7.47.
4. Jaeger & Blalock Problem 7.62.
5. Jaeger & Blalock Problem 7.64.
6. Jaeger & Blalock Problem 7.73.
7. Jaeger & Blalock Problem 7.95. Calculate using the method taught in class ($\Delta t = C\Delta V / I_{avg}$). If the current varies by more than a factor of 2, divide up voltage swing into multiple substeps. Compare to the method in text and Multisim simulation.
8. Jaeger & Blalock Problem 7.116.