
EE 331 Devices and Circuits I

Lecture 1

March 31, 2014

Four Main Topics

(Welcome to the Real World!)

- Physics of conduction in semiconductors (Chap 2)
- Solid-state diodes – physics, applications, and analysis (Chap 3)
- Field effect transistors (FETs) – physics, applications and analysis (Chap 4)
- Logic circuit design (Chap 6,7)

Links

- Class Webpage:

<http://dunham.ee.washington.edu/ee331/>


- Class discussion board:

<https://catalyst.uw.edu/gopost/board/dunham/36452/>

Announcements

- No lab in this week!
- HW0 to be posted online this afternoon.
- Multisim tutorial this week (see GoPost)

What is electronics?

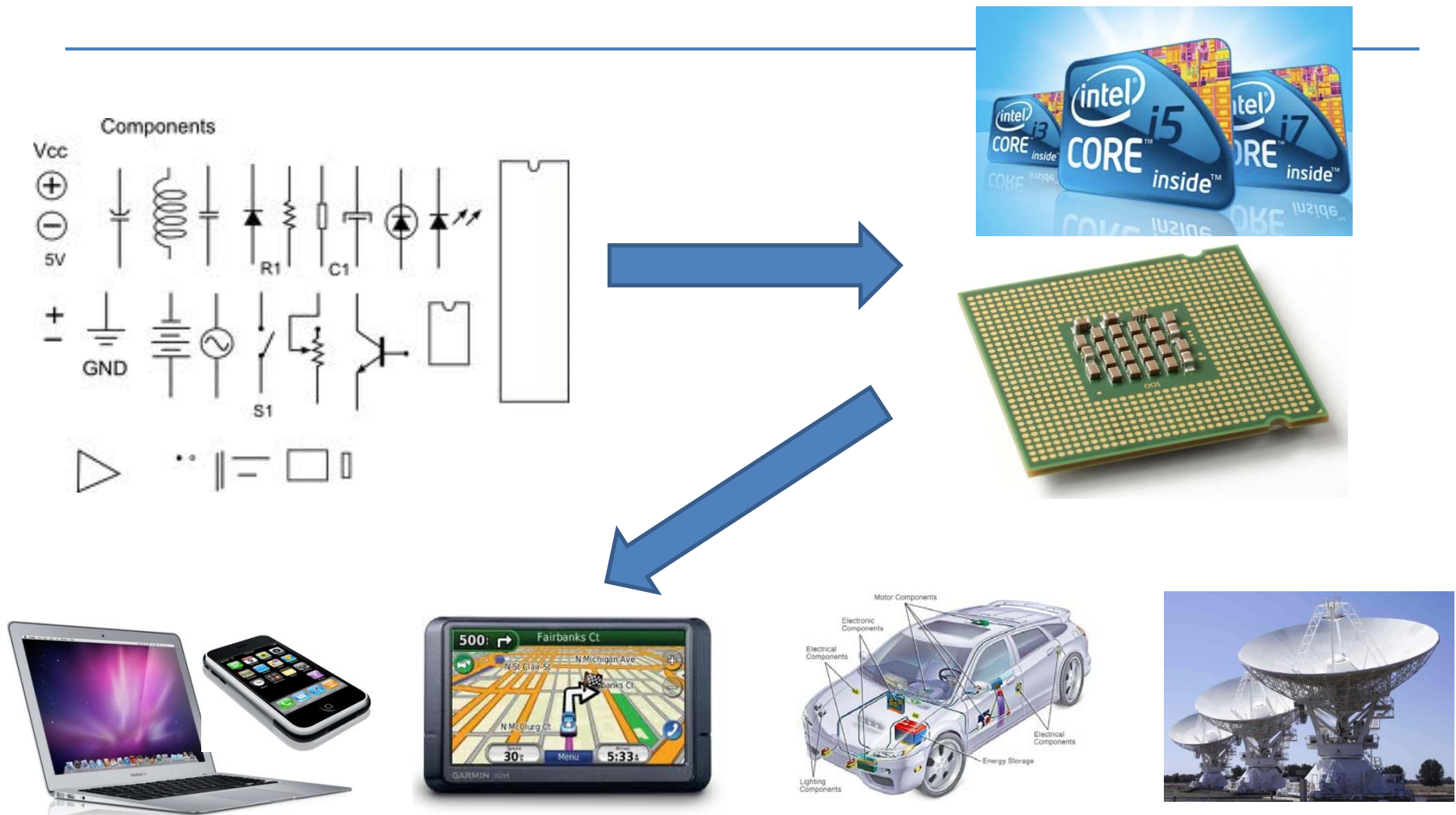

Evolution of Electronic Devices

Vacuum
Tubes



(a)

Discrete
Transistors



(b)

Integrated
Circuits



(c)

Surface-Mount
Circuits




(d)


Transistors and Moore's Law

- Transistor: The fundamental building block of modern electronic devices.
- Moore's Law: the number of transistor that can be placed inexpensively on an integrated circuit die **doubles** every 18 months.

Transistors and Moore's Law

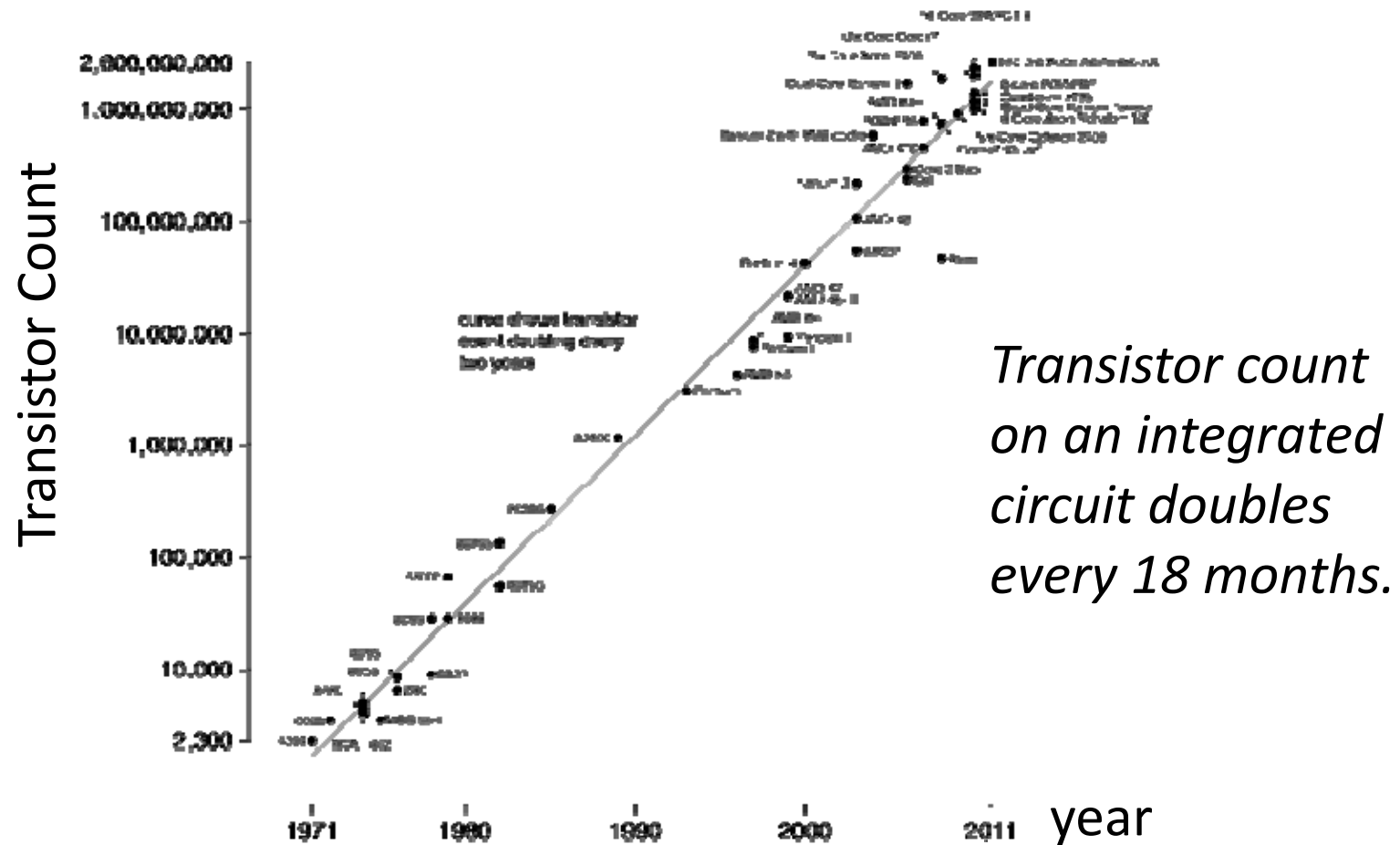


Minimum Feature Size

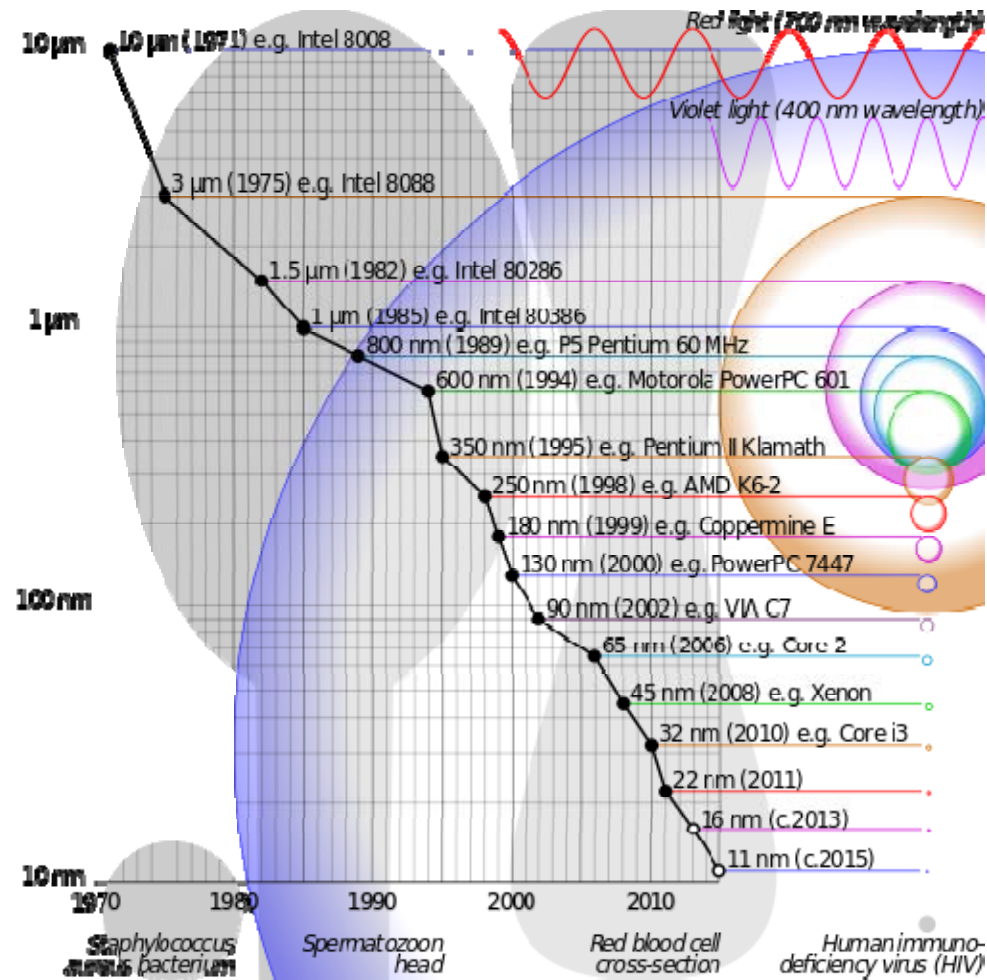


32 nm technology (2010)

- Intel's Core i3, i5, i7 processors

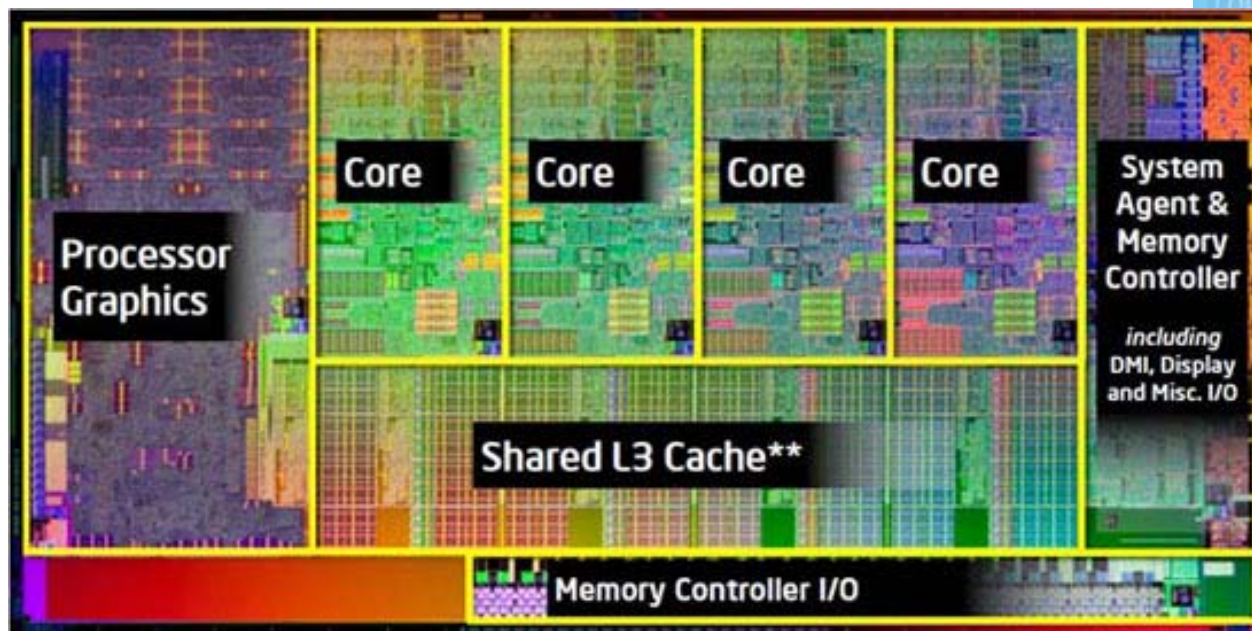

22/14 nm technology (2011/14)

- Intel's 3D Tri-gate transistor

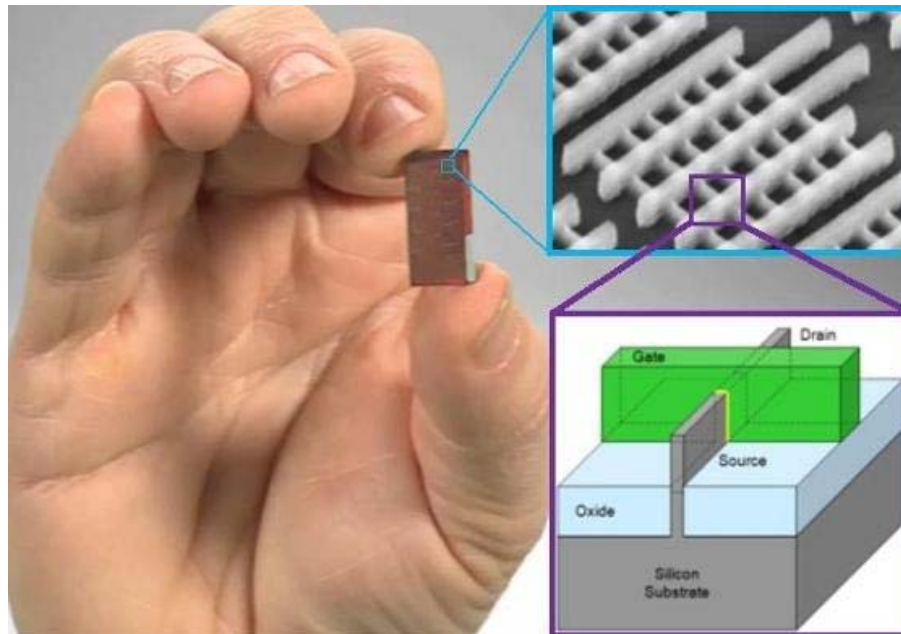

- Check this video:

<http://www.youtube.com/watch?v=7xANivRKuGI>

About electronics ...

- Electronics is everywhere
- A field at the leading edge of technology, with rapid rate of progress
- Pushes the limits in speed, degree of integration, automation ...

Where do we start?

- Materials => Devices => Circuits
- We already know about passive **linear** components: resistors, capacitors, inductors
- We will learn about new **nonlinear** components: **diodes, field effect transistors**
- We will use them to design and build circuits

After this course, you'll be able to ...

- **Calculate** conduction properties of materials and simple device structures
- **Explain** the operating principles of semiconductor diodes and FETs
- **Determine** the in-circuit operating state of diodes and FETs
- **Perform** large signal analysis of circuits containing diodes and FETs
- **Use** a modern schematic capture and computer-aided circuit analysis program (SPICE)
- **Calculate** the performance parameters for different MOS logic families to design and build circuits

EE 331 Devices and Circuits I


Chapter 1

Circuit Review

Circuit Theory Review

- Starting point:
 - Ohm's Law (OL)
 - Kirchhoff's voltage law (KVL)
 - Kirchhoff's current law (KCL)
- Derive:
 - Voltage Division
 - Current Division
 - Thevenin Equivalent Circuits
 - Norton Equivalent Circuits

Voltage Division

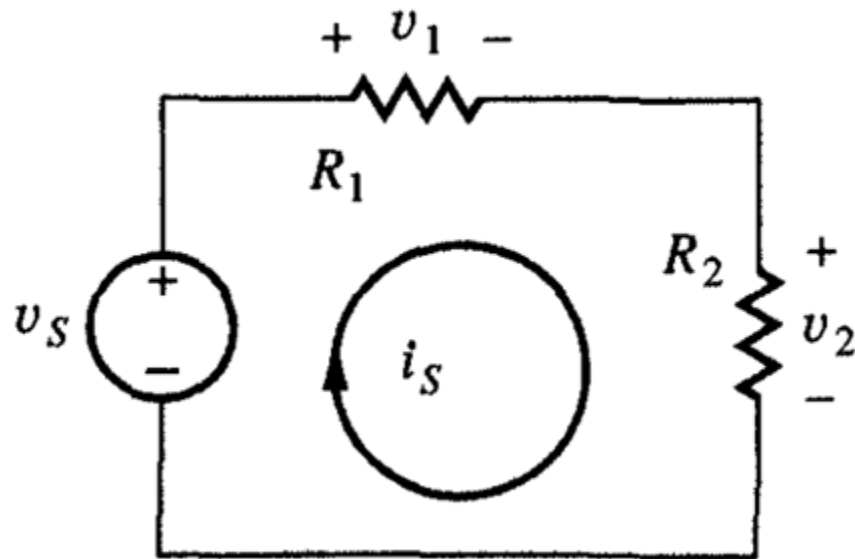

$$\text{OL: } v_1 = i_s R_1$$

$$\text{OL: } v_2 = i_s R_2$$


$$\begin{aligned} \text{KVL: } v_s &= v_1 + v_2 \\ &= i_s (R_1 + R_2) \end{aligned}$$



$$v_1 = v_s \frac{R_1}{R_1 + R_2}$$

$$v_2 = v_s \frac{R_2}{R_1 + R_2}$$

Current Division

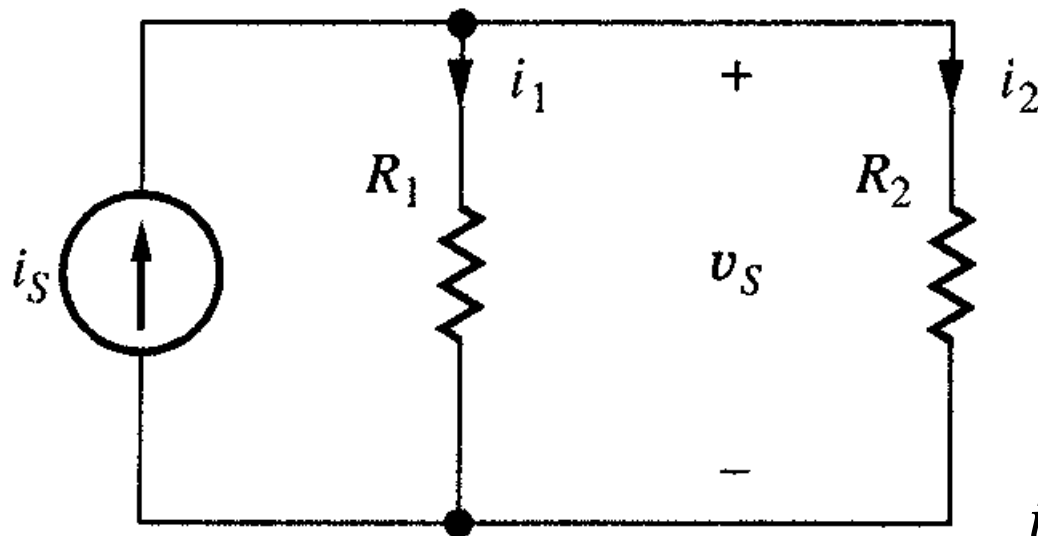

$$\text{OL: } i_1 = \frac{v_S}{R_1}$$

$$\text{OL: } i_2 = \frac{v_S}{R_2}$$

$$\begin{aligned} \text{KCL: } i_S &= i_1 + i_2 \\ &= \frac{v_S}{R_1} + \frac{v_S}{R_2} = \frac{v_S}{(R_1 || R_2)} \end{aligned}$$




$$i_1 = i_S \frac{R_1 || R_2}{R_1} = i_S \frac{R_2}{R_1 + R_2}$$


$$i_2 = i_S \frac{R_1 || R_2}{R_2} = i_S \frac{R_1}{R_1 + R_2}$$

Thevenin Equivalent Circuits

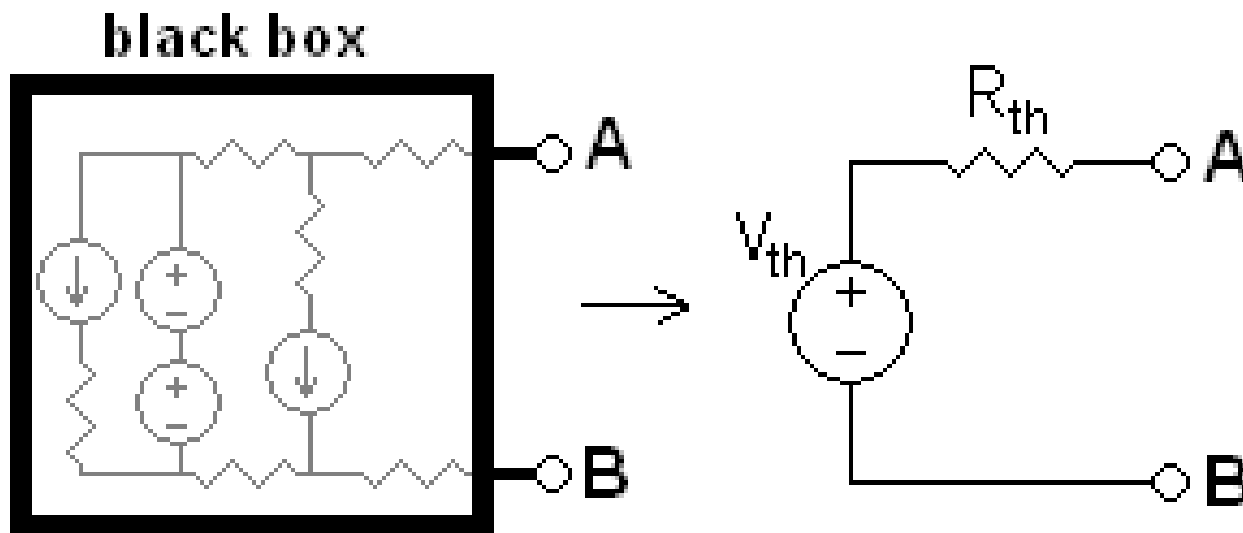- Voltage source V_{Th} is the **open circuit** voltage at the output terminals
- R_{Th} : equivalent resistance present at the output terminals with all **independent** sources **set to zero**



Thevenin Equivalent Circuits (e.g. 1)

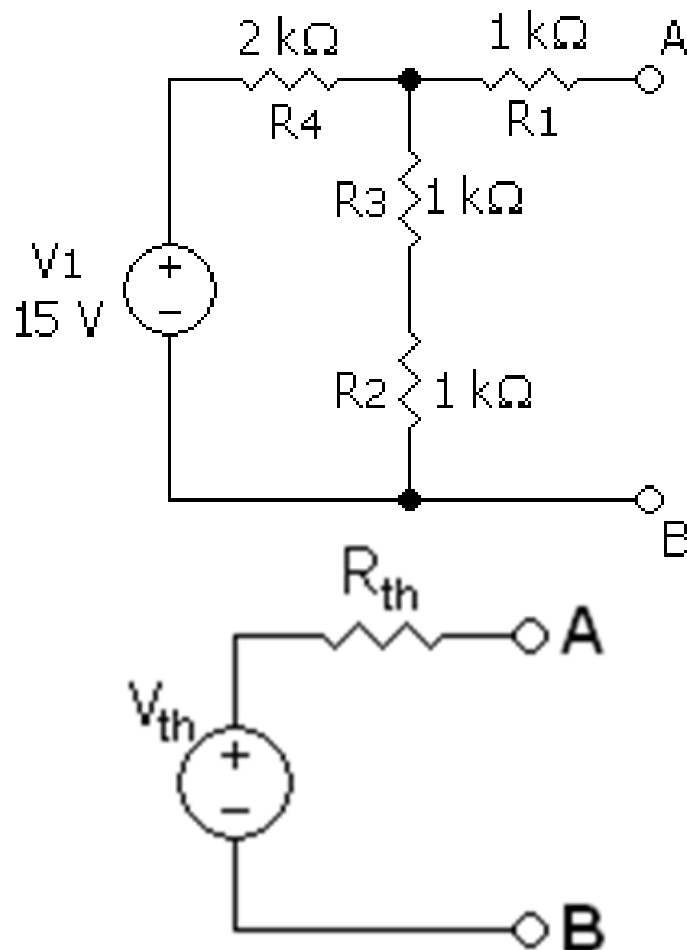


Open circuit voltage:

$$V_{Th} = V_{23} \quad \text{voltage division}$$
$$= V_1 \frac{R_4}{R_4 + R_2 + R_3} = 7.5 \text{ V}$$

Set V_1 to zero.

$$R_{Th} = R_1 + R_4 || (R_2 + R_3)$$
$$= 1 \text{ k}\Omega + 2 \text{ k}\Omega || 2 \text{ k}\Omega = 2 \text{ k}\Omega$$

Thevenin Equivalent Circuits (e.g. 2)

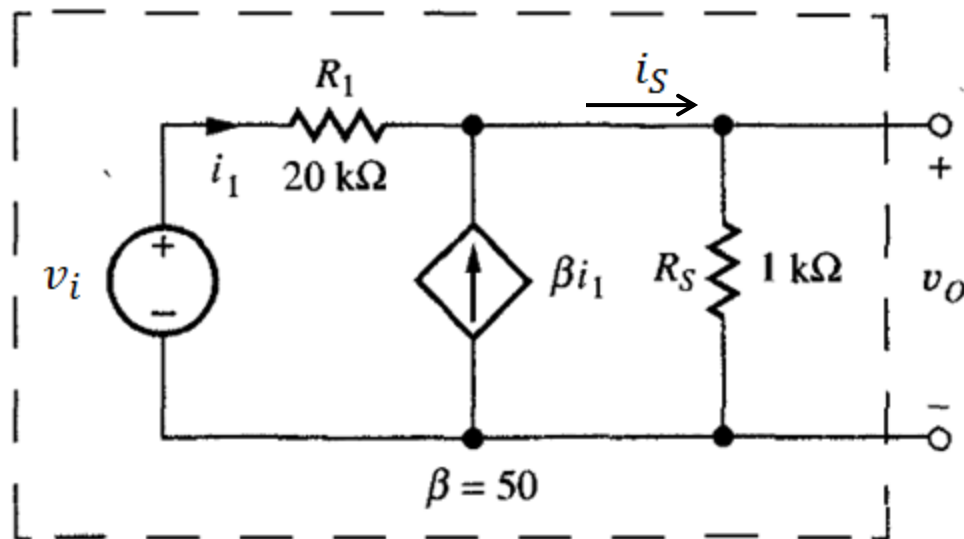

$$V_{Th} = i_S R_S$$

$$\text{KCL: } i_S = (1 + \beta)i_1$$


$$\Rightarrow V_{Th} = (1 + \beta)i_1 R_S$$

KVL:


$$v_i = i_1 R_1 + (1 + \beta)i_1 R_S$$


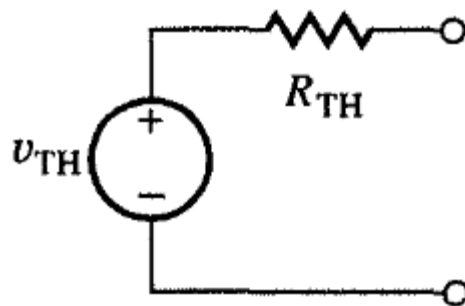
$$V_{Th} = v_i \frac{(1 + \beta)R_S}{R_1 + (1 + \beta)R_S}$$



Thevenin Equivalent Circuits (e.g. 2)

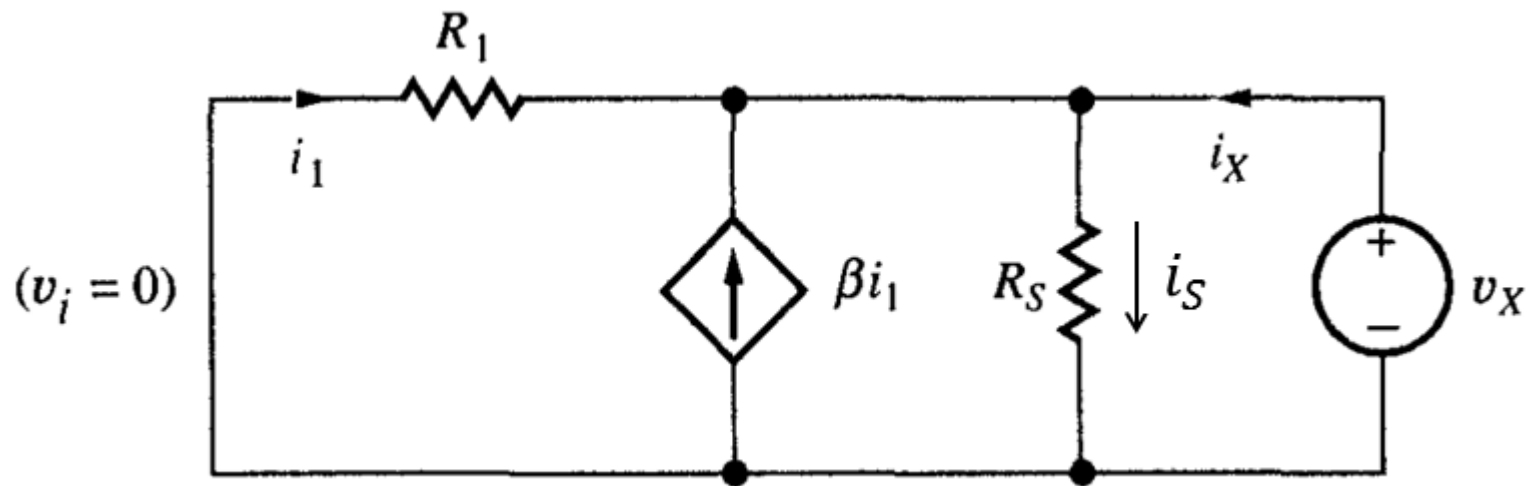

$$\text{KVL: } v_X = -i_1 R_1; v_X = i_S R_S$$


$$\text{KCL: } i_S = i_X + (1 + \beta) i_1$$

$$\Rightarrow v_X = [i_X + (1 + \beta) i_1] R_S = \left[i_X - (1 + \beta) \frac{v_X}{R_1} \right] R_S$$


$$\Rightarrow R_{Th} = \frac{v_X}{i_X} = v_S \frac{R_S}{1 + (1 + \beta) R_S / R_1}$$

Norton Equivalent Circuits

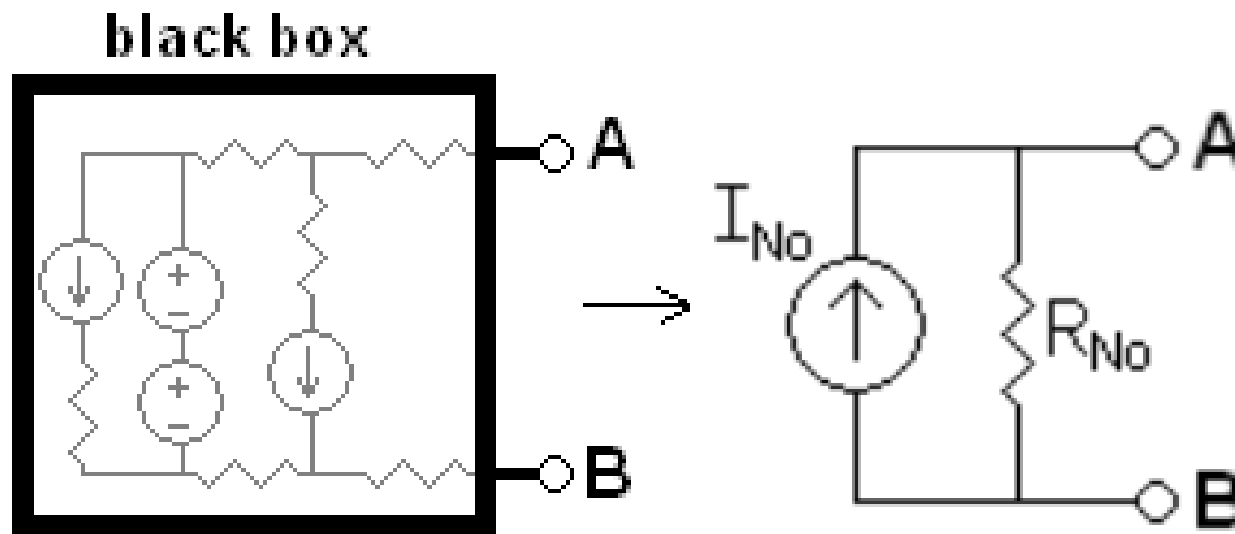- I_{No} : current coming out of the network when terminals are **shorted**
- R_{No} : equivalent resistance present at the output terminals with all **independent** sources **set to zero** ($R_{No} = R_{Th}$)



Norton Equivalent Circuits (e.g. 1)

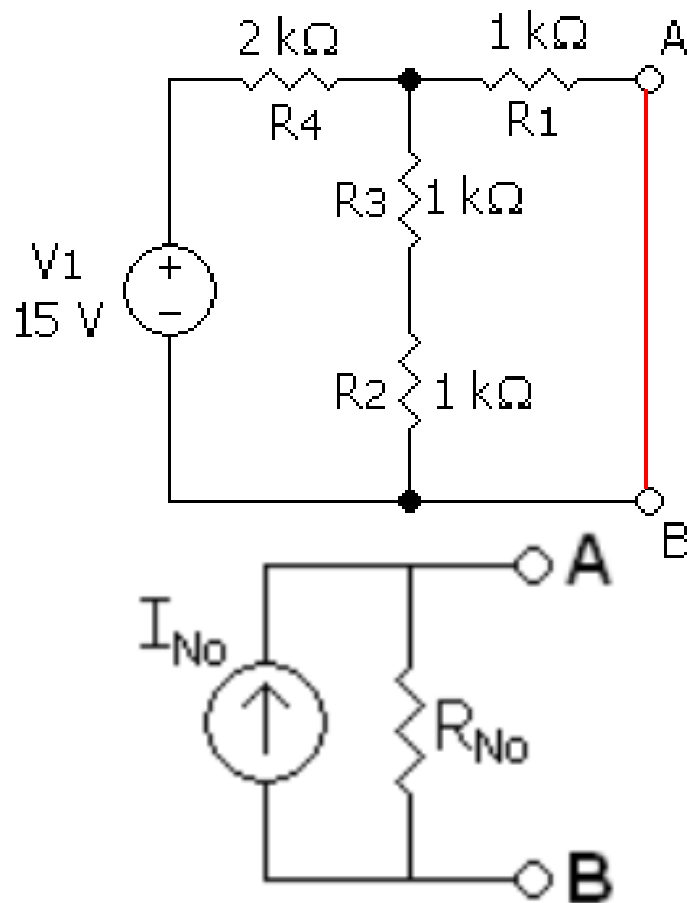

$$i_{tot} = \frac{V_1}{R_{tot}} = \frac{V_1}{R_4 + R_1 || (R_2 + R_3)} = 5.63 \text{ mA}$$

Short Circuit current:




$$I_{No} = i_{tot} \frac{R_2 + R_3}{R_2 + R_3 + R_4} = 3.75 \text{ mA}$$

current division

Set V_1 to zero.

$$R_{No} = R_1 + R_4 || (R_2 + R_3) \\ = 1 \text{ k}\Omega + 2 \text{ k}\Omega || 2 \text{ k}\Omega = 2 \text{ k}\Omega$$

Norton Equivalent Circuits (e.g. 2)

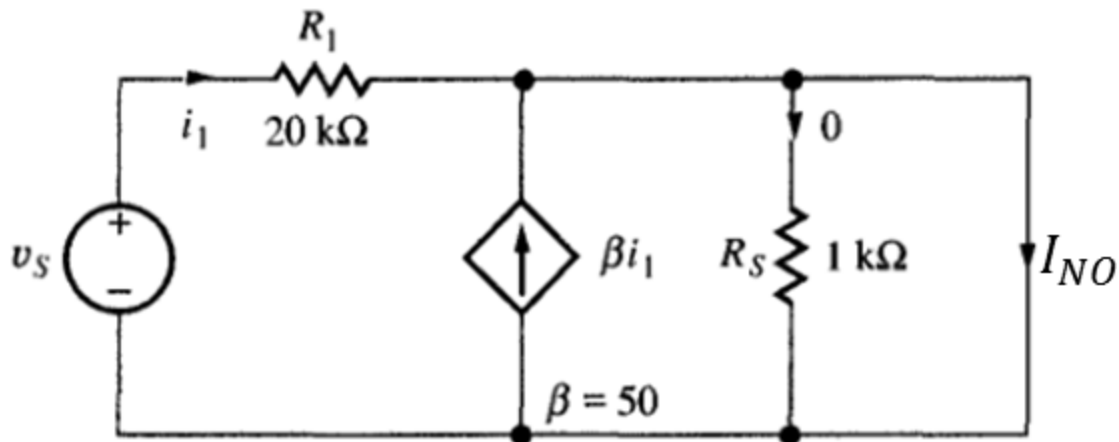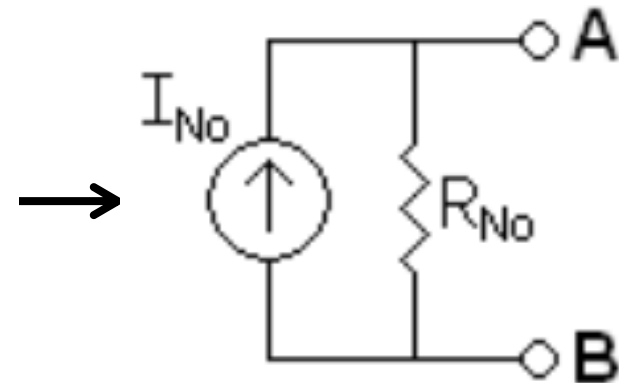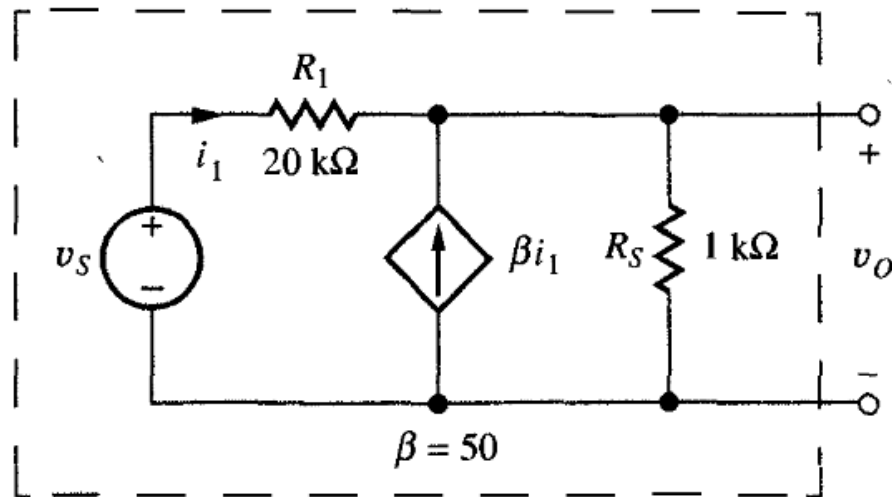

$$I_{No} = (1 + \beta)i_1$$

$$= (1 + \beta)v_S/R_1$$

R_{No} is the same as R_{Th} in Thevenin equivalent circuits

$$V_{Th} = I_{No}R_{Th}$$