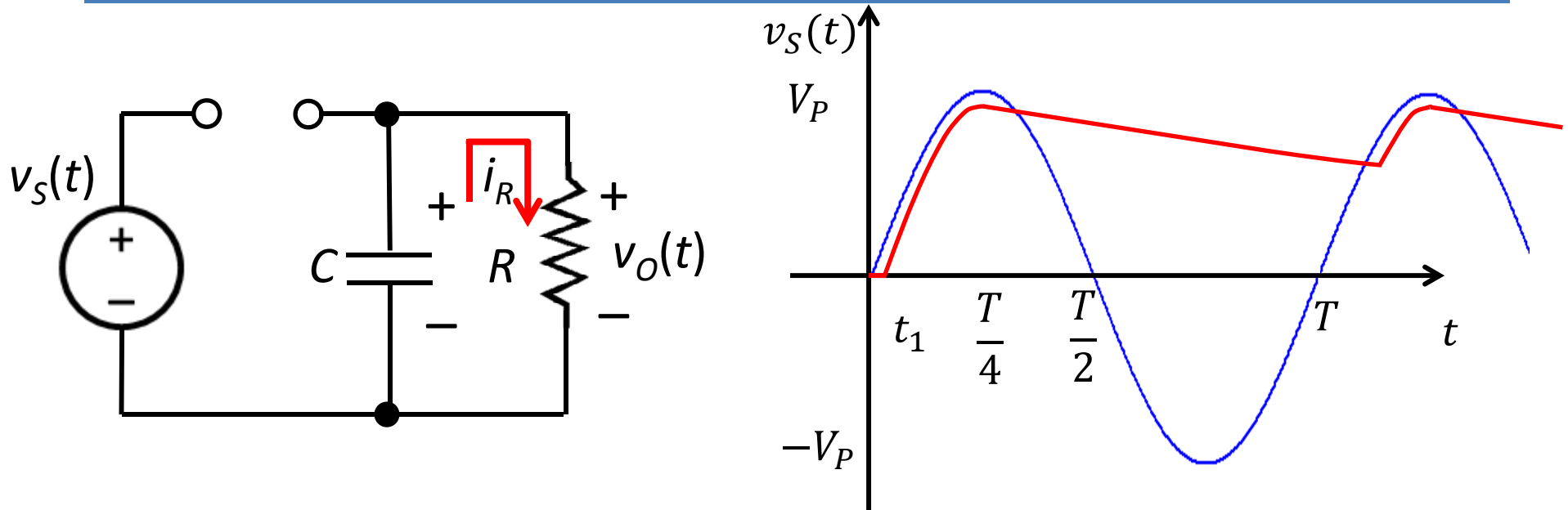


Announcements


- HW #2 due today.

Half-wave rectifier w/ RC Load



After $t = T/4$, diode OFF, capacitor discharge via R , $v_O(t)$ slowly decreases (exponentially), until in the next period, $v_S(t)$ becomes larger than $v_O(t) + V_{on}$ again

Half-wave rectifier w/ RC Load

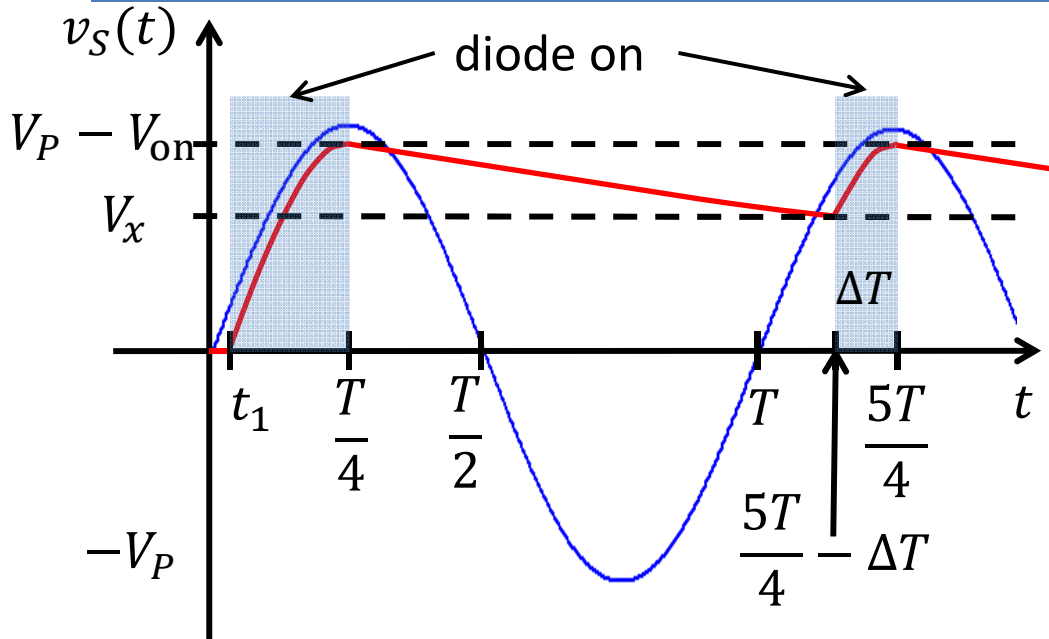


- At $t = \frac{T}{4}$, $v_O(t) = V_P - V_{on}$
- Between $\frac{T}{4} < t < \frac{5T}{4} - \Delta T$, $v_O(t)$ drops exponentially:

$$v_o(t) = v_o\left(\frac{T}{4}\right) \exp\left(-\frac{t - \frac{T}{4}}{RC}\right)$$

- At time point $t = \frac{5T}{4} - \Delta T$, we have, $v_S(t) = v_O(t) + V_{on}$
- Thus: $V_P \sin \omega(T/4 - \Delta T) = (V_P - V_{on}) \exp\left(-\frac{T-\Delta T}{RC}\right) + V_{on}$
- ΔT can be solved numerically.

Half-wave rectifier w/ RC Load

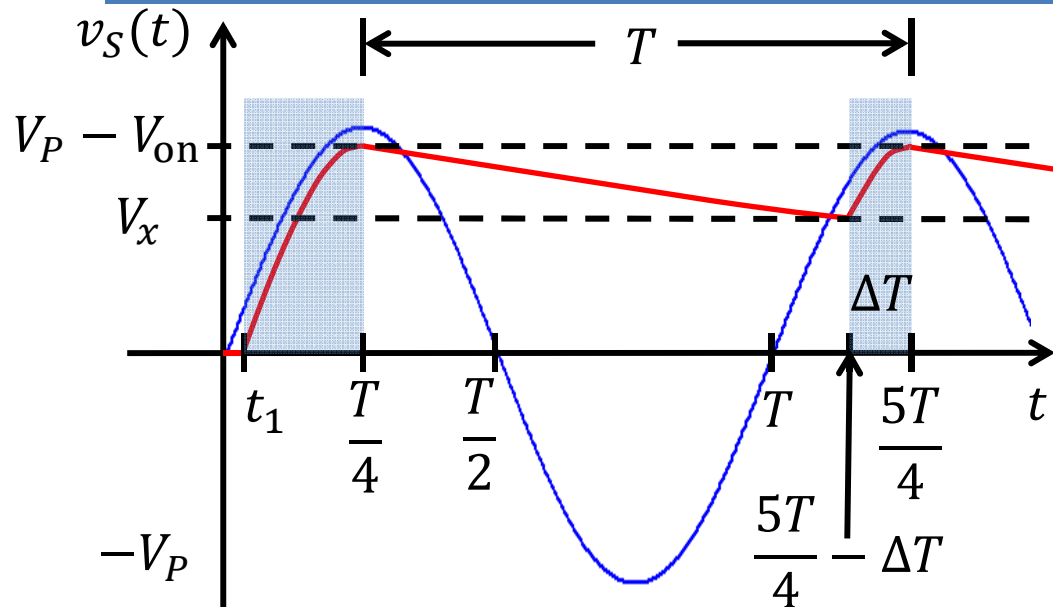

- Approx #1: RC large, $v_O(t)$ drops slowly and thus **linearly**:


- Between $\frac{T}{4} < t < \frac{5T}{4} - \Delta T$,

$$v_O(t) = (V_P - V_{on}) \left(1 - \frac{t - \frac{T}{4}}{RC} \right)$$

$$\exp(\epsilon) \cong 1 + \epsilon \text{ if } \epsilon \ll 1 \text{ (} T \ll RC \text{)}$$

- Approx #2: Conduction time ΔT much smaller than T ($\Delta T \ll T$)
- **Ripple voltage:** $V_r = v_O\left(\frac{T}{4}\right) - v_O\left(\frac{5T}{4} - \Delta T\right) \approx \frac{V_P - V_{on}}{RC} T$
- **Equivalent DC current:** $I_{dc} = \frac{V_P - V_{on}}{R}$


Half-wave rectifier w/ RC Load

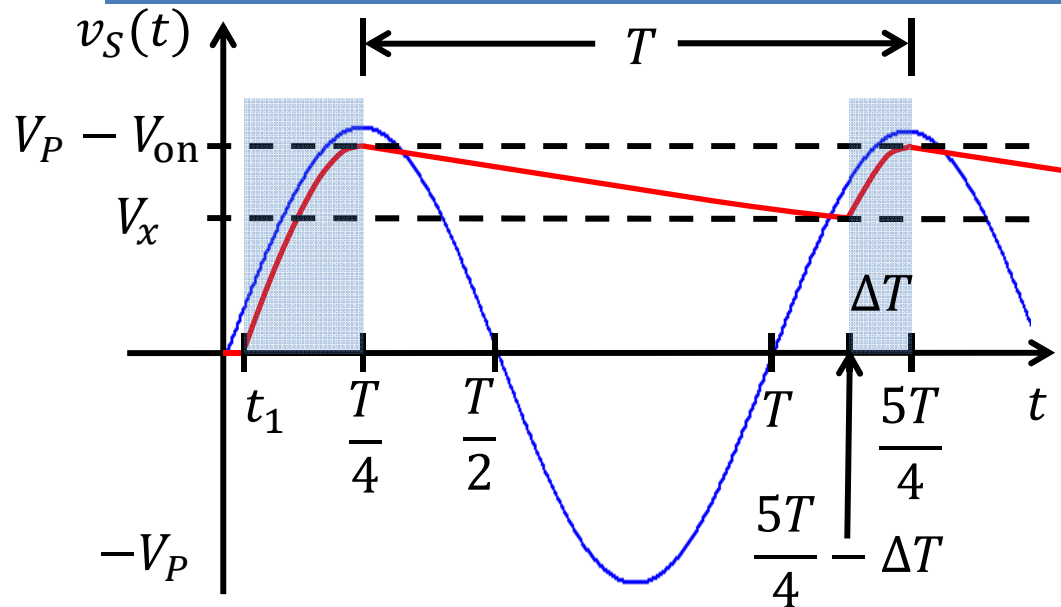

- To Find ΔT , look at time point $t_2 = \frac{5T}{4} - \Delta T$:
- $v_S(t_2) - V_{on} = V_x$

- $V_x = V_P - V_{on} - V_r = (V_P - V_{on})\left(1 - \frac{T}{RC}\right)$ ①
- $V_x = V_P \sin \omega \left(\frac{5T}{4} - \Delta T\right) - V_{on} = V_P \cos \omega \Delta T - V_{on} \approx V_P \left(1 - \frac{[\omega \Delta T]^2}{2}\right) - V_{on}$ ②
- ① = ② $\Rightarrow \Delta T = \frac{1}{\omega} \sqrt{\frac{2V_r}{V_P}} \Rightarrow$ conduction angle: $\theta_c = \omega \Delta T = \sqrt{\frac{2V_r}{V_P}}$

Diode Currents

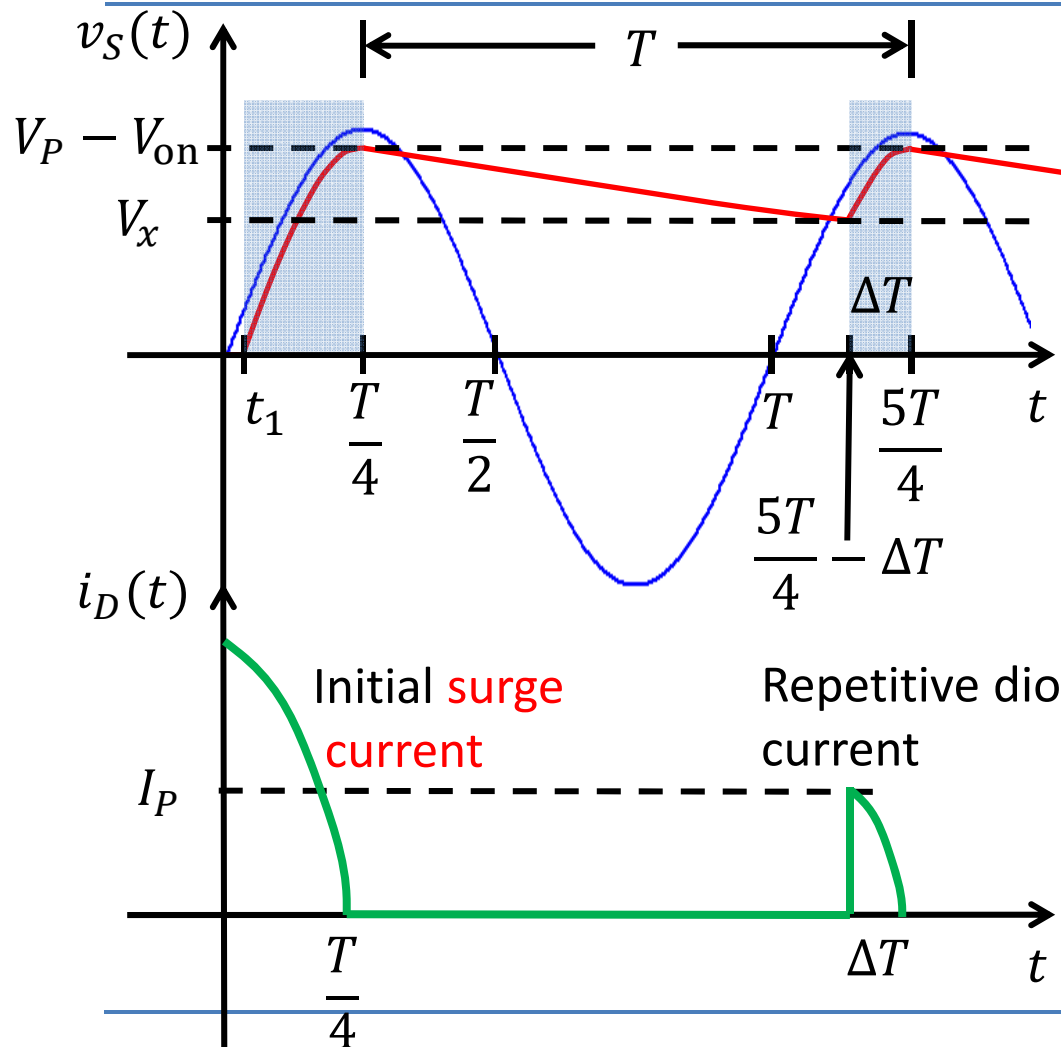

- Charge lost due to discharging replenished by charging current during ΔT :

$$Q = I_{dc}T \approx I_P \frac{\Delta T}{2}$$

$$\Rightarrow I_P \approx I_{dc} \frac{2T}{\Delta T}$$


I_P usually large (tens of A!)

- Initial surge current even larger (> 100 A!)

$$I_{SC} = \omega C V_P$$

Series resistances reduce this current

Diode Peak-Inverse-Voltage (PIV) Rating

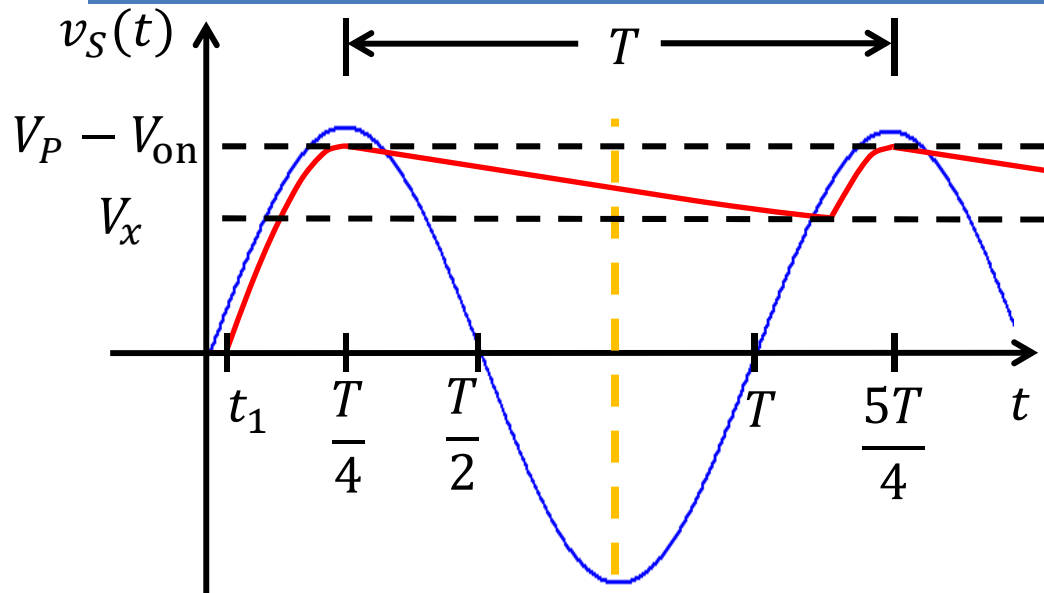

Worse case situation for
reverse biasing the diode


- $PIV \geq V_{dc} - v_I^{\min} = V_P - V_{on} - (-V_P) \approx 2V_P$

PIV corresponds to the minimum value of Zener breakdown voltage for the rectifier diode.

Safety margin of 25-50 % is usually specified for the diode PIV.

$$V_Z > (1 + SM)2V_P$$

Example: HWR w/ RC Load

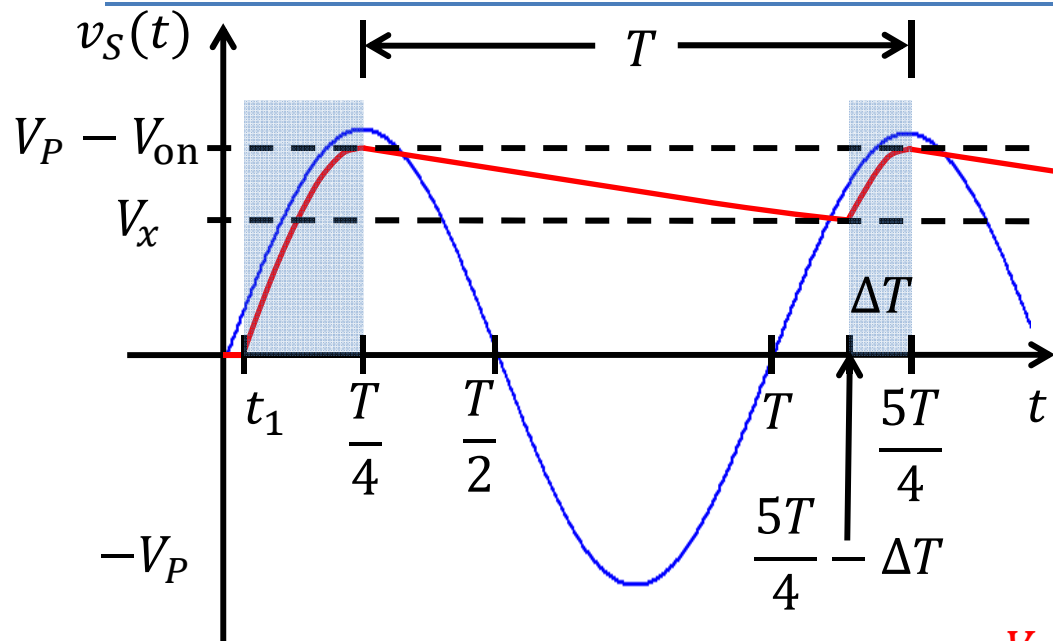

$V_P \approx 12 \text{ V @ } 60 \text{ Hz,}$
 $R = 5 \text{ k}\Omega, C = 100 \mu\text{F}, I_s = 10 \text{ pA}$
 $T = 1/60 \text{ s} = 0.0167 \text{ s}$
 $I_d \sim 0.1 \text{ A, } v_{\text{on}} \approx V_T \ln(10^{10}) = 0.6 \text{ V}$

$$V_r \approx \frac{V_P - V_{\text{on}}}{RC} T = 0.38 \text{ V}$$

- Equivalent DC current: $I_{dc} = \frac{V_P - V_{\text{on}}}{R} = 2.28 \text{ mA}$
- Conduction angle: $\theta_c = \omega \Delta T = \sqrt{\frac{2V_r}{V_P}} = 0.25 \text{ rad, } \Delta T = 0.04 T$
- $I_P \approx I_{dc} \frac{2T}{\Delta T} = 114 \text{ mA; } I_{SC} = \omega C V_P = 0.45 \text{ A}$