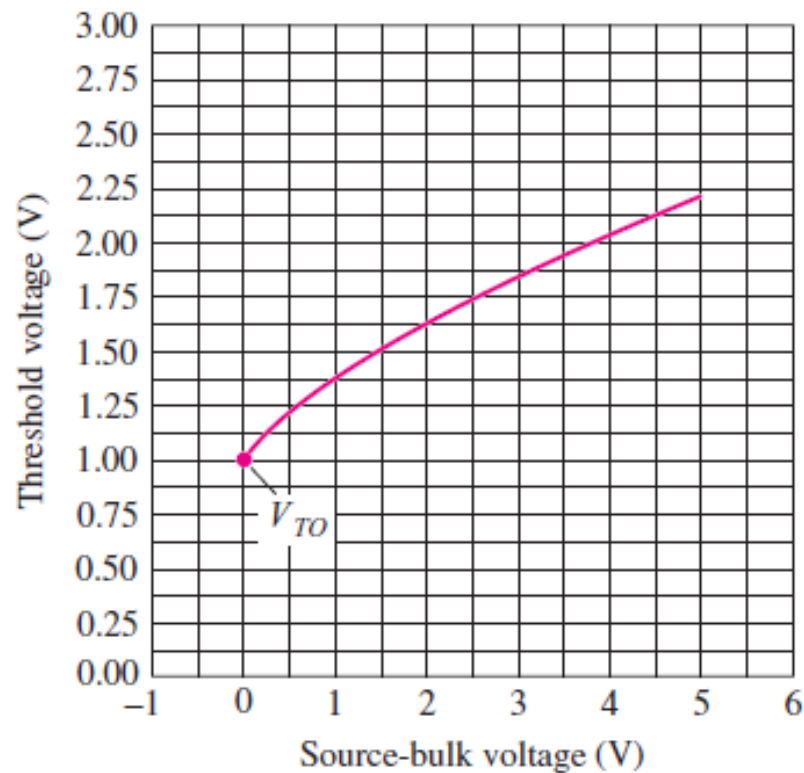


Announcements


- Exam 1 grading issues:
 - Write out the basis for your request for regrading and staple it to your exam.
 - Return to me by class on Tuesday.
 - Grades can either rise or fall on regrade (will look at whole problem).

Body Effect (Substrate Sensitivity)




$$V_{TN} = V_{TO} + \gamma(\sqrt{v_{SB} + 2\phi_F} - \sqrt{2\phi_F})$$

Body Effect (Substrate Sensitivity)

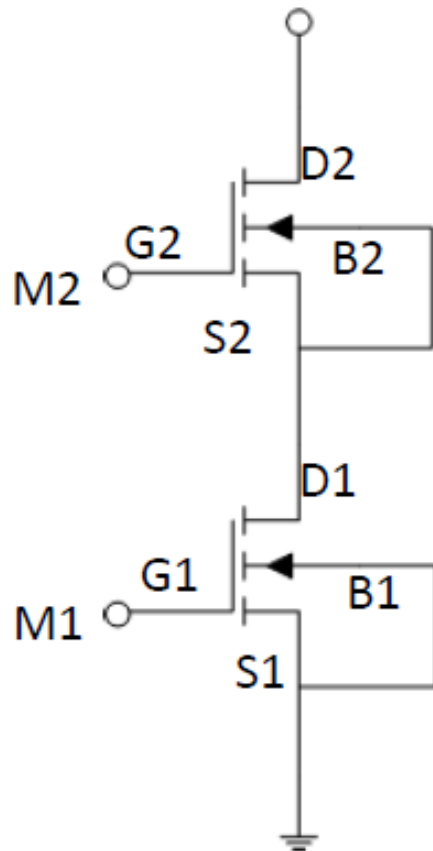


- Transistor M1: S1 and B1 tied together, $v_{SB1} = 0$. No Body effect
- Same as Transistor M2.

Body Effect (Substrate Sensitivity)

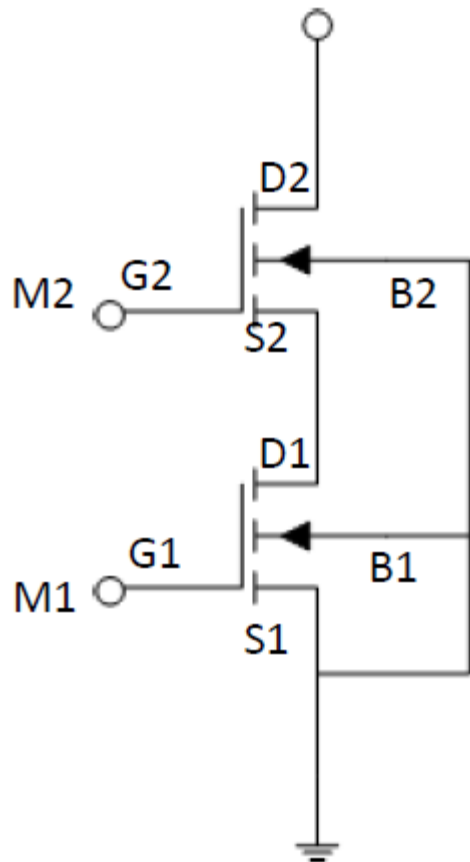

- Transistor M1: S1 and B1 tied together, $v_{SB1} = 0$.
No Body effect
- Transistor M2:
 $v_{B2} = 0$, $v_{S2} = v_{D1} \neq 0$
 $v_{SB2} \neq 0$. Body effect exists!

MOSFET Circuit Analysis (e.g. 1)

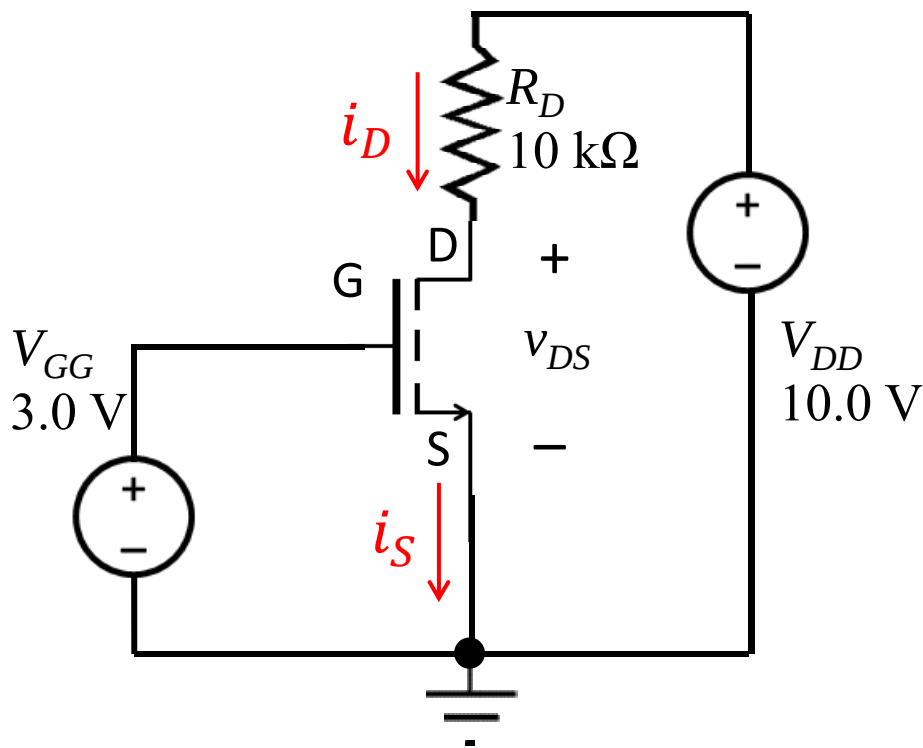

Known: NMOS, $V_{TO} = 1.0 \text{ V}$, $\lambda = 0$, $K'_n = 25 \mu\text{A}/\text{V}^2$, $\frac{W}{L} = 10$

Solve: Q-point (i_D , v_{DS})


- **First determine threshold voltage:**

Since $v_{SB} = 0$, so no body effect.
 $V_{TN} = V_{TO} = 1.0 \text{ V}$

- **Step #1: Guess operation region.**

$v_{GS} = 3.0 \text{ V} > V_{TN}$, $V_{DD} = 10 \text{ V}$,
guess ON and saturation.

MOSFET Circuit Analysis (e.g. 1)

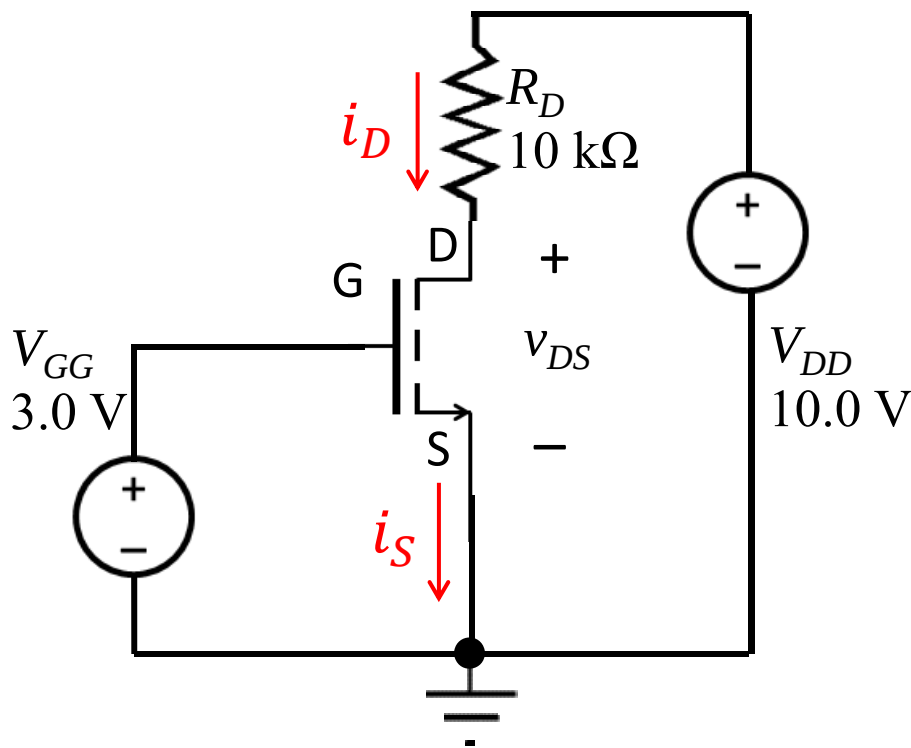

- Step #2: Use proper equation

$$i_D = \frac{K'_n}{2} \frac{W}{L} (v_{GS} - V_{TN})^2$$

- Step #3: Solve the circuit

$$i_D = \frac{K'_n}{2} \frac{W}{L} (v_{GS} - V_{TN})^2 = \frac{25 \mu\text{A}}{2} \cdot 10 \cdot (3 - 1)^2 \text{V}^2 = 500 \mu\text{A}$$

$$v_{DS} = V_{DD} - i_D \cdot R_D = 10 \text{ V} - 500 \mu\text{A} \cdot 10 \text{ k}\Omega = 5 \text{ V}$$


- Step #4: Double check

$v_{DS} > v_{GS} - V_{TN} = 2 \text{ V} \Rightarrow$
Saturation. Correct!

Q-point: (500 μA , 5.0 V)

MOSFET Circuit Analysis (e.g. 1')

Now R_D changes to 50 k Ω

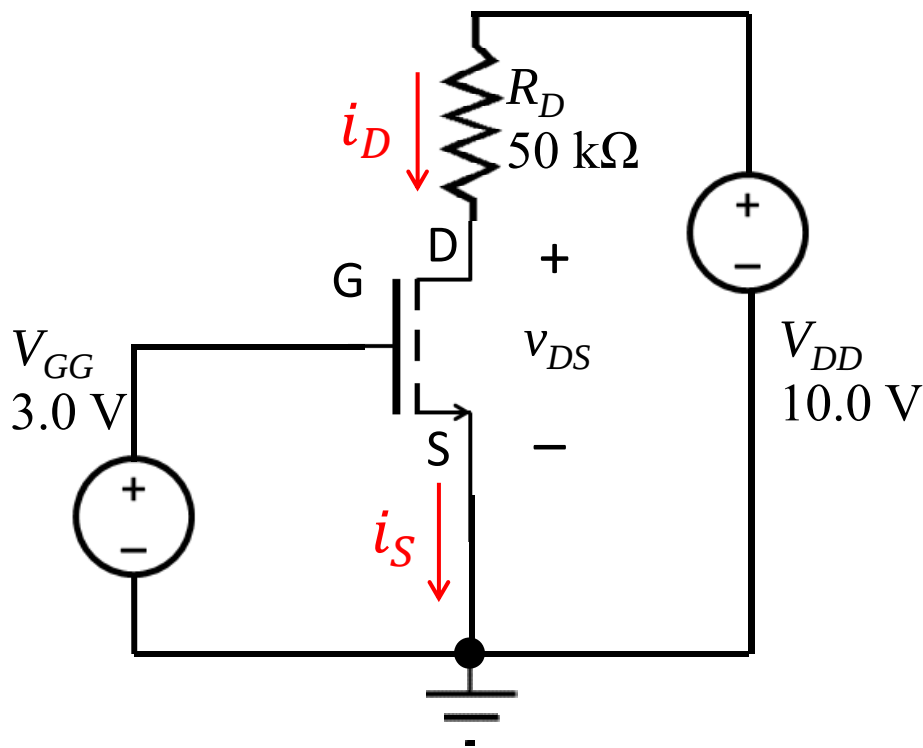

Known: NMOS, $V_{TO} = 1.0 \text{ V}$, $\lambda = 0$, $K'_n = 25 \mu\text{A}/\text{V}^2$, $\frac{W}{L} = 10$

Solve: Q-point (i_D , v_{DS})


- **First determine threshold voltage:**

Since $v_{SB} = 0$, so body effect.
 $V_{TN} = V_{TO} = 1.0 \text{ V}$

- **Step #1: Guess operation region.**

$v_{GS} = 3.0 \text{ V} > V_{TN}$, $V_{DD} = 10 \text{ V}$,
guess ON and saturation.

MOSFET Circuit Analysis (e.g. 1')

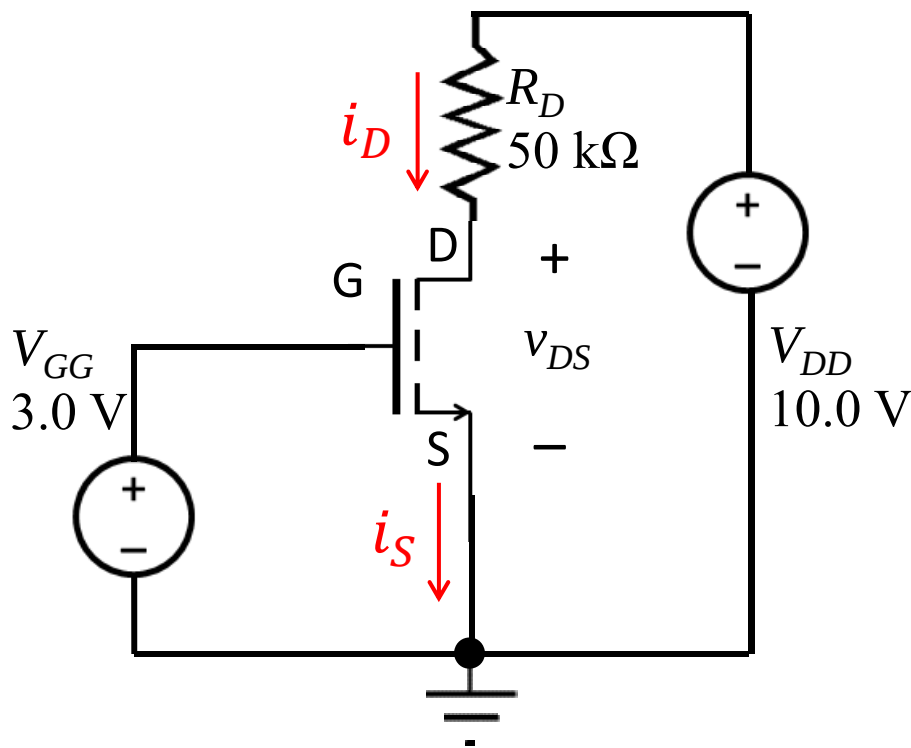

- Step #2: Use proper equation

$$i_D = \frac{K'_n}{2} \frac{W}{L} (v_{GS} - V_{TN})^2$$

- Step #3: Solve the circuit


$$i_D = \frac{K'_n}{2} \frac{W}{L} (v_{GS} - V_{TN})^2 = \frac{25 \mu\text{A}}{2} \cdot 10 \cdot (3 - 1)^2 \text{V}^2 = 500 \mu\text{A}$$

$$v_{DS} = V_{DD} - i_D \cdot R_D = 10 \text{ V} - 500 \mu\text{A} \cdot 50 \text{ k}\Omega = -15 \text{ V}$$

- Step #4: Double check

$v_{DS} < v_{GS} - V_{TN} = 2 \text{ V} \Rightarrow$ NOT in saturation. Wrong guess!

MOSFET Circuit Analysis (e.g. 1')

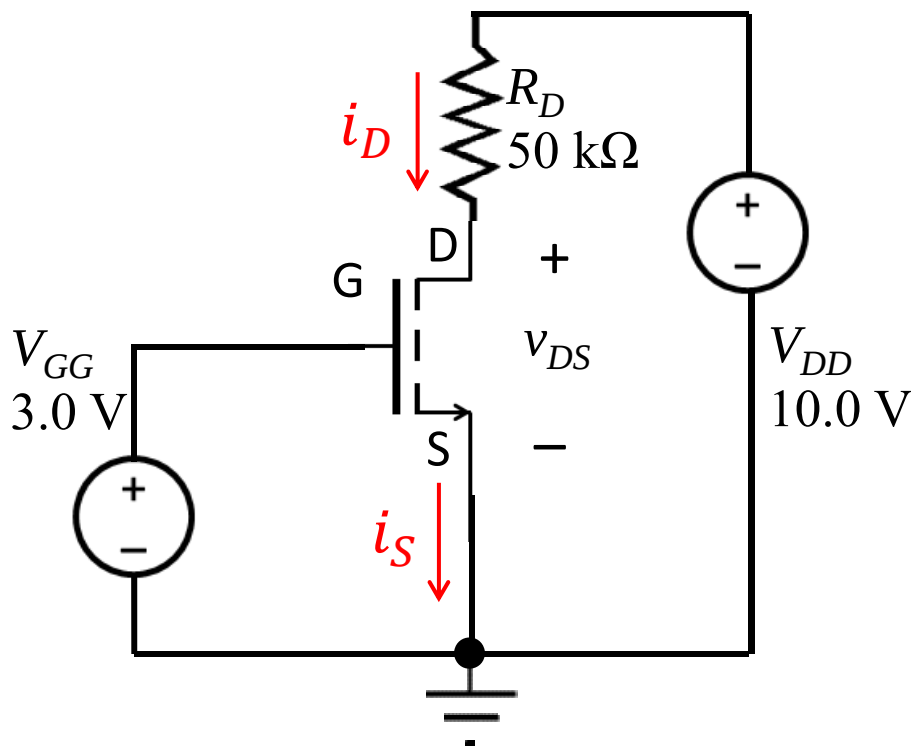

- Guess ON and triode.

$$i_D = K'_n \frac{W}{L} \left(v_{GS} - V_{TN} - \frac{v_{DS}}{2} \right) v_{DS} \quad (1)$$

- KVL: $v_{DS} = V_{DD} - i_D R_D \Rightarrow i_D = \frac{V_{DD} - v_{DS}}{R_D}$ (2)

- Eliminating i_D using (1) (2), and plugging in numbers, we get

$$25v_{DS}^2 - 104v_{DS} + 40 = 0$$

- Solving the quadratic equation:

$$v_{DS} = 0.43 \text{ V or } 3.73 \text{ V}$$


- Triode region:

$$v_{GS} > v_{DS} + V_{TN} \Rightarrow v_{DS} < 2 \text{ V}$$

- Thus $v_{DS} = 0.43 \text{ V}$, $i_D = \frac{10 - 0.43 \text{ V}}{50 \text{ k} \Omega} = 191 \mu\text{A}$

Q-point: (191 μA , 0.43 V)

MOSFET Circuit Analysis (e.g. 2)

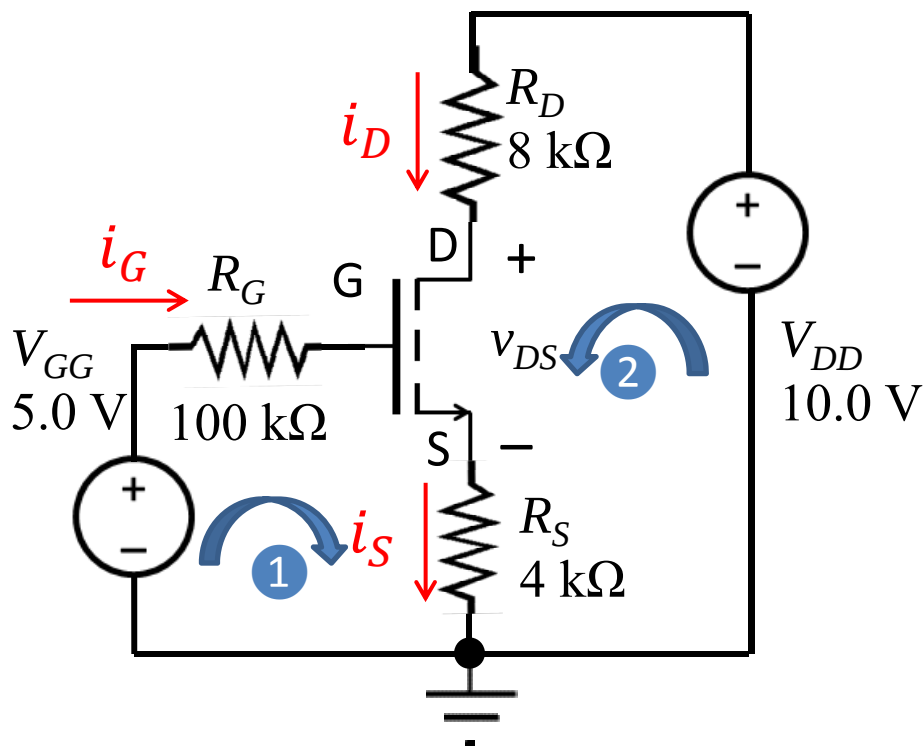

Known: NMOS, $V_{TO} = 1.0 \text{ V}$, $\lambda = 0$, $K'_n = 25 \mu\text{A}/\text{V}^2$, $\frac{W}{L} = 10$

Solve: Q-point (i_D , v_{DS})


- **First determine threshold voltage:** Since $v_{SB} = 0$, so body effect. $V_{TN} = V_{TO} = 1.0 \text{ V}$

- **Analyze circuit loops:**

Loop ①: $V_{GG} = i_G R_G + v_{GS} + i_S R_S = v_{GS} + i_S R_S$

Loop ②: $V_{DD} = i_D R_D + v_{DS} + i_S R_S$

MOSFET Circuit Analysis (e.g. 2)

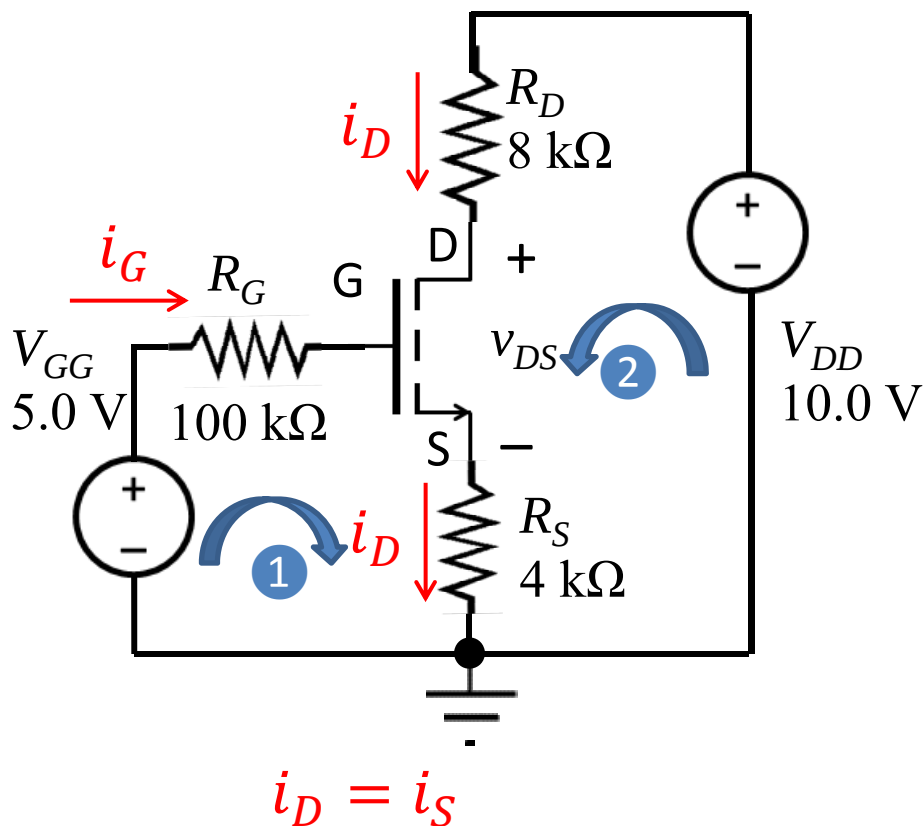

- **Guess: CUTOFF**
- $i_D = 0, v_{GS} = V_{GG} = 5\text{ V} > V_T = 1\text{ V}$
Not CUTOFF!
- **Guess: Saturation**

$$i_D = \frac{K'_n}{2} \frac{W}{L} (v_{GS} - V_{TN})^2 \quad (1)$$

$$v_{GS} = V_{GG} - i_D R_S \Rightarrow i_D = \frac{V_{GG} - v_{GS}}{R_S} \quad (2)$$


- Eliminating i_D using (1) (2), and plugging in numbers, we get

$$v_{GS}^2 - 9 = 0$$

- Solving the quadratic equation:

$$v_{GS} = 3\text{ V or } -3\text{ V}$$

MOSFET Circuit Analysis (e.g. 2)

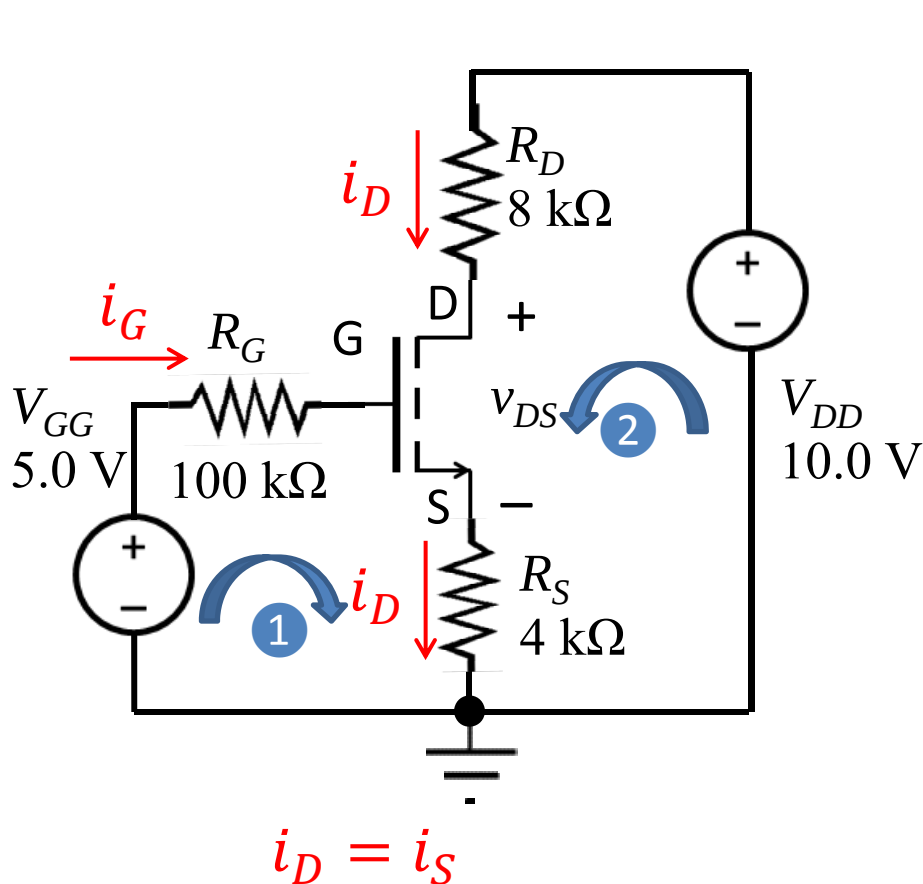

$$v_{GS} = 3 \text{ V or } \cancel{-3 \text{ V}}$$

$$i_D = \frac{(5-3)\text{V}}{4\text{k}\Omega} = 500 \mu\text{A}$$

$$v_{DS} = V_{DD} - i_D(R_D + R_S) = 4 \text{ V}$$

• Check:

$$v_{GS} = 3 \text{ V} > V_{TN} = 1 \text{ V}$$


$$v_{DS} = 4 \text{ V} > V_{GS} - V_{TN} = 2 \text{ V}$$

So, Saturation it is!

Q-point: ($i_D=500 \mu\text{A}$, $v_{DS}=4.0 \text{ V}$)

MOSFET Circuit Analysis (e.g. 2')

Now R_D changes to 16 k Ω

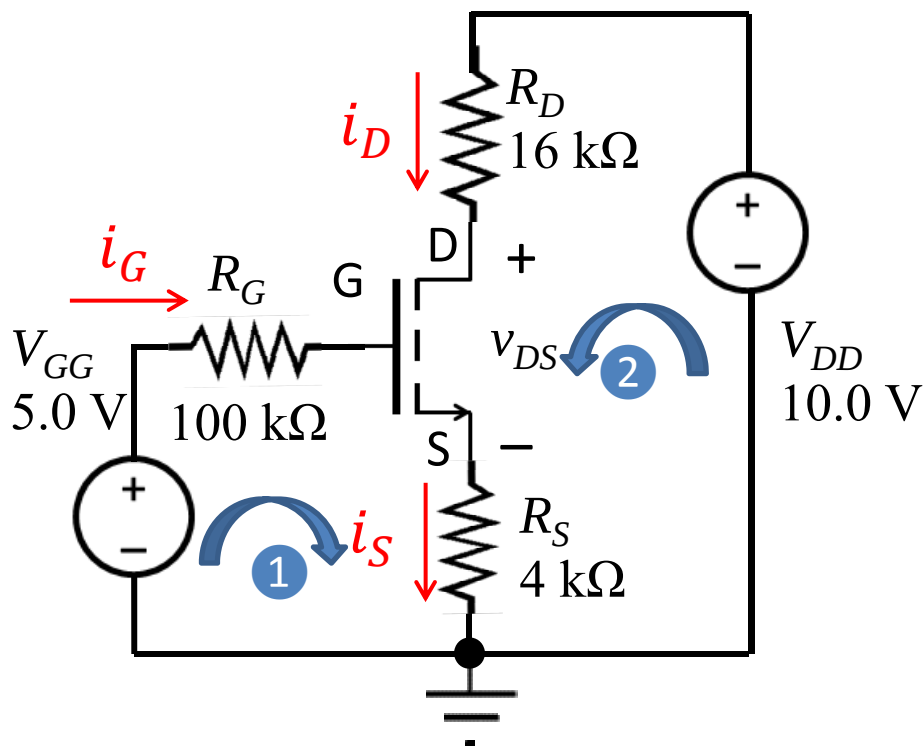

Known: NMOS, $V_{TO} = 1.0 \text{ V}$, $\lambda = 0$, $K'_n = 25 \mu\text{A}/\text{V}^2$, $\frac{W}{L} = 10$

Solve: Q-point (i_D , v_{DS})

- Everything would be the same until the last check for saturation:

$$v_{DS} = V_{DD} - i_D(R_D + R_S) \\ = 10\text{V} - 500\mu\text{A} \cdot 20\text{k}\Omega = 0\text{V}$$


$v_{DS} = 0 \text{ V} < V_{GS} - V_{TN} = 2 \text{ V}$. **Not in saturation.**

- Guess in triode:

$$i_D = K'_n \frac{W}{L} \left(v_{GS} - V_{TN} - \frac{v_{DS}}{2} \right) v_{DS} \quad (1)$$

MOSFET Circuit Analysis (e.g. 2')

Now R_D changes to 16 k Ω

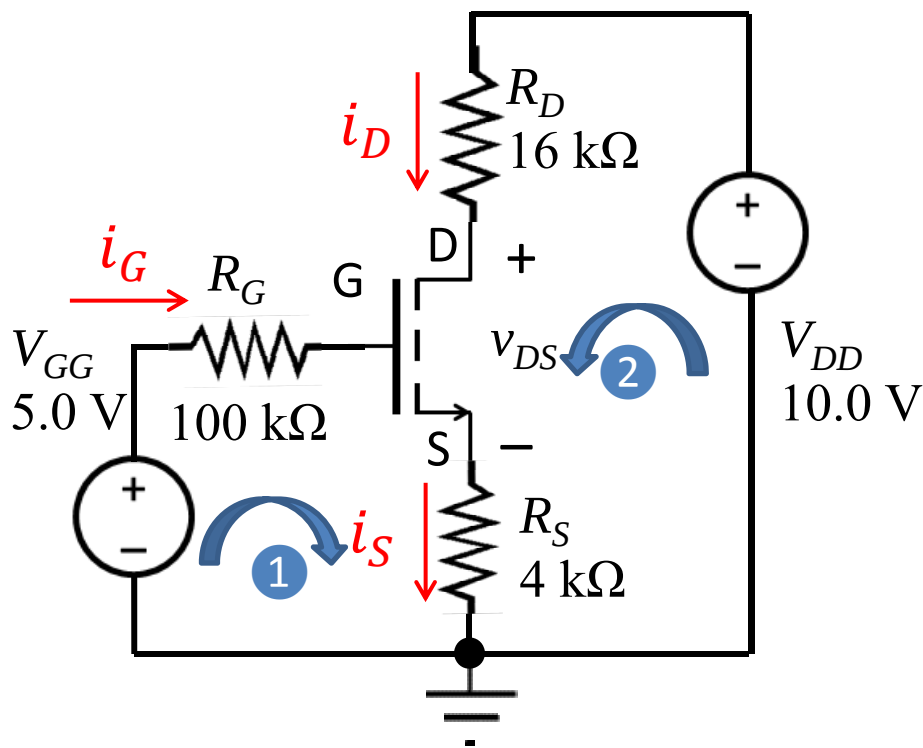

Q-point: (447 μ A, 1.06 V)

- KVL:**

$$v_{DS} = V_{DD} - i_D(R_D + R_S) \quad (2)$$

$$v_{GS} = V_{GG} - i_D R_S \quad (3)$$

- Substituting (2) (3) into (1), we get a quadratic equation of i_D . Solution is:

$$i_D = 186 \mu\text{A} \text{ or } 447 \mu\text{A}$$

- Check:**

- First root:

$$v_{GS} = V_{GG} - i_D R_S = 4.25 \text{ V} > V_T \quad \checkmark$$

$$v_{DS} = V_{DD} - i_D(R_D + R_S) = 6.27 \text{ V} > v_{GS} - V_{TN} \quad \times$$

- Second root:

$$v_{GS} = V_{GG} - i_D R_S = 3.21 \text{ V} > V_T \quad \checkmark$$

$$v_{DS} = 1.06 \text{ V} < v_{GS} - V_{TN} \quad \checkmark$$