 


NMOS resistive load inverter




$$v_I = v_{GS}, v_O = v_{DS}$$

Design: Chose R and W/L of M_S

- A resistor load to “pull” the output up toward the power supply V_{DD} .
- Switch between two states:
 - Triode region: $v_I = V_H \Rightarrow v_O = V_L$
 - Cutoff region: $v_I = V_L \Rightarrow v_O = V_H$

NMOS resistive load inverter
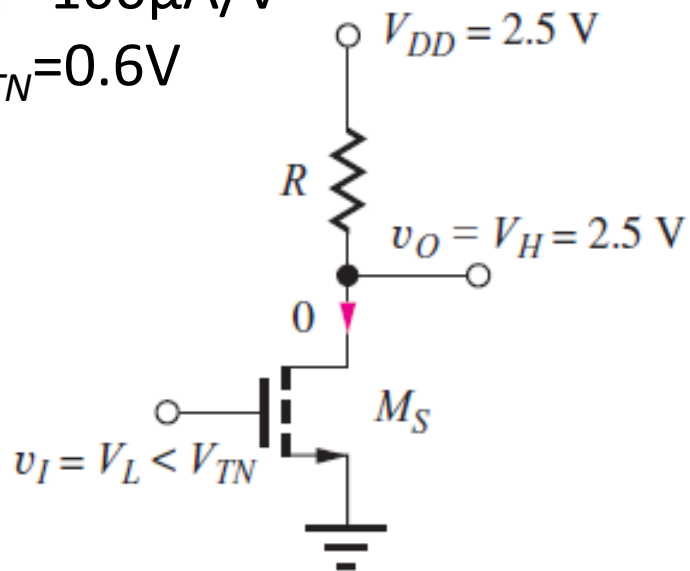
$$K_n' = 100 \mu\text{A}/\text{V}^2$$
$$V_{TN} = 0.6 \text{ V}$$



$$v_I = V_L, v_O = V_H$$

$v_I = V_L$, M_S cutoff

- $i_D = 0 \Rightarrow v_O = V_H = V_{DD}$
- V_H is set by power supply voltage V_{DD} .
- V_L should be less than V_{TN} , typically $V_L \sim 0.2 \text{ V}$


Announcements

- HW #5 due today
- Exam 2 in class on Monday 5/19
 - MOSFETs
 - MOSFETs in circuits and NMOS Logic
 - HWs 4-6

Design of $\left(\frac{W}{L}\right)_S$ and R

$$K'_n = 100 \mu\text{A}/\text{V}^2$$

$$V_{TN} = 0.6\text{V}$$

 

$$v_I = V_H, v_O = V_L$$

Current determined by
permissible power dissipation
of the NMOS, $P = V_{DD}I_{DD}$

$v_I = V_H$, M_S triode

- Drain current ($P = 0.20\text{ mW}$, $V_{DD} = 2.5\text{V}$)

$$I_{DD} = \frac{P}{V_{DD}} = 80\text{ }\mu\text{A}$$

- Triode region equation:


$$i_D = K'_n \left(\frac{W}{L}\right)_S \left(v_{GS} - V_{TN} - \frac{v_{DS}}{2}\right) v_{DS}$$

- $v_{GS} = V_H = 2.5\text{ V}$, $v_{DS} = V_L = 0.2\text{ V}$
 $\Rightarrow \left(\frac{W}{L}\right)_S = \frac{2.22}{1}$

- Load resistor:

$$R = \frac{V_{DD} - V_L}{i_D} = 28.8\text{ k}\Omega$$

Noise Margin Analysis

 


Procedure:

- Find relation between v_O and v_I
- Calculate (V_{IL}, V_{OH}) and (V_{IH}, V_{OL}) by $\frac{dv_O}{dv_I} = -1$
- Calculate noise margin by

$$NM_L = V_{IL} - V_{OL}$$

$$NM_H = V_{OH} - V_{IH}$$

Calculate (V_{IL} , V_{OH})

 

- v_{GS} small and v_{DS} large, **saturation**:

$$i_D = \frac{K_n}{2} (v_I - V_{TN})^2 \quad (1)$$

- Load Line: $v_O = V_{DD} - i_D R \quad (2)$

- Combine (1)(2):


$$v_O = V_{DD} - \frac{K_n R}{2} (v_I - V_{TN})^2$$

$$\Rightarrow \frac{dv_O}{dv_I} = -K_n R (v_I - V_{TN})$$

- Setting $\frac{dv_O}{dv_I} = -1$, we get

- $V_{IL} = V_{TN} + \frac{1}{K_n R}$
- $V_{OH} = V_{DD} - \frac{1}{2K_n R}$

Calculate (V_{IH} , V_{OL})

 

You can write v_O in terms of v_I and solve for $\frac{dv_O}{dv_I} = -1$, but that's tedious!

- v_{GS} large and v_{DS} small, **triode**:
- $i_D = K_n \left(v_I - V_{TN} - \frac{v_O}{2} \right) v_O$ ①
- Load Line: $v_O = V_{DD} - i_D R$ ②
- Combine ① ②:


$$v_I = V_{TN} + \frac{v_O}{2} + \frac{V_{DD} - v_O}{K_n R v_O}$$

$$\Rightarrow \frac{dv_I}{dv_O} = \frac{1}{2} - \frac{V_{DD}}{K_n R v_O^2}$$

- Setting $\frac{dv_I}{dv_O} = -1$, we get

- $V_{OL} = \sqrt{\frac{2V_{DD}}{3K_n R}} = 0.816 \sqrt{\frac{V_{DD}}{K_n R}}$
- $V_{IH} = V_{TN} - \frac{1}{K_n R} + 2 \sqrt{\frac{2V_{DD}}{3K_n R}}$

Calculate noise margin

 

A long chain of such inverters can tolerate noise and process variations around 0.25 V in the low-input state and 0.96 V in the high state.

$$NM_H = V_{DD} - V_{TN} + \frac{1}{2K_n R} - 1.63 \sqrt{\frac{V_{DD}}{K_n R}}$$


$$NM_L = V_{TN} + \frac{1}{K_n R} - 0.816 \sqrt{\frac{V_{DD}}{K_n R}}$$

- Noise margins increase as $K_n R$ increases for typical values of $K_n R$ greater than 2.

• For the previous design

- $V_{IL} = 0.756 \text{ V}$, $V_{OH} = 2.42 \text{ V}$
- $V_{IH} = 1.46 \text{ V}$, $V_{OL} = 0.51 \text{ V}$
- $NM_H = 0.96 \text{ V}$, $NM_L = 0.25 \text{ V}$

Load resistor

 

Geometry of a simple rectangular resistor

t : typically $1\text{ }\mu\text{m}$

ρ : $10^{-3}\text{ }\Omega\text{ cm}$

- Resistance of the resistor:

$$R = \frac{\rho L}{tW}$$

- Consider a $28.8\text{ k}\Omega$ load:

$$\begin{aligned}\frac{L}{W} &= \frac{Rt}{\rho} = \frac{2.88 \times 10^4\text{ }\Omega\text{ } 10^{-4}\text{ cm}}{0.001\text{ }\Omega\text{ cm}} \\ &= \frac{2880}{1}\end{aligned}$$

- If width is $1\text{ }\mu\text{m}$, length has to be 2.88 mm !
- Load resistor takes too much area on a chip
- Alternatives ??