

Announcements

- Homework 7 due Friday in class.
- Design project posted: LED driver with XOR input.
- Office hours today W 2-3pm, Th 1-2pm in EE218.

Dynamic Power Dissipation

- Each cycle, the load C is charged (from V_{DD}) and discharged (to ground).
- Thus, the energy dissipated per cycle is:



$$E_D = V_{DD} \int_0^\infty i(t) dt \cong V_{DD} \int_0^\infty C \frac{dv_c}{dt} dt$$

$$= V_{DD} C \Delta v \cong C V_{DD}^2$$

- Dynamic power dissipation is:

$$P_D = E_D f = C \Delta v V_{DD} f \cong C V_{DD}^2 f$$

  - Energy stored in C is $CV_{DD}^2/2$, so half the energy is dissipated each half-cycle



Inverter Comparison

- To get same V_L , same load current when $v_o = V_L$.
- For fast switching (and best VTC), want maximum pull-up (load) current.
 - PMOS > Depletion > R > Linear > Saturation
 - Body effect degrades Depl, Lin, Sat

 


Figure 6.47 A comparison of NMOS inverter load device characteristics with current normalized to $80 \mu\text{A}$ for $v_o = V_L = 0.20 \text{ V}$. (a) Saturated load including body effect, (b) saturated load without body effect, (c) linear load with body effect, (d) linear load without body effect, (e) $28.8\text{-k}\Omega$ load resistor, (f) depletion-mode load with body effect, (g) depletion-mode load with no body effect, (h) PMOS load transistor for the pseudo NMOS inverter.

PMOS Logic

- PMOS logic is just like NMOS logic, except polarities are reversed.
- Could replace (-2.5V, 0V) with (0V, 2.5V), B at 2.5 V.

 


Figure 6.50 Two-input PMOS gates: (a) NOR gate and (b) NAND gate.

EE 331 Devices and Circuits I

Chapter 7


CMOS Logic Design

CMOS Technology

- NMOS microprocessors dissipates too much **static** power
- CMOS solves the power dissipation problem and dominates digital IC design today
- CMOS: **Complementary** MOS
 - Needs both PMOS and NMOS transistors to be built in the substrate
 - Increase of process complexity, more area, higher cost


CMOS Technology

 - PMOS and NMOS fabricated on the same wafer
- “n-well” implantation needed
- Diode between N/P MOS body terminals reverse biased




CMOS Connections

 - V_{DD} connected to Source of PMOS
- V_{SS} connected to Source of NMOS
- Both gates are connected to input
- Both drains are connected as output
- Bodies are connected to their respective sources
 - No body effect!




CMOS Inverter static behavior

 

- $v_I = V_{DD}$ (High), M_N on, M_P off, $v_O = 0$ (Low)
- $v_I = 0$ (Low), M_N off, M_P on, $v_O = V_{DD}$ (High)
- $i_D = 0$ for both cases: **No static power dissipation!**


CMOS Voltage Transfer Characteristics

 

- Region 1:
 $v_I < V_{TN} = 0.6 \text{ V}$,
 M_N off, $v_O = 2.5 \text{ V}$
- Region 5:
 $v_I > V_{DD} + V_{TP} = 1.9 \text{ V}$,
 M_P off, $v_O = 0 \text{ V}$

Symmetrical CMOS Inverter ($K_p = K_n$)

CMOS Voltage Transfer Characteristics

 


- Region 2:
 M_N saturated, M_P triode
- Region 3:
 M_N saturated, M_P saturated
- Boundary between 2-3:

$$v_{DSP} = v_{GSP} - V_{TP} \Rightarrow$$

$$v_O = v_I + 0.6$$

Symmetrical CMOS Inverter ($K_p = K_n$)

CMOS Voltage Transfer Characteristics

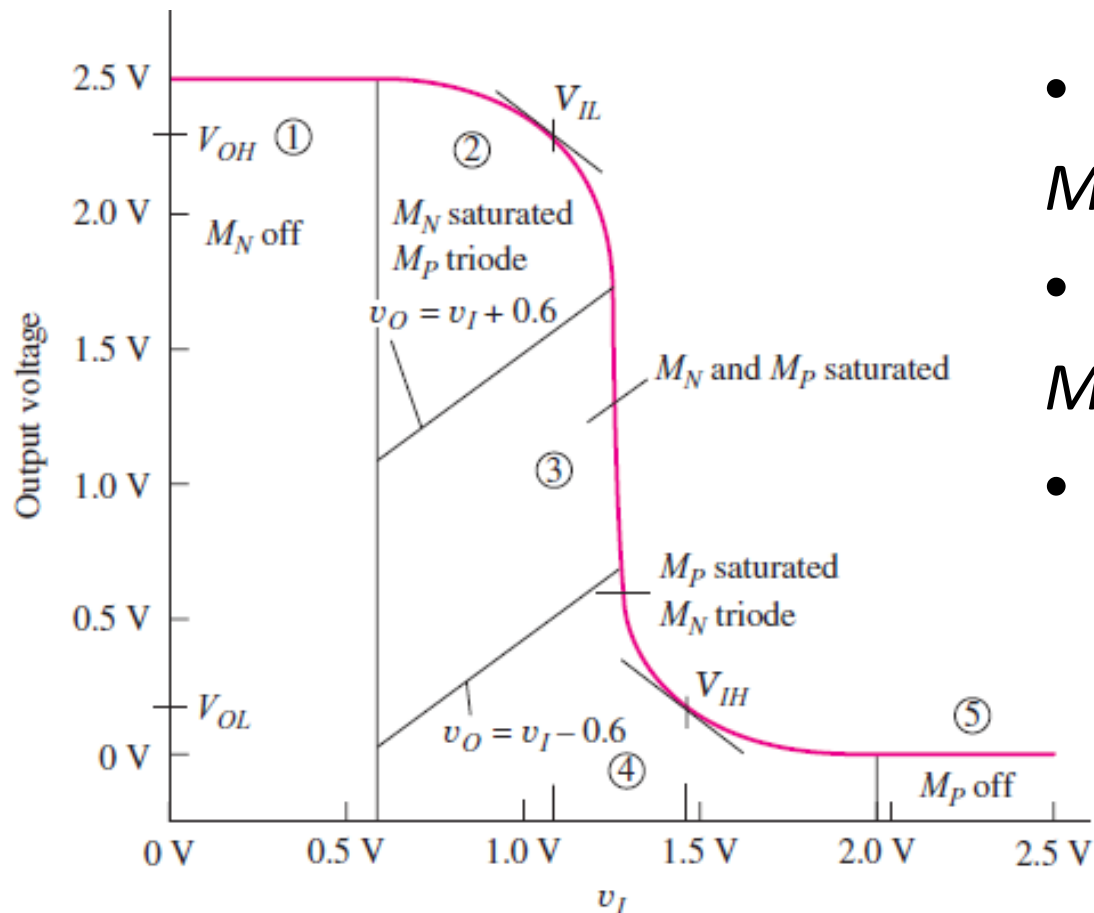


- Region 4:
 M_P saturated, M_N triode
- Region 3:
 M_P saturated, M_N saturated
- Boundary between 3-4:

$$v_{DSN} = v_{GSN} - V_{TN} \Rightarrow$$

$$v_O = v_I - 0.6$$

Symmetrical CMOS Inverter ($K_p = K_n$)


CMOS Voltage Transfer Characteristics

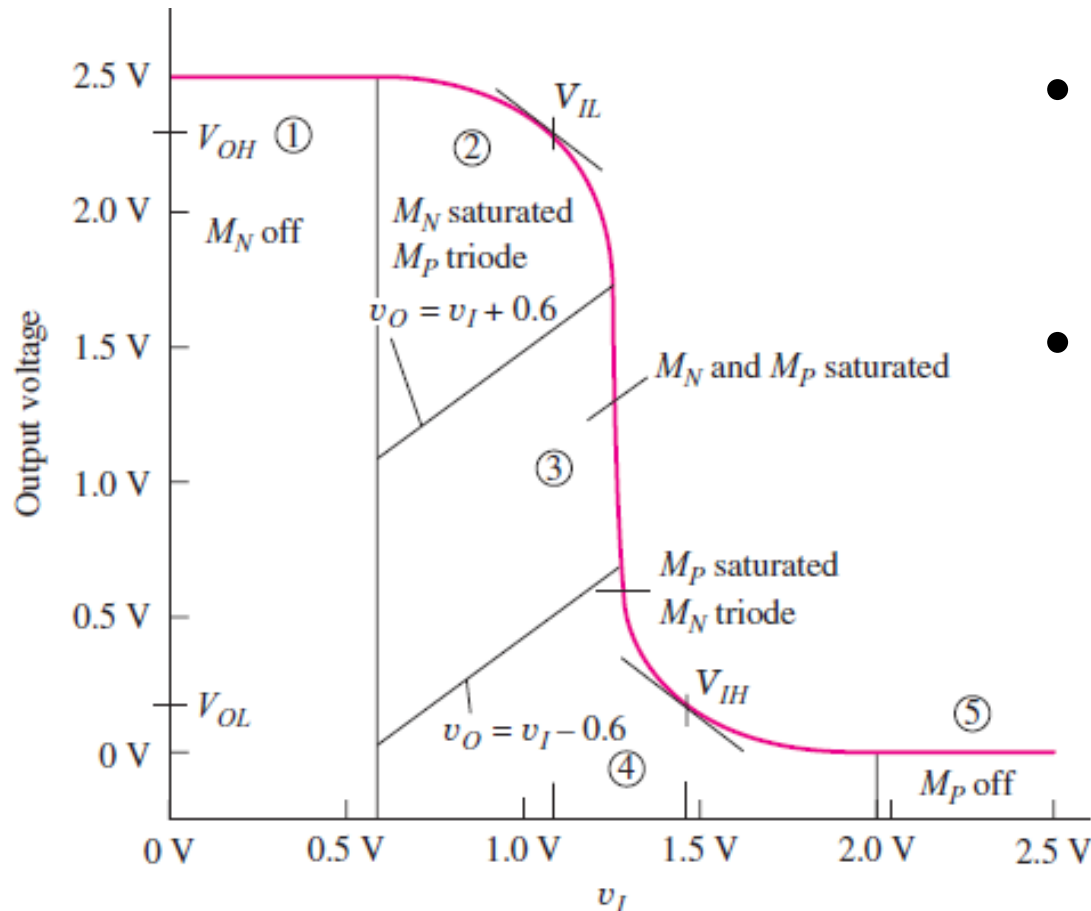

- For CMOS
 - $V_H = V_{DD}$, $V_L = 0$.
 - $\Delta V = V_H - V_L = V_{DD}$
- For symmetrical design ($K_p = K_n$):
 - Transition between V_H and V_L centered at $V_I = V_{DD}/2$


Symmetrical CMOS Inverter ($K_p = K_n$)

VTC of symmetrical CMOS inverter

 


$$\mu_n = 2.5\mu_p \Rightarrow \left(\frac{W}{L}\right)_p = 2.5 \left(\frac{W}{L}\right)_n$$

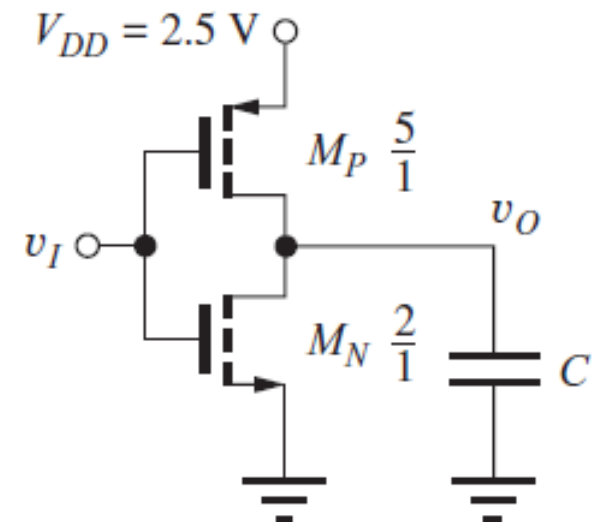- If $K_n = K_p$, transition between V_H and V_L centered at $V_I = V_{DD}/2$



VTC of asymmetrical CMOS inverter

 

- If $K_n \neq K_p$, transition between V_H and V_L shifts from $V_{DD}/2$
- Define $K_R = K_n / K_p$
- $K_R > 1$, transition shifts to left
- $K_R < 1$, transition shifts to right