 


Announcements


- Homework #8 due Friday.
- Exam solution posted.
 - Submit regrades by Friday in class.

Multi-Input CMOS NAND Gates




Five-input CMOS NAND gate: $Y = \overline{ABCDE}$

Capacitances in Logic Circuits

 


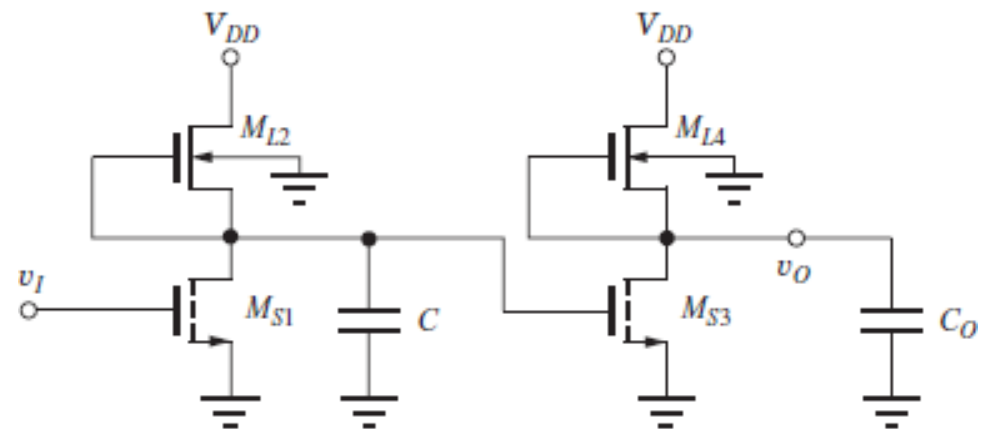Various capacitances associated with transistors







The capacitances on a given node can be lumped into a fixed effective nodal capacitance C

Logic Gate Dynamic Responses

 

- **Rise time (t_r):** time required from 10% point to 90% point
- **Fall time (t_f):** time required from 90% point to 10% point
- **Propagation delay (τ_p):** difference in time between the input and output signals reaching the 50% points
 - for output high-to-low: τ_{PHL}
 - for output low-to-high: τ_{PLH}
 - average propagation delay $\tau_p = (\tau_{PLH} + \tau_{PHL})/2$

Dynamic Response of CMOS Inverter

   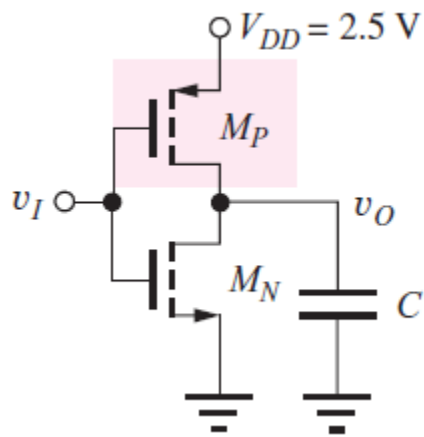


- Assume abrupt V_I change from V_L to V_H
- V_O changes from V_H to V_L by **discharging C via M_N**
- Same as the resistive load

$$\tau_{PHL} = 1.2 R_{onn} C$$

$$R_{onn} = \frac{1}{K_n (V_H - V_{TN})}$$

Dynamic Response of CMOS Inverter

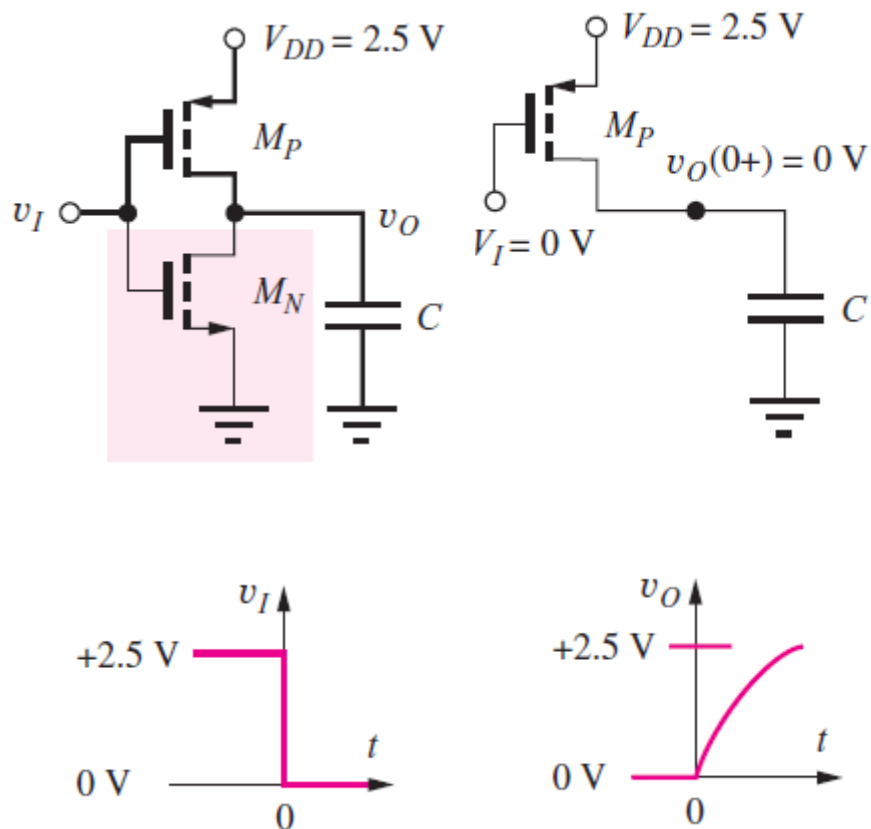


- Assume abrupt V_I change from V_H to V_L
- V_O changes from V_L to V_H by **charging C via M_P**
- Similarly we get

$$\tau_{PLH} = 1.2 R_{onp} C$$

$$R_{onp} = \frac{1}{K_p (V_H + V_{TP})}$$

CMOS Inverter with Symmetrical Delay

 
- CMS inverter with symmetrical delay has
$$\tau_{PLH} = \tau_{PHL} \Rightarrow R_{onn} = R_{onp} \Rightarrow K_n = K_p$$
- This is exactly the “symmetrical” inverter



$$\mu_n = 2.5\mu_p \Rightarrow \left(\frac{W}{L}\right)_p = 2.5 \left(\frac{W}{L}\right)_n$$

$$\tau_P = \frac{\tau_{PLH} + \tau_{PHL}}{2} = 1.2R_{onn}C$$

CMOS Switching Speed

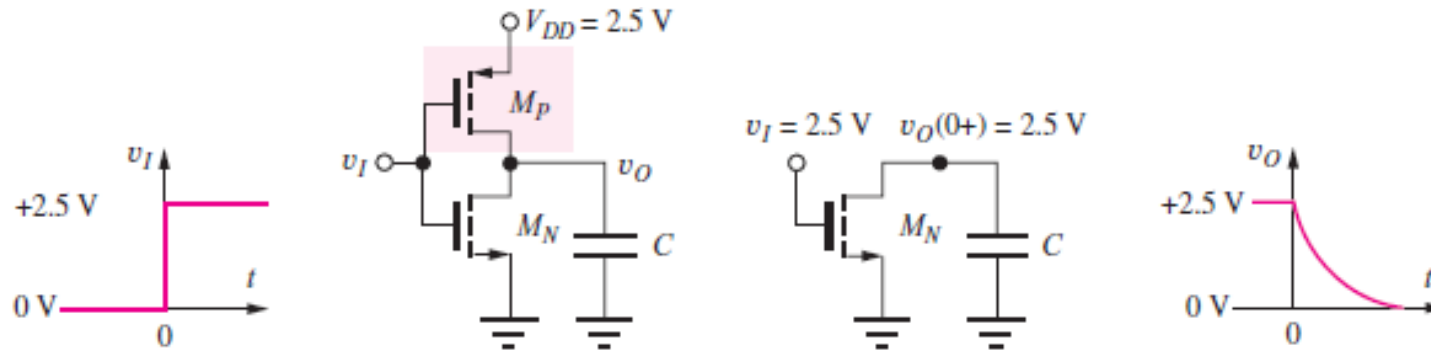

- Can estimate switching time for capacitive load very simply:

$$\Delta t = \frac{C_{\text{total}} \Delta v}{i_{\text{avg}}} = \frac{\Delta Q}{i_{\text{avg}}}$$

- For τ_{PHL} , $v_I = V_{DD}$, PMOS OFF, NMOS ON.
- NMOS saturated for $v_O > V_{DD} - V_{TN}$, linear for $v_O < V_{DD} - V_{TN}$
- Just the opposite for LH transition.

Symmetrical CMOS Inverter

- Symmetrical CMOS inverter:

- $K_n = K_p, V_{Tn} = -V_{Tp} = V_T$


- $\tau_{PLH} = \tau_{PHL}, R_{onn} = R_{onp}$

- If $V_T < V_{DD}/2$

- $V_{OL} = \frac{V_{DD}}{8} - \frac{V_T}{4}, V_{OH} = V_{DD} - V_{OL}$

- $V_{IL} = \frac{3V_{DD}}{8} + \frac{V_T}{4}, V_{IH} = V_{DD} - V_{IL}$

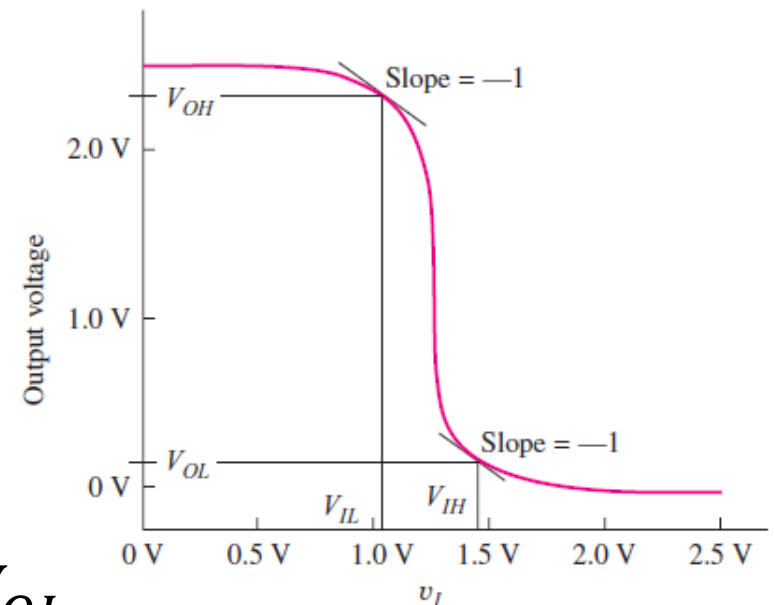- $NM_L = NM_H = \frac{V_{DD}}{4} + \frac{V_T}{2}$




CMOS Performance Scaling


- $\tau_P = \frac{\tau_{PHL} + \tau_{PLH}}{2}$
 - $\tau_P \propto C$
 - $\tau_P \propto R_{on} \propto \left(\frac{W}{L}\right)^{-1}$
- Delay is proportional to total load capacitance C , and inversely proportional to W/L .
- Larger size (larger W/L) => shorter delay

Power Dissipation

 - Switching: CV_{DD}^2 per cycle
- Transition conduction: when $V_{TN} < v_{in} < V_{DD} + V_{TP}$, both transistors are on.
 - Depends on amount of time with $v_{in} \sim V_{DD}/2$ (t_r, t_f).
 - Can be 20-30% of CV_{DD}^2
- Subthreshold conduction: small currents even when devices are “off.”



Subthreshold Conduction

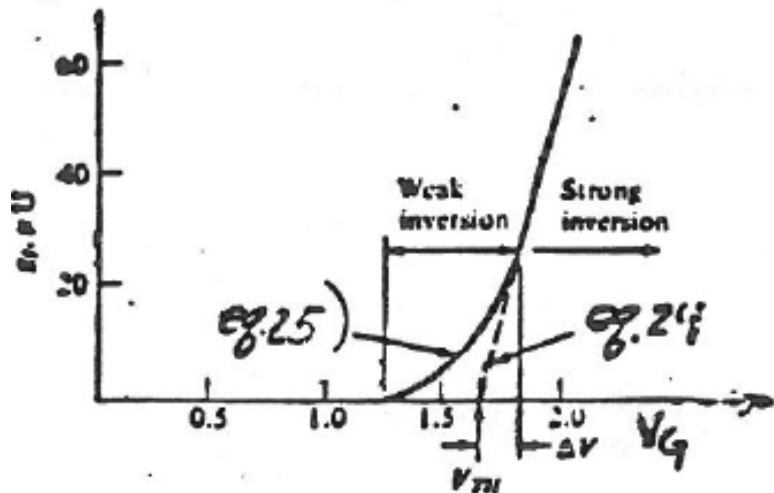

Note that the linear relationship between g_I and $V_G - V_{th}$ agrees with experiment except for V_G very close to V_{th} .

$$Q'_I \cong -WC''_{ox}(V_{GS} - V_T) \quad [24]$$

$$Q'_I \cong -WC''_{ox}\Delta V \exp\left(\frac{V_{GS} - V_T - \Delta V}{\Delta V}\right) \quad [25]$$

Subthreshold slope
 $(1+\alpha)60$ mV/decade
 Typical is 70-100 mV/dec

$$\Delta V = (1 + \alpha) \frac{kT}{q} = \left(1 + \frac{C_d''}{C_{ox}''}\right) \frac{kT}{q}$$

Subthreshold Conduction

$$Q'_I \cong -WC''_{ox}\Delta V \exp\left(\frac{V_{GS} - V_T - \Delta V}{\Delta V}\right)$$

$$\Delta V = (1 + \alpha) \frac{kT}{q} = \left(1 + \frac{C_d''}{C_{ox}''}\right) \frac{kT}{q}$$

$$i_{Dsub} = \left(\frac{Q'_I}{L}\right) \mu \frac{kT}{q} \left(1 - e^{-qv_{DS}/kT}\right)$$

Subthreshold slope

$(1+\alpha)60$ mV/decade

Typical is 70-100 mV/dec

(60 mV/dec for $\alpha = 0$)


 
 


Figure 4.19 Subthreshold conduction in an NMOS transistor with $V_{TN} = 1$ V.

Power Dissipation


 
- V_{GS} must drop significantly below V_T to fully turn off MOSFET (lower limit on $V_T \sim 0.3$ V)
- Standby power significant in modern technology.



- Can turn off blocks of logic when not needed.


Distributed Body Effect

  - Threshold voltage actually changes with $V_{CB}(x)$ rather than just V_{SB} .



$$\begin{aligned}
 V_{TNeff} &= V_{TO} + \gamma(\sqrt{v_{CB} + 2\phi_F} - \sqrt{2\phi_F}) \\
 &\cong V_{TO} + \alpha v_{CB}(x) \\
 &\cong V_{TN} + \alpha v_{CS}(x)
 \end{aligned}$$

n-MOSFET Analysis (Triode)

 

- Goal: Find $i_D = f(v_{GS}, v_{DS})$ when v_{DS} is small and $v_{SB} = 0$
- Inversion charge line density at any point in the channel:

$$Q' = -WC''_{ox}(v_{GC} - V_{TN}) = -WC''_{ox}(v_{GS} - v(x) - V_{TN}) \quad (1)$$

- Current in the channel:

$$i(x) = Q'(x)(-\mu_n E_x) \quad (2)$$

- Electric field:

$$E_x = -\frac{dv(x)}{dx} \quad (3)$$

n-MOSFET Analysis (Triode)

- Combining ①②③:

$$i(x) = -\mu_n C_{ox}'' W (v_{GS} - v(x) - [V_{TN} + \alpha v(x)]) \frac{dv(x)}{dx}$$

- Integrate between 0 and L : $v(0) = 0, v(L) = v_{DS}$

$$\int_0^L i(x) dx = \int_0^{v_{DS}} -\mu_n C_{ox}'' W (v_{GS} - [1 + \alpha]v(x) - V_{TN}) dv(x)$$


- Current must be equal in the channel: $i(x) = -i_D$ Notice the sign!

- We get the **triode region formula**:

$$i_D = K_n' \frac{W}{L} \left(v_{GS} - V_{TN} - \frac{[1+\alpha]v_{DS}}{2} \right) v_{DS} \text{ where } K_n' = \mu_n C_{ox}''.$$

- The channel exists as long as $v_{GC} = v_{GS} - v(x) > V_{TN\text{eff}}$ for all $0 < x < L$. This requires $v_{GS} \geq [1 + \alpha]v_{DS} + V_{TN} = v_{DS} + V_{TN}$
- Thus condition for triode region operation is: $v_{GS} - [1 + \alpha]v_{DS} \geq V_{TN}$

Saturation (Pinch-off) region

 

- $v_{DSAT} = (v_{GS} - V_{TN})/[1 + \alpha]$
 - $v_{DS} \geq v_{DSAT}$:
- $$i_D = \frac{K'_n}{2[1 + \alpha]} \frac{W}{L} (v_{GS} - V_{TN})^2$$

Example, $V_{TN}=1V$, $\alpha = 0.25 V^{-1}$:

- $V_{GS}=1V$, $V_{DS}=1V$: cutoff
- $V_{GS}=3.3V$, $V_{DS}=1V$: linear
- $V_{GS}=3.3V$, $V_{DS}=2V$: saturation
 $V_{GD}=1.3V < V_{TNeff}(L) = 1 + (0.25)2$ or
 $V_{DS} > (V_{GS} - V_{TN})/(1 + \alpha)$