
 


Announcements

- Homework #8 due Friday in class.
- Office hours today 2-3 pm and Th 12-1 pm
- Exam 2 regrade requests by in-class Friday.
- Grades online at
catalyst.uw.edu/gradebook/dunham/86375

The CMOS Transmission Gate


Bilateral Switch

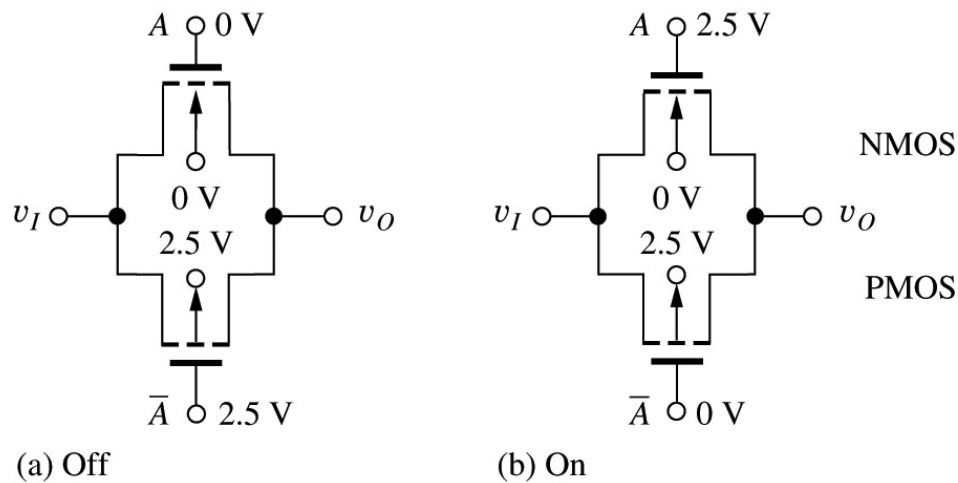

- The CMOS transmission gate (T-gate) is a useful circuit for both analog and digital applications
- It acts as a switch that can operate up to V_{DD} and down to V_{SS} .
- Either side can be input/output.

The CMOS Transmission Gate


Equivalent On-Resistance

 


- Primary consideration is equivalent on-resistance which is given by the following expression:

$$R_{EQ} = \frac{R_{onp} R_{onn}}{R_{onp} + R_{onn}}$$

 - NMOS conducts for $v_I < V_{DD} - V_{TN}$
- PMOS conducts for $v_I > -V_{TP}$



 NMOS Output Characteristics with Linearized Distributed Body Effect



Region	Current Equation	Condition
Cutoff	$i_D = 0$	$v_{GS} \leq V_{TN}$
Triode	$i_D = K_n \left(v_{GS} - V_{TN} - [1 + \alpha] \frac{v_{DS}}{2} \right) v_{DS}$	$v_{GS} > V_{TN}$ $v_{GS} - V_{TN} > [1 + \alpha] v_{DS}$
Saturation	$i_D = \frac{K_n}{2[1 + \alpha]} (v_{GS} - V_{TN})^2$	$v_{GS} > V_{TN}$ $v_{GS} - V_{TN} \leq [1 + \alpha] v_{DS}$

Transconductance (Saturation)

$$i_D = \frac{K'_n}{2(1 + \alpha)} \frac{W}{L} (v_{GS} - V_{TN})^2$$


$$v_{DSAT} = (v_{GS} - V_{TN})/[1 + \alpha]$$

- Transconductance (change in i_D vs. change in v_{GS}):

$$g_m = \frac{di_D}{dv_{GS}} = K'_n \frac{W}{L(1 + \alpha)} (v_{GS} - V_{TN})$$

CMOS Technology

Inverter Layout

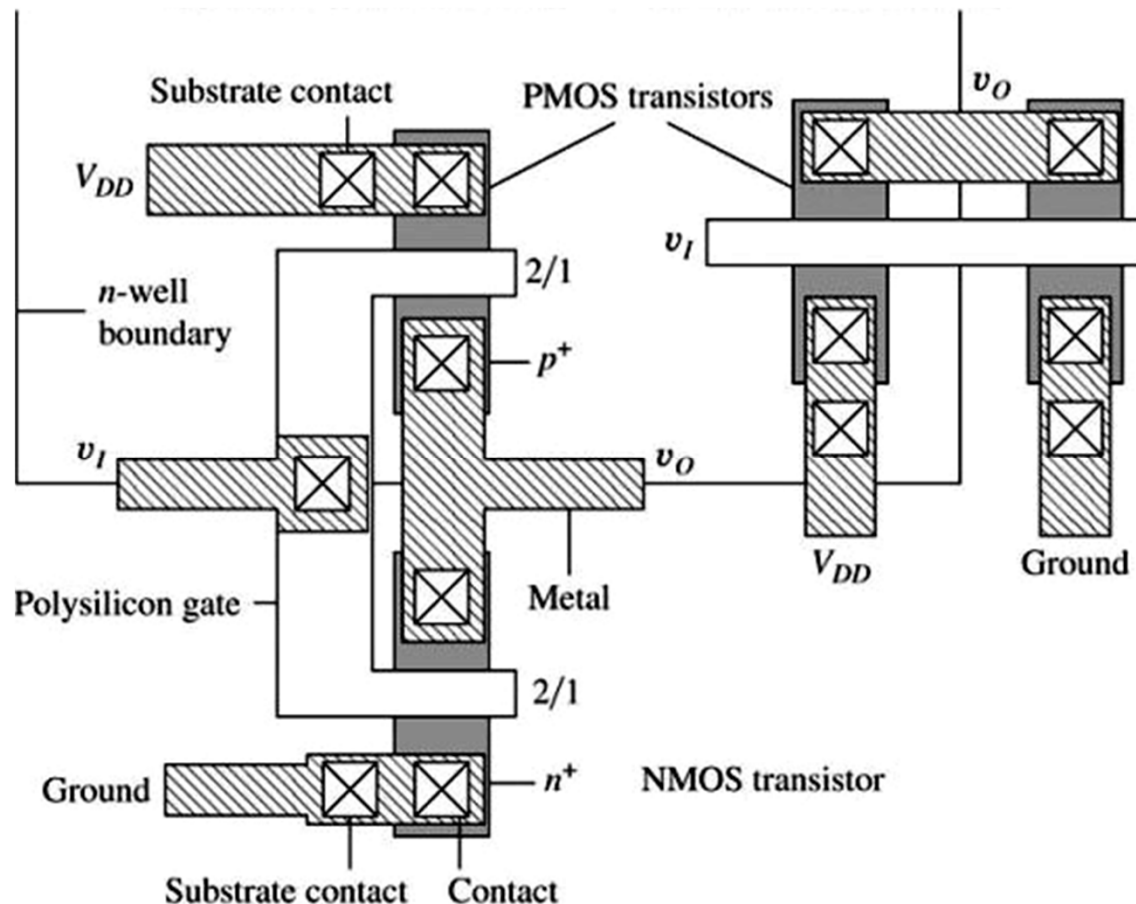



- Two methods of laying out a CMOS inverter are shown
- The PMOS transistors lie within the n-well, whereas the NMOS transistors lie in the p-substrate
- Polysilicon is used to form common gate connections, and metal is used to tie the two drains together

Minimum Size Gate

Design and Performance

- With CMOS technology, there is an area/delay tradeoff that needs to be considered
- If minimum feature sized are used for both devices, then the τ_{PLH} will be increased compared to the symmetrical reference inverter

Complex Gate Design

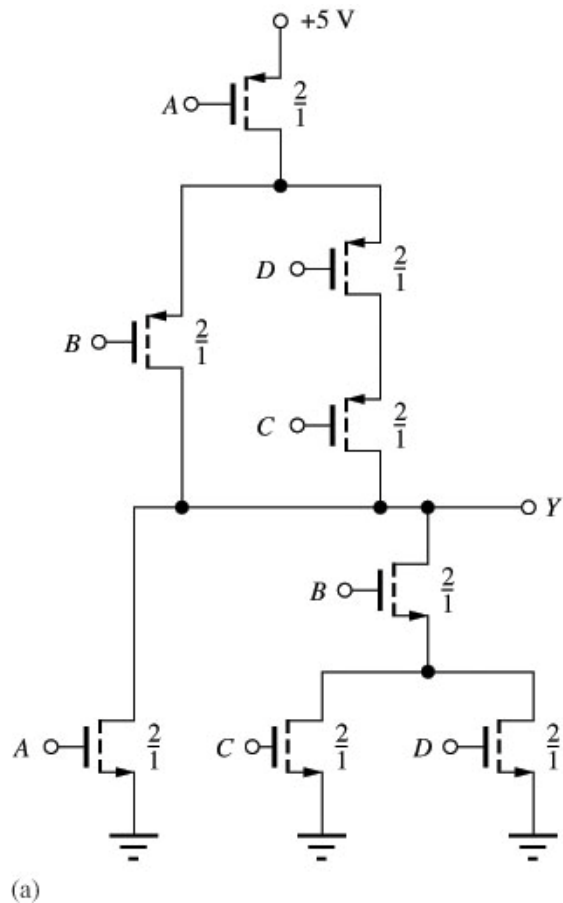 

NMOS pull-down:

$$\begin{aligned}
 Y &= \overline{A + B \cdot (C + D)} \\
 &= \bar{A} \cdot \overline{B \cdot (C + D)} \\
 &= \bar{A} \cdot [\bar{B} + \overline{(C + D)}] \\
 &= \bar{A} \cdot [\bar{B} + \bar{C} \cdot \bar{D}]
 \end{aligned}$$

which is PMOS pull-up circuit.

Minimum Size Complex Gate

Design and Layout

- The following shows the layout of a complex minimum size logic gate

