

# Announcements

---


- Homework #9 due Friday.
- Addition to Final Project:  
**Evaluation (10 points)**  
Evaluate and compare your two designs regarding performance, reliability, cost, and power dissipation. Discuss the extent to which these factors could be improved or traded-off in a final product.
- Schedule Final Project demo with TAs for this Thursday and Friday.

# Dynamic Memory Cells
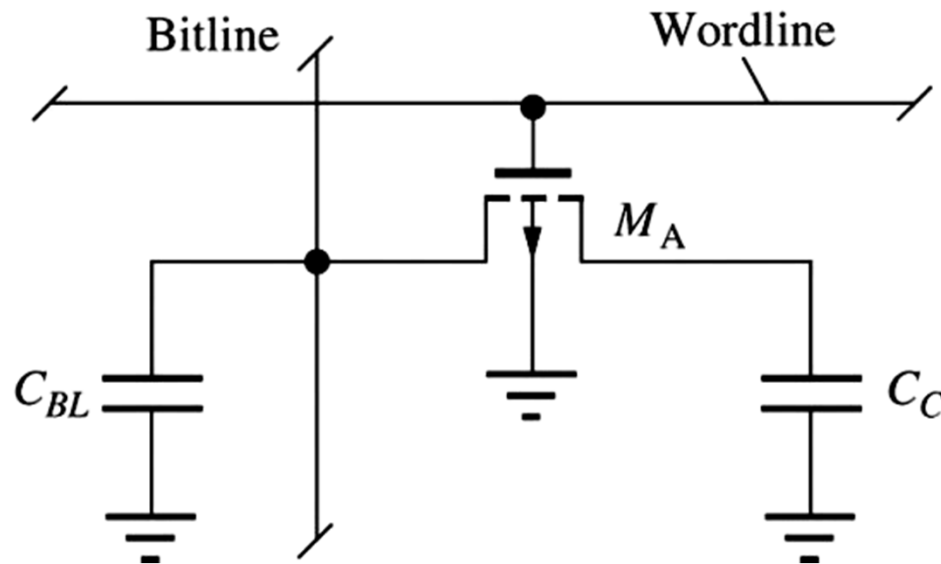
## The One-Transistor (1-T) Cell


---

- The 1-T cell uses a capacitor for its storage element (data is represented as either a presence or absence of a charge)
- Due to leakage currents in  $M_A$ , the data will eventually be corrupted, hence it needs to be refreshed





# The 1-T Cell


## Data Storage

 

Storing a  
“0”

  

Storing a “1”

 

# The 1-T Cell

## Data Storage (cont.)

---

- Notice that the voltage stored on the storage capacitor on the previous slide does not reach  $V_{DD}$
- It instead is determined by the following:

$$V_C = V_G - V_{TN}$$

$$V_C = V_G - \left[ V_{TO} + \gamma \left( \sqrt{V_C + 2\phi_F} - \sqrt{2\phi_F} \right) \right]$$



- This is similar to the impact of body effect in the saturated load inverter.

# The 1-T Cell
  
## Data Storage (cont.)

---

- To read a DRAM cell, the bitline is precharged to either  $V_{DD}$  or  $V_{DD}/2$ , and then  $M_A$  is turned on



# The 1-T Cell

## Data Storage (cont.)

---

- The charge stored on  $C_C$  will be shared with  $C_{BL}$  through the process of charge sharing, where the read voltage varies slightly

$$V_F = \frac{C_{BL}V_{BL} + C_C V_C}{C_{BL} + C_C} \cong V_{BL}$$

- Normally  $C_{BL} \gg C_C$ , and the charging time constant is:

$$\tau = R_{ON} \frac{C_{BL}C_C}{C_{BL} + C_C} \cong R_{ON}C_C$$