

Announcements


- Lab #1 this week. Read ahead of time so you are prepared.

Diode Circuit Analysis

- Goal: find quiescent operating point (Q-point) of the diode (I_D, V_D)
 - Analytical tools:
 - Kirchhoff's voltage law (KVL)
 - Kirchhoff's current law (KCL)
 - Element relations
 - Solution methods (Often can't solve analytically due to non-linearity)
 - Graphical methods
 - Numerical iteration
 - Linearization
-

Diode Circuit Analysis

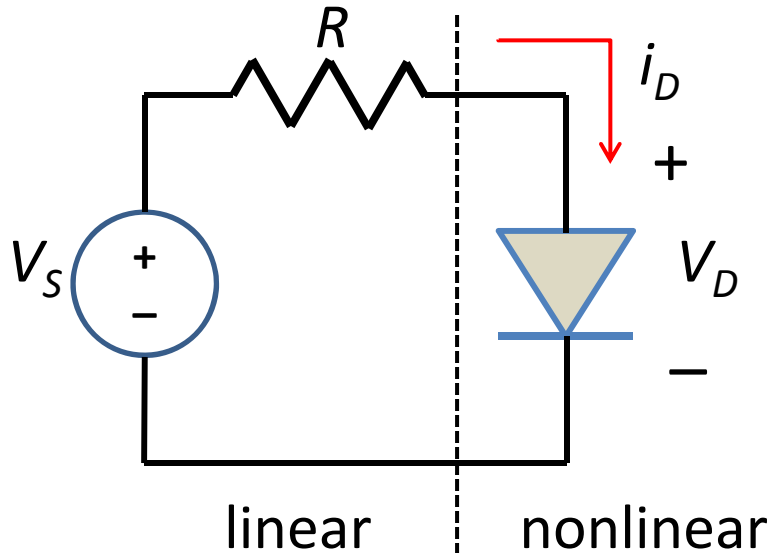- Example: Given v_D , R , and parameters for the diode (I_S , V_T), find Q-point (I_D , V_D).



- Linear Part (resistor, load)

$$V_S = i_D R + v_D$$

- Nonlinear part (diode)

$$i_D = I_S \left(e^{\frac{v_D}{V_T}} - 1 \right)$$



- Two equations, two unknowns I_D , V_D .

Load Line Analysis (Graphical)

- Write the two equations in the form of i_D v.s. v_D .

$$i_D = -\frac{v_D}{R} + \frac{V_S}{R}, \quad i_D = I_S(e^{\frac{v_D}{V_T}} - 1)$$

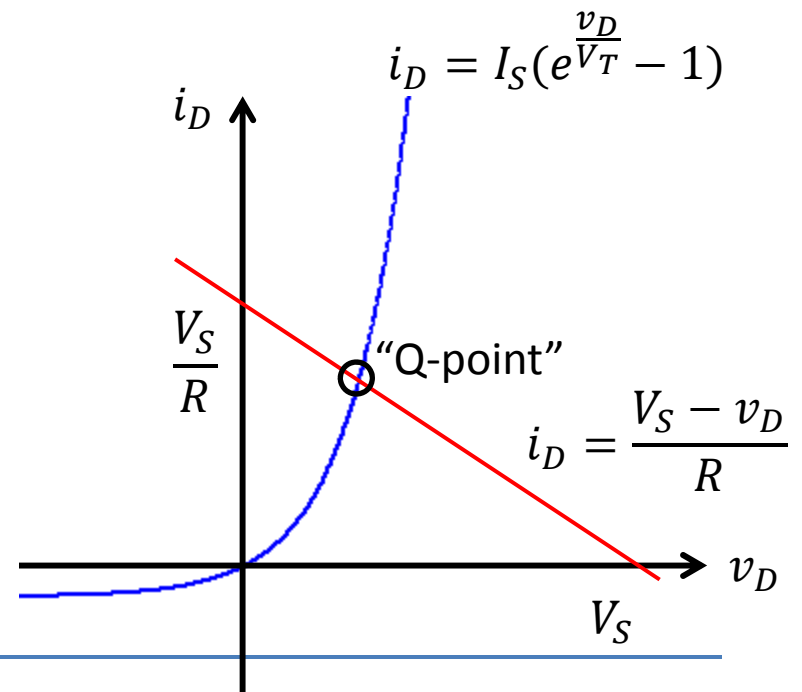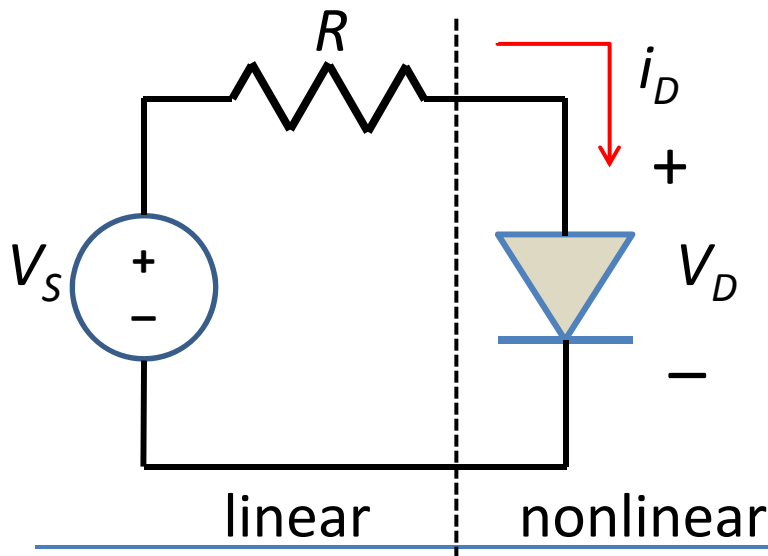- Plot them on a same graph, find the intersection.



Numerical Analysis

- Combining:

$$i_D = -\frac{v_D}{R} + \frac{V_S}{R}, \quad i_D = I_S(e^{\frac{v_D}{V_T}} - 1)$$

- We have: $-\frac{v_D}{R} + \frac{V_S}{R} = I_S(e^{\frac{v_D}{V_T}} - 1) \Rightarrow v_D = V_T \ln \left(1 + \frac{V_S - v_D}{I_S R} \right)$
- Let $R = 1\text{k}\Omega$, $I_S = 10^{-10}\text{A}$, $v_T = 26\text{ mV}$, $V_S = 10\text{ V}$. we have

$$v_D = 0.026 \ln \left(1 + \frac{10 - v_D}{10^{-7}} \right)$$
- Make an initial guess ($v_D = 0.5\text{ V}$) and solve by iteration:

Iteration #	0	1	2	3
$v_D\text{ (V)}$	0.5	0.4776	0.4777	0.4777

← converged !

$$i_D = -\frac{v_D}{R} + \frac{V_S}{R} = 9.522\text{ mA} \quad \text{Q-point} = (9.522\text{ mA}, 0.4777\text{ V})$$

Numerical Analysis


- Now use $V_S = -10$ V. Expect diode to be reverse biased.
- From graphical analysis, $i_D \approx -I_S$. Thus

$$v_D = V_S - i_D R = -10 \text{ V} - 10^{-10} \text{ A} \cdot 10^3 \Omega = -10 \text{ V}$$

- Check for i_D : $i_D = I_S \left(e^{\frac{v_D}{V_T}} - 1 \right) \approx -I_S = -10^{-10} \text{ A}$
- Q-point = $(-10^{-10} \text{ A}, -10 \text{ V})$
- Be careful of round-off error:


$$i_D = -\frac{v_D}{R} + \frac{V_S}{R} = \frac{10 \text{ V} - 10 \text{ V}}{10^3 \Omega} = 0.00 \text{ A} \quad \times$$

should be 9.999999999 V

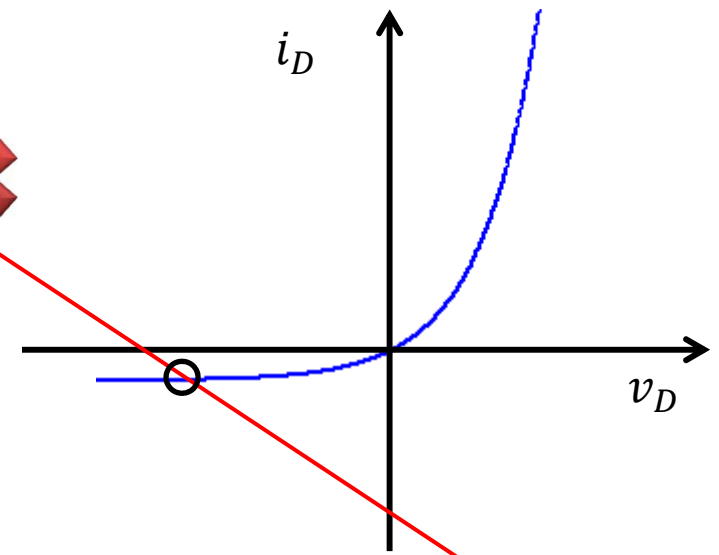

Simplified Diode Models


General diode

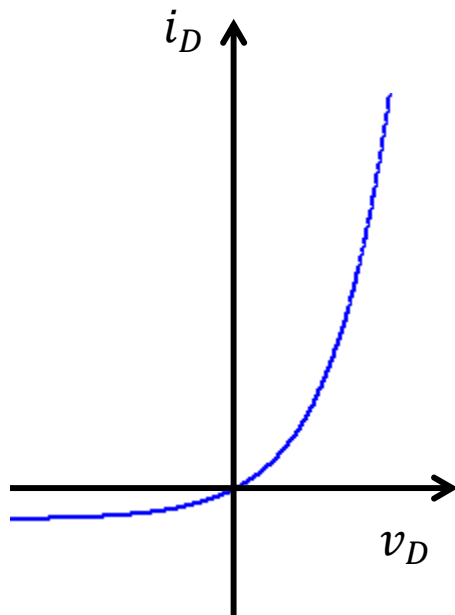

ON: short circuit
OFF: open circuit




Ideal diode

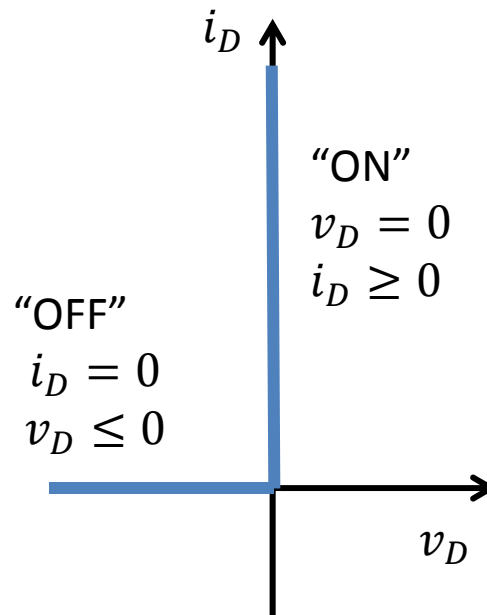

"OFF"
 $i_D = 0$
 $v_D \leq 0$

"ON"
 $v_D = 0$
 $i_D \geq 0$


Constant voltage drop

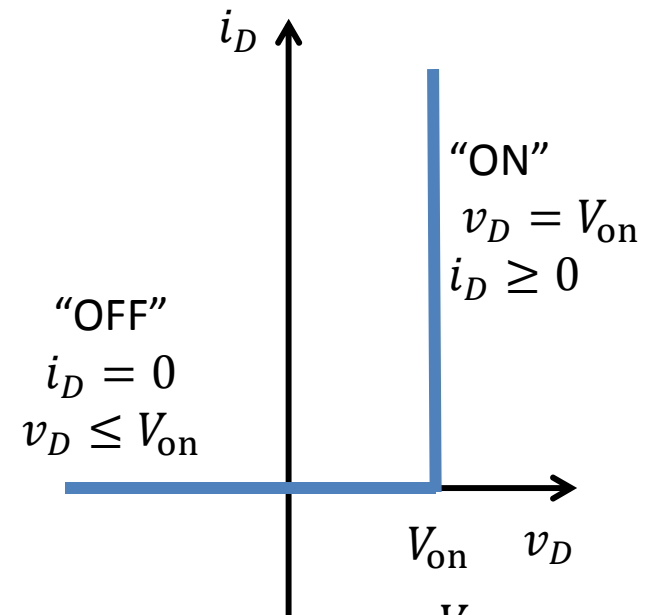

"OFF"
 $i_D = 0$
 $v_D \leq V_{on}$

"ON"
 $v_D = V_{on}$
 $i_D \geq 0$

ON: voltage source
OFF: open circuit

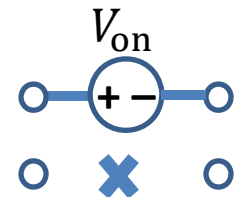


Diode Circuit Analysis – simplified model


- Analysis Method:
 - Guess a state for the diode, ON or OFF
 - Replace the diode by its equivalent model for this state
 - Analyze the circuit using this equivalent model
 - Verify that the guess was correct

Diode Circuit Analysis

Ideal model

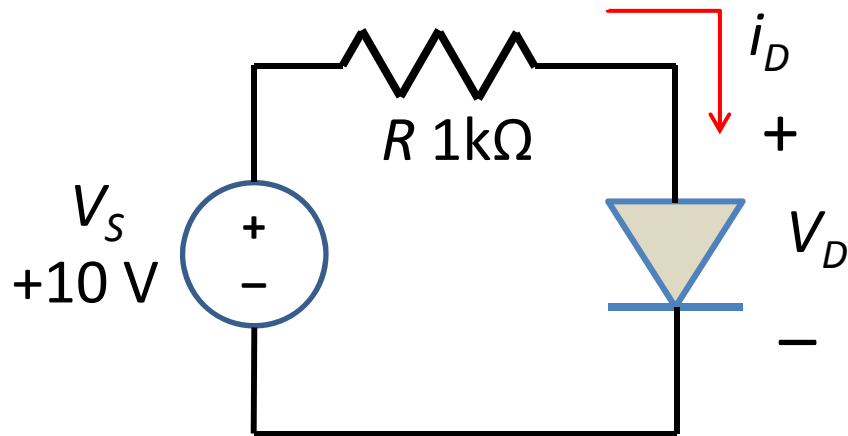

Guess **ON**:

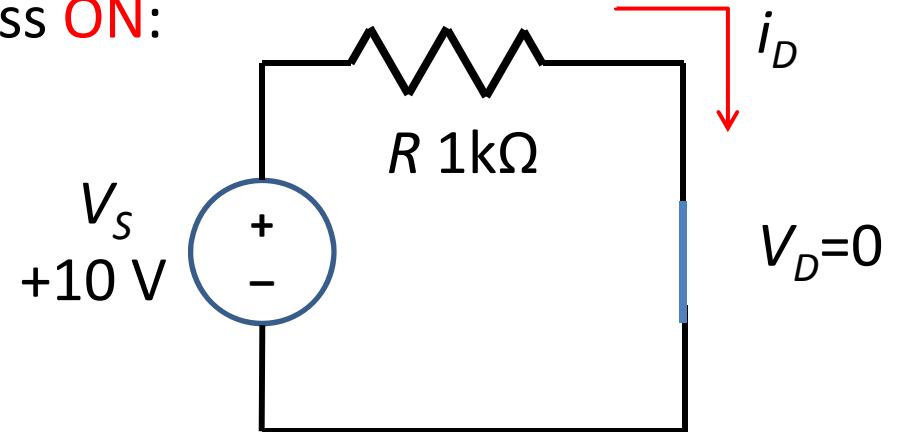


Since $I_D = 10\text{ mA} \geq 0$, D = ON correct


“ON” condition: $v_D = 0, i_D \geq 0$

Diode Circuit Analysis

LVD model

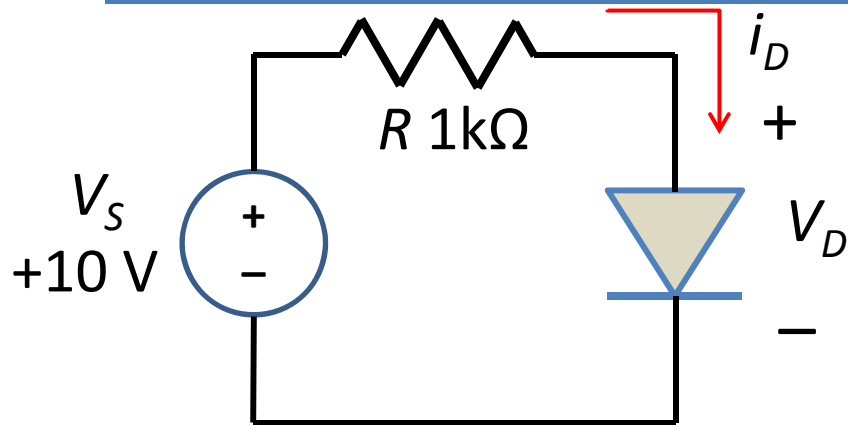


$$V_{\text{on}} = 0.6\text{ V}$$

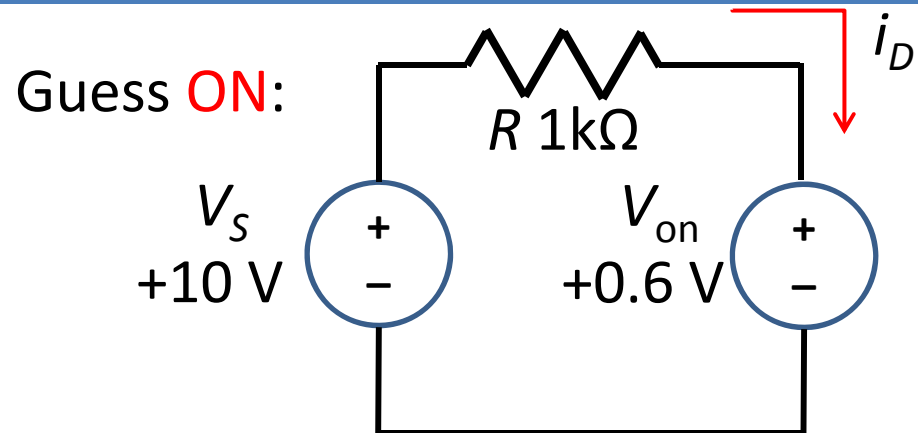

Since $i_D = 9.4\text{ mA} \geq 0$, D = ON correct

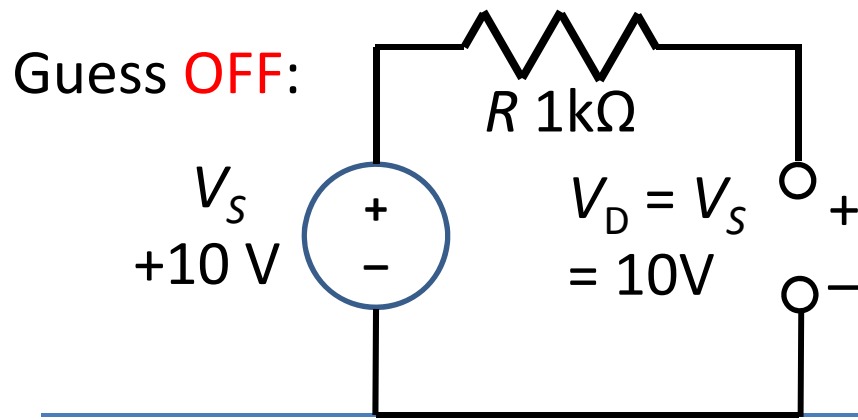
“ON” condition: $v_D = V_{\text{on}}, i_D \geq 0$



Since $V_D = 10\text{ V} \geq V_{\text{on}}$, D = OFF wrong!

“OFF” condition: $i_D = 0, v_D \leq V_{\text{on}}$


Multiple Diode Circuits

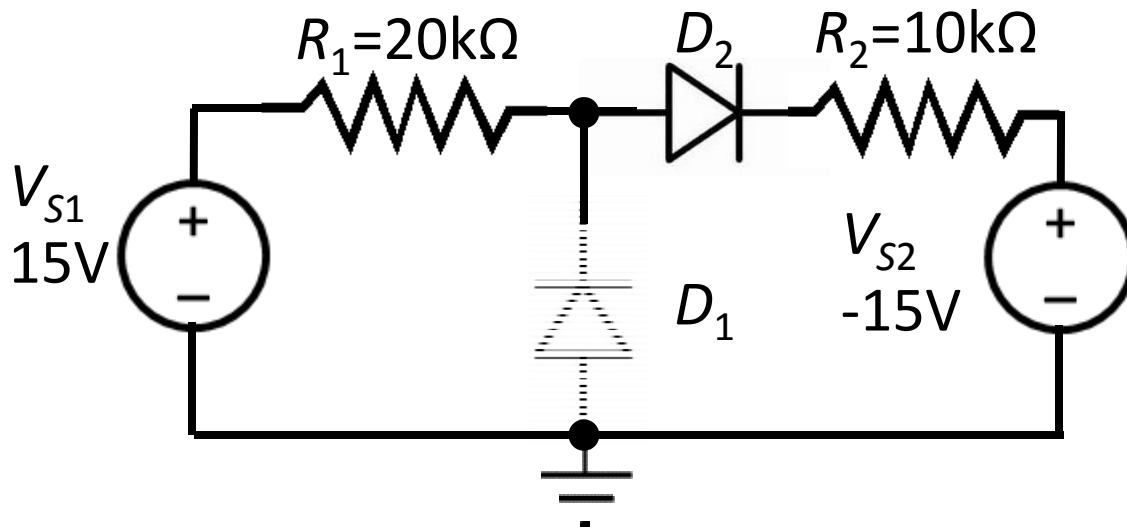

$D_1, D_2 = \text{Ideal diodes}$

Textbook Schematic

Engineering Schematic

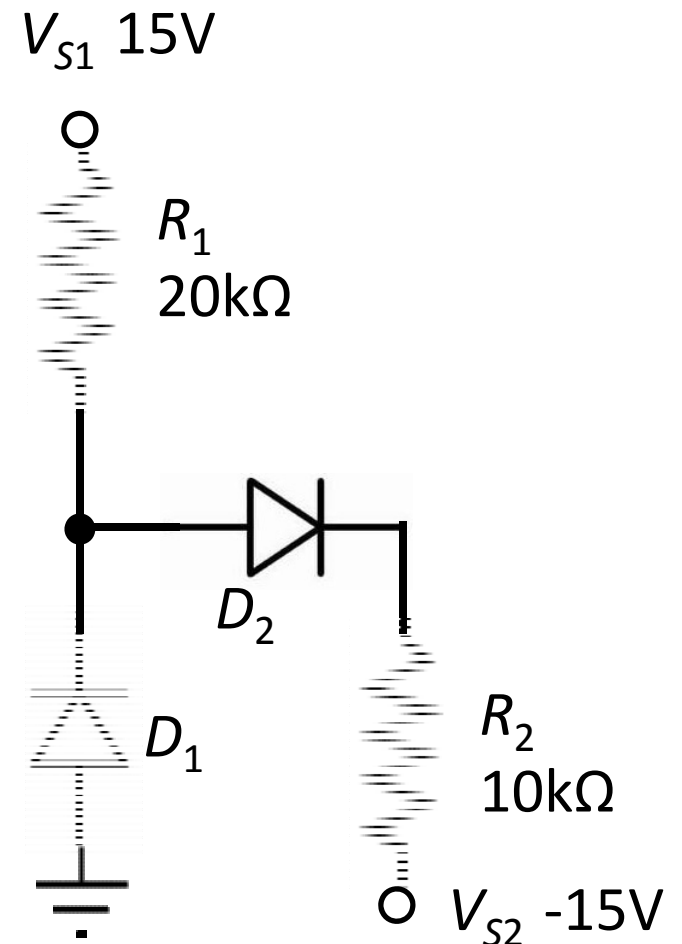

Multiple Diode Circuits

Guess: D_1, D_2 both ON

$$i_{R1} = \frac{15\text{ V} - 0\text{ V}}{20\text{ k}\Omega} = 0.75\text{ mA}$$


$$i_{D2} = \frac{0\text{ V} - (-15)\text{ V}}{10\text{ k}\Omega} = 1.50\text{ mA}$$

$$i_{D1} = i_{D2} - i_{R1} = 0.75\text{ mA}$$

Check:

$$i_{D1} \geq 0, i_{D2} \geq 0$$

both D_1 and D_2 are ON. Correct!

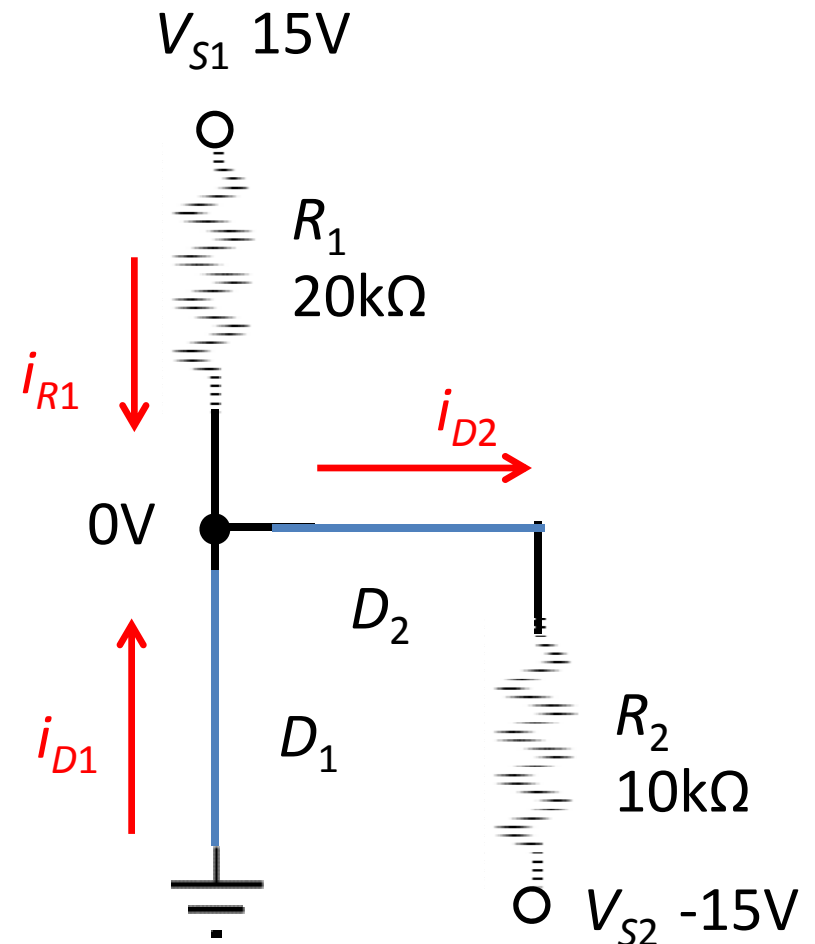

Multiple Diode Circuits

Now: Swap resistors

Guess: D_1 , D_2 both ON


$$i_{R1} = \frac{15\text{ V} - 0\text{ V}}{10\text{ k}\Omega} = 1.50\text{ mA}$$

$$i_{D2} = \frac{0\text{ V} - (-15)\text{ V}}{20\text{ k}\Omega} = 0.75\text{ mA}$$

$$i_{D1} = i_{D2} - i_{R1} = -0.75\text{ mA}$$

Check:

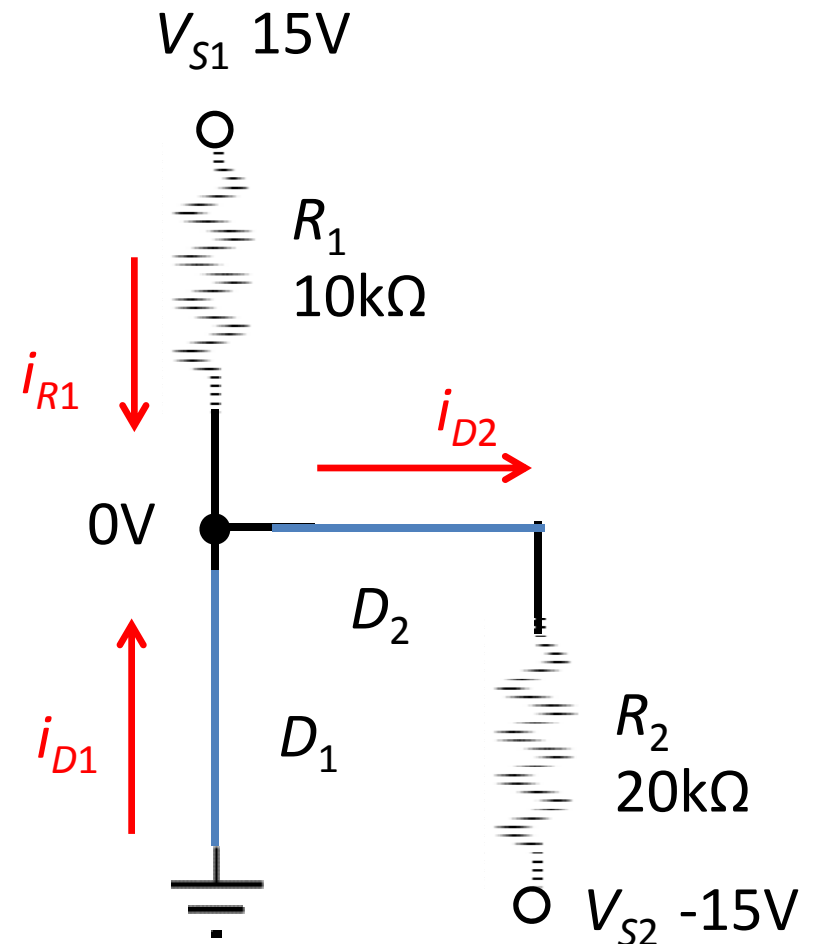$i_{D1} < 0 \Rightarrow$ **Contrary to D_1 ON!**



Multiple Diode Circuits

Guess: D_1 OFF, D_2 ON

$$i_{R1} = i_{D2} \frac{15\text{ V} - (-15)\text{V}}{30\text{ k}\Omega} = 1.00\text{ mA}$$

$$v_A = 15\text{ V} - 10\text{ k}\Omega \cdot 1\text{mA} = 5\text{ V}$$

$$v_{D1} = 0 - v_A = -5\text{ V}$$

Check:

$v_{D1} < 0 \Rightarrow D_1$ off. Correct.

$i_{D2} > 0 \Rightarrow D_2$ on. Correct.

