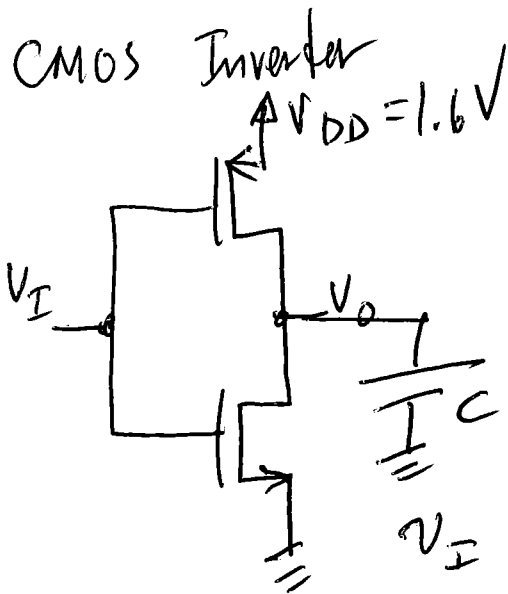


Notes on Switching Calculation Example




$$K_n = K_p = 200 \mu A/V^2$$

$$V_{TN} = -V_{TP} = 0.4V$$

$$\alpha = 0.2 \quad \lambda = 0.1 \quad C = 10pF$$

Calculate τ_{PHL}

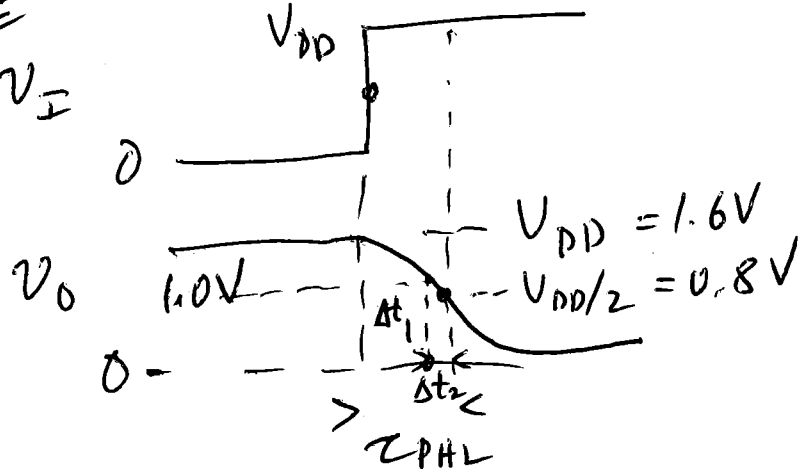

@ $t=0^+$

$$V_I = 1.6V$$

$$V_O = 1.6V$$

PMOS off,

NMOS $V_{GS} = 1.6V, V_{DS} = 1.6V \Rightarrow$ saturated

$$i_{DS} = \frac{K_n}{2(1+\alpha)} (V_{GS} - V_{TN})^2 \frac{1}{[1+\lambda(V_{DS} - V_{DSat})]} = \frac{200 \mu A/V^2}{2(1.2)} (1.6V - 0.4V)^2 \frac{1}{1.06} = 127 \mu A$$

NMOS saturated until $V_{DS} = V_{DSat} = \frac{V_{GS} - V_T}{1+\alpha} = \frac{1.6 - 0.4}{1.2} = 1.0V$

When $V_O = V_{DSat}, i_{DS} = 120 \mu A$

When $V_O = V_{DD}/2 = 0.8V$ NMOS in (linear/triode region) ($V_{DS} \leq V_{DSat}$)

$$i_{DS} = K_n (V_{GS} - V_{TN} - (1+\alpha) \frac{V_{DS}}{2}) V_{DS} = 200 \frac{\mu A}{V^2} (1.6 - 0.4 - \frac{(1.2)(0.8)}{2}) (0.8) = 115.2 \mu A$$

$$\Delta t_1 \quad V_0: 1.6V \Rightarrow 1.0V$$

$$\Delta t_2 \quad V_0: 1.0V \Rightarrow 0.8V$$

$$\tau_{PHL} = \Delta t_1 + \Delta t_2$$

$$\Delta t_1 = \frac{C \Delta V_1}{I_{avg}^1} = \frac{(10 \times 10^{-12} F)(1.6V - 1.0V)}{\frac{1}{2}(127.2 \mu A + 120 \mu A)} = 48.5 \times 10^{-9} s = 48.5 ns$$

$$\Delta t_2 = \frac{C \Delta V_2}{I_{avg}^2} = \frac{(10 \times 10^{-12} F)(1.0V - 0.8V)}{\frac{1}{2}(120 \mu A + 115.2 \mu A)} = 17 ns$$

$$\underline{\tau_{PHL} = 65.5 ns}$$