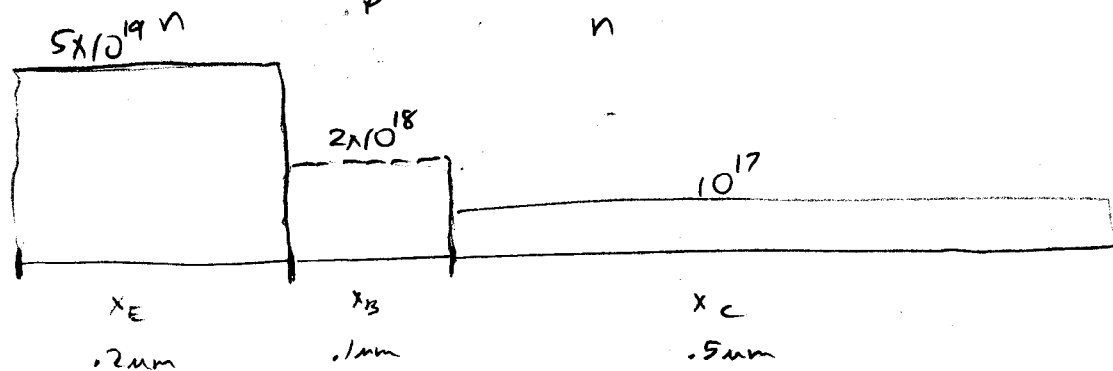




1. a)

(eg 30)

$$\alpha_F = \frac{I_C}{I_E} = \alpha_T \gamma_S$$

From plot in notes:

$$D_{PE} \approx 7.29 \frac{\text{cm}^2}{\text{s}} ; D_{NB} = 5.18 \frac{\text{cm}^2}{\text{s}} ; D_{PC} = 6.47 \frac{\text{cm}^2}{\text{s}}$$

$$L_{NB} = \sqrt{D_{NB} \tau_{NB}} = (5.18 \times 0.5 \times 10^{-6} \text{ s})^{1/2} \quad \text{all } \tau\text{'s} = 0.5 \mu\text{s}$$

$$= 1.6 \times 10^{-3} \text{ cm} \left(\frac{1 \text{ mm}}{10^4 \text{ cm}} \right) = 16.1 \mu\text{m}$$

$$\alpha_T \approx 1 - \frac{x_B^2}{2L_{PB}^2} \quad x_B \ll L_{NB} \quad \text{or}$$

$$= 1 - \frac{(0.1 \text{ mm})^2}{2(16.1 \mu\text{m})^2} = 0.99998 \approx 1 \Rightarrow (\alpha_F \approx \gamma_F)$$

$$\alpha_F = \gamma_F = \frac{1}{1 + \frac{x_B}{x_E} \frac{N_{AB}}{N_{DE}} \frac{D_{PE}}{D_{NB}}} = \frac{1}{1 + \frac{0.1 \text{ mm}}{0.2 \text{ mm}} \left(\frac{2 \times 10^{18}}{5 \times 10^{19}} \right) \frac{7.29}{5.18}}$$

$$\alpha_F = 0.99504$$

$$\beta_F = \frac{\alpha_F}{1 - \alpha_F} = 201$$

1. b)


$$\alpha_R = \alpha_T \gamma_R \approx \gamma_R$$

$$\gamma_R = \frac{1}{1 + \frac{x_B}{x_C} \frac{D_{pC}}{D_{pB}} \frac{N_{AB}}{N_{dC}}} = \frac{1}{1 + \frac{.1}{.5} \left(\frac{6.47}{5.18} \right) \frac{2 \times 10^{18}}{10^{17}}}$$


$$\gamma_R = \gamma_R = .1668 \Rightarrow \beta_R = \frac{\alpha_R}{1 - \alpha_R} = .2$$

c) - Minority Charge Densities -

fwd Active

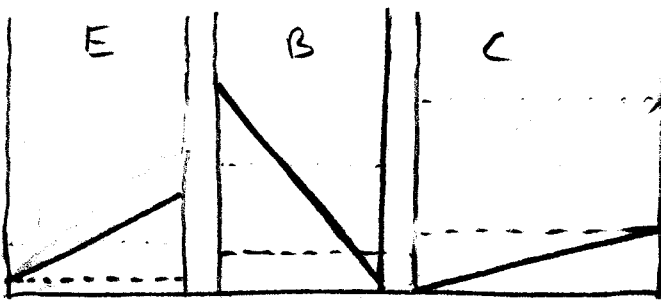


rev active

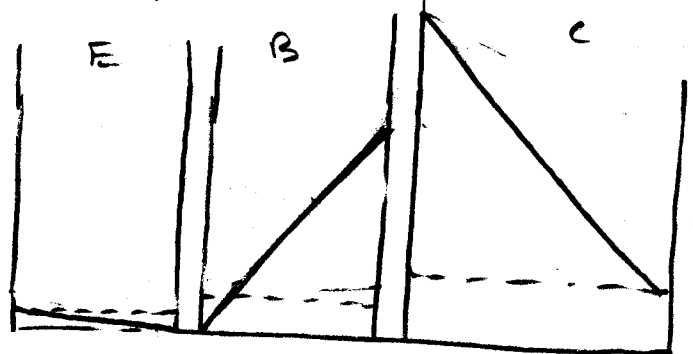

- Current Densities -
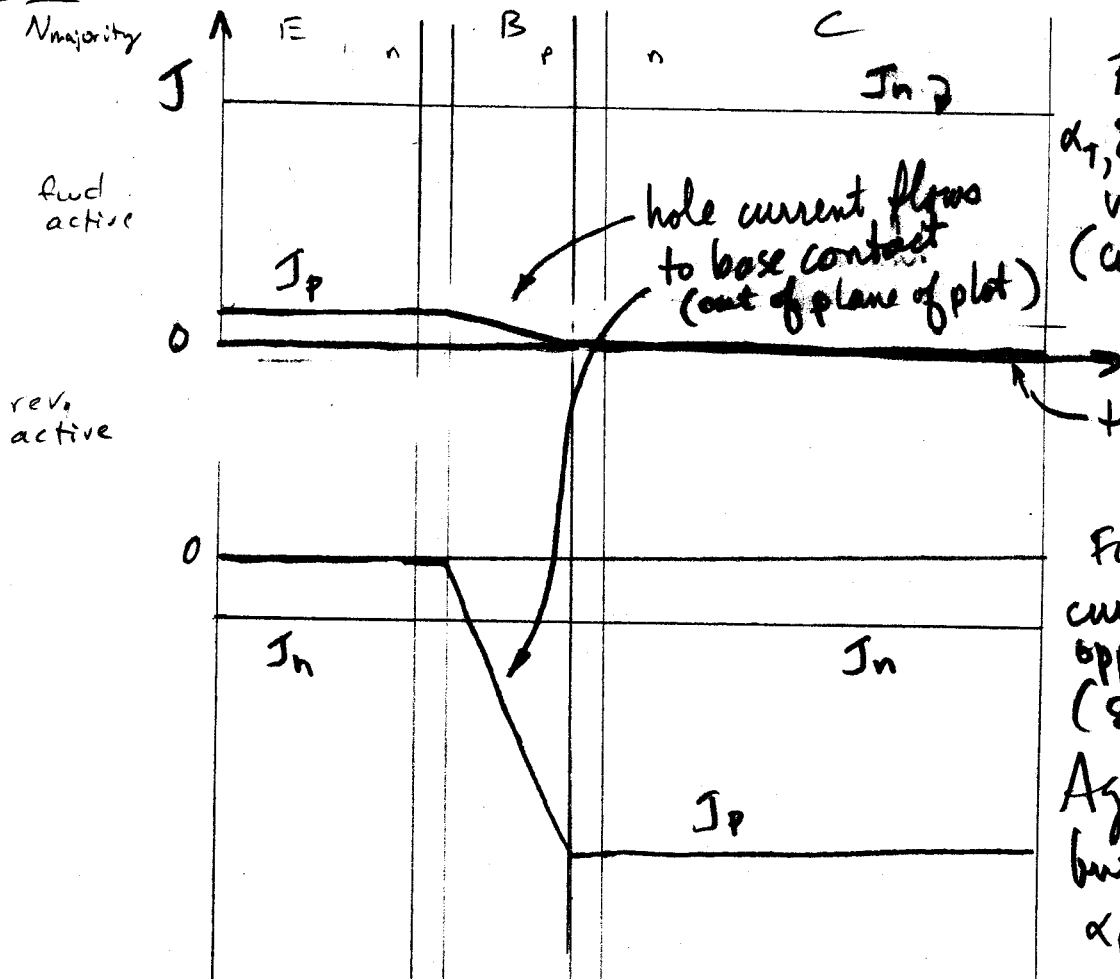
$$\text{Minority} = \frac{n_i^2}{N_{\text{majority}}}$$



For forward active
 $\alpha_T, \delta \approx 1$, so J_n
nearly constant
(current from C to E)


For reverse active,
current flows in
opposite direction
(shown as negative)

Again $J_n \approx$ constant,
but $J_p < J_n$ since
 $\alpha_R \ll 1$

npn $\alpha_F = .995$ $\alpha_R = .2$

$V_{CE} = 3V$; $I_B = 1\mu A$
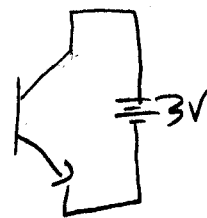
$$\beta_F = \frac{\alpha_F}{1 - \alpha_F} = 199$$




$V_{CE} = 3V$

$V_{CB} > 0$


$V_{BE} > 0$

fund active

Ebers-Moll Model

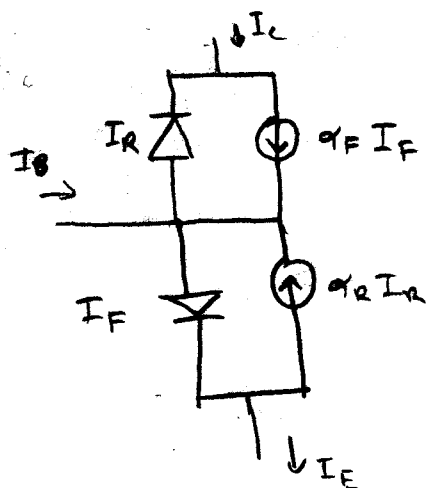

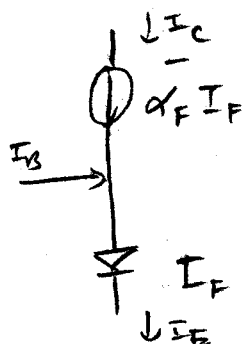since it is fund active neglect reverse currents



$$I_E = I_B + I_C$$

$$I_C = I_F - I_B \stackrel{\text{also}}{=} \alpha_F I_F$$

$$I_B = (1 - \alpha_F) I_F \Rightarrow I_F = \frac{I_B}{1 - \alpha_F} = 200\mu A$$

$$I_C = (995) 200\mu A$$

$$\underline{I_C = 199\mu A}$$

Also we can find this by using

$$\beta_F = \frac{\alpha_F}{1 - \alpha_F} = 199$$

$$I_C = \beta_F I_B = 199\mu A \quad \checkmark$$

2b)
 $V_{CE} = ?$

$\alpha_F = .995$

$\beta_F = \frac{\alpha_F}{1 - \alpha_F} = 199$


$\alpha_R = .2$

$I_B = 10 \mu A$

expected $I_C = \beta I_B = (199)(10 \mu A) \approx 2 \text{ mA}$

$I_C = 100 \mu A$

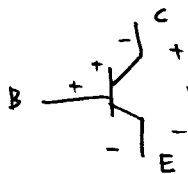but $I_C \ll 2 \text{ mA}$ so there must be loss due to significant reverse current.




$V_{BE} > 0$ because I_B is positive.

$V_{BC} > 0$ because of reverse current.

SATURATION MODE

Ebers-Moll Model

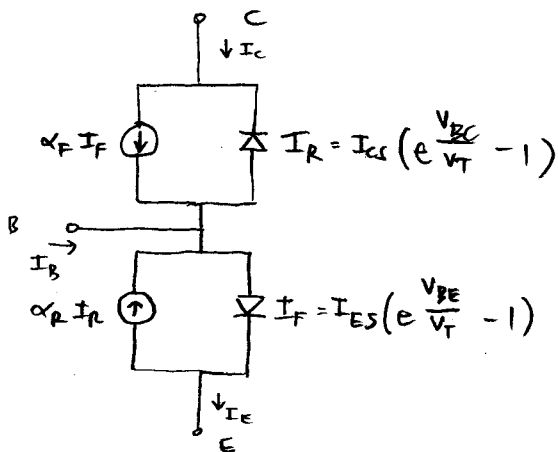

(1) $I_C + I_B = I_E$

(2) $I_C = \alpha_F I_F - I_R$

(3) $I_E = I_F - \alpha_R I_R$

(2) $I_R = \alpha_F I_F - I_C$

(3) $I_R = \frac{I_F - I_E}{\alpha_R}$

$\alpha_F I_F - I_C = \frac{I_F - I_E}{\alpha_R} \Rightarrow \alpha_R \alpha_F I_F - \alpha_R I_C = I_F - I_E \Rightarrow$

$I_F (\alpha_R \alpha_F - 1) = \alpha_R I_C - I_E \Rightarrow I_F = \frac{\alpha_R I_C - I_E}{(\alpha_R \alpha_F - 1)}$

$I_F = \frac{(.2)(100 \mu A) - (100 \mu A + 10 \mu A)}{(.2)(.995) - 1} = 112.4 \mu A$

$I_R = \alpha_F I_F - I_C$

$= (.995)(112.4 \mu A) - (100 \mu A)$

$= 11.8 \mu A$

$I_R = I_{CS} (e^{\frac{V_{BC}}{V_T}} - 1) \Rightarrow V_{BC} = V_T \ln \left(\frac{I_R}{I_{CS}} + 1 \right) \Rightarrow V_{BC} = V_T \ln \left(\frac{I_R}{I_{CS}} \right)$

$I_F = I_{ES} (e^{\frac{V_{BE}}{V_T}} - 1) \Rightarrow V_{BE} = V_T \ln \left(\frac{I_F}{I_{ES}} + 1 \right) \Rightarrow V_{BE} = V_T \ln \left(\frac{I_F}{I_{ES}} \right)$

ASSUME $I_R \gg I_{CS}$ and $I_F \gg I_{ES}$

continued $\rightarrow$

$$V_{CE} = V_{BE} - V_{BC}$$

2b)
cont.

$$= V_T \ln \left(\frac{I_F}{I_{ES}} \right) - V_T \ln \left(\frac{I_R}{I_{CS}} \right)$$

$$= V_T \left[\ln(I_F) - \ln(I_{ES}) - \ln(I_R) + \ln(I_{CS}) \right] \quad (\text{identity for natural logs})$$

$$= V_T \left[\ln(I_F) - \ln(I_R) - \ln(I_{ES}) + \ln \left(\frac{\alpha_F}{\alpha_R} I_{ES} \right) \right] \quad (\text{reciprocity } \alpha_F I_{ES} = \alpha_R I_{CS})$$

$$= V_T \left[\ln(I_F) - \ln(I_R) - \cancel{\ln(I_{ES})} + \ln \left(\frac{\alpha_F}{\alpha_R} \right) + \cancel{\ln(I_{ES})} \right] \quad (\text{identity})$$

$$= (.026) \left[\ln(112.4 \mu A) - \ln(11.8 \mu A) + \ln \left(\frac{.995}{.2} \right) \right]$$

$$= \underline{\underline{0.10 \text{ V}}}$$

check using eqn. (41) [p. 18]

$$V_{CE_{sat}} = (.026) \ln \left[\frac{\left[1 + \frac{100 \mu A}{10 \mu A} (1 - .2) \right]}{(.2) \left[1 - \frac{100 \mu A}{10 \mu A} \left(\frac{1 - .995}{.995} \right) \right]} \right]$$

$$= (.026)(3.86)$$

$$= \underline{\underline{0.10 \text{ V}}} \quad \text{ok.}$$